 


CMOS Sequential Circuits


- **Static CMOS Latch:**

- A basic memory element (2 back-to-back CMOS inverters)




Back to Back Inverters will hold data as long as there is a supply voltage. Also will resist noise

- To add writing capability, we use:

 

- when **En** = 1, **Q** = **D**
- when **En** = 0, **Q** stays the same

 
⇒ We get contention between the gate trying to write the new data and the backward inverter which is trying to retain the old data:



⇒ To eliminate the contention, we add a 2nd transmission gate to break the feedback loop during writing:

- When **En** = 0 → **TG₁** is OFF & **TG₂** is ON, **INV₁** & **INV₂** are connected back to back, **Q** stay the same.

 
- When **En** = 1 → **TG₁** is ON & **TG₂** is OFF, **Q** = **D**, and no contention since the O/P of **INV₂** is isolated from the I/P



⇒ This is a transparent, level sensitive latch; i.e. it is enabled by the level of the signal En:
 If $En = 1$, Q "sees" D ; whatever happens to D is transferred to Q


⇒ So, Latches cannot be used in Synchronous Circuits, since they will cause several state transitions per clock cycle.

 ↳ What we need is a memory element that is **Edge-Triggered**, since the clock has only one positive edge & one negative edge per cycle:



→ So, what we need is an Edge-Triggered Flip Flop (FF).

 
- The edge triggered effect could be obtained by using two Latches connected as **Master & Slave**:



- When $CK = 0$, **Master** is enabled while **Slave** is disabled,
 Q stays the same ⇒ $D \rightarrow Q'$

- As soon as $CK = 1$, **Master** is disabled while **Slave** is enabled,
 Q' stays constant and $Q \leftarrow D$ this happens with the clock edge (since D is already at Q'), so it appears that Q is edge-triggered. Q will change only once per clock period.


- **Time Diagram:**

 

❖ here Q "never" sees D → no transparency


- **The Edge-Triggered FF:**

- **The Positive Edge-Triggered:**

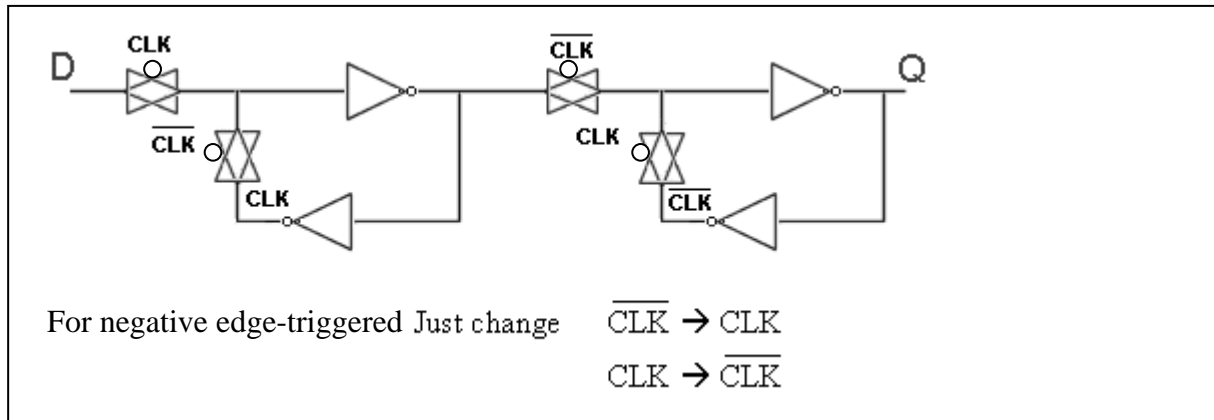


- **FFs with Direct (i.e. asynchronous) Inputs:**

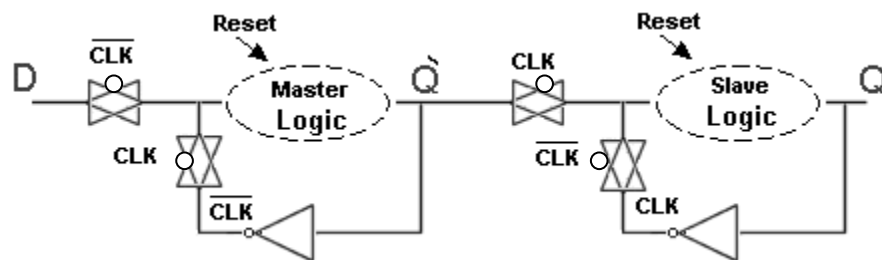- Direct I/Ps can be added by replacing the forward inverters in **Master & Slave**, by inverting logic that gives us the function we want.



 - In a **Negative Edge-Triggered FF** with **Active Low Direct Reset**:



CLK	Reset	Q+
X	0	0
1	1	Q
	1	D


- ❖ to **Reset a FF**, we need to **Reset the Slave & Set the Master**.

○ Master Logic:

D	Reset	Q'
X	0	1
0	1	1
1	1	0

→ when Reset is active, Q' = 1 ~ whatever D is
 } → when Reset is inactive, it works like an inverter
 
$$Q' = \overline{D} + \overline{Reset} = \overline{D \cdot Reset}$$




○ Slave Logic:

Q'	Reset	Q
X	0	0
0	1	1
1	1	0


acts like an inverter

$$Q = \overline{Q'} \cdot Reset$$

$$Q = \overline{Q' + \overline{Reset}}$$

 


○ The final solution:

 

Example 1:

Implement a **Positive Edge-Triggered FF with Active High Direct Set**


Sol:

 

○ **Master Logic:**

D	Set	Q'
X	1	0
0	0	1
1	0	0

 
$Q' = \overline{D} \cdot \overline{\text{Set}} = \overline{D + \text{Set}}$



○ **Slave Logic:**

Q'	Set	Q
X	1	1
0	0	1
1	0	0

 $Q = \overline{Q'} + \text{Set} = \overline{Q' \cdot \overline{\text{Set}}}$



○ **The final solution:**

