 


Design of Synchronous Circuit, continued:

Example 1: continued

Assume the wire capacitance is $C_{w1} = 50\text{fF}$



- ➔ Start designing the logic
- ➔ starting from Last level first

The AOI222

$$W_{Neff} = W_N/2$$

$$W_{Peff} = W_P/3$$

For Symmetrical NMOS

- ➔ Equal T_f and T_r : $W_{Peff} = 2 W_{Neff}$


$$\rightarrow W_P/3 = 2W_N/2 \rightarrow \boxed{W_P = 3W_N}$$

$$T_{Dave} = 71 \text{ ps} = T_r = T_f = R_N C_L$$

$$\rightarrow R_N = 71/12.8 = 5\text{K}\Omega$$

$$W_{Neff} = 4.2 / (1000 \times 10^{-6} \times 5 \times 10^3) \approx 0.8 \text{ um}$$
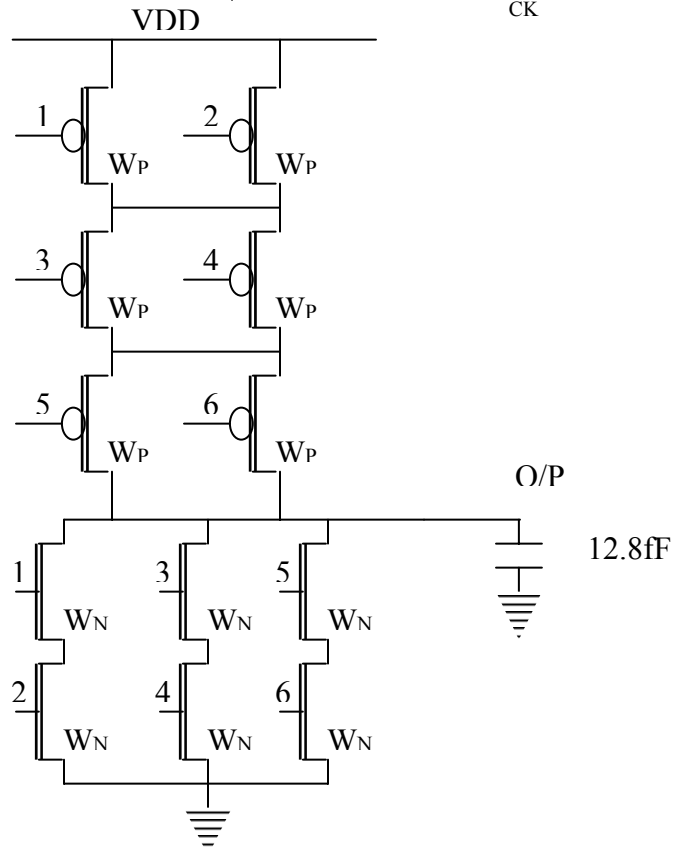
$$W_N = 2W_{Neff} = 1.6 \text{ um} \rightarrow W_P = 4.8 \text{ um}$$



$$C_{inAOI222} = 2fF \times (1.6 + 4.8) = 12.8fF$$

NAND Gate - AI2: $C_L = C_{W1} + C_{inAOI222} + C_{inFF}$
 $C_L = 50fF + 12.8fF + 12.8fF = 75.6fF$


$$T_f = 71 \text{ ps} = R_N C_L \rightarrow R_N = 71 \text{ ps} / 75.6fF = 940 \Omega$$

$$W_{Neff} = W_N / 2$$

$$W_{Peff} = W_P$$

$$\rightarrow W_{Peff} = \rightarrow \boxed{W_P = W_N}$$
 
$$W_{Neff} = 4.2 / (1000 \times 10^6 \times 0.94 \times 10^3) \approx 4.8 \text{ um}$$



$$\rightarrow W_N = 2W_{Neff} = 9.6 \text{ um} = W_P$$

$$C_{in} = 2 \times 1 \times (9.6 + 9.6) = 38fF < 50fF \text{ ((assumed } C_L \text{ for FF))}$$

→ Our FF will work fine

INV1:

$$W_{Neff} = W_N$$


$$W_{Peff} = W_P$$

$$\boxed{2W_N = W_P}$$

$$R_N = 71 / 12.8 = 6K\Omega$$

$$W_N = 4.2 / (1000 \times 10^6 \times 6 \times 10^3) < 1 \text{ um}$$

 So let $W_N = 1 \text{ um}$ and $W_P = 2 \text{ um}$



We have to make sure that the direct connection O3 dose not violate the hold time of the 2nd set of FFs

Our $T_{CK \rightarrow q1} = 142 \text{ ps}$ assuming load of 50 fF

But for O3, $C_L = 12.8fF$

$$T_{CK \rightarrow q1} = T_{DG1} + T_{Dslave \text{ logic}} = 71 + 71 \times 12.8 / 50 \approx 89 \text{ ps}$$


Now assuming that $T_{hold} = 100$ ps

The condition for satisfying the hold time

$$T_{hold} + T_{skew} + T_{jitter} < T_{CK \rightarrow q1} + T_D$$

$\underbrace{\hspace{10em}}_{170 \text{ ps}} \quad \cancel{<} \quad \underbrace{\hspace{10em}}_{89 \text{ ps}} \quad \text{VIOLATION!!}$

 We need to DELAY O3 \rightarrow use 2 inverters, same one that was designed. And check for both, T_{hold} and T_{SU} violations.



$T_{Di2} = 71$ ps (it was designed to have $T_D = 71$ ps at $C_L = 12.8\text{fF}$)

$$C_{in \text{ inv1}} = 2 \times 1 \times (2 + 1) = 6\text{fF}$$

For a Designed gate with a delay T_{D1} at load C_{L1} , the new delay T_{D2} for a different load C_{L2} is

$$T_{D2} = T_{D1} \cdot C_{L2} / C_{L1}$$

$$\rightarrow T_{Di1} = 71 \times 6 / 12.8 \approx 33 \text{ ps}$$

$$\rightarrow T_{DO3} = 71 + 33 \approx 104 \text{ ps}$$

Now we check T_{hold} violation:

$$\text{For O3 } T_{CK \rightarrow q1} + T_D = 190 \text{ ps} > T_{hold} + T_{skew} + T_{jitter}$$


Now we check T_{SU} violation:

$$T_{CK \rightarrow q1} + T_D + T_{SU} = 190 \text{ ps} + 142 \text{ ps} = 332 \text{ ps} < T_{CK}$$

So no T_{hold} or T_{SU} violations

An Alternative FF Circuits:

Using tri-state Buffers:

 


Tri-State Buffer


EN	I/P	O/P	
0	X	Z	→ high impedance or open circuit
1	0	1	} → work as inverter when it is enabled
1	1	0	

Used in Buses:

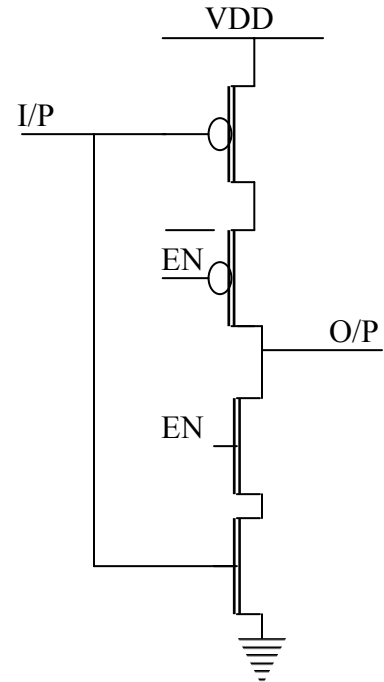
A Bus: A connection with multiple Drivers and Receivers



It can be used as a latch:

 

 A MASTER-SLAVE FF (Positive edge triggered)



For Negative edge triggered → exchange the positions of CK and \overline{CK}

True-Single-Phase-Clock(TSPC) FF:

All FFs seen so far need both CK and \overline{CK} (2 phase clocks)

