

King Fahd University of Petroleum and Minerals
College of Computer Sciences and Engineering
Department of Computer Engineering

COE 202 – Fundamentals of Computer Engineering (T061)

Homework # 04 (due date & time: Monday 27/11/2006 during class period)

*** Show all your work. No credit will be given if work is not shown! ***

Problem # 1 (20 points): The following truth table is for a circuit that accepts two 2-bit unsigned numbers A (A_1A_0) and B (B_1B_0). The circuit has one output, X , that is equal to 1 when $(A - B) \geq 0$. Use a 4×16 decoder and external gate(s) to implement the circuit.

A_1	A_0	B_1	B_0	X
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Problem # 2 (20 points): Repeat problem # 1 but use a 4×16 inverted-output decoder and external gate(s).

Problem # 3 (20 points): Repeat problem # 1 but use a 16×1 MUX and external gate(s).

Problem # 4 (20 points): Repeat problem # 1 but use an 8×1 MUX and external gate(s). Connect A_1 , A_0 , and B_1 to S_2 , S_1 , and S_0 , respectively.

Problem # 5 (20 points): Repeat problem # 1 but use an 8×1 MUX and external gate(s). Connect A_0 , B_1 , and B_0 to S_2 , S_1 , and S_0 , respectively.