



King Fahd University of Petroleum and Minerals
Department of Computer Engineering

DIGITAL LOGIC DESIGN COE 202

Section 5

**Homework 2, November 17, 2008
(Due on Nov 29, 2008)**

Problems	Grading
1	
2	
3	
4	
5	
TOTAL	

Student Name:.....

Student ID:.....

1. Question-1: Answer each of the following three problems:

I. Using Algebraic manipulation prove the following algebraic identities:

- a. $X'Y' + X'Y + XY = X' + Y$
- b. $A'B + B'C' + AB + B'C = 1$
- c. $Y + X'Z + XY' = X + Y + Z$
- d. $X'Y' + Y'Z + XZ + XY + YZ = X'Y' + XZ + YZ$

II. Convert the following expressions into (1) Sum-of-Product, and (2) Product-of-Sum forms:

- a. $(AB + C)(B + C'D)$
- b. $X' + X(X + Y')(Y + Z')$
- c. $(A + BC' + CD)(B' + EF)$

III. Draw the logic diagram for the following logical expressions:

- a. $WX'Y' + W'Z + YZ$
- b. $A(BD' + B'D) + D(BC + B'C')$
- c. $WY'(X + Z) + X'Z(W + Y) + WX'(Y + Z)$

2. Question-2: Write the *sum-of-minterms* and *product-of-maxterms* expressions for both the *true* and the *complement* form of the following Boolean expressions:

- a. $\overline{XZ} + Y\overline{Z} + XYZ$
- b. $\overline{AB} + A\overline{CD} + \overline{BC} + \overline{ABC\overline{D}}$

3. Question-3: For the given truth table and using a K-map:

- a. Find all *prime implicants* and *essential prime implicants* of F .
- b. Write an optimized SOP **and** POS expressions for the function F .

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

4. For the Boolean function E and F, as given in the following truth table:

X	Y	Z	E	F
0	0	0	1	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	0	1

- List the minterms and the maxterms of each function.
- List the minterms of E' and F' .
- List the minterms of $E + F$ and $E \cdot F$.
- Express E and F in sum-of-minterms and product-of-maxterms algebraic form.