



**King Fahd University of Petroleum and Minerals
Department of Computer Engineering**

DIGITAL LOGIC DESIGN COE 202

Homework 3, December 21, 2008

Problems	Grading
1	
2	
3	
4	
5	
6	
TOTAL	


Student Name:.....

Student ID:.....


Question1:

As a *design engineer* your manager asks you to design a circuit that will be used in an electronic safety device used for toddlers. The circuit monitors an area that will be used by toddlers. The area is divided into 4 zones, Z_1 , Z_2 , Z_3 , and Z_4 . Each zone has an installed body-heat sensor. If the sensor detects the presence of a toddler in its zone, then the sensor produces a binary “1,” and it produces a binary “0” otherwise. Your circuit receives the readings from each sensor installed in each of the 4 zones. Furthermore, your circuit controls 2 light bulbs, L_1 and L_2 . Both L_1 and L_2 will be turned **off** (i.e. binary “0”) if the circuit detects the presence of **no** toddlers in all 4 zones. Only L_1 will be turned **on** if the circuit detects the presence of toddler(s) in exactly **one** of the 4 zones. Only L_2 will be turned **on** if the circuit detects the presence of toddler(s) in either **two** or **three** of the 4 zones. Both L_1 and L_2 will be turned **on** if the circuit detects the presence of toddler(s) in all 4 zones. Design the circuit using all **NAND** gates.


Z_1	Z_2	Z_3	Z_4	L_1	L_2
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	0	1
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	1

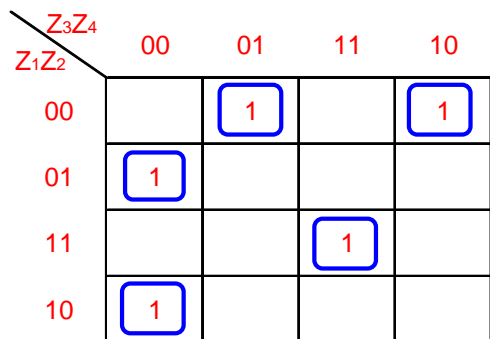
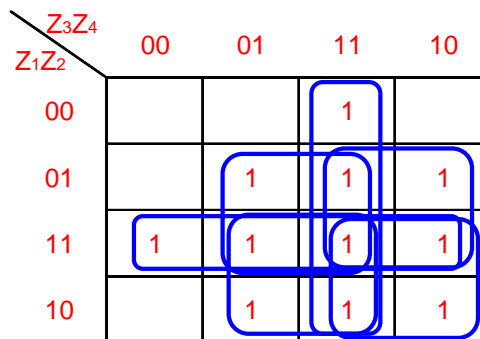
$$L_1 = \bar{Z}_1 \bar{Z}_2 \bar{Z}_3 Z_4 + \bar{Z}_1 \bar{Z}_2 Z_3 \bar{Z}_4 + \bar{Z}_1 Z_2 \bar{Z}_3 \bar{Z}_4 + Z_1 \bar{Z}_2 \bar{Z}_3 \bar{Z}_4 + Z_1 Z_2 Z_3 Z_4$$



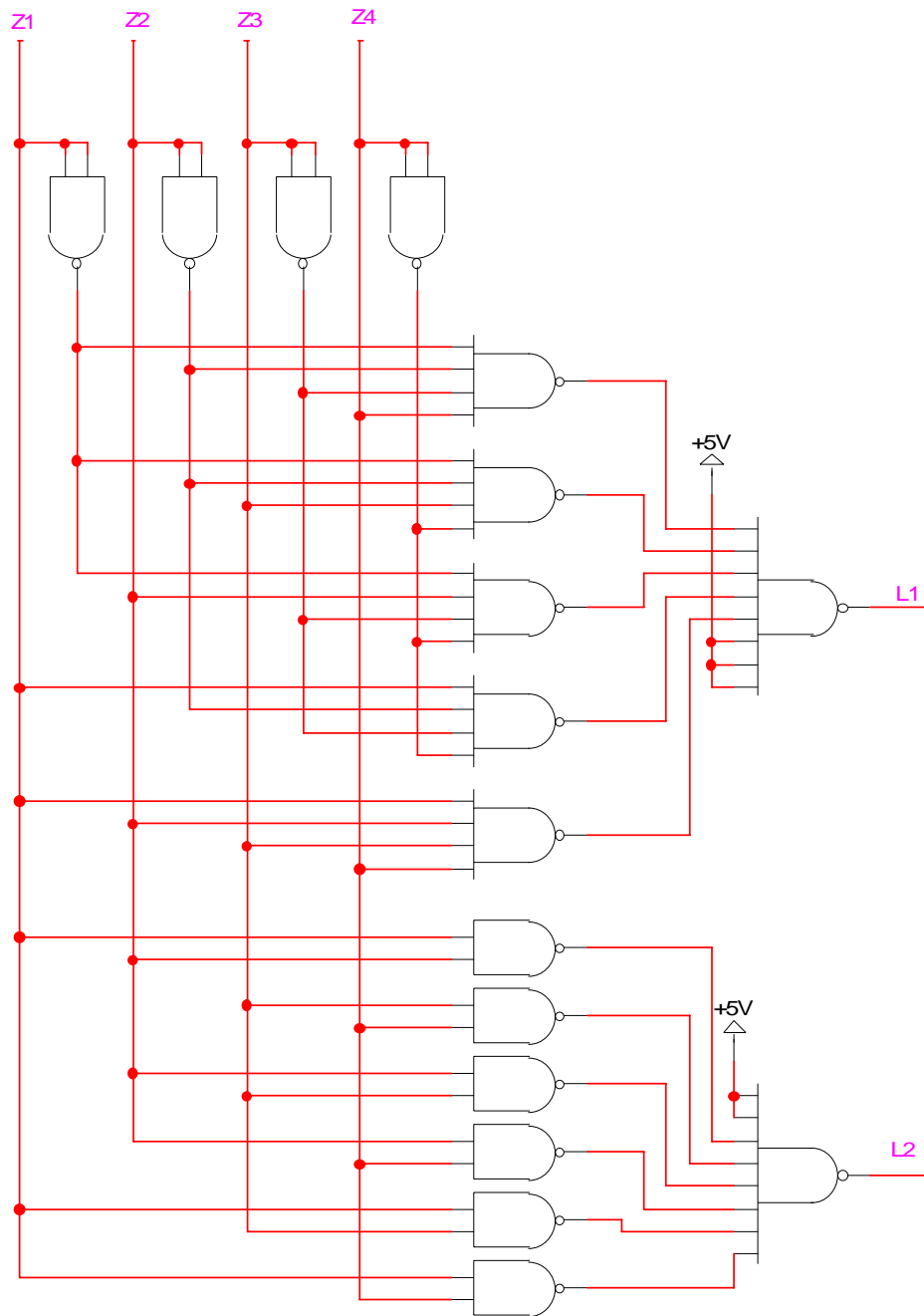
$$L_2 = Z_1 Z_2 + Z_3 Z_4 + Z_1 Z_3 + Z_1 Z_4 + Z_2 Z_3 + Z_2 Z_4$$




Problem # 2 (10 points): Use a 4×16 non-inverted-output decoder and external gate(s) to implement the following function:

$$X_{A,B,C,D} = \sum(0,4,5,8,9,10,12)$$

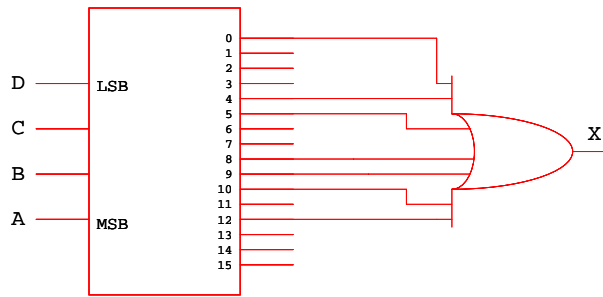


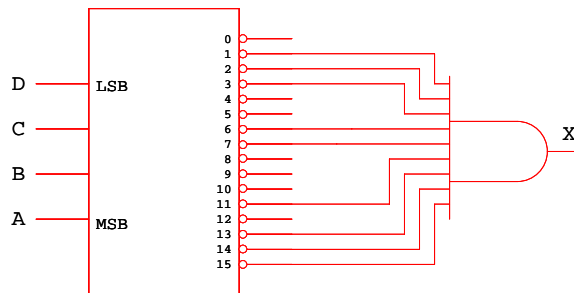Problem # 3 (10 points): Repeat problem # 2 but use a **4x16 inverted-output decoder** and external gate(s).

$$X_{A,B,C,D} = \sum (0, 4, 5, 8, 9, 10, 12) = \prod (1, 2, 3, 6, 7, 11, 13, 14, 15)$$




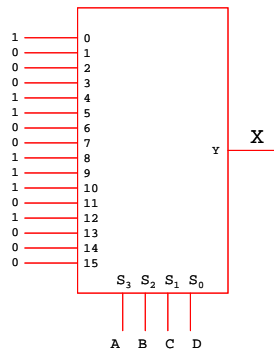Problem # 4 (10 points): Repeat problem # 2 but use a **16x1 MUX** and external gate(s).



Problem # 5 (10 points): Repeat problem # 2 but use an **8×1 MUX** and external gate(s). Connect **A**, **B**, and **C** to S_2 , S_1 , and S_0 , respectively.

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
D'	0	2	4	6	8	10	12	14
D	1	3	5	7	9	11	13	15
D'	0	1	0	1	D'	D'	0	

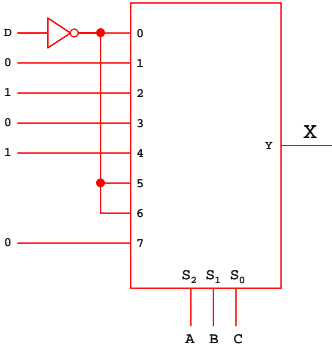

Problem # 6 (10 points): Repeat problem # 2 but use an **8×1 MUX** and external gate(s). Connect **A**, **C**, and **D** to S_2 , S_1 , and S_0 , respectively.

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
B'	0	1	2	3	8	9	10	11
B	4	5	6	7	12	13	14	15
	1	B	0	0	1	B'	B'	0

