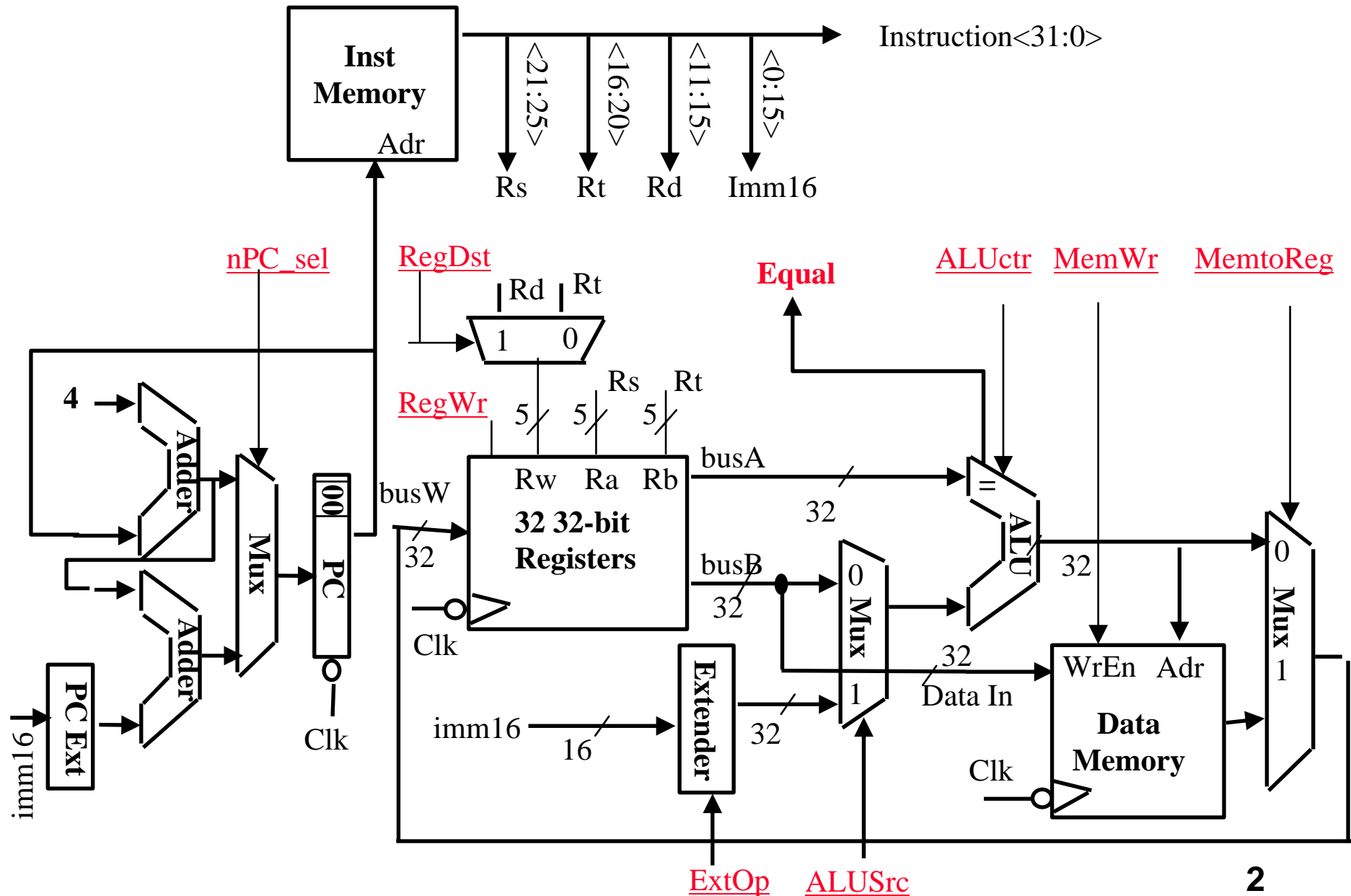


# Processor Design - 2

Computer Architecture


# Summary: A Single Cycle Datapath


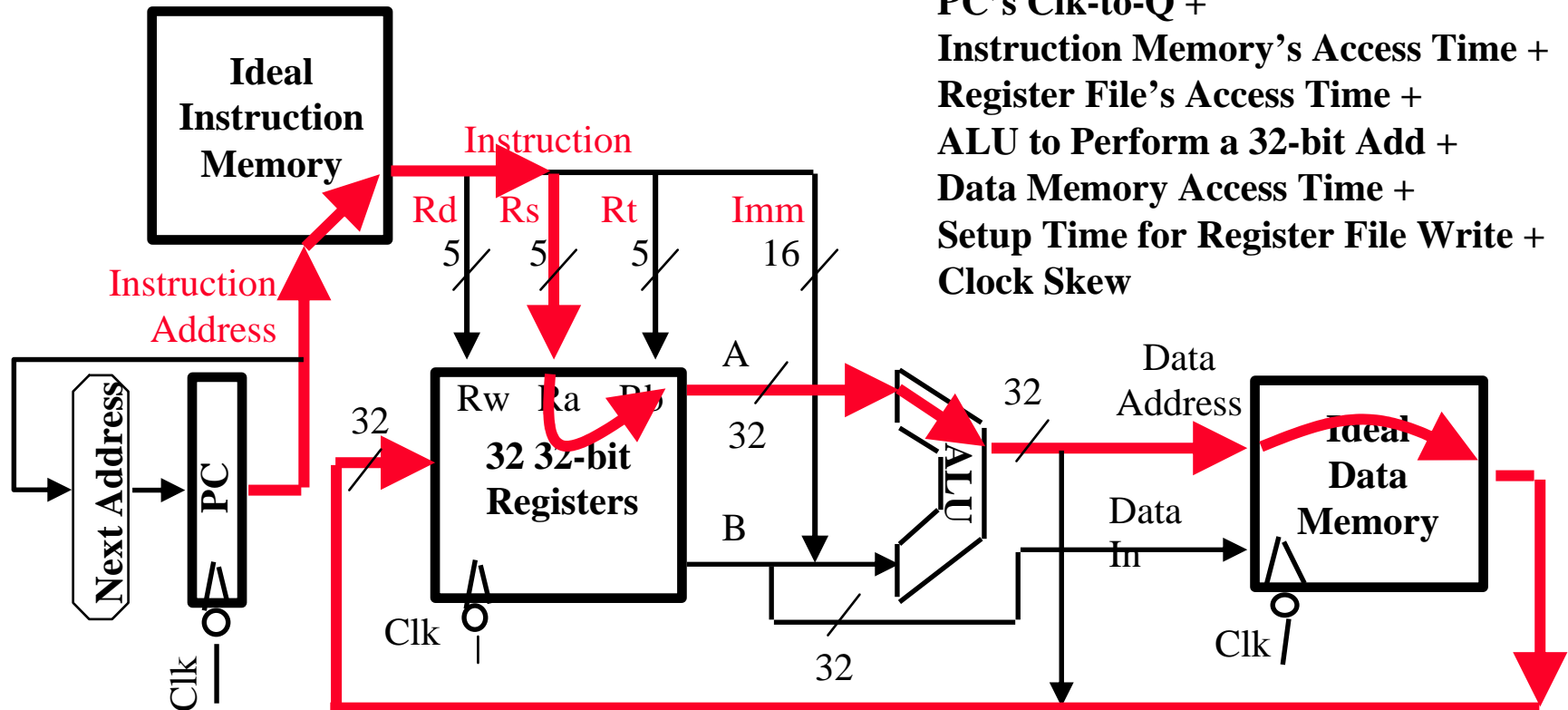
# An Abstract View of the Critical Path

- **Register file and ideal memory:**


- The CLK input is a factor ONLY during write operation
- During read operation, behave as combinational logic:
  - Address valid => Output valid after “access time.”



**Critical Path (Load Operation) =**  
PC's Clk-to-Q +  
Instruction Memory's Access Time +  
Register File's Access Time +  
ALU to Perform a 32-bit Add +  
Data Memory Access Time +  
Setup Time for Register File Write +  
Clock Skew

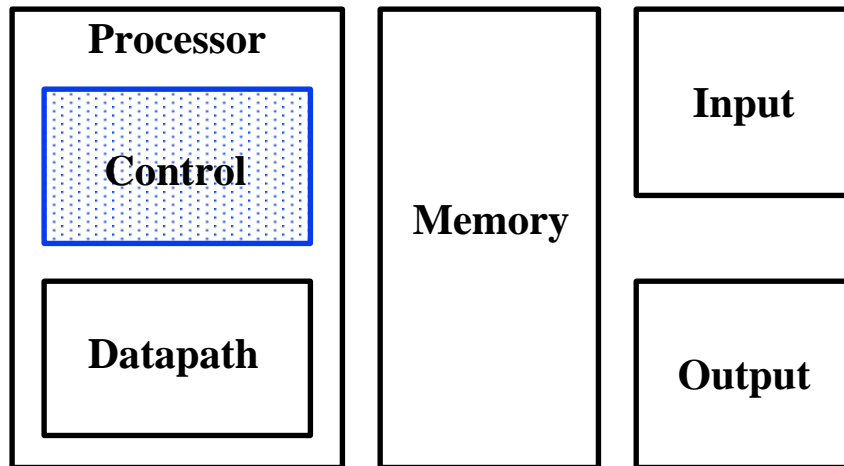
# The Big Picture: Where are We Now?

- The Five Classic Components of a Computer




- Next Topic: Designing the Control for the Single Cycle Datapath

# An Abstract View of the Implementation

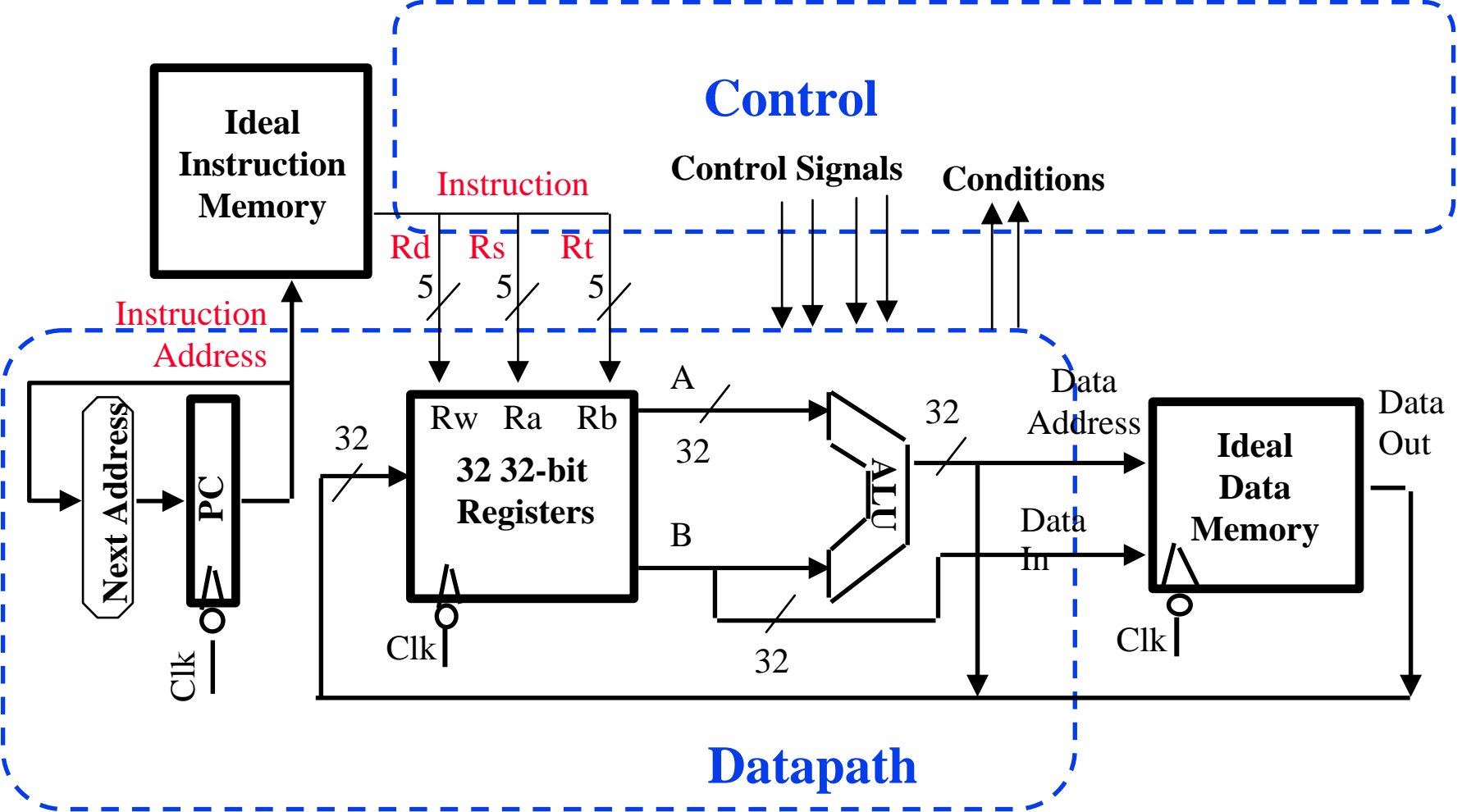

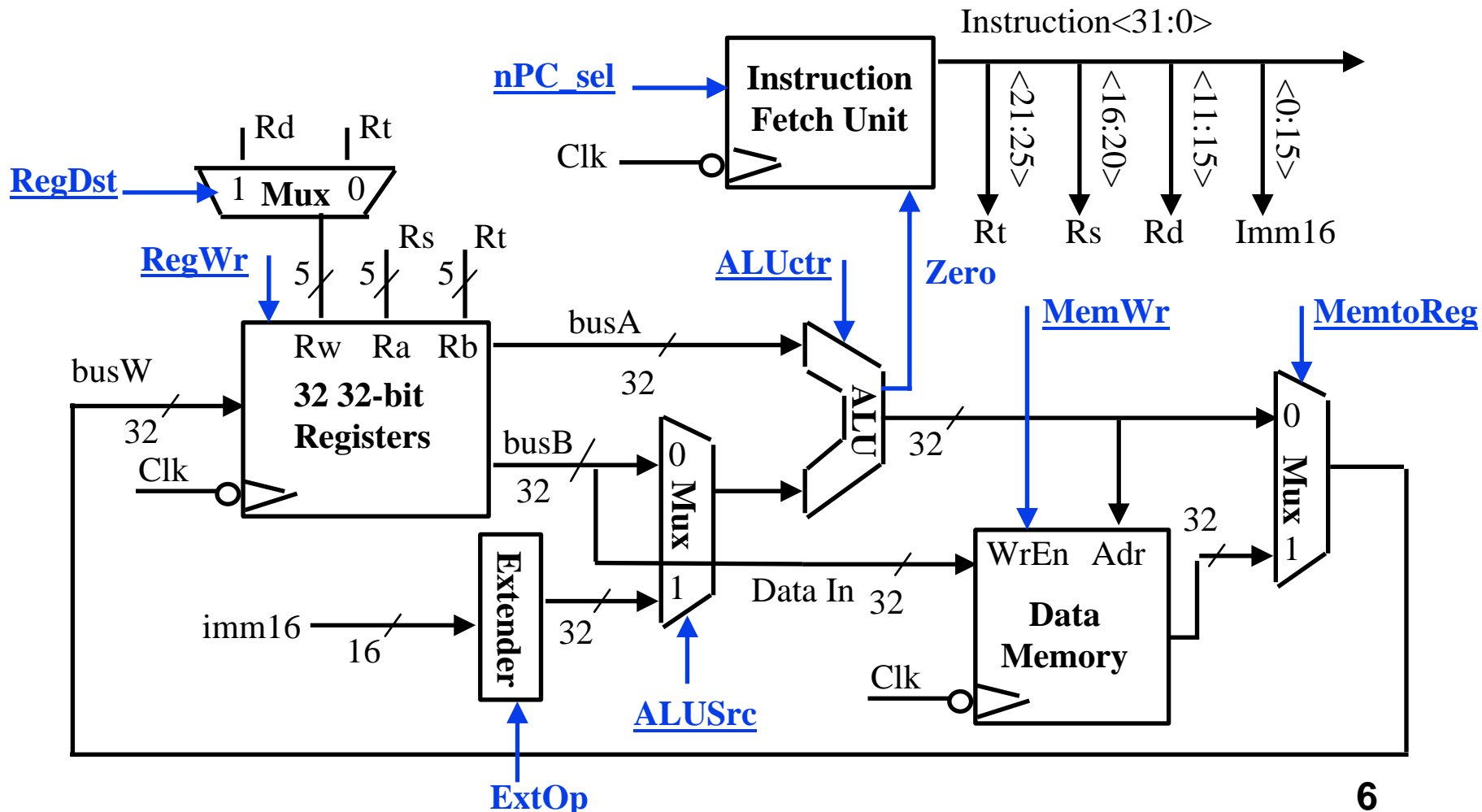
# Recap: A Single Cycle Datapath

- Rs, Rt, Rd and Imed16 hardwired into datapath from Fetch Unit
- We have everything except control signals (underline)
  - Today's lecture will show you how to generate the control signals



# Recap: Meaning of the Control Signals


- **nPC\_sel:**     0  $\Rightarrow$  PC  $\leftarrow$  PC + 4  
                  1  $\Rightarrow$  PC  $\leftarrow$  PC + 4 + SignExt(Im16) || 00
- Later in lecture: higher-level connection between mux and branch cond

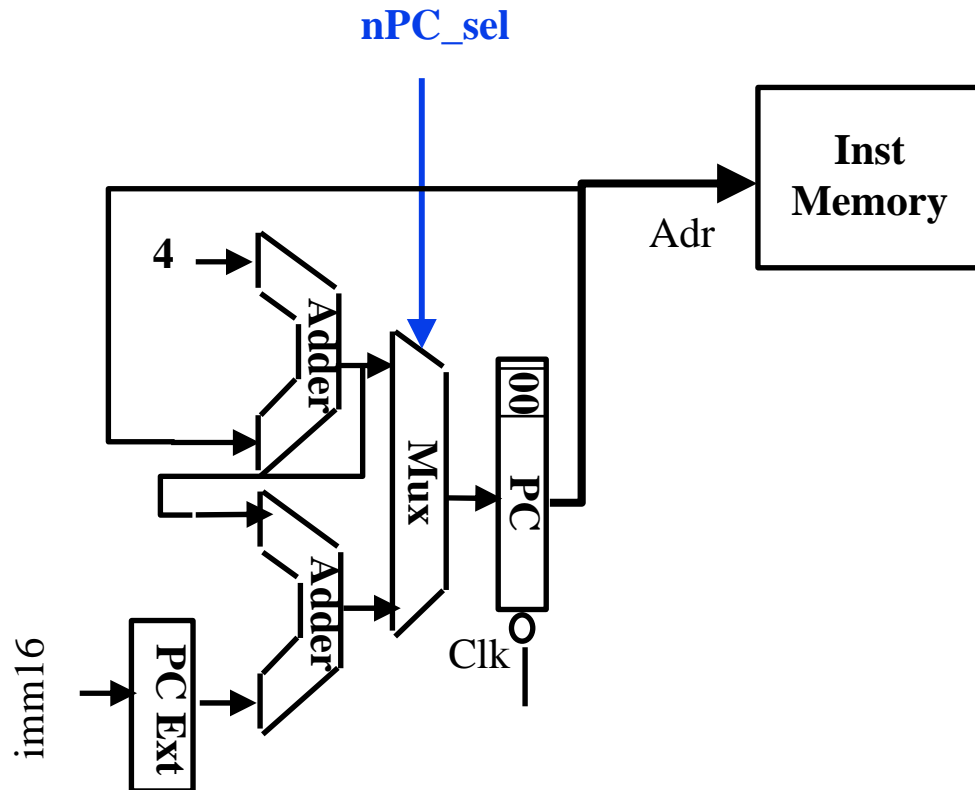





# The add Instruction

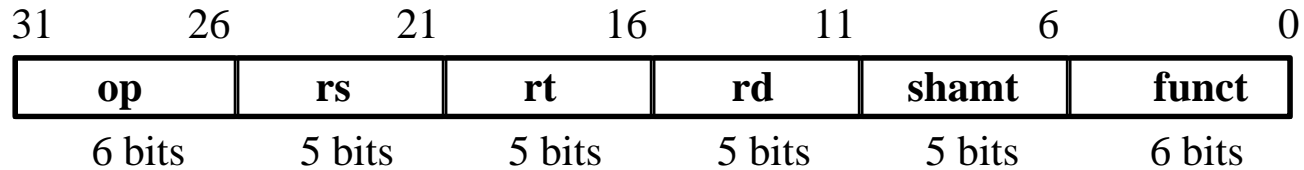

• **add rd, rs, rt**

**mem[PC]**

**Fetch the instruction from memory**

**$R[rd] \leftarrow R[rs] + R[rt]$**


**The actual operation**

**$PC \leftarrow PC + 4$**


**Calculate the next instruction's address**
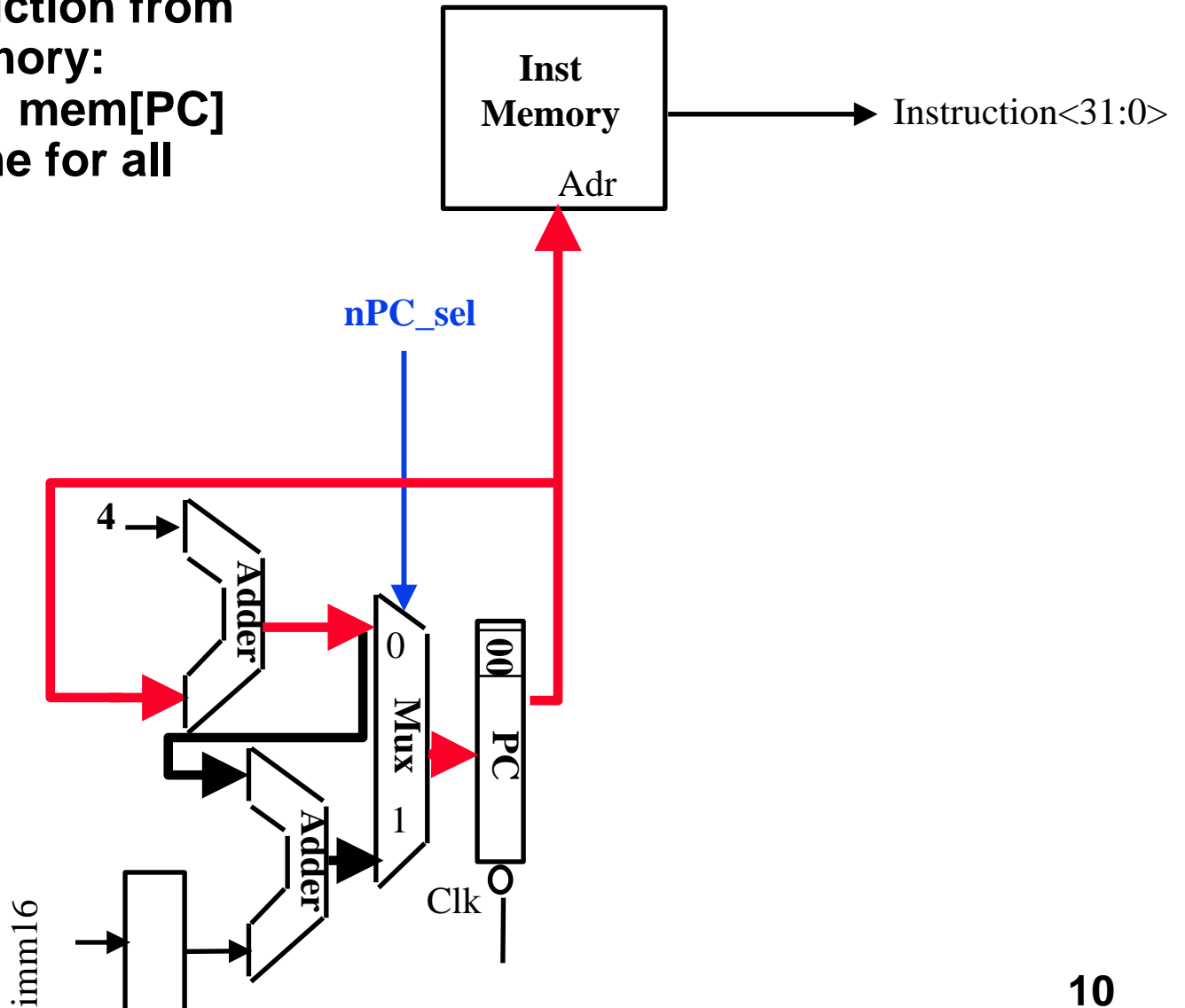
# Fetch Unit at the Beginning of add


- Fetch the instruction from Instruction memory:  
 $\text{Instruction} \leftarrow \text{mem}[\text{PC}]$   
(This is the same for all instructions)



# The Single Cycle Datapath during add

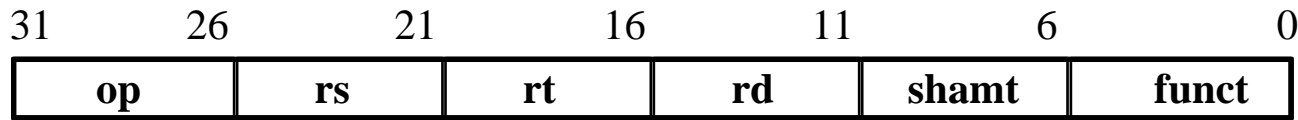


•  $R[rd] \leftarrow R[rs] + R[rt]$

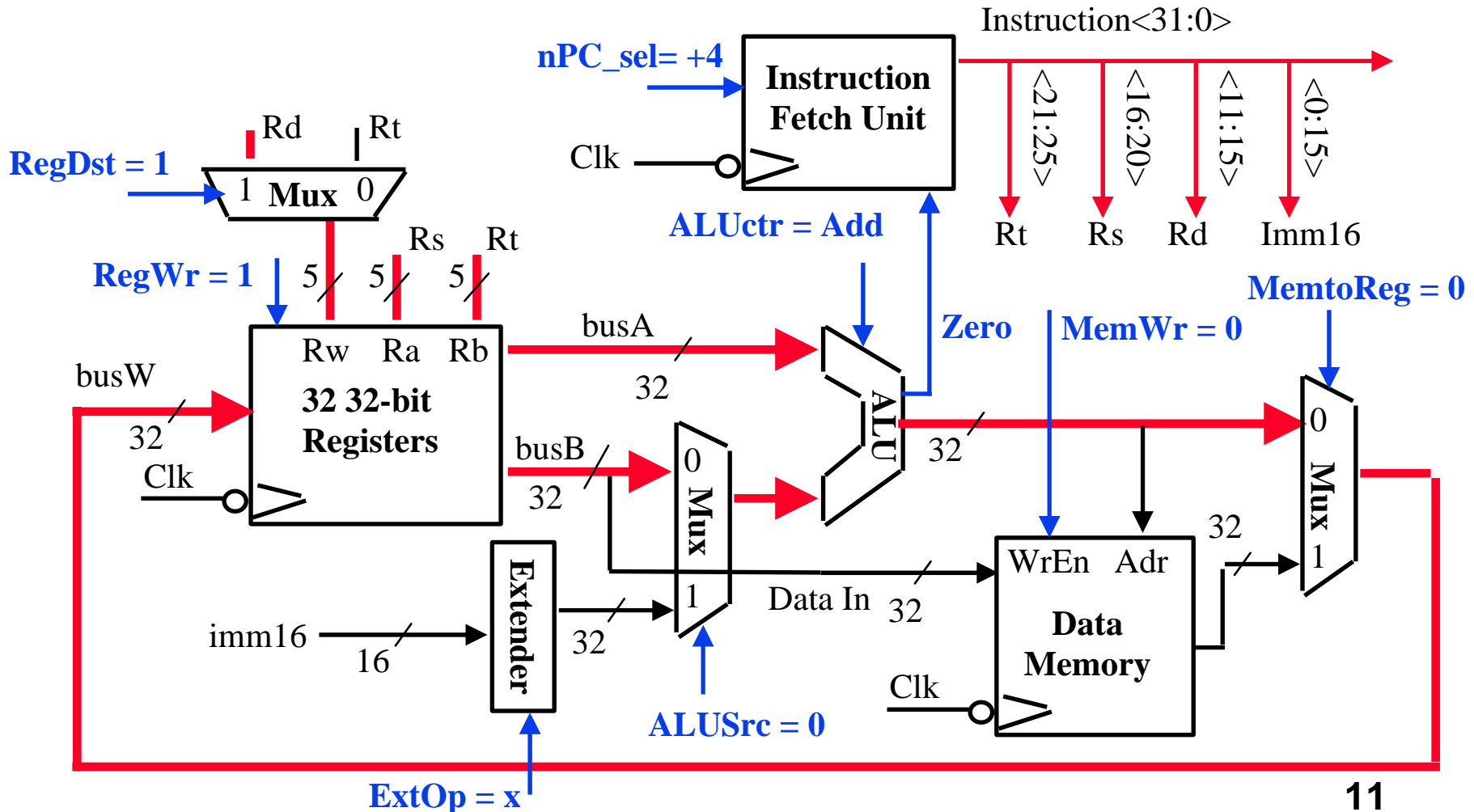

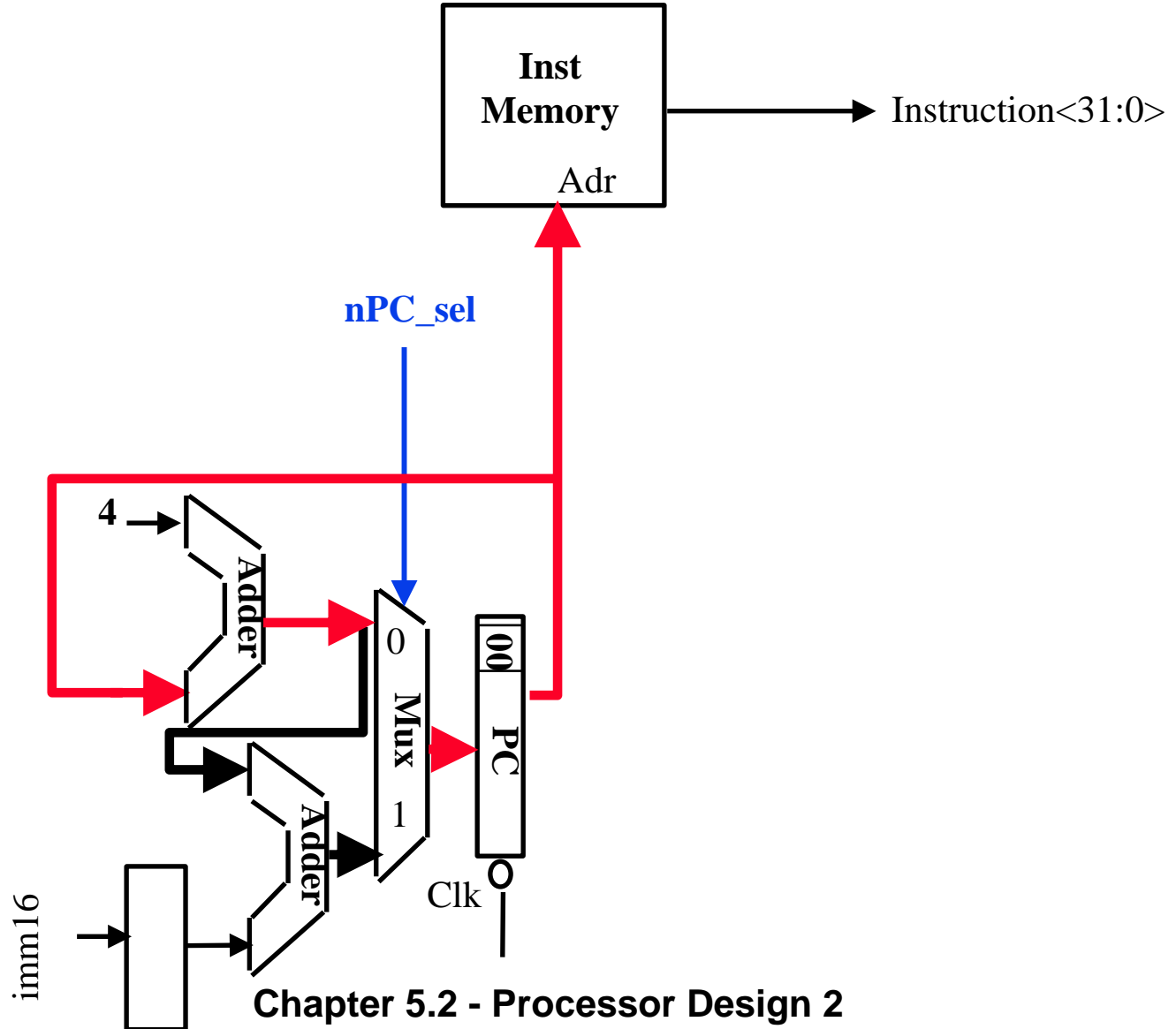
# Instruction Fetch Unit at the End of add


- $PC \leftarrow PC + 4$ 
  - This is the same for all instructions except: Branch and Jump


 
# The Single Cycle Datapath during Or Immediate




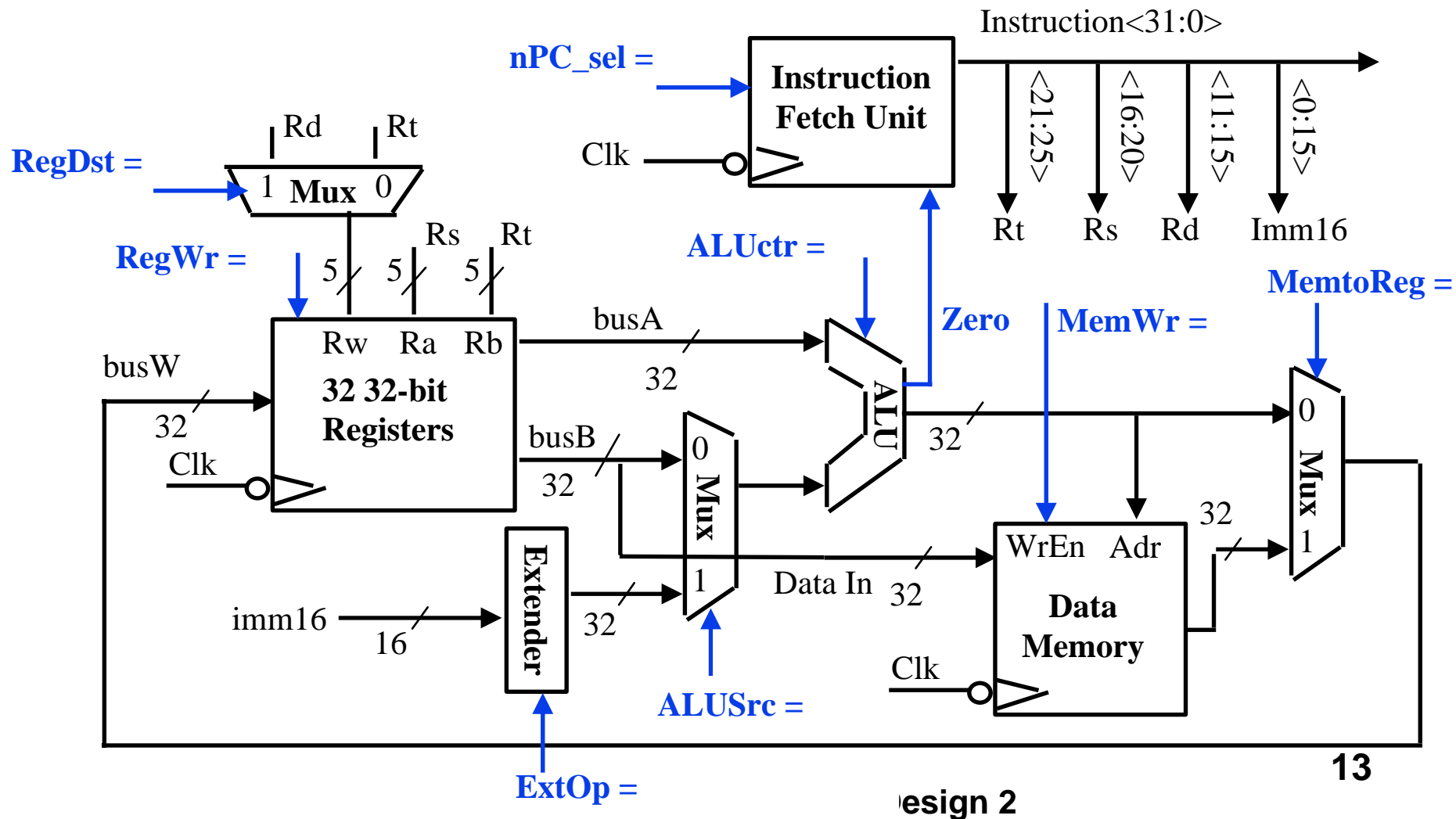- $R[rt] \leftarrow R[rs] \text{ or } \text{ZeroExt}(\text{Imm16})$







# The Single Cycle Datapath during Load

 

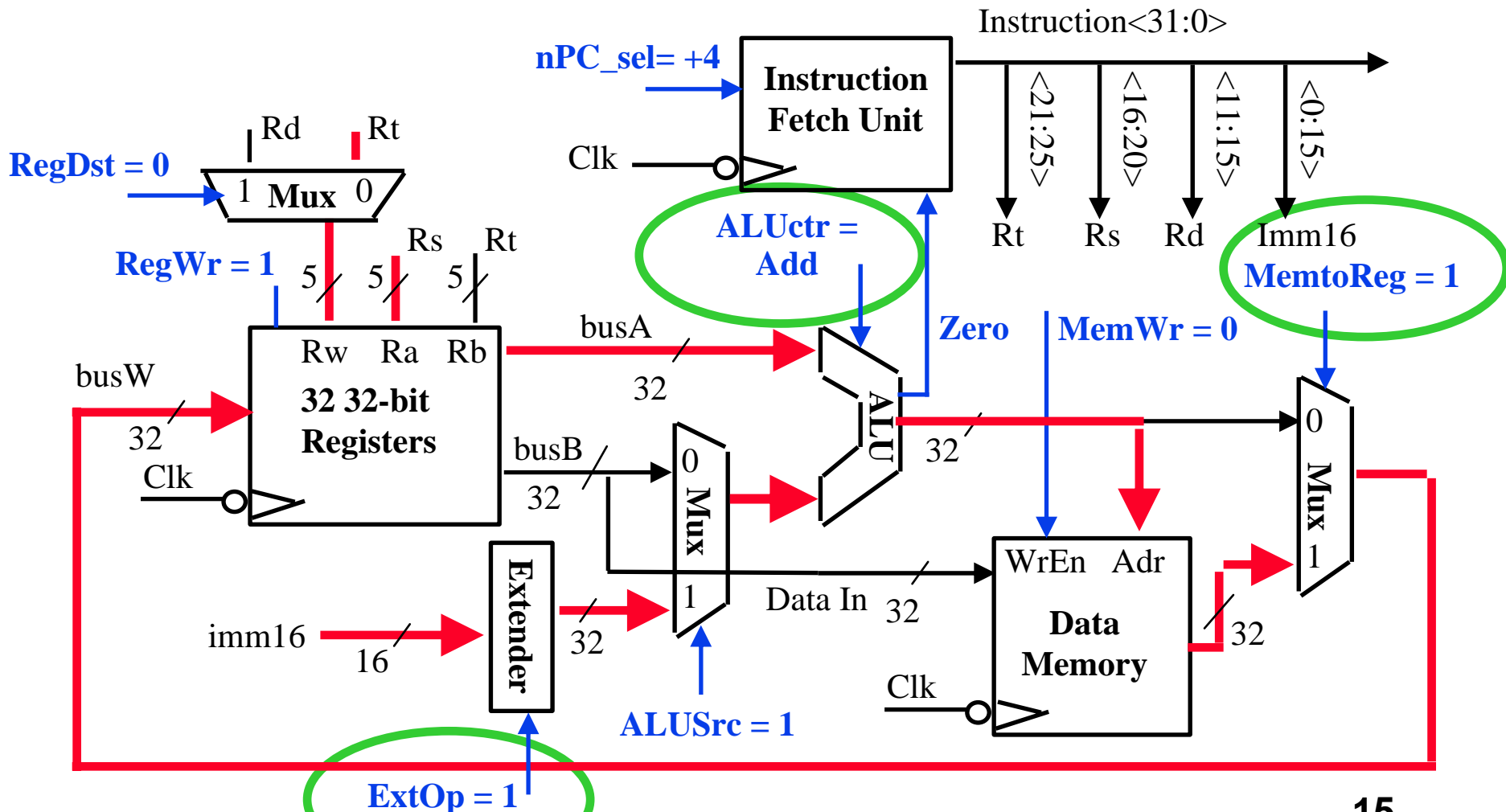
•  $R[rt] \leftarrow \text{Data Memory} \{R[rs] + \text{SignExt}[imm16]\}$



# The Single Cycle Datapath during Store

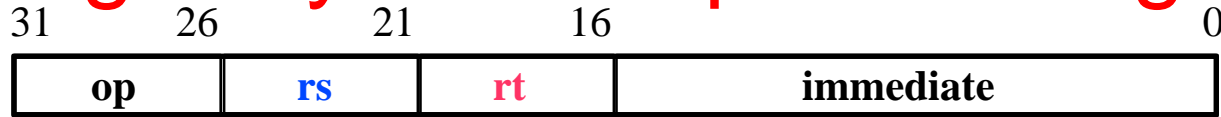


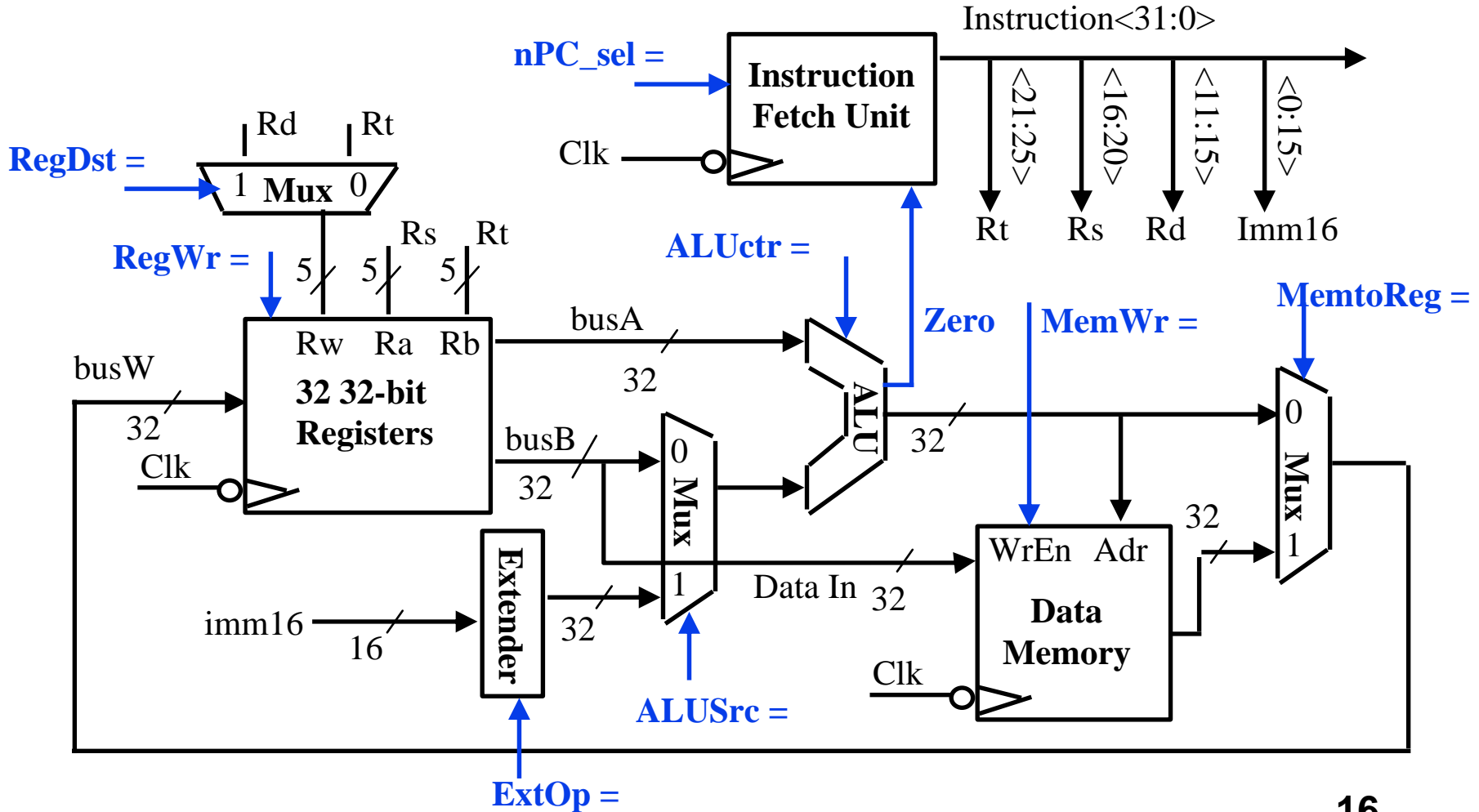- Data Memory  $\{R[rs] + \text{SignExt}[imm16]\} \leftarrow R[rt]$






# The Single Cycle Datapath during Store

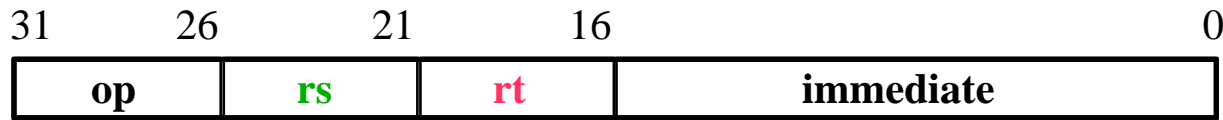


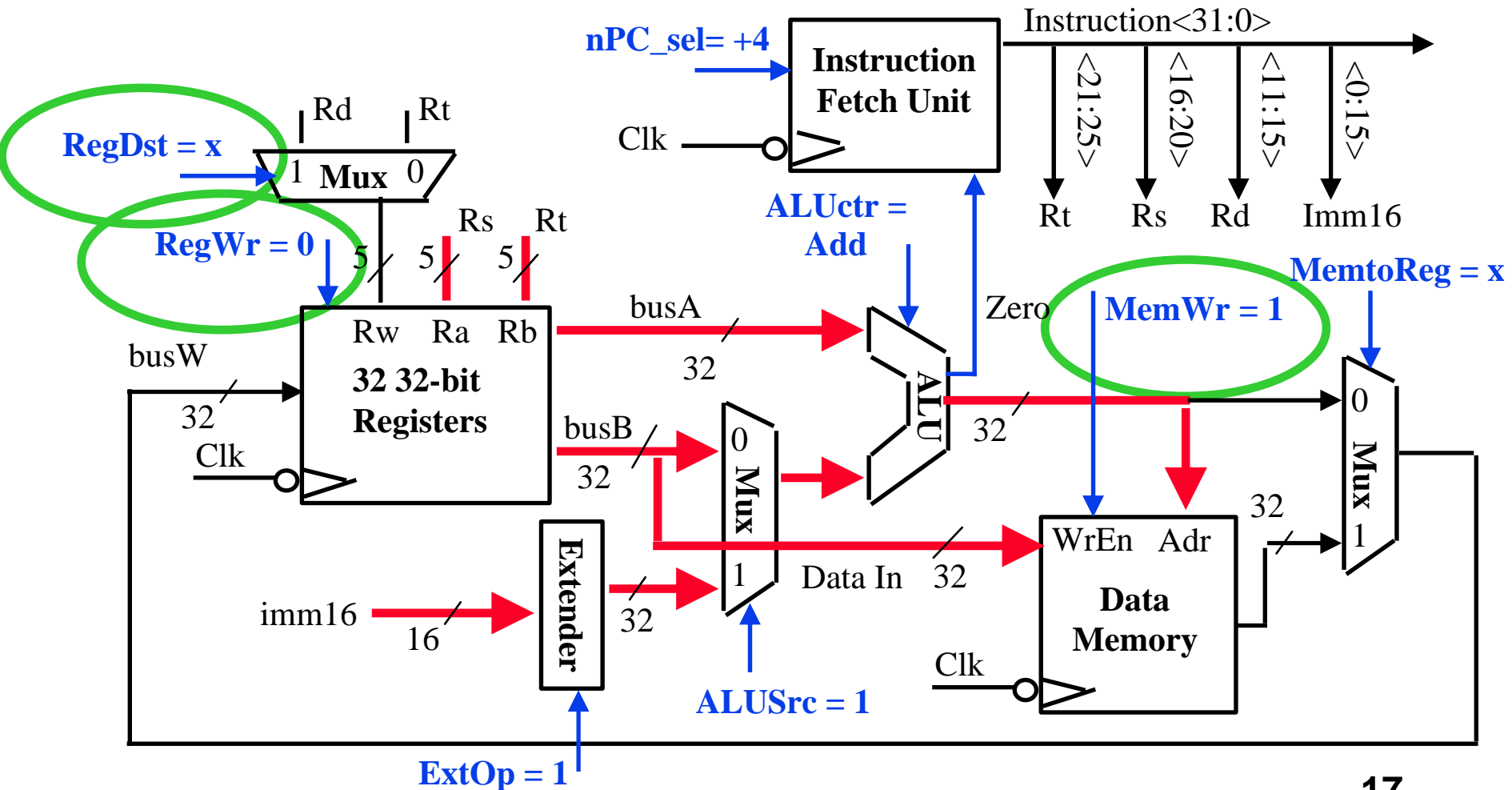• Data Memory  $\{R[rs] + \text{SignExt}[imm16]\} \leftarrow R[rt]$





 
# Instruction Fetch Unit at the End of Branch



 
- if (Zero == 1) then PC = PC + 4 + SignExt(imm16)×4 ; else PC = PC + 4



- What is encoding of nPC\_sel?
  - Direct MUX select?
  - Branch / not branch
- Let's choose second option

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1
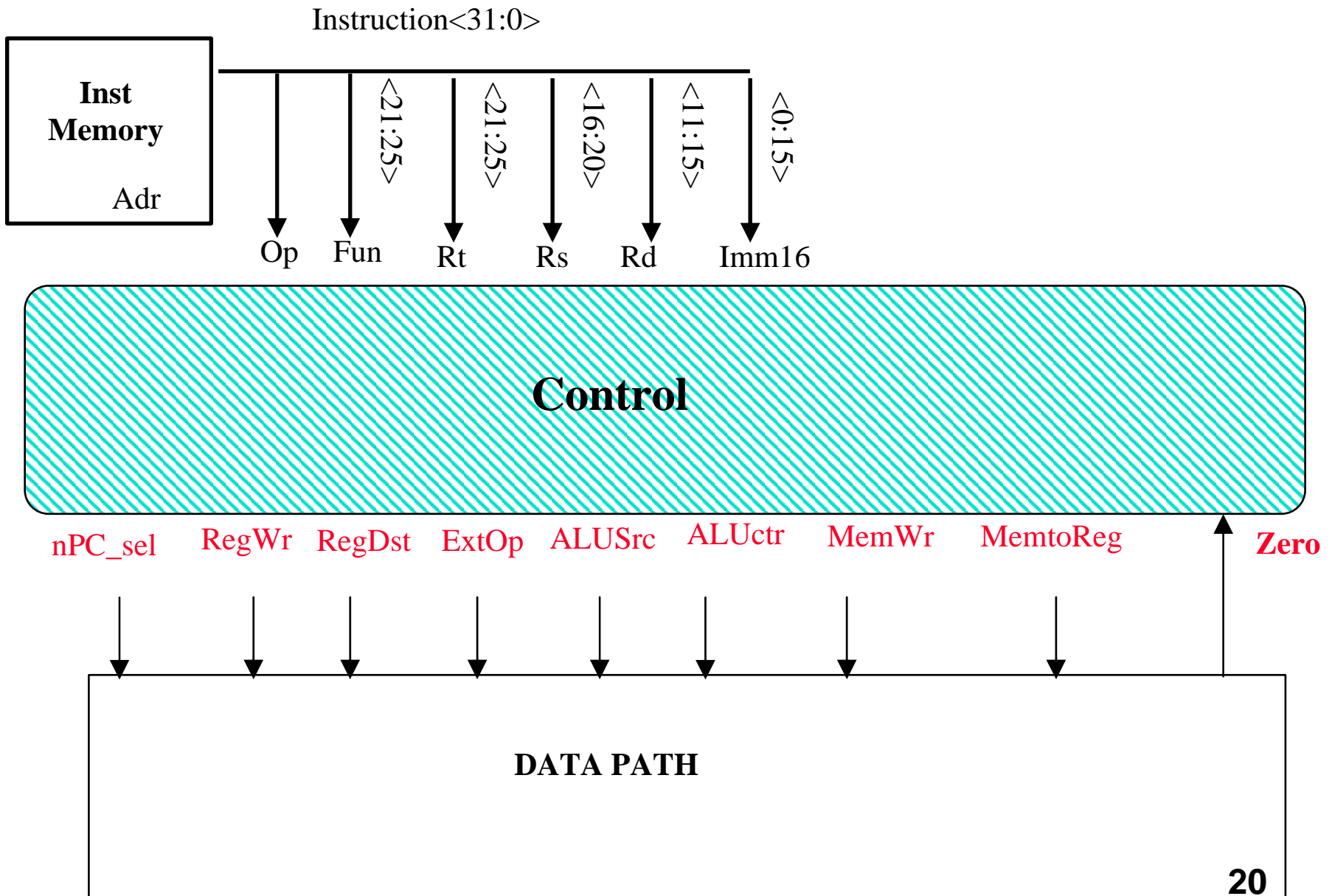
# Step 4: Given Datapath: RTL $\rightarrow$ Control



# A Summary of Control Signals

## inst      Register Transfer

**ADD**       $R[rd] \leftarrow R[rs] + R[rt];$                        $PC \leftarrow PC + 4$

*ALUsrc = RegB, ALUctr = “add”, RegDst = rd, RegWr, nPC\_sel = “+4”*

**SUB**       $R[rd] \leftarrow R[rs] - R[rt];$                        $PC \leftarrow PC + 4$

*ALUsrc = RegB, ALUctr = “sub”, RegDst = rd, RegWr, nPC\_sel = “+4”*

**ORi**       $R[rt] \leftarrow R[rs] + \text{zero\_ext}(\text{Imm16});$                        $PC \leftarrow PC + 4$

*ALUsrc = Im, Extop = “Z”, ALUctr = “or”, RegDst = rt, RegWr, nPC\_sel = “+4”*

**LOAD**       $R[rt] \leftarrow \text{MEM}[ R[rs] + \text{sign\_ext}(\text{Imm16})];$                        $PC \leftarrow PC + 4$

*ALUsrc = Im, Extop = “Sn”, ALUctr = “add”,*

*MemtoReg, RegDst = rt, RegWr,                      nPC\_sel = “+4”*

**STORE**       $\text{MEM}[ R[rs] + \text{sign\_ext}(\text{Imm16}) ] \leftarrow R[rs];$                        $PC \leftarrow PC + 4$

*ALUsrc = Im, Extop = “Sn”, ALUctr = “add”, MemWr, nPC\_sel = “+4”*


**BEQ**       $\text{if } ( R[rs] == R[rt] ) \text{ then } PC \leftarrow PC + \text{sign\_ext}(\text{Imm16}) \parallel 00 \text{ else } PC \leftarrow PC + 4$

*nPC\_sel = “Br”, ALUctr = “sub”*

# A Summary of Control Signals


See Appendix A → **func**  
 See Appendix A → **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	<b>add</b>	<b>sub</b>	<b>ori</b>	<b>lw</b>	<b>sw</b>	<b>beq</b>	<b>jump</b>
<b>RegDst</b>	1	1	0	0	x	x	x
<b>ALUSrc</b>	0	0	1	1	1	0	x
<b>MemtoReg</b>	0	0	0	1	x	x	x
<b>RegWrite</b>	1	1	1	1	0	0	0
<b>MemWrite</b>	0	0	0	0	1	0	0
<b>nPCsel</b>	0	0	0	0	0	1	0
<b>Jump</b>	0	0	0	0	0	0	1
<b>ExtOp</b>	x	x	0	1	1	x	x
<b>ALUctr&lt;2:0&gt;</b>	Add	Subtract	Or	Add	Add	Subtract	xxx

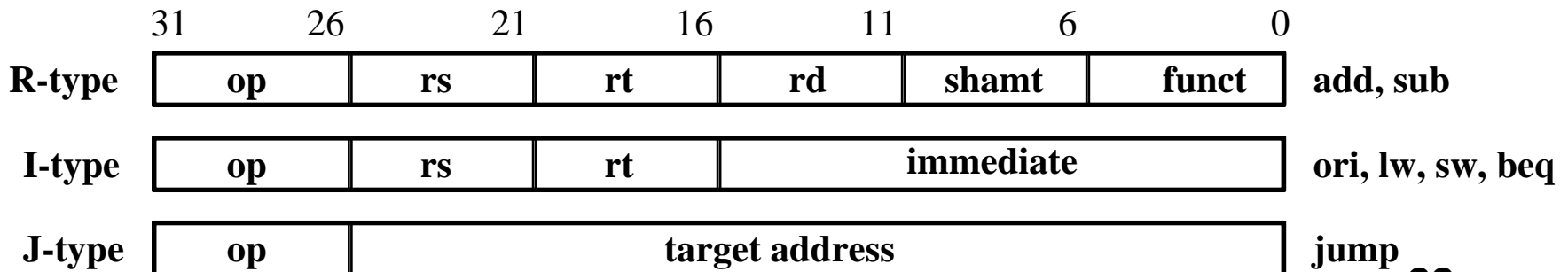


# The Concept of Local Decoding

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	<b>R-type</b>	<b>ori</b>	<b>lw</b>	<b>sw</b>	<b>beq</b>	<b>jump</b>
<b>RegDst</b>	1	0	0	x	x	x
<b>ALUSrc</b>	0	1	1	1	0	x
<b>MemtoReg</b>	0	0	1	x	x	x
<b>RegWrite</b>	1	1	1	0	0	0
<b>MemWrite</b>	0	0	0	1	0	0
<b>Branch</b>	0	0	0	0	1	0
<b>Jump</b>	0	0	0	0	0	1
<b>ExtOp</b>	x	0	1	1	x	x
<b>ALUop&lt;N:0&gt;</b>	"R-type"	Or	Add	Add	Subtract	xxx

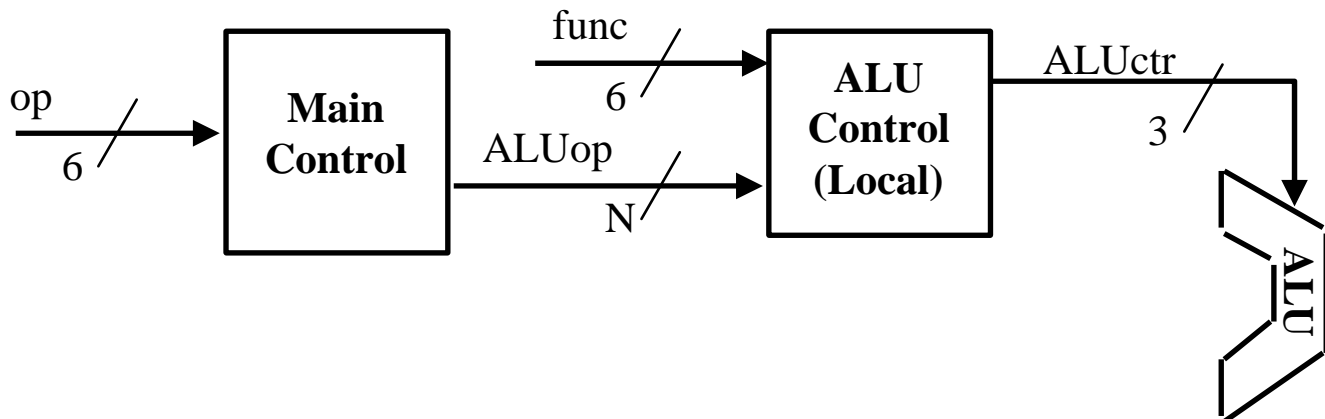

# The Encoding of ALUop

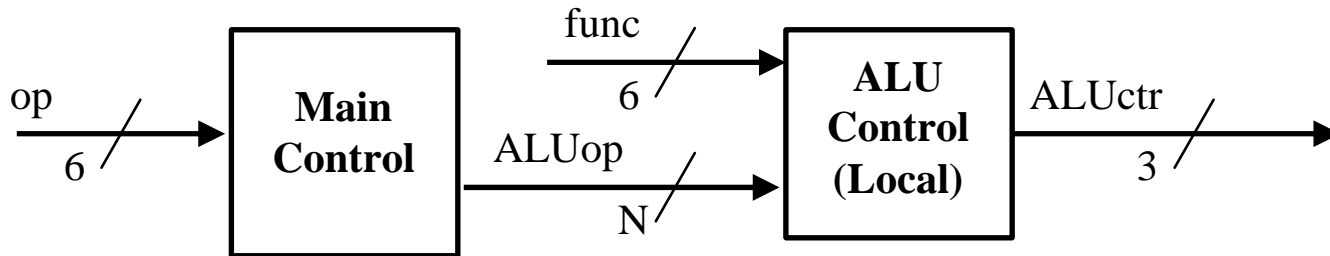


- In this exercise, ALUop has to be 2 bits wide to represent:
  - “R-type” instructions (1)
  - “I-type” instructions that require the ALU to perform:
    - (2) Or, (3) Add, and (4) Subtract
- To implement the full MIPS ISA, ALUop has to be 3 bits to represent:
  - “R-type” instructions (1)
  - “I-type” instructions that require the ALU to perform:
    - (2) Or, (3) Add, (4) Subtract, and (5) And (Example: andi)


	R-type	ori	lw	sw	beq	jump
ALUop (Symbolic)	“R-type”	Or	Add	Add	Subtract	xxx
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01	xxx



# The Decoding of the “func” Field

 


	<b>R-type</b>	<b>ori</b>	<b>lw</b>	<b>sw</b>	<b>beq</b>	<b>jump</b>
<b>ALUop (Symbolic)</b>	“R-type”	Or	Add	Add	Subtract	xxx
<b>ALUop&lt;2:0&gt;</b>	1 00	0 10	0 00	0 00	0 01	xxx

 

P. 286 text:

<b>funct&lt;5:0&gt;</b>	<b>Instruction Operation</b>
10 0000	add
10 0010	subtract
10 0100	and
10 0101	or
10 1010	set-on-less-than

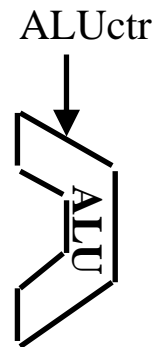

<b>ALUctr&lt;2:0&gt;</b>	<b>ALU Operation</b>
000	And
001	Or
010	Add
110	Subtract
111	Set-on-less-than

# The Truth Table for ALUctr

ALUop (Symbolic)	R-type	ori	lw	sw	beq
	"R-type"	Or	Add	Add	Subtract
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01

func<3:0>	Instruction Op.
0000	add
0010	subtract
0100	and
0101	or
1010	set-on-less-than

ALUop			func				ALU Operation	ALUctr		
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>		bit<2>	bit<1>	bit<0>
0	0	0	x	x	x	x	Add	0	1	0
0	x	1	x	x	x	x	Subtract	1	1	0
0	1	x	x	x	x	x	Or	0	0	1
1	x	x	0	0	0	0	Add	0	1	0
1	x	x	0	0	1	0	Subtract	1	1	0
1	x	x	0	1	0	0	And	0	0	0
1	x	x	0	1	0	1	Or	0	0	1
1	x	x	1	0	1	0	Set on <	1	1	1

# The Logic Equation for ALUctr<2>

ALUop			func				ALUctr<2>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	x	1	x	x	x	x	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

This makes func<3> a don't care

- $ALUctr<2> = !ALUop<2> \& ALUop<0> + ALUop<2> \& !func<2> \& func<1> \& !func<0>$

# The Logic Equation for ALUctr<1>

ALUop			func				ALUctr<1>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	0	0	x	x	x	x	1
0	x	1	x	x	x	x	1
1	x	x	0	0	0	0	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

- $ALUctr<1> = !ALUop<2> \& !ALUop<0> + ALUop<2> \& !func<2> \& !func<0>$

# The Logic Equation for ALUctr<0>

ALUop			func				ALUctr<0>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	1	x	x	x	x	x	1
1	x	x	0	1	0	1	1
1	x	x	1	0	1	0	1

- $ALUctr<0> = !ALUop<2> \& ALUop<0>$   
+  $ALUop<2> \& !func<3> \& func<2> \& !func<1> \& func<0>$   
+  $ALUop<2> \& func<3> \& !func<2> \& func<1> \& !func<0>$



# Step 5: Logic for Each Control Signal


- **nPC\_sel**      <= if (OP == BEQ) then “Br” else “+4”
- **ALUsrc**      <= if (OP == “Rtype”) then “regB” else “immed”
- **ALUctr**      <= if (OP == “Rtype”) then funct  
                  elseif (OP == ORi) then “OR”  
                  elseif (OP == BEQ) then “sub”  
                  else “add”
  
- **ExtOp**        <= \_\_\_\_\_
- **MemWr**        <= \_\_\_\_\_
- **MemtoReg**    <= \_\_\_\_\_
- **RegWr:**        <= \_\_\_\_\_
- **RegDst:**      <= \_\_\_\_\_

# Step 5: Logic for each control signal

- **nPC\_sel**       $\leq$  if (OP == BEQ) then “Br” else “+4”
- **ALUsrc**       $\leq$  if (OP == “Rtype”) then “regB” else “immed”
- **ALUctr**       $\leq$  if (OP == “Rtype”) then funct  
                              elseif (OP == ORi) then “OR”  
                              elseif (OP == BEQ) then “sub”  
                              else “add”
- **ExtOp**         $\leq$  if (OP == ORi) then “zero” else “sign”
- **MemWr**         $\leq$  (OP == Store)
- **MemtoReg**     $\leq$  (OP == Load)
- **RegWr:**         $\leq$  if ((OP == Store) || (OP == BEQ)) then 0 else 1
- **RegDst:**       $\leq$  if ((OP == Load) || (OP == ORi)) then 0 else 1





# The “Truth Table” for the Main Control

 


op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	<b>R-type</b>	<b>ori</b>	<b>lw</b>	<b>sw</b>	<b>beq</b>	<b>jump</b>
<b>RegDst</b>	1	0	0	x	x	x
<b>ALUSrc</b>	0	1	1	1	0	x
<b>MemtoReg</b>	0	0	1	x	x	x
<b><u>RegWrite</u></b>	<u>1</u>	<u>1</u>	<u>1</u>	<u>0</u>	<u>0</u>	<u>0</u>
<b>MemWrite</b>	0	0	0	1	0	0
<b>nPC_sel</b>	0	0	0	0	1	0
<b>Jump</b>	0	0	0	0	0	1
<b>ExtOp</b>	x	0	1	1	x	x
<b>ALUOp (Symbolic)</b>	“R-type”	Or	Add	Add	Subtract	xxx
<b>ALUOp &lt;2&gt;</b>	1	0	0	0	0	x
<b>ALUOp &lt;1&gt;</b>	0	1	0	0	0	x
<b>ALUOp &lt;0&gt;</b>	0	0	0	0	1	x

# A Real MIPS Datapath (CNS T0)

 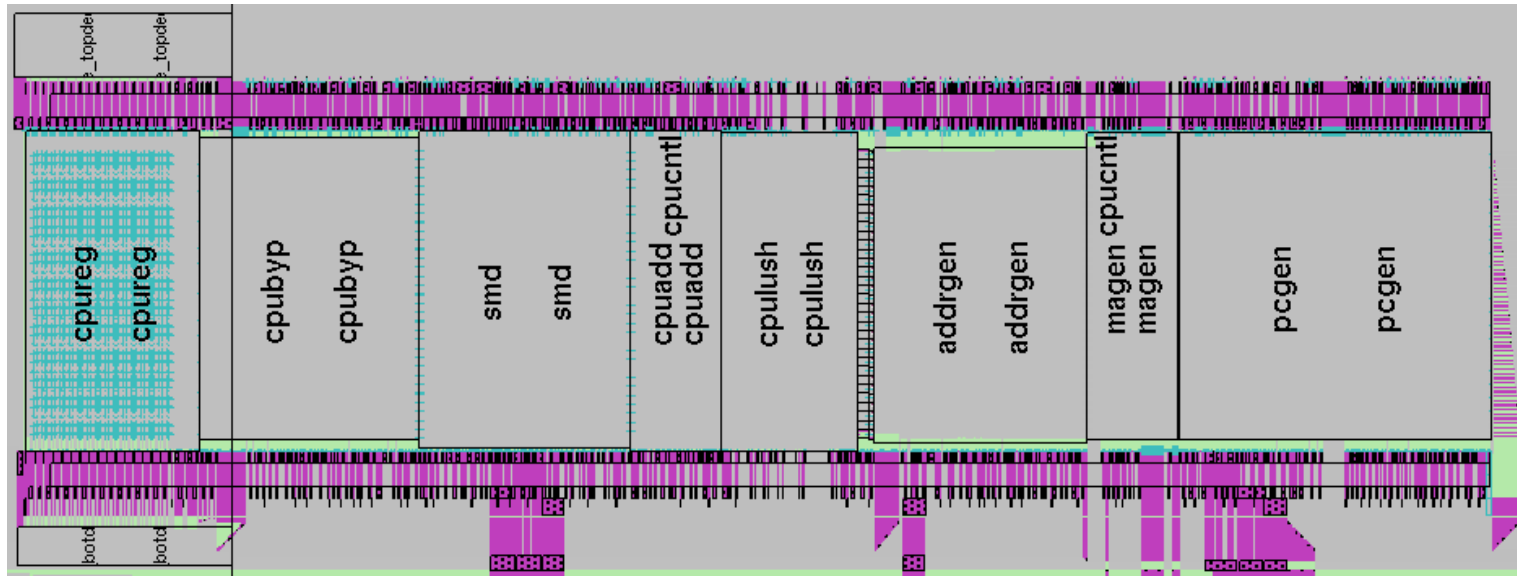


# Summary: A Single Cycle Processor

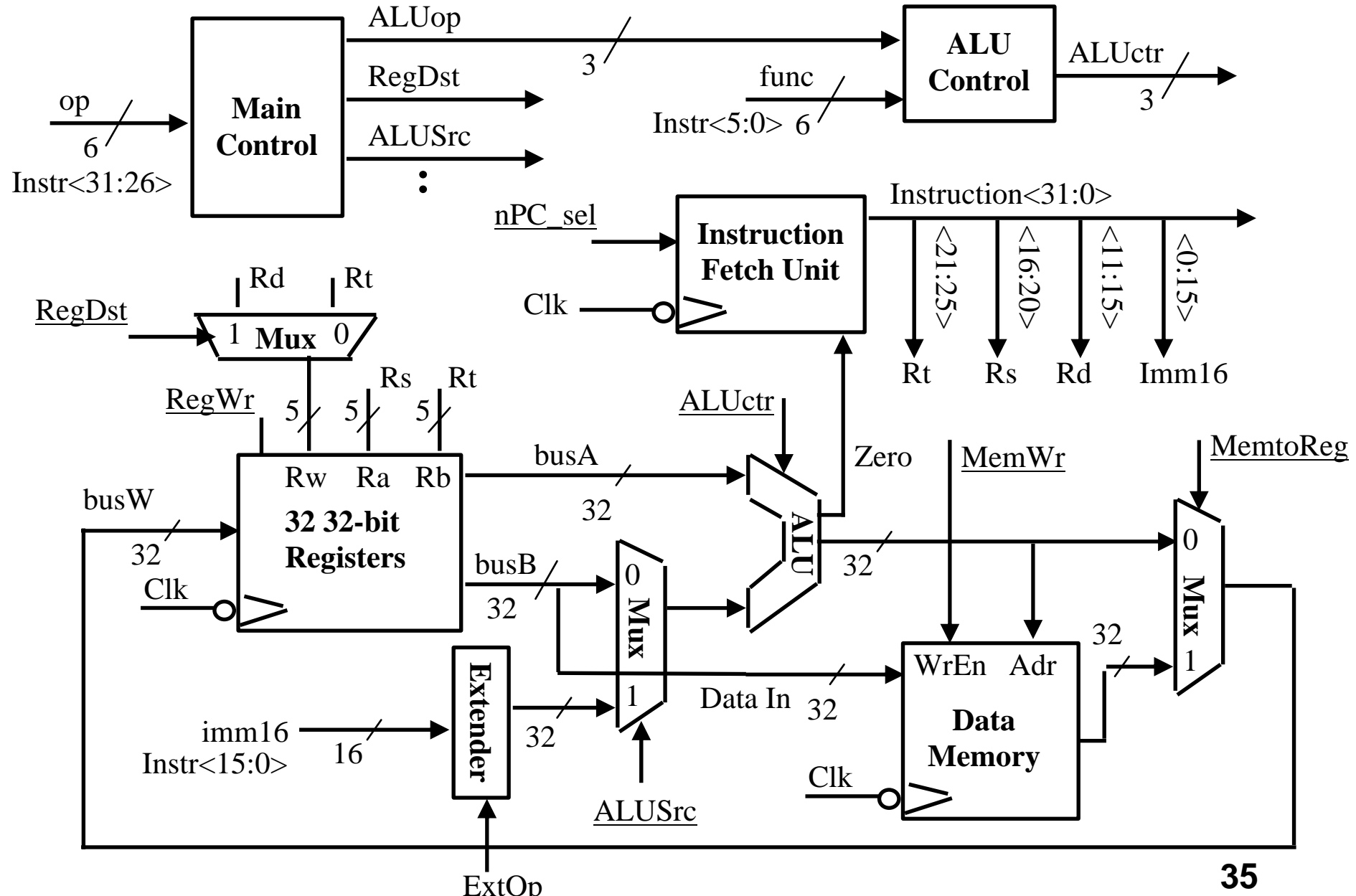
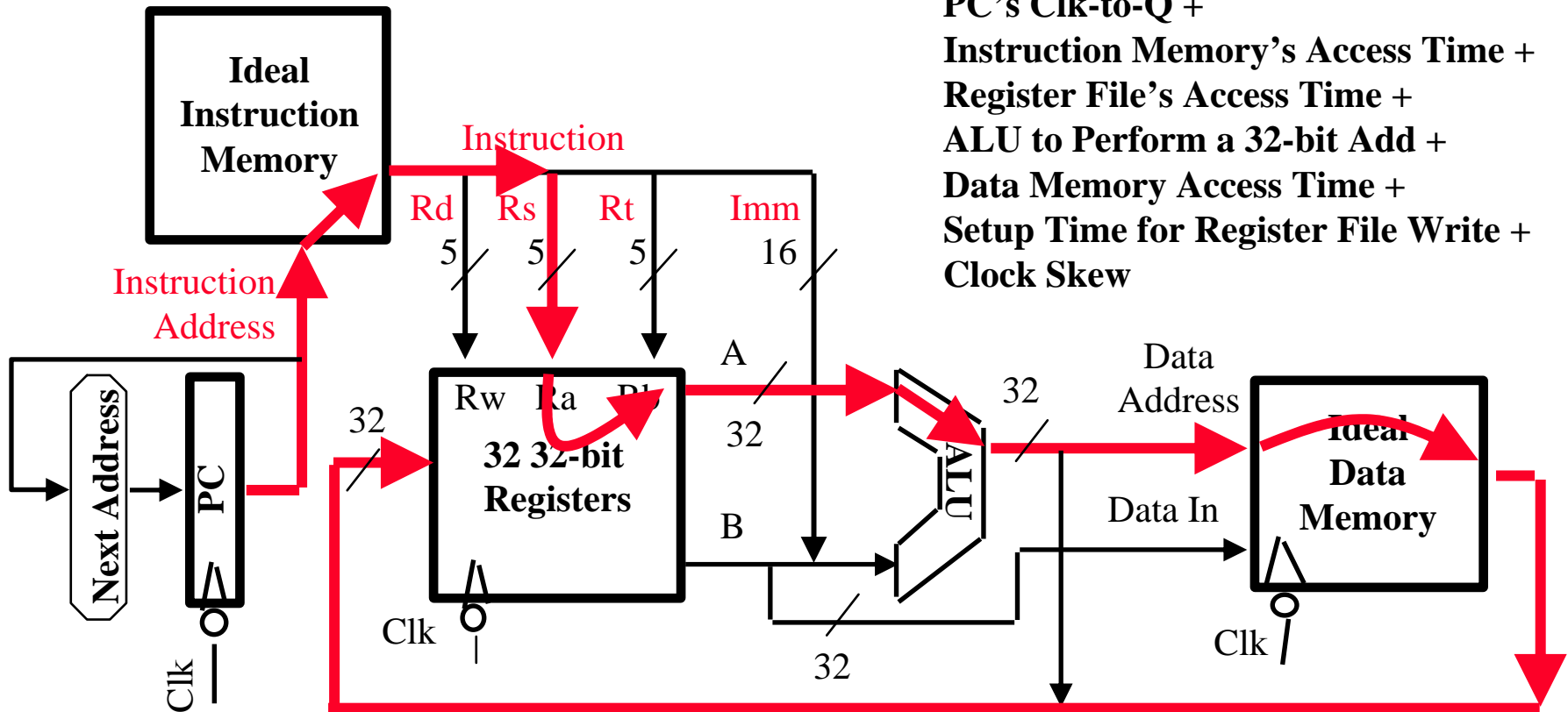
# Recap: An Abstract View of the Critical Path (Load)


- **Register file and ideal memory:**

- The CLK input is a factor ONLY during write operation
- During read operation, behave as combinational logic:
  - Address valid → Output valid after “access time.”



**Critical Path (Load Operation) =**  
PC's Clk-to-Q +  
Instruction Memory's Access Time +  
Register File's Access Time +  
ALU to Perform a 32-bit Add +  
Data Memory Access Time +  
Setup Time for Register File Write +  
Clock Skew

# Worst Case Timing (Load)

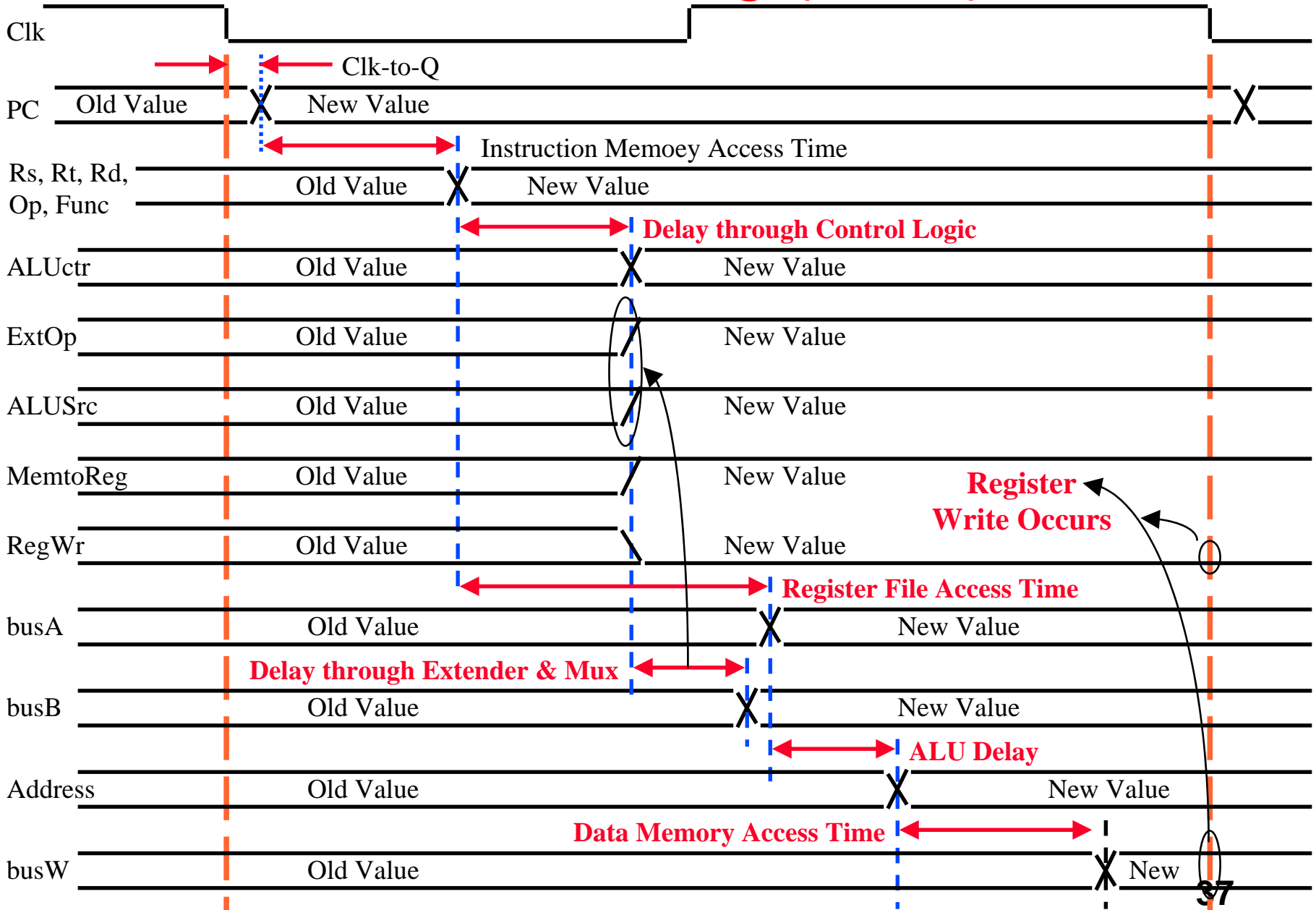

# Drawback of this Single Cycle Processor

- **Long cycle time:**
  - Cycle time must be long enough for the load instruction:  
**PC's Clock -to-Q +**  
**Instruction Memory Access Time +**  
**Register File Access Time +**  
**ALU Delay (address calculation) +**  
**Data Memory Access Time +**  
**Register File Setup Time +**  
**Clock Skew**
- **Cycle time for load is much longer than needed for all other instructions**

# Summary

- **Single cycle datapath: CPI = 1, CCT → long**
- **5 steps to design a processor**
  - 1. Analyze instruction set => datapath requirements
  - 2. Select set of datapath components & establish clock methodology
  - 3. Assemble datapath meeting the requirements
  - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
  - 5. Assemble the control logic

◦ **Control is the hard part**

◦ **MIPS makes control easier**

- Instructions same size
- Source registers always in same place
- Immediates same size, location
- Operations always on registers/immediates

