

Computer Architecture


Processor Design - 1

Outline of These Slides


- **Overview**
- **Design a processor: step-by-step**
- **Requirements of the instruction set**
- **Components and clocking**
- **Assembling an adequate Data path**
- **Controlling the data path**

The Big Picture: Where Are We Now?

 - The five classic components of a computer



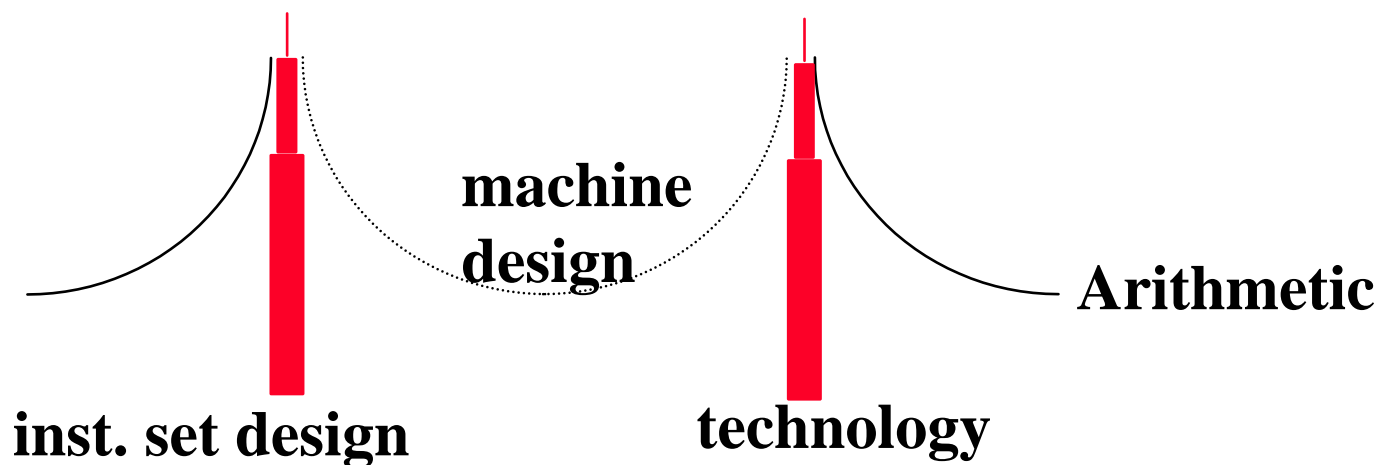- Today's topic: design a single cycle processor



The CPU

° **Processor (CPU)**: the active part of the computer, which does all the work (data manipulation and decision-making)


° **Datapath**: portion of the processor which contains hardware necessary to perform operations required by the processor (the brawn)

° **Control**: portion of the processor (also in hardware) which tells the datapath what needs to be done (the brain)

Big Picture: The Performance Perspective

- **Performance of a machine is determined by:**

 - Instruction count
- Clock cycle time
- Clock cycles per instruction



- **Processor design (datapath and control) will determine:**

- Clock cycle time
- Clock cycles per instruction

- **What we will do Today:**

- Single cycle processor:
 - **Advantage: One clock cycle per instruction**
 - **Disadvantage: long cycle time**


How to Design a Processor: Step-by-step

- **1. Analyze instruction set → datapath requirements**
 - the meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - possibly more
 - datapath must support each register transfer
- **2. Select set of datapath components and establish clocking methodology**
- **3. Assemble datapath meeting the requirements**
- **4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- **5. Assemble the control logic**


The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. The three instruction formats:


– R-type

 

– I-type

 

– J-type

 


- The different fields are:

- op: operation of the instruction
- rs, rt, rd: the source and destination register specifiers
- shamt: shift amount
- funct: selects the variant of the operation in the “op” field
- address / immediate: address offset or immediate value
- target address: target address of the jump instruction

Step 1a: The MIPS-lite Subset for Today

- **ADD and SUB**

 


- addU rd, rs, rt

- subU rd, rs, rt

- **OR Immediate:**


- ori rt, rs, imm16

 

- **LOAD / STORE Word**


- lw rt, rs, imm16

- sw rt, rs, imm16

 

- **BRANCH:**

- beq rs, rt, imm16

 

Logical Register Transfers

- Register Transfer Logic gives the meaning of the instructions
- All start by fetching the instruction

op | rs | rt | rd | shamt | funct = MEM[PC]

op | rs | rt | Imm16 = MEM[PC]

inst Register Transfers

ADDU $R[rd] \leftarrow R[rs] + R[rt]; \quad PC \leftarrow PC + 4$

SUBU $R[rd] \leftarrow R[rs] - R[rt]; \quad PC \leftarrow PC + 4$

ORi $R[rt] \leftarrow R[rs] | \text{zero_ext}(\text{Imm16}); \quad PC \leftarrow PC + 4$

LOAD $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})]; \quad PC \leftarrow PC + 4$

STORE $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rt]; \quad PC \leftarrow PC + 4$

BEQ if ($R[rs] == R[rt]$) then $PC \leftarrow PC + 4 + \text{sign_ext}(\text{Imm16})$ || 00
else $PC \leftarrow PC + 4$

Step 1: Requirements of the Instruction Set


- **Memory**
 - instruction & data
- **Registers (32 x 32)**
 - read RS
 - read RT
 - Write RT or RD
- **PC**
- **Extender**
- **Add and Sub register or extended immediate**
- **Add 4 or extended immediate to PC**

Step 2: Components of the Datapath


- **Combinational Elements**
- **Storage Elements**
 - Clocking methodology

Combinational Logic Elements (Basic Building Blocks)


- Adder

 

- MUX

 

- ALU

 

Storage Element: Register File

- **Register File consists of 32 registers:**

- Two 32-bit output busses:

busA and busB


- One 32-bit input bus: busW

- **Register is selected by:**

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- **Clock input (CLK)**

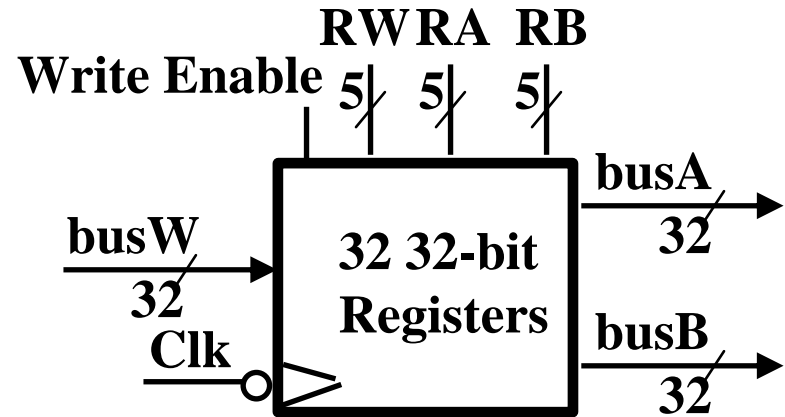- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - RA or RB valid → busA or busB valid after “access time.”



Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: Data In
- One output bus: Data Out

- **Memory word is selected by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus

- **Clock input (CLK)**

 - The CLK input is a factor ONLY during **write** operation
- During read operation, behaves as a **combinational logic block**:
 - Address valid → Data Out valid after “access time.”



Memory Hierarchy (Ch. 7)


- Want a single main memory, both large and fast
- **Problem 1:** large memories are **slow** while fast memories are **small**
 - Example: MIPS registers (fast, but few)
- **Solution:** mix of memories provides illusion of single large, fast memory
 - Cache: a small, fast memory; Holds a copy of part of a larger, slower memory
 - Imem, Dmem are really separate **caches memories**

Digression: Sequential Logic, Clocking

- **Combinational circuits: no memory**
 - Output depends only on the inputs
- **Sequential circuits: have memory**
 - How to ensure memory element is updated neither too soon, nor too late?
 - Recall hardware multiplier
 - Product/multiplier register is the writable memory element
 - Gate propagation delay means ALU result takes time to stabilize; Delay varies with inputs
 - Must wait until result stable before write to product/multiplier register else get garbage
 - How to be certain ALU output is stable?

Adding a Clock to a Circuit

 
- **Clock: free running signal with fixed *cycle time (clock period)***





- **Clock determines *when* to write memory element**
 - **level-triggered - store clock high (low)**
 - **edge-triggered - store only on clock edge**
- **We will use negative (falling) edge-triggered methodology**

Role of Clock in MIPS Processors

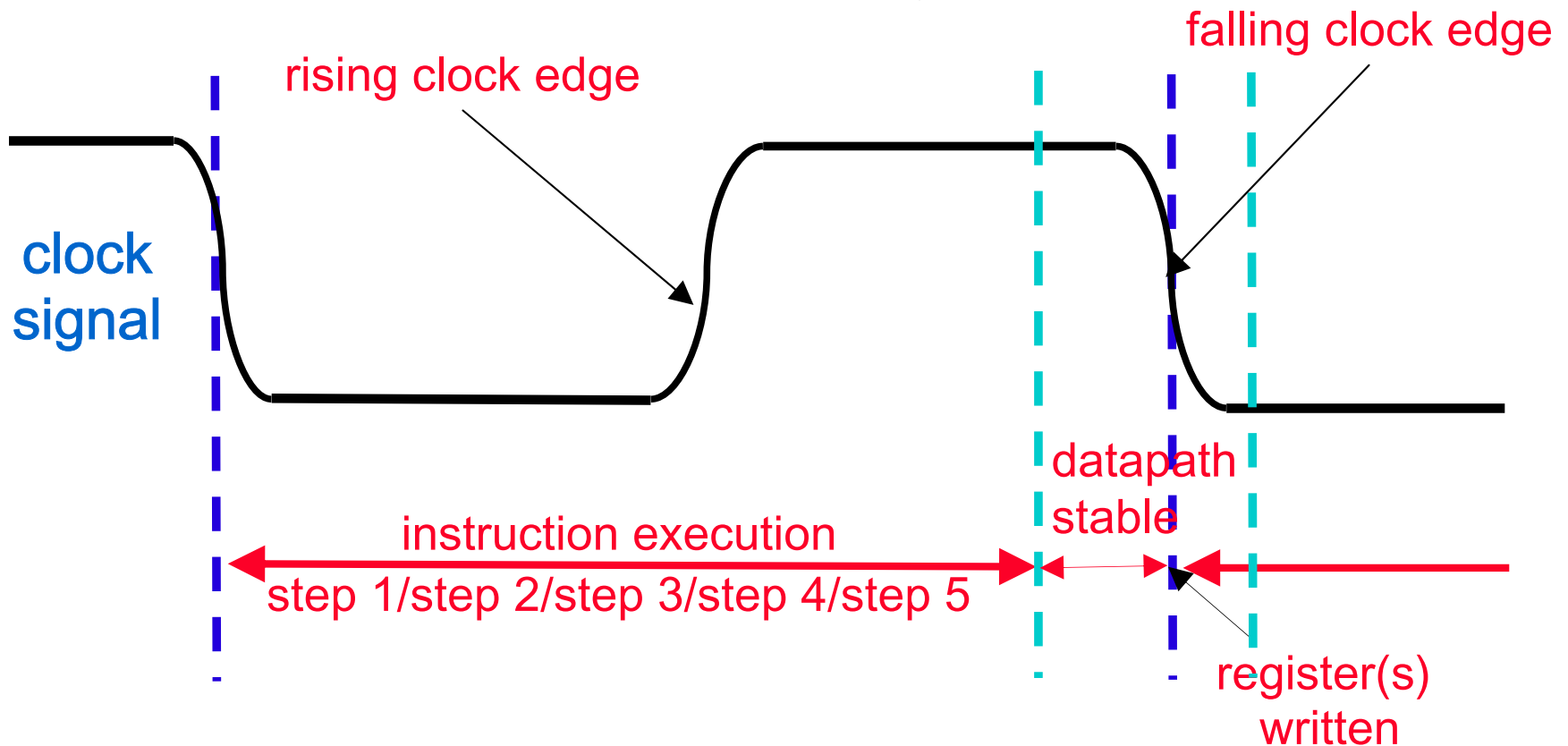- single-cycle machine: does everything in one clock cycle
 - instruction execution = up to 5 steps
 - must complete 5th step *before* cycle ends





SR-Latches

  

- **Symbol for SR-Latch with NOR gates**


SR-Latches

 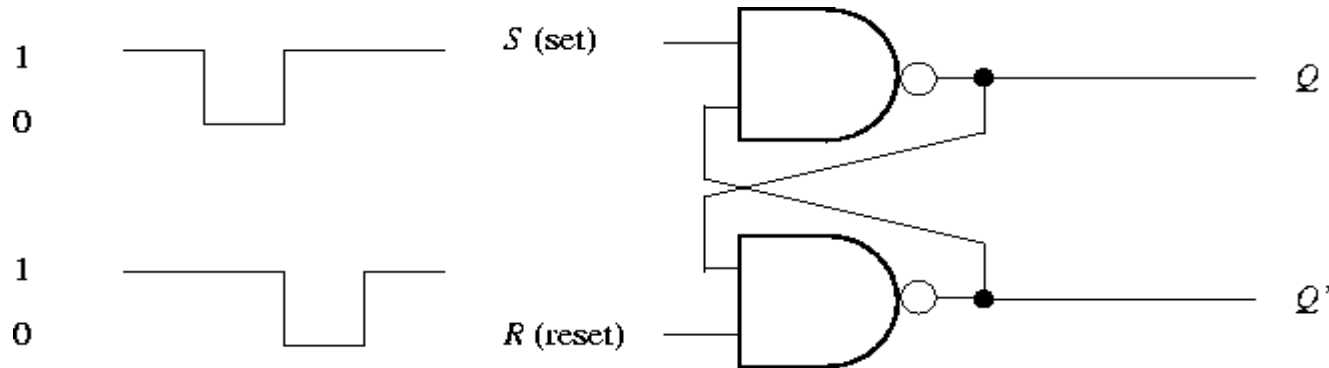- SR-latch with NAND Gates, also known as $S'R'$ -latch
- $S = 0$ and $R = 0$ not allowed





- Symbol for SR-Latch with NAND gates

SR-Latches with Control Input

 

- $C = 0$, no change of state;
- $C = 1$, change is allowed;
 - If $S = 1$ and $R = 1$, Q and Q' are Indetermined


D-Latches

  


- **$C = 0$, no change of state;**
 - $Q(t + \delta t) = Q(t)$
- **$C = 1$, change is allowed;**
 - $Q(t + \delta t) = D(t)$
 - **No Indetermined Output**

Master-Slave Flip-Flop

- Negative-edge triggered D-Flip Flop

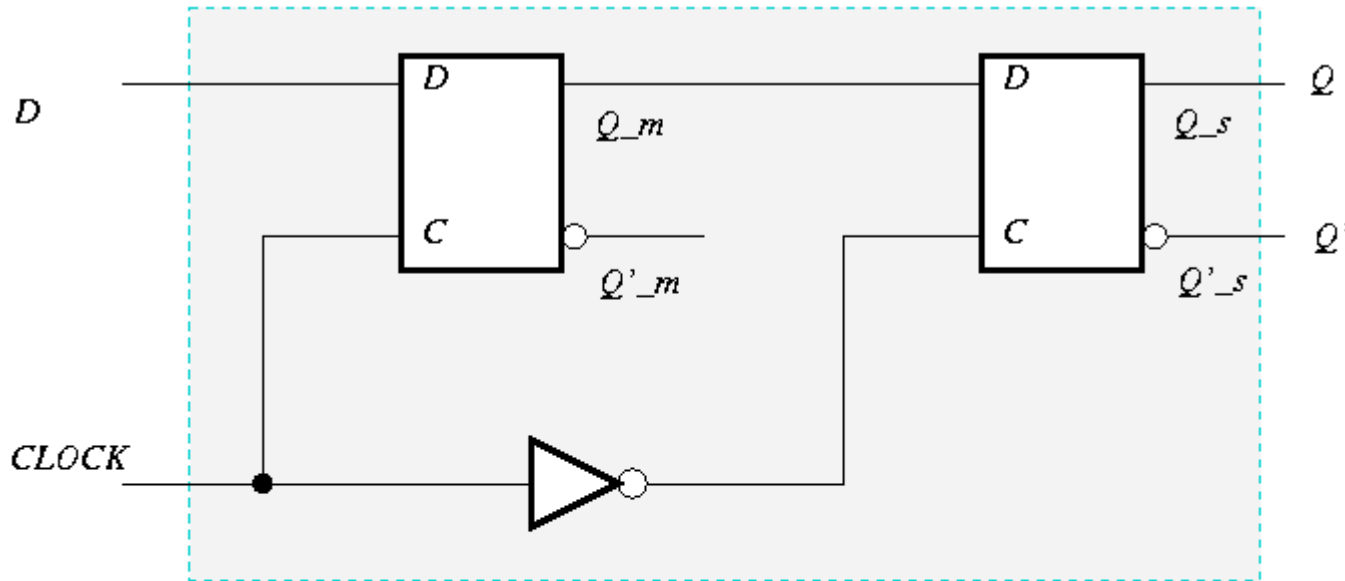


- **Symbol for D-Flip Flop.**

 

- **Arrowhead (>) indicates an edge-triggered sequential circuit.**

- **Bubble means that triggering is effective during the High→Low C transition**

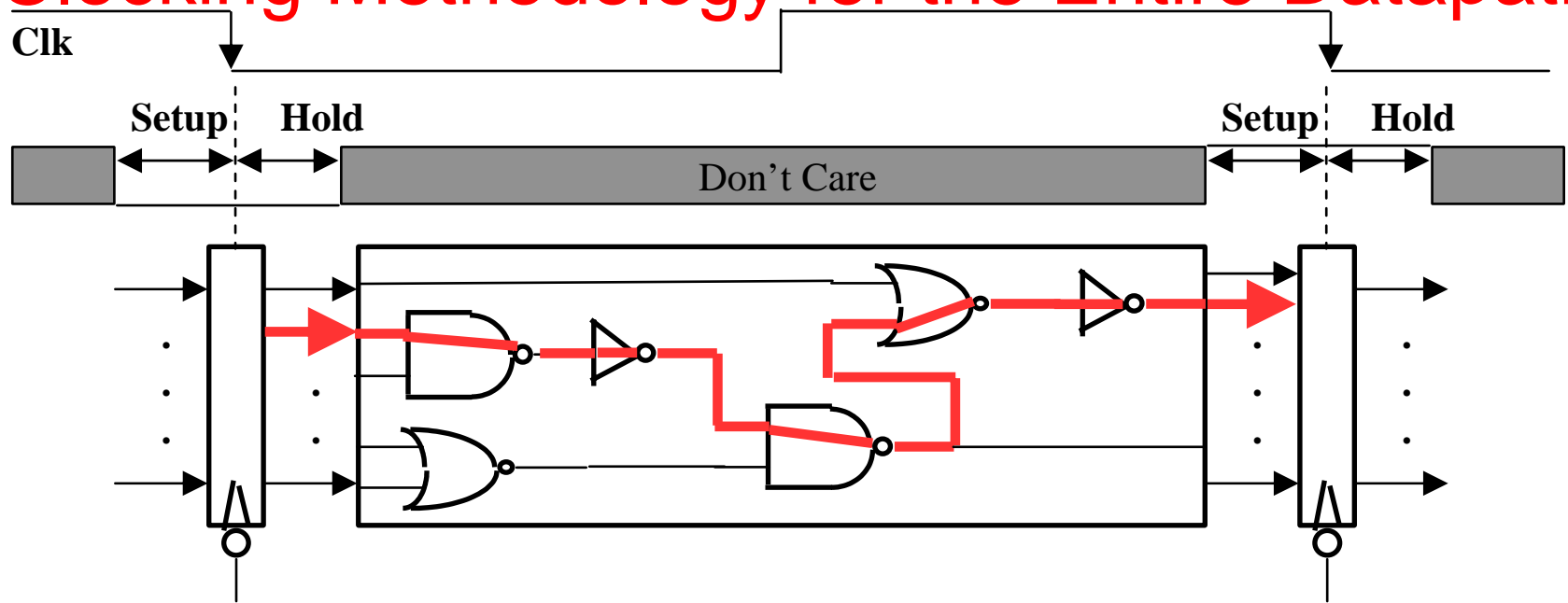Clocking Methodology for the Entire Datapath



- **Design/synthesis based on *pulsed-sequential circuits***
 - *All combinational inputs remain at constant levels and only clock signal appears as a pulse with a fixed period T_{cc}*
- **All storage elements are clocked by the same clock edge**
- **Cycle time $T_{cc} = \text{CLK-to-q} + \text{longest delay path} + \text{Setup time} + \text{clock skew}$**
- **$(\text{CLK-to-q} + \text{shortest delay path} - \text{clock skew}) > \text{hold time}$**

Step 3: Assemble Data Path Meeting Requirements

- Register Transfer Requirements
⇒ Datapath “Assembly”
- Instruction Fetch
- Read Operands and Execute Operation

Stages of the Datapath (1/6)

Problem: a single, atomic block which “executes an instruction” (performs all necessary operations beginning with fetching the instruction) would be too bulky and inefficient

Solution: break up the process of “executing an instruction” into stages, and then connect the stages to create the whole datapath

- **Smaller stages are easier to design**
- **Easy to optimize (change) one stage without touching the others**

Stages of the Datapath (2/6)

There is a *wide* variety of MIPS instructions: so what general steps do they have in common?

Stage 1: instruction fetch

- No matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
- Also, this is where we **increment PC** (that is, $PC = PC + 4$, to point to the next instruction: byte addressing so + 4)

Stages of the Datapath (3/6)

Stage 2: Instruction Decode

- upon fetching the instruction, we next gather data from the fields (*decode* all necessary instruction data)
- first, read the Opcode to determine instruction type and field lengths
- second, read in data from all necessary registers
 - for add, read two registers
 - for addi, read one register
 - for jal, no reads necessary

Stages of the Datapath (4/6)

° Stage 3: *ALU* (Arithmetic-Logic Unit)

- ***the real work of most instructions is done here: arithmetic (+, -, *, /), shifting, logic (&, |), comparisons (slt)***

- ***what about loads and stores?***

 - ***lw \$t0, 40(\$t1)***

 - ***the address we are accessing in memory = the value in \$t1 + the value 40***

 - ***so we do this addition in this stage***

Stages of the Datapath (5/6)

° Stage 4: Memory Access


- actually only the load and store instructions do anything during this stage; the others remain idle
- since these instructions have a unique step, we need this extra stage to account for them
- as a result of the cache system, this stage is expected to be just as fast (on average) as the others

Stages of the Datapath (6/6)

° Stage 5: Register Write

- most instructions write the result of some computation into a register
- examples: arithmetic, logical, shifts, loads, slt
- what about stores, branches, jumps?
 - don't write anything into a register at the end
 - these remain idle during this fifth stage

Generic Steps: Datapath

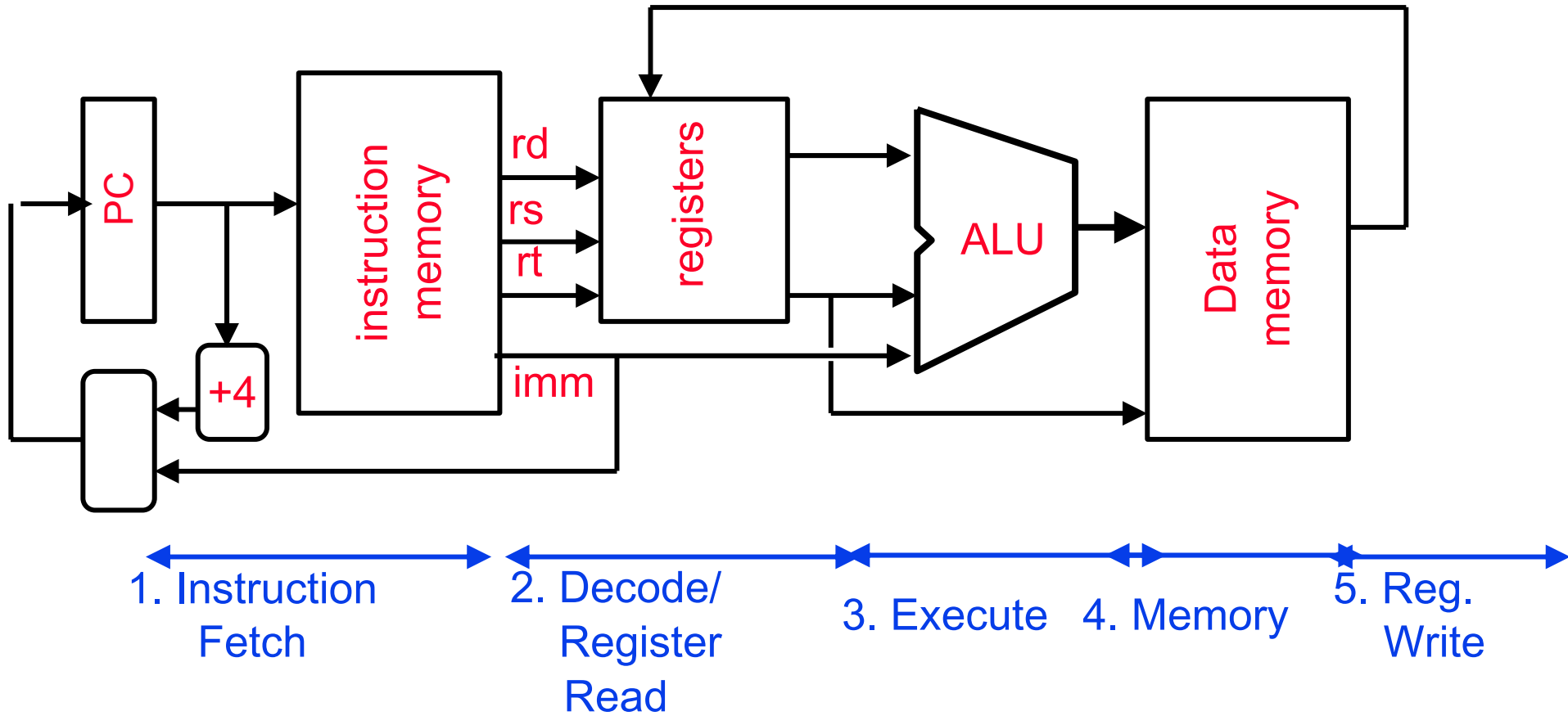


Datapath Walkthroughs (1/3)

`add $r3, $r1, $r2 # r3 = r1+r2`

- Stage 1: fetch this instruction, incr. PC ;
- Stage 2: decode to find it's an `add`, then read registers `$r1` and `$r2` ;
- Stage 3: add the two values retrieved in Stage 2 ;
- Stage 4: idle (nothing to write to memory) ;
- Stage 5: write result of Stage 3 into register `$r3` ;

Example: add Instruction

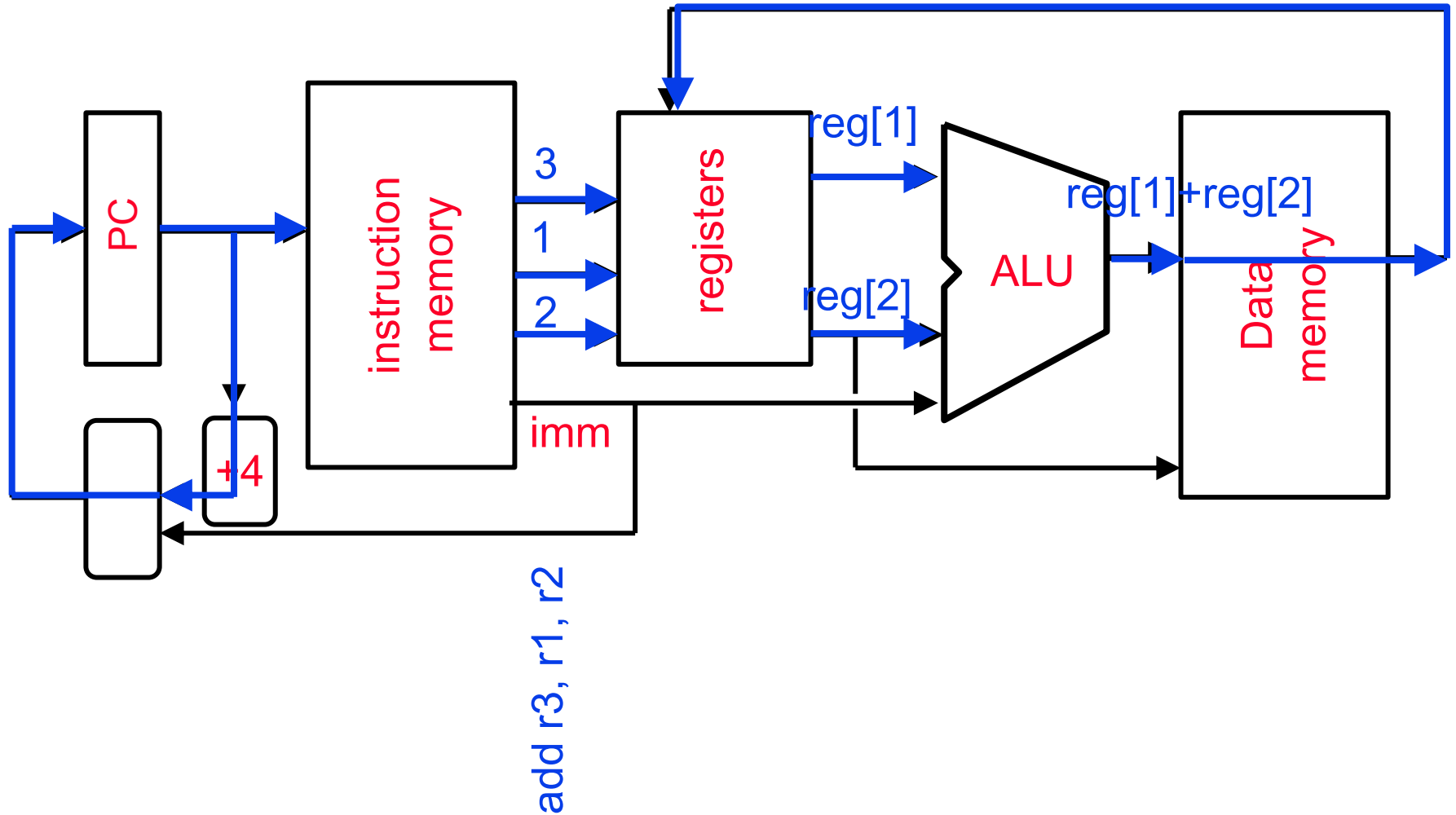


Datapath Walkthroughs (2/3)

slt **i** **\$r3, \$r1, 17**

- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's an `slt`, then read register `$r1`
- Stage 3: compare value retrieved in Stage 2 with the integer 17
- Stage 4: go idle
- Stage 5: write the result of Stage 3 in register `$r3`

Example: slti Instruction

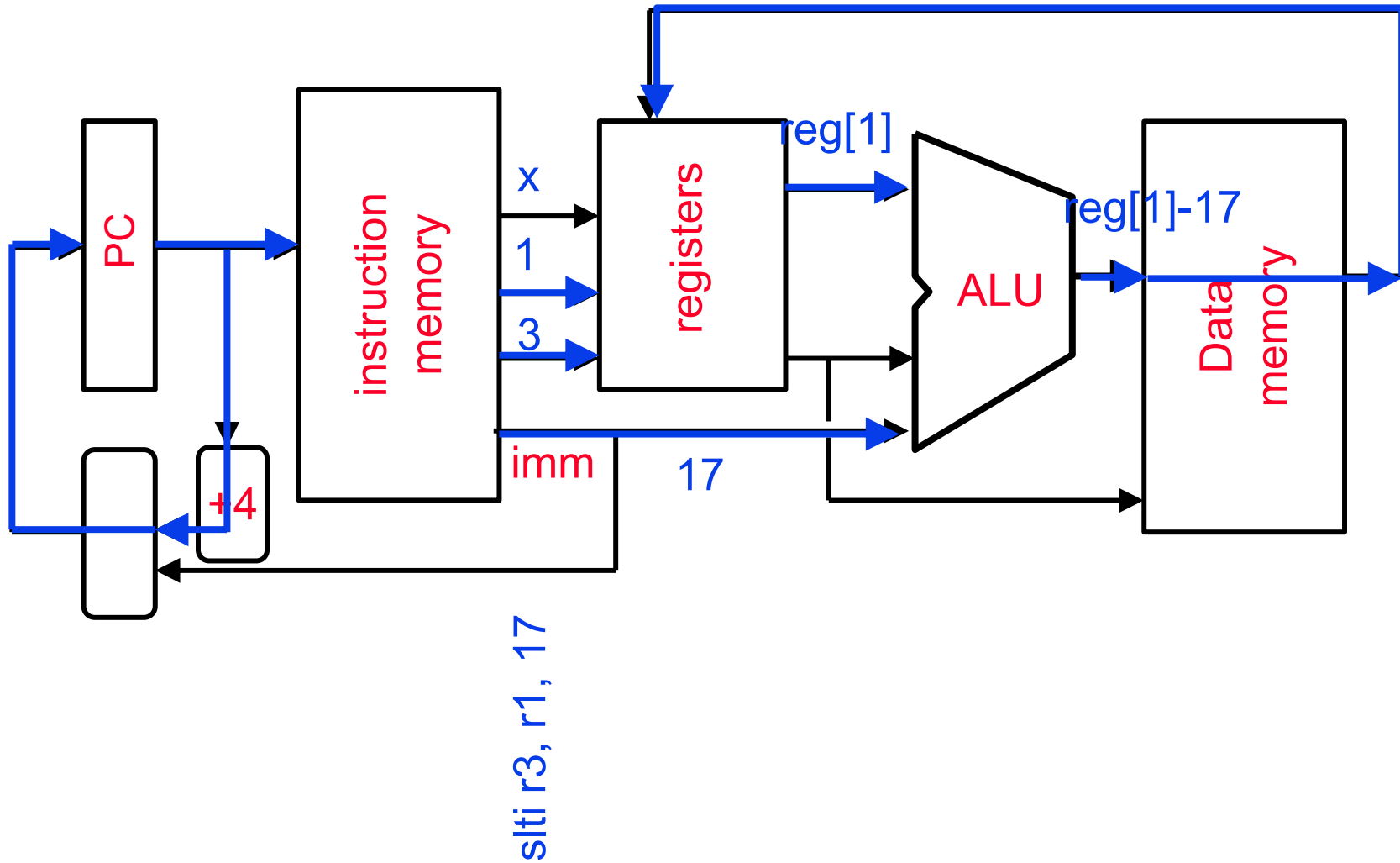


Datapath Walkthroughs (3/3)

sw **\$r3, 17(\$r1)**

- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's a sw, then read registers \$r1 and \$r3
- Stage 3: add 17 to value in register \$r1 (retrieved in Stage 2)
- Stage 4: write value in register \$r3 (retrieved in Stage 2) into memory address computed in Stage 3
- Stage 5: go idle (nothing to write into a register)

Example: `sw` Instruction

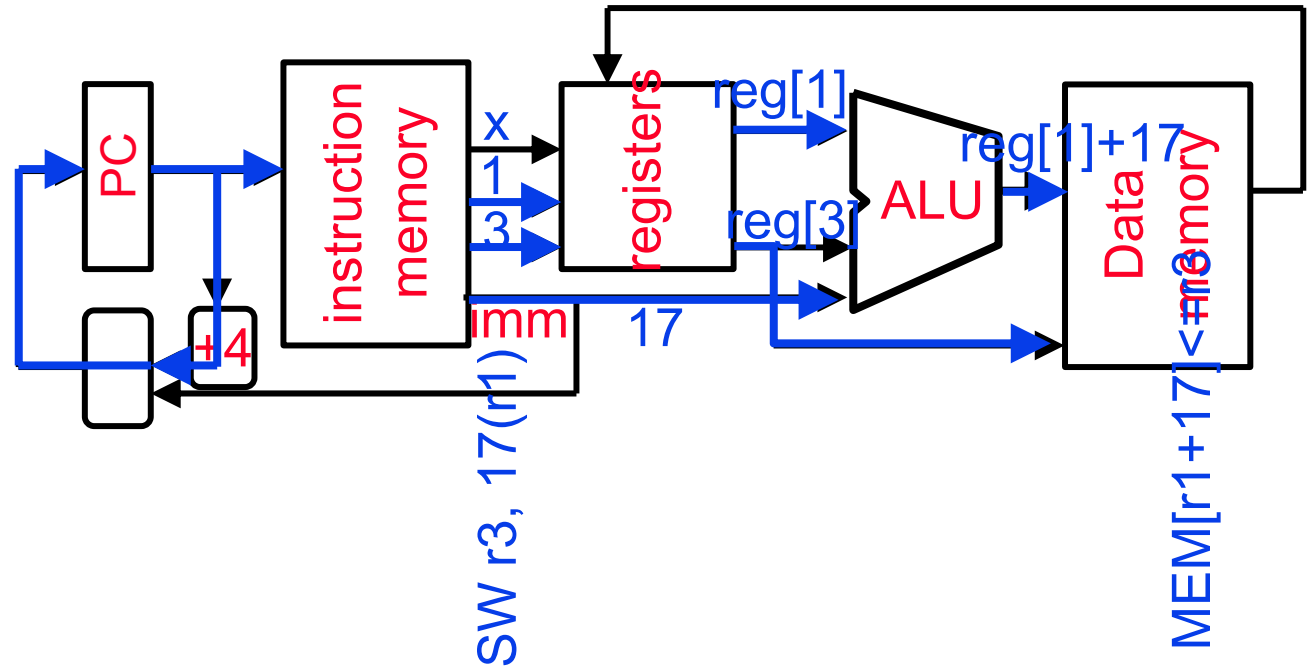

Why Five Stages? (1/2)

Could we have a different number of stages?

Yes, and other architectures do

So why does MIPS have five if instructions tend to go idle for at least one stage?


There is one instruction that uses all five stages: the load

Why Five Stages? (2/2)

lw \$r3, 17(\$r1)


- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's a lw, then read register \$r1
- Stage 3: add 17 to value in register \$r1 (retrieved in Stage 2)
- Stage 4: read value from memory address compute in Stage 3
- **Stage 5:** write value found in Stage 4 into register \$r3

Example: lw Instruction

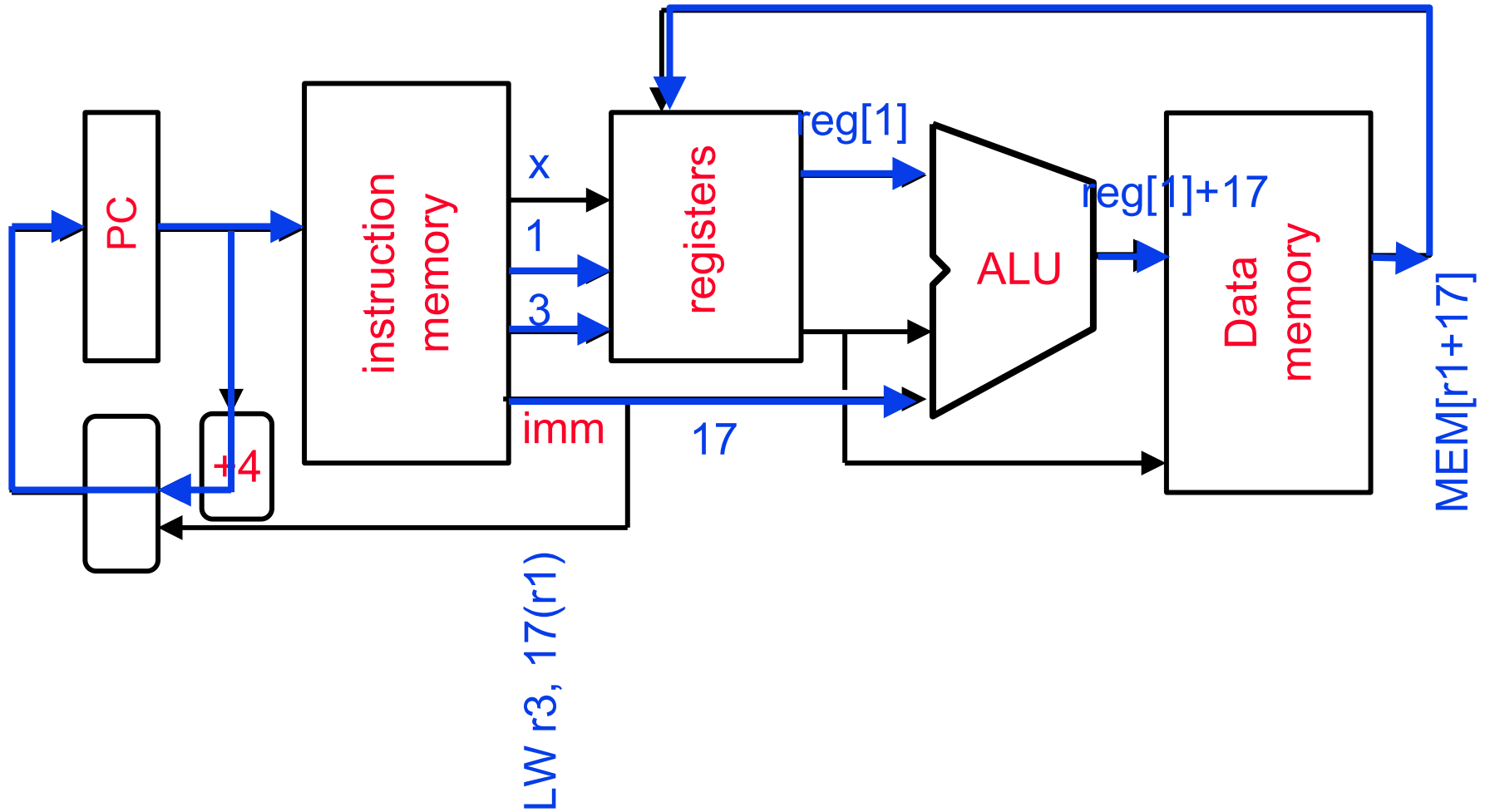

Datapath Summary

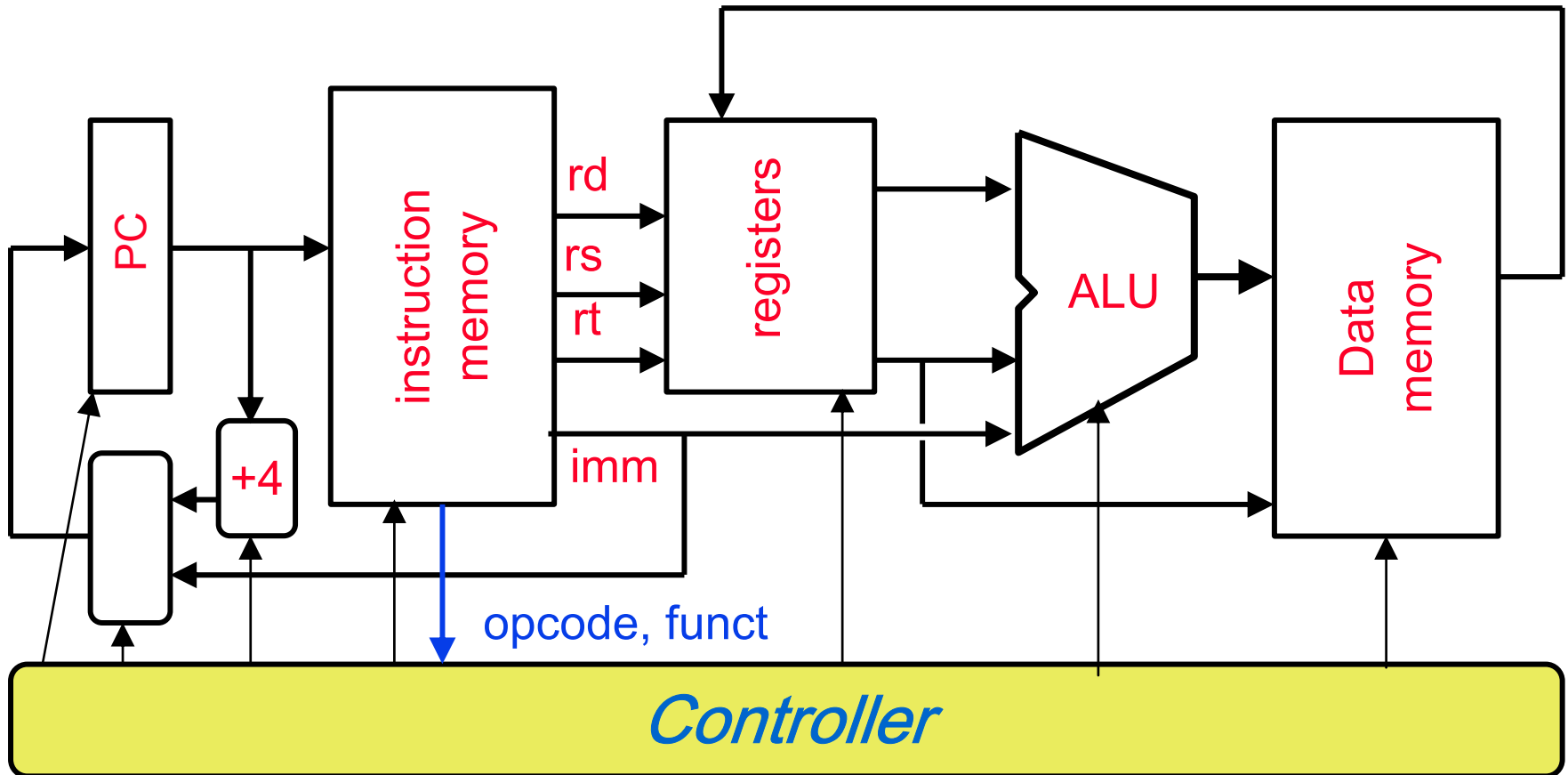- °The datapath based on data transfers required to perform instructions
- °A controller causes the right transfers to happen



Overview of the Instruction Fetch Unit


- **The common operations**

- Fetch the Instruction: $\text{mem}[\text{PC}]$

- Update the program counter:

- Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$


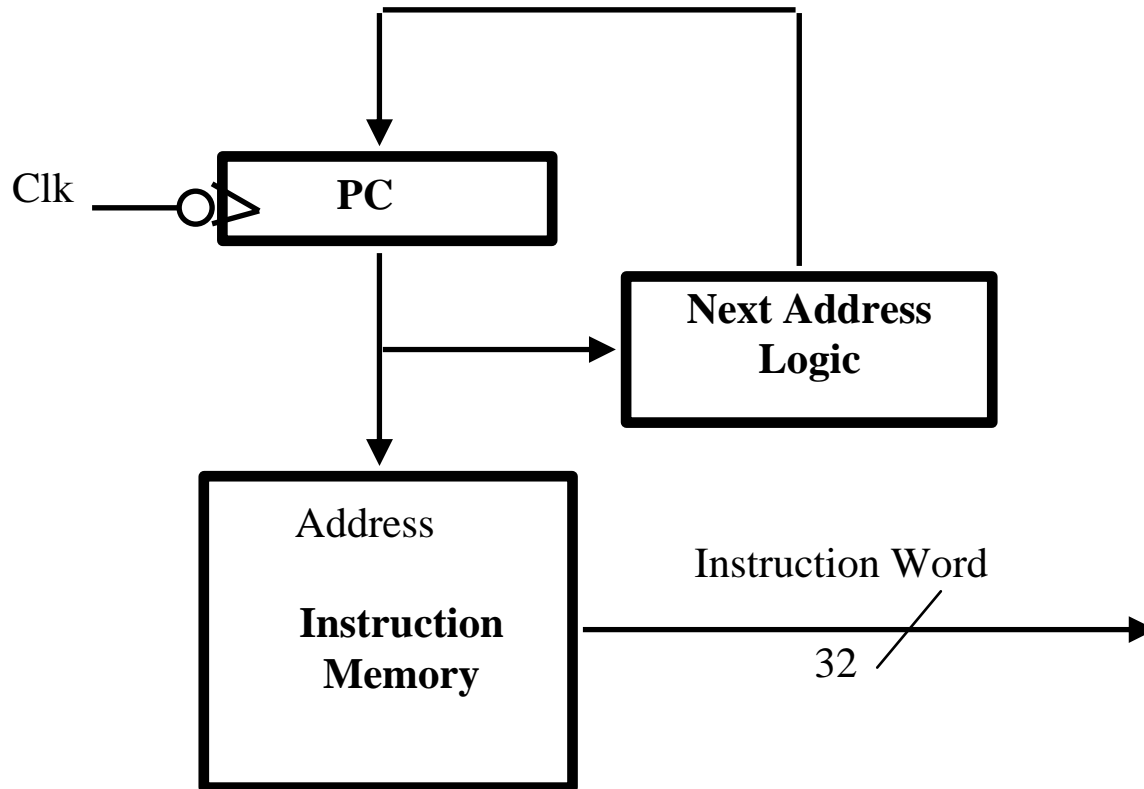
- Branch and Jump: $\text{PC} \leftarrow \text{“something else”}$




Add & Subtract

$R[rd] \leftarrow R[rs] \text{ op } R[rt]$; Example: `addu rd, rs, rt`

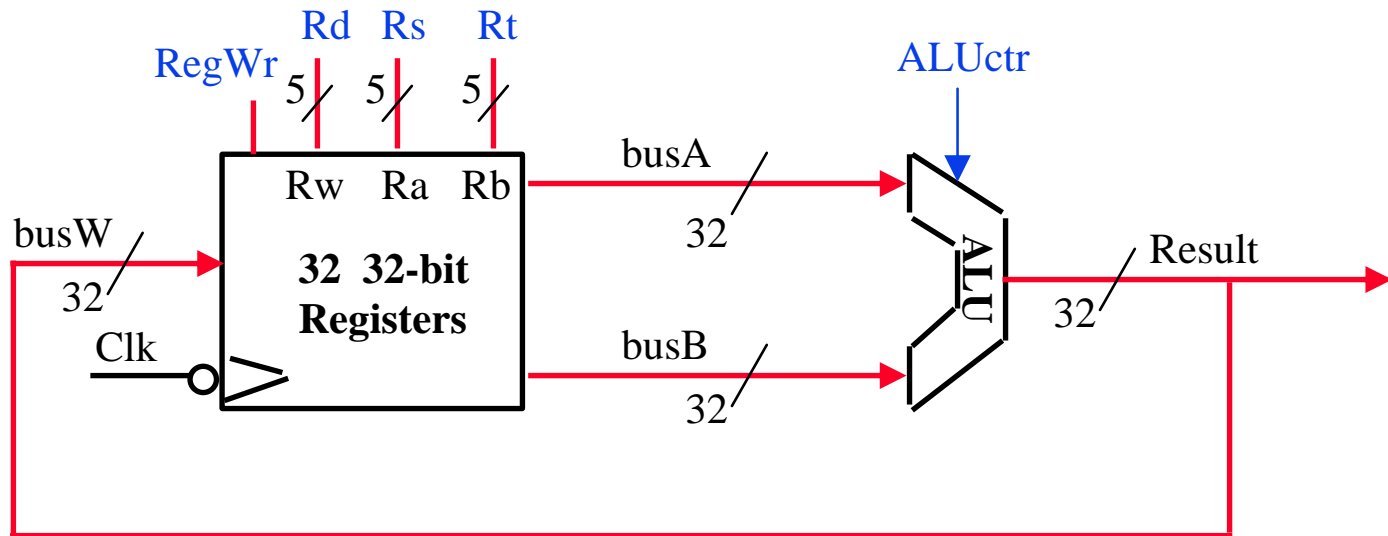 
- Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
- ALUctr and RegWr: control logic after decoding the instruction



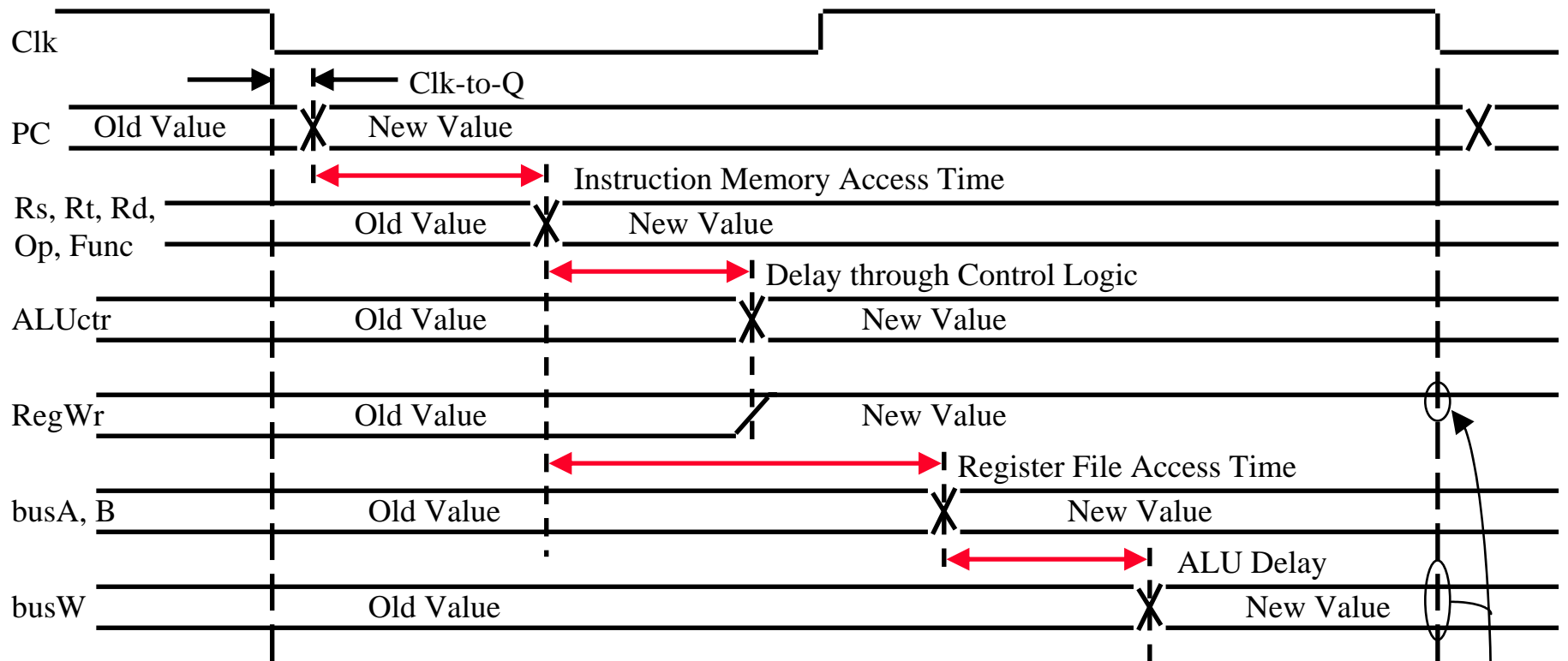Register-Register Timing: One complete cycle





Register Write Occurs Here

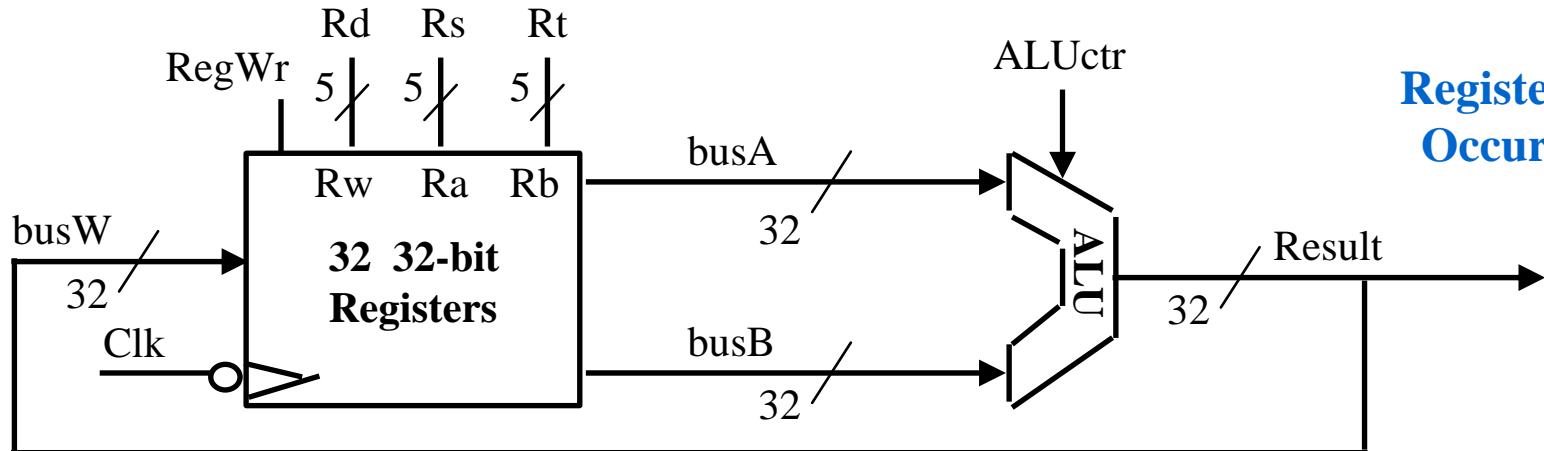


Logical Operations With Immediate

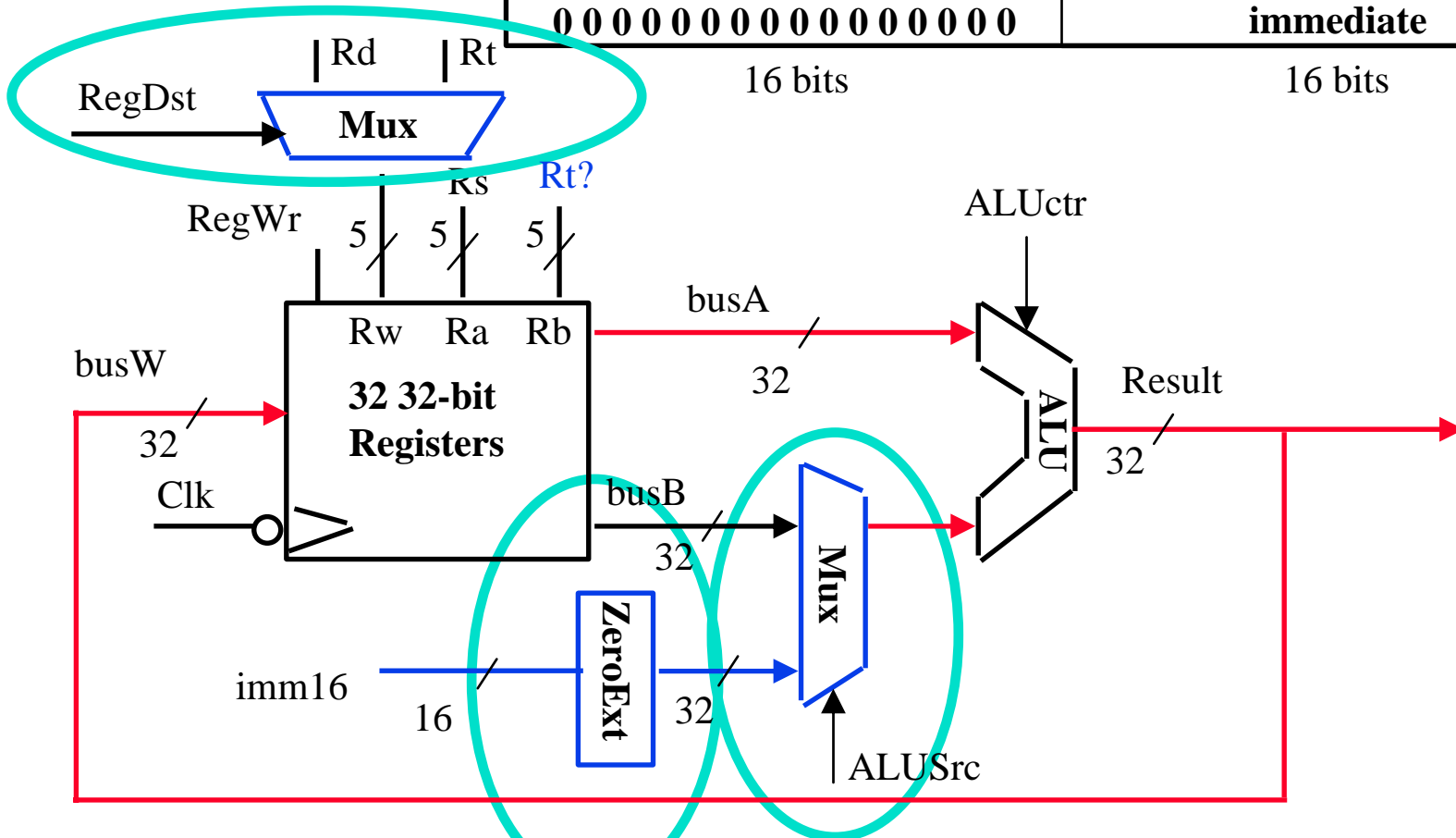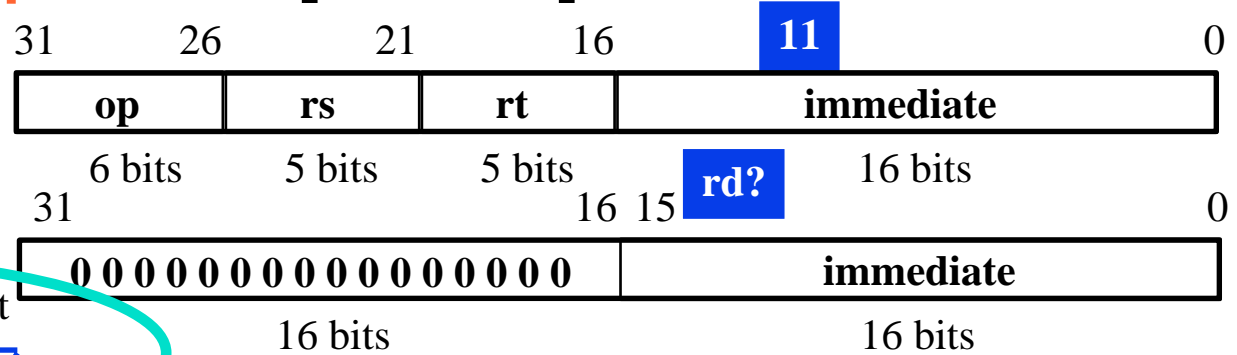- $R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$





Load Operations

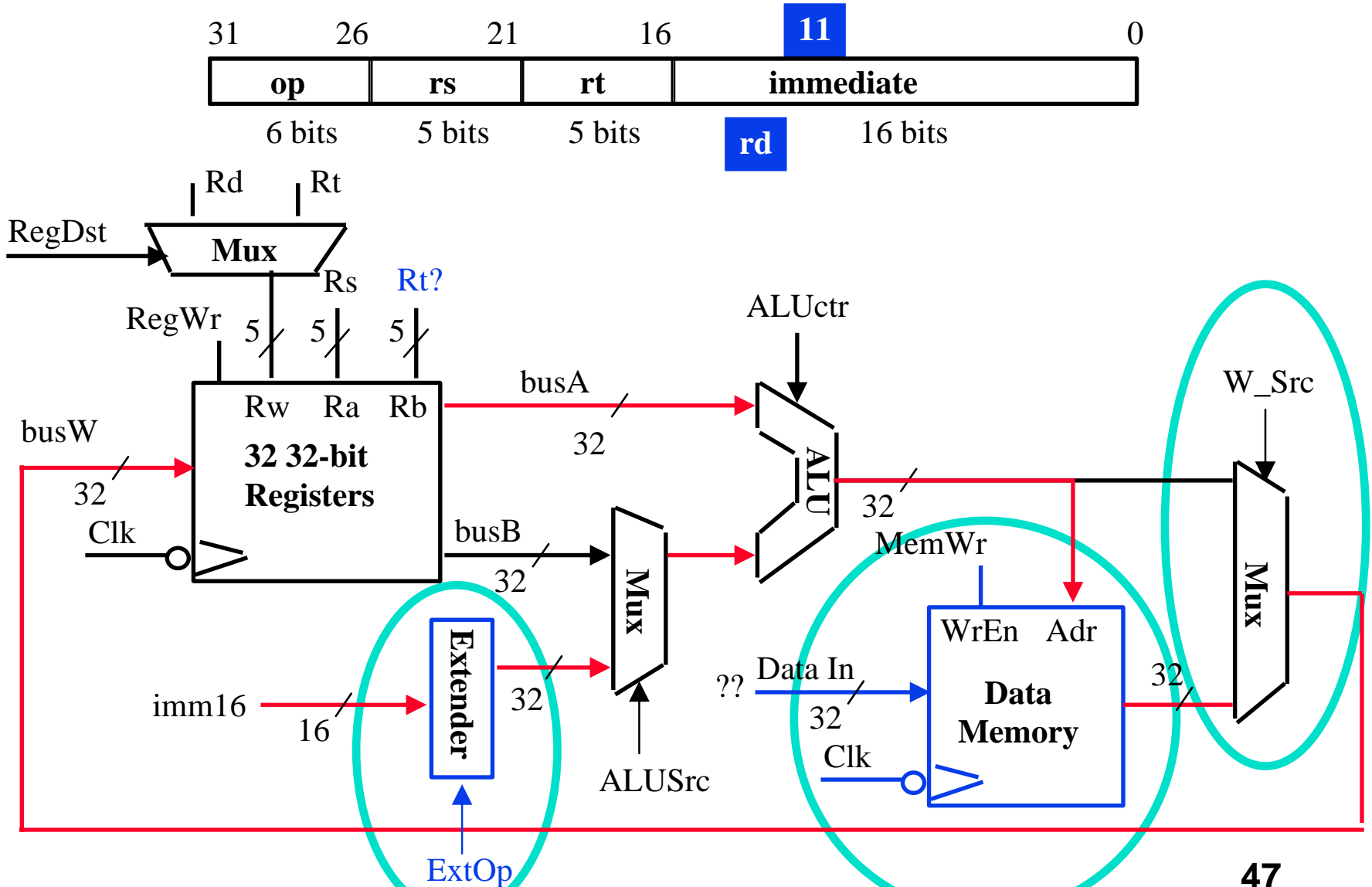- $R[rt] \leftarrow Mem[R[rs] + SignExt[imm16]]$; Example: `lw rt, rs, imm16`




Store Operations

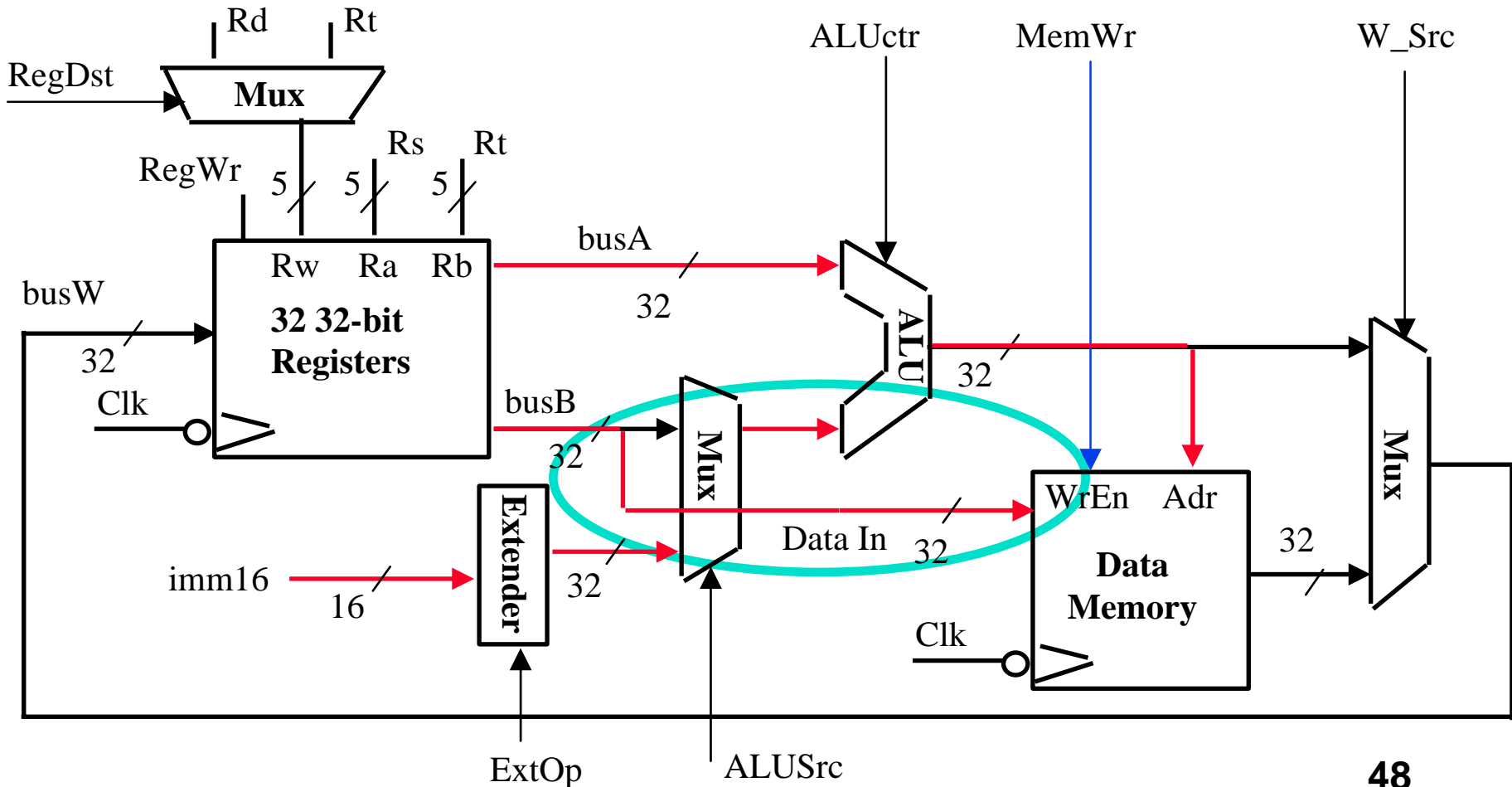 - $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}] \leftarrow R[\text{rt}]]$; Example: `sw rt, rs, imm16`




Datapath for Branch Operations

 


- **beq** **rs, rt, imm16**
(equal)

Datapath generates condition

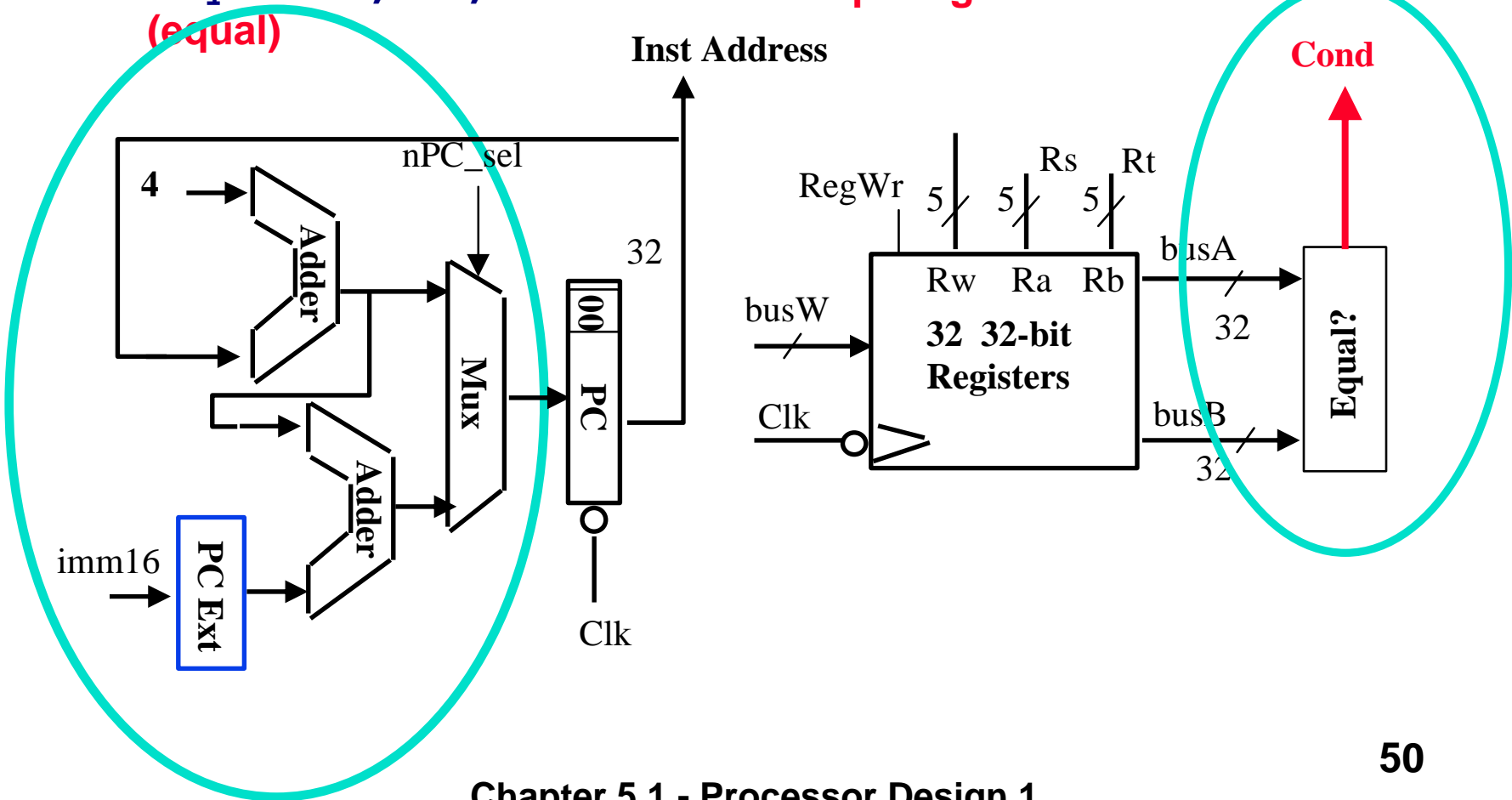

Summary: A Single Cycle Datapath

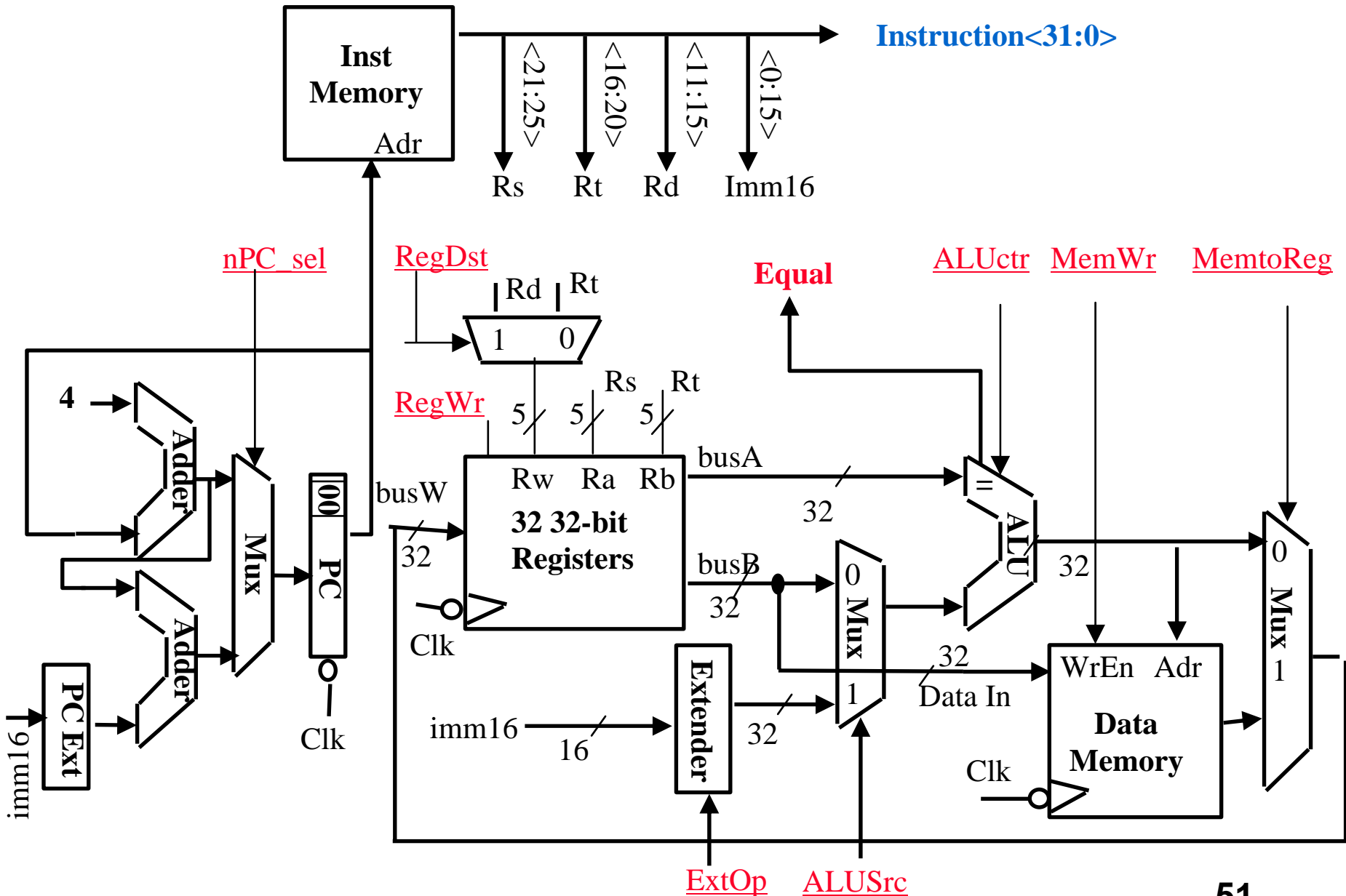


An Abstract View of the Critical Path


- **Register file and ideal memory:**

- The CLK input is a factor ONLY during *write* operation
- During read operation, behave as combinational logic:
 - Address valid → Output valid after “access time.”

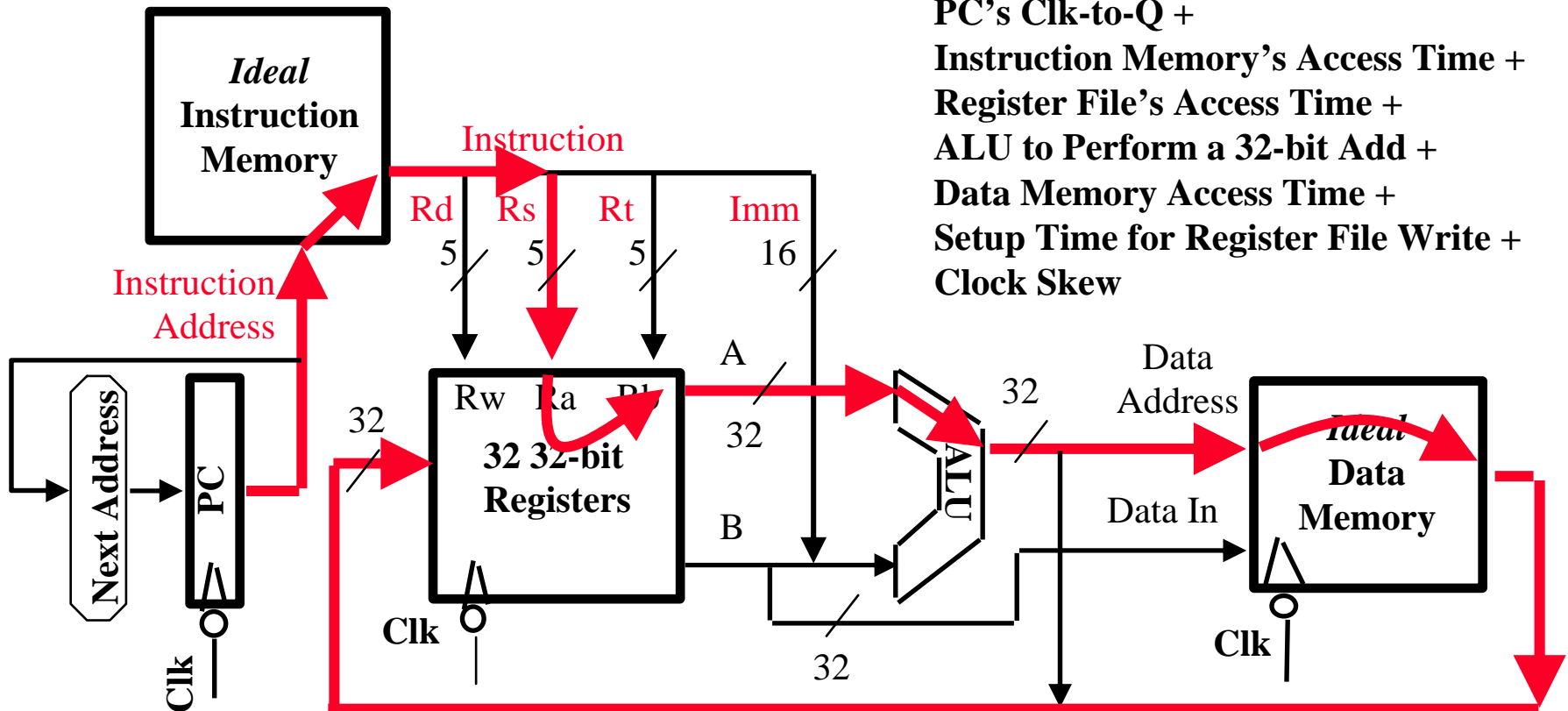Critical Path (Load Operation) =
PC's Clk-to-Q +
Instruction Memory's Access Time +
Register File's Access Time +
ALU to Perform a 32-bit Add +
Data Memory Access Time +
Setup Time for Register File Write +
Clock Skew



An Abstract View of the Implementation

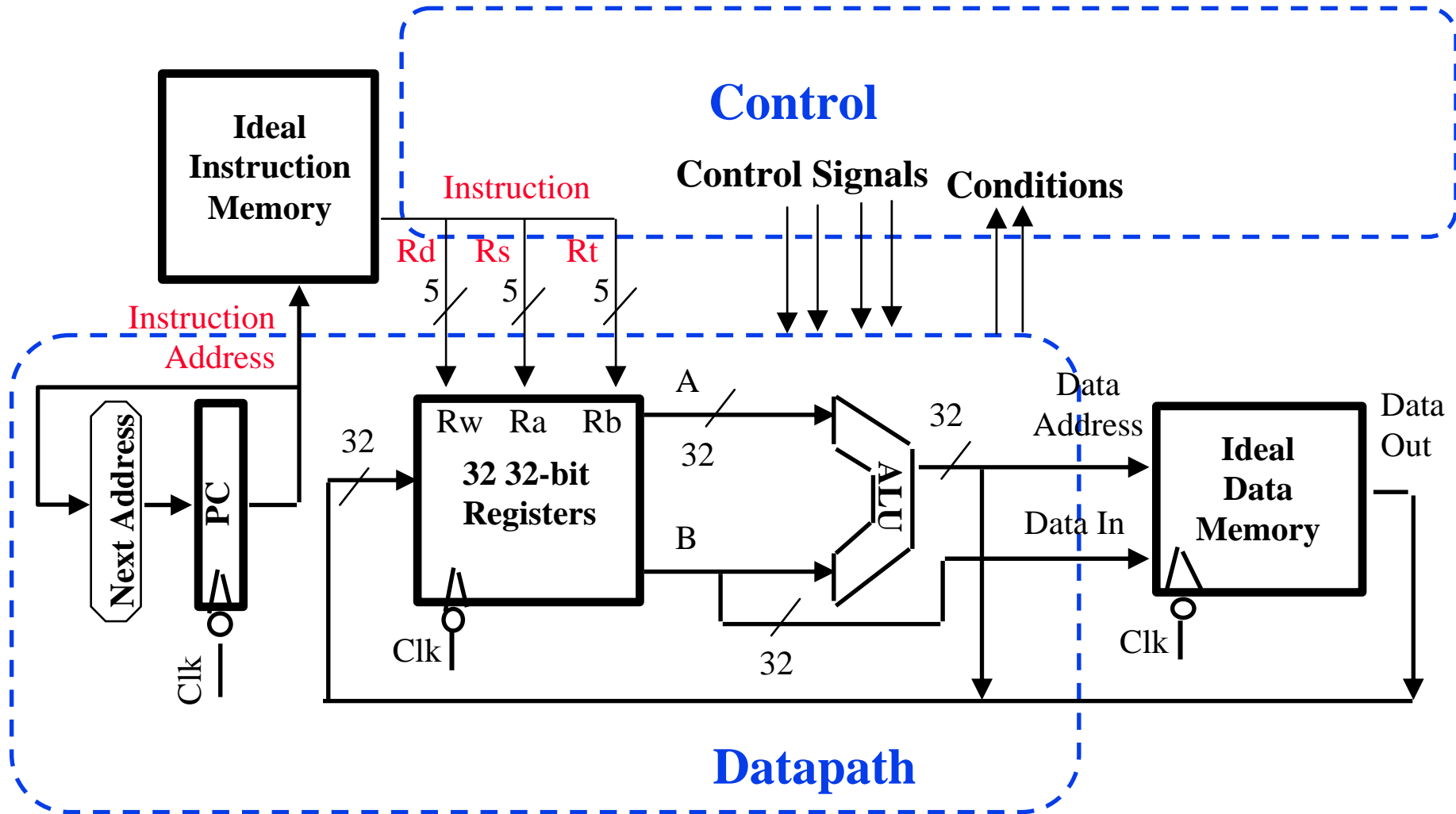

Steps 4 & 5: Implement the control

In The Next Section

Summary: MIPS-lite Implementations

- **single-cycle: uses single l-o-n-g clock cycle for each instruction executed**
- **Easy to understand, but not practical**
 - slower than implementation that allows instructions to take different numbers of clock cycles
 - fast instructions: (`beq`) fewer clock cycles
 - slow instructions (`mult?`): more cycles
 - multicycle, pipelined implementations later
- **Next time, finish the single-cycle implementation**

Summary

- **5 steps to design a processor**

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

- **MIPS makes it easier**

- Instructions same size
- Source registers always in same place
- Immediates same size, location
- Operations always on registers/immediates

- **Single cycle datapath: $CPI = 1$, $T_{CC} \rightarrow$ long**

- **Next time: implementing control**