


Computer Architecture

Designing a Multicycle Processor

Recap: Processor Design is a Process


- **Bottom-up**
 - assemble components in target technology to establish critical timing
- **Top-down**
 - specify component behavior from high-level requirements
- **Iterative refinement**
 - establish partial solution, expand and improve

Instruction Set =>
Architecture

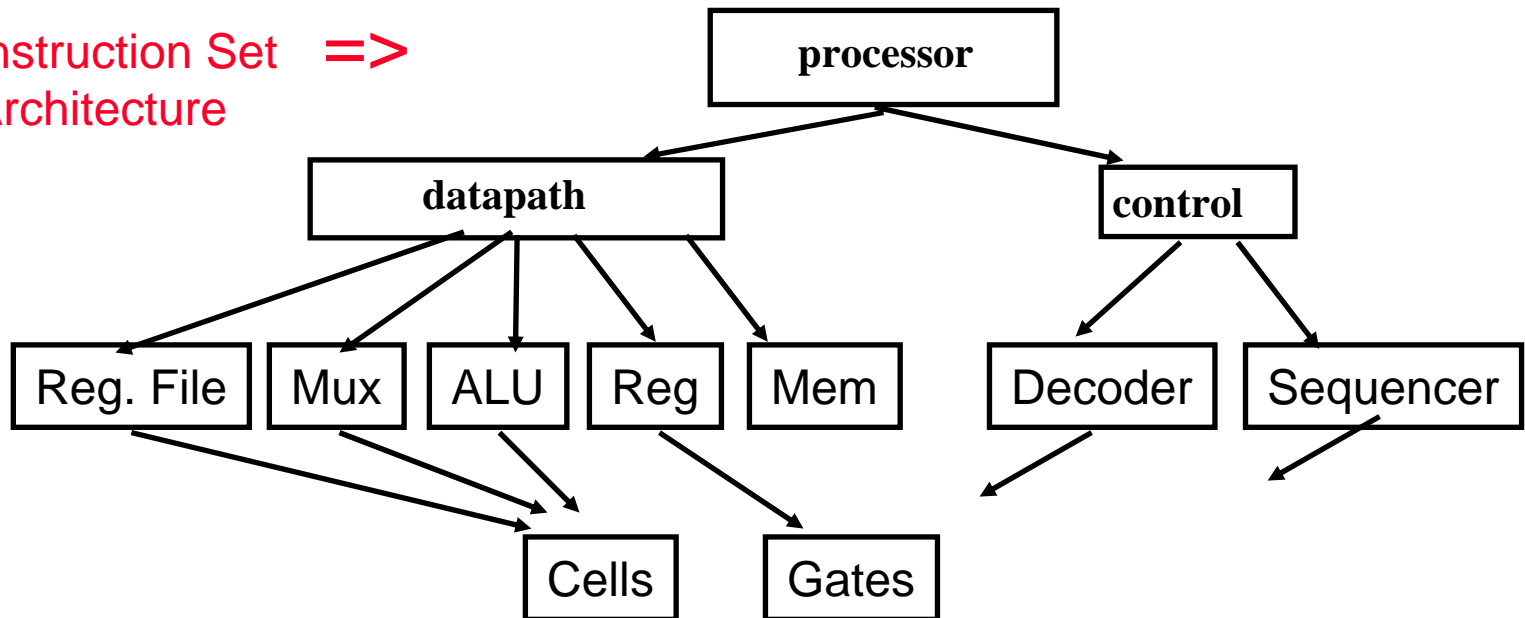


Recap: A Single Cycle Datapath

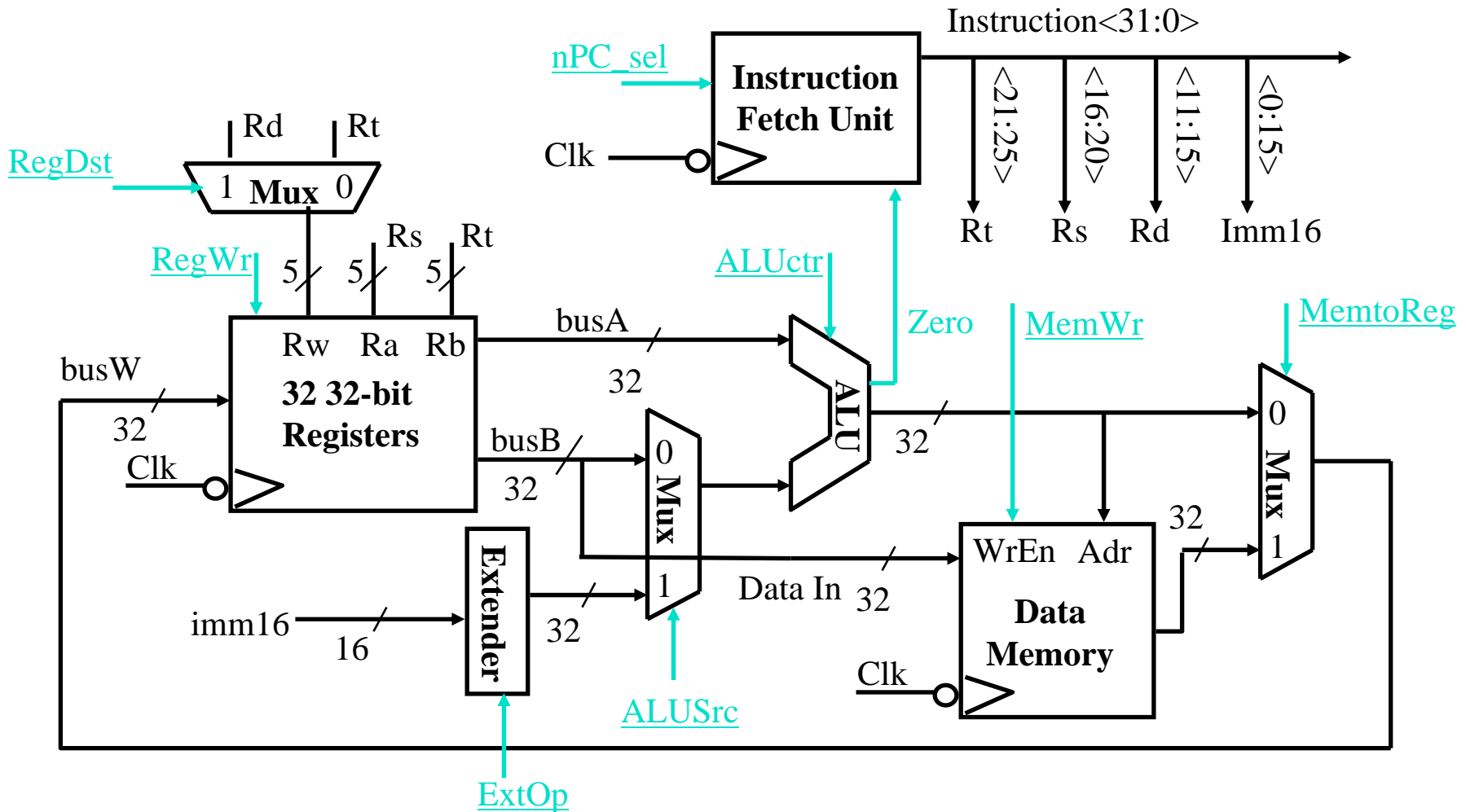- We have everything except control signals (underline)
 - Today's lecture will show you how to generate the control signals




 Recap: The “Truth Table” for the Main Control




op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUOp (Symbolic)	“R-type”	Or	Add	Add	Subtract	xxx
ALUOp <2>	1	0	0	0	0	x
ALUOp <1>	0	1	0	0	0	x
ALUOp <0>	0	0	0	0	1	x

 Recap: PLA Implementation of the Main Control




Recap: Systematic Generation of Control

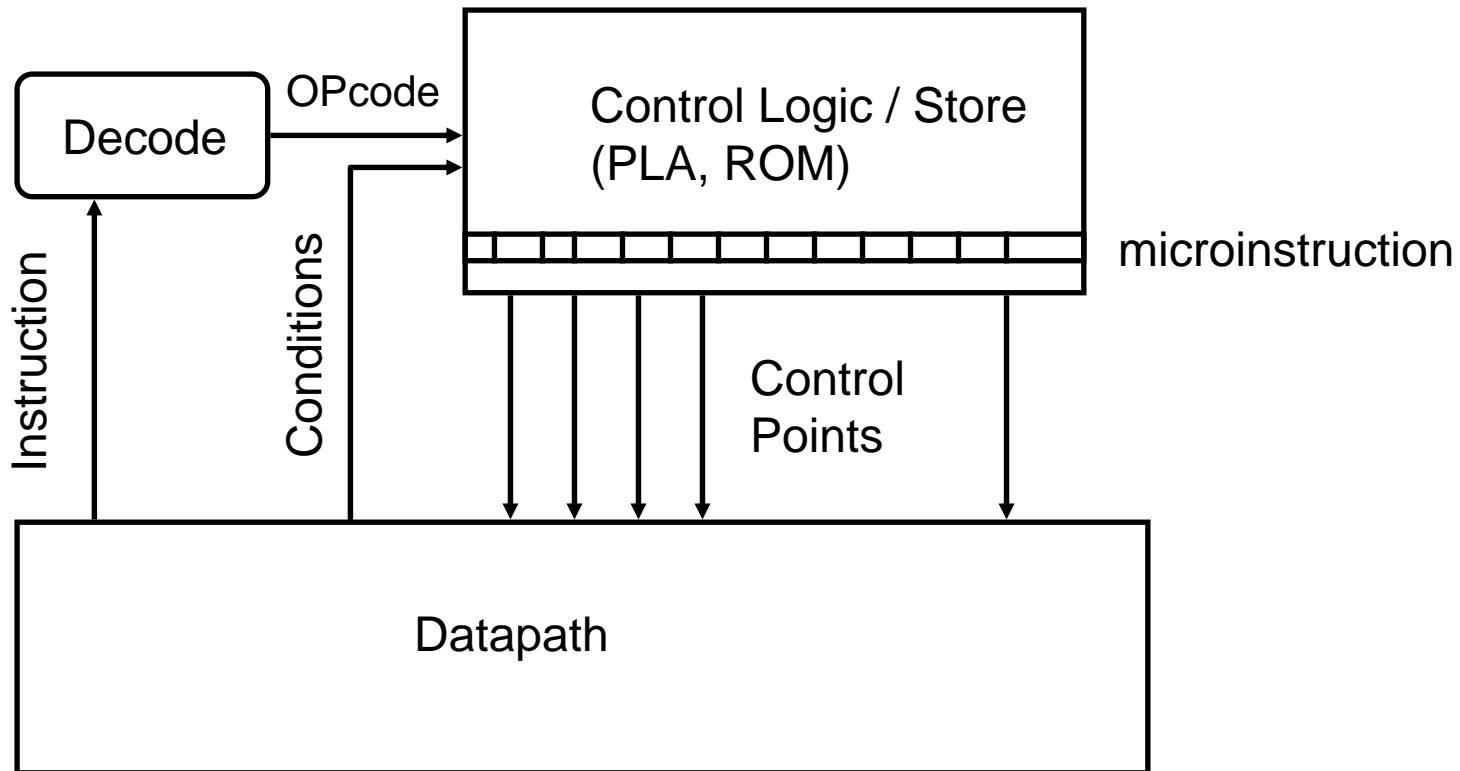

- In our single-cycle processor, each instruction is realized by exactly one control command or “*microinstruction*”
 - in general, the controller is a finite state machine
 - microinstruction can also control sequencing (see later)

The Big Picture: Where are We Now?

 ◦ The Five Classic Components of a Computer




◦ Today's Topic: Designing the Datapath for the Multiple Clock Cycle Datapath

Outline of Today's Lecture

- **Recap: single cycle processor**
- **VHDL versions**
- **Faster designs**
- **Multicycle Datapath**
- **Performance Analysis**
- **Multicycle Control**

Behavioral models of Datapath Components
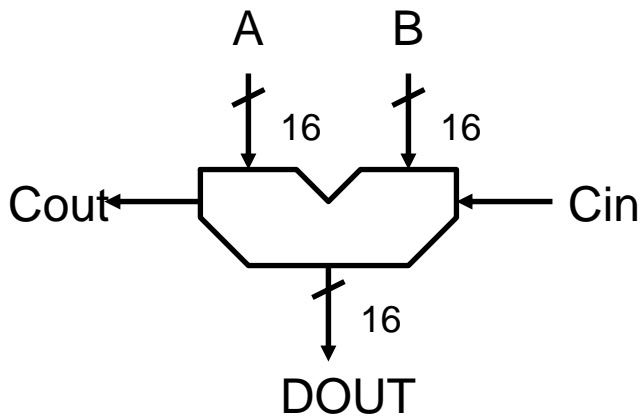
```
entity adder16 is
generic (ccOut_delay : TIME := 12 ns;
        adderOut_delay: TIME := 12 ns);
port(A, B:   in vlbit_1d(15 downto 0);
      DOUT:  out vlbit_1d(15 downto 0);
      CIN:   in vlbit;
      COUT:  out vlbit);
end adder16;
```



```
architecture behavior of adder32 is
begin
    adder16_process: process(A, B, CIN)

        variable tmp    : vlbit_1d(18 downto 0);
        variable adder_out : vlbit_1d(31 downto 0);
        variable carry: vlbit;

    begin
        tmp := addum (addum (A, B), CIN);
        adder_out := tmp(15 downto 0);
        carry :=tmp(16);

        COUT <= carry after ccOut_delay;
        DOUT <= adder_out after adderOut_delay;
    end process;
end behavior;
```

Behavioral Specification of Control Logic


```
entity maincontrol is
port(opcode:      in vlbit_1d(5 downto 0);
      equal_cond: in vlbit;

      extop       out vlbit;
      ALUsrc      out vlbit;
      ALUop       out vlbit_1d(1 downto 0);
      MEMwr       out vlbit;
      MemtoReg    out vlbit;
      RegWr       out vlbit;
      RegDst      out vlbit;
      nPC         out vlbit;
end maincontrol;
```



- **Decode / Control-store address modeled by Case statement**
- **Each arm drives control signals for that operation**
 - just like the microinstruction
 - either can be symbolic

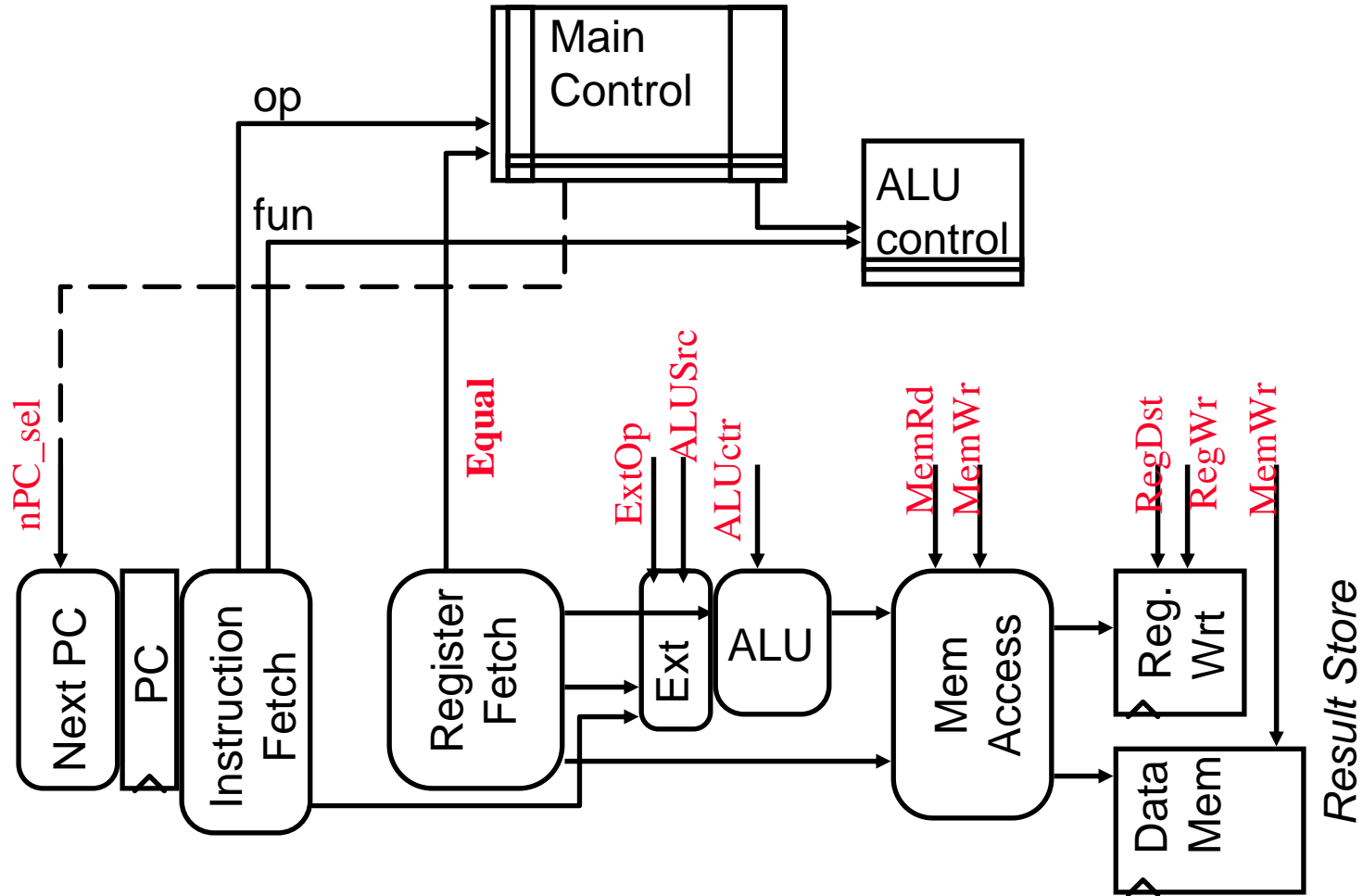
Abstract View of our single cycle processor



◦ looks like a FSM with PC as state

What's wrong with our CPI=1 processor?

Arithmetic & Logical

 

Load



Store




Branch



- **Long Cycle Time**
- **All instructions take as much time as the slowest**
- **Real memory is not so nice as our idealized memory**
 - cannot always get the job done in one (short) cycle


Memory Access Time

 - **Physics => fast memories are small (large memories are slow)**




- **question: register file vs. memory**

- **=> Use a hierarchy of memories**

 


Reducing Cycle Time

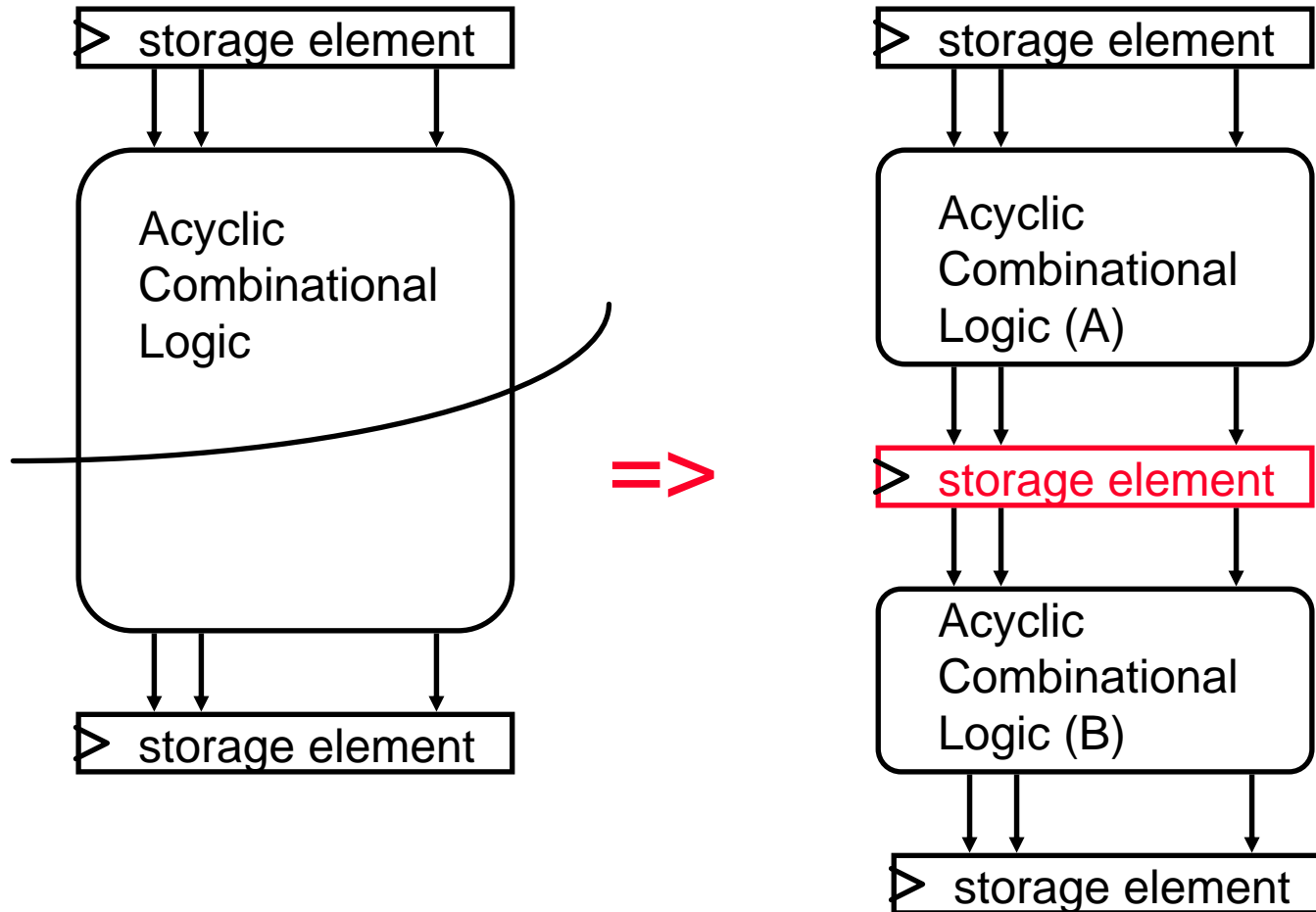- Cut combinational dependency graph and insert register / latch
- Do same work in two fast cycles, rather than one slow one




Basic Limits on Cycle Time

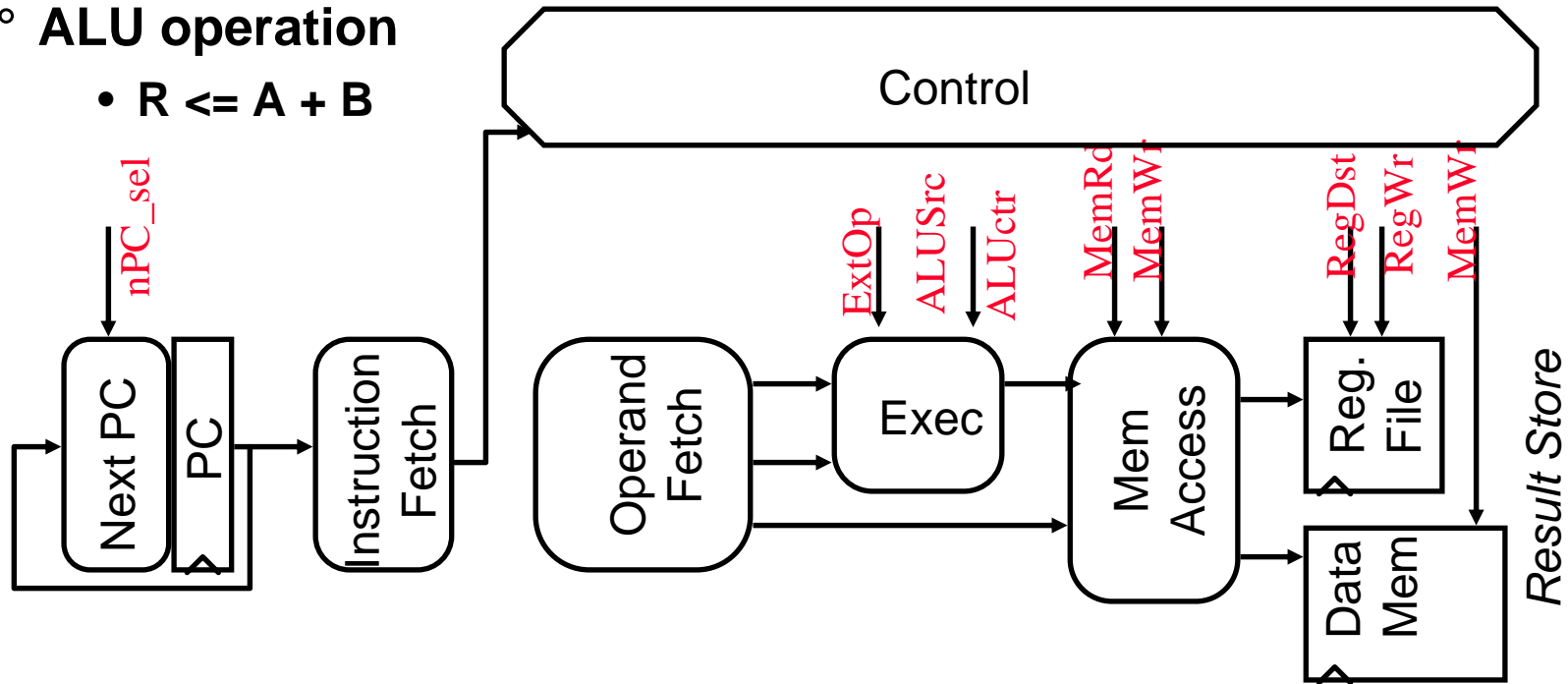- Next address logic
 - $PC \leq \text{branch} ? PC + \text{offset} : PC + 4$
- Instruction Fetch
 - $\text{InstructionReg} \leq \text{Mem}[PC]$
- Register Access
 - $A \leq R[\text{rs}]$
- ALU operation
 - $R \leq A + B$




Partitioning the CPI=1 Datapath

- Add registers between smallest steps

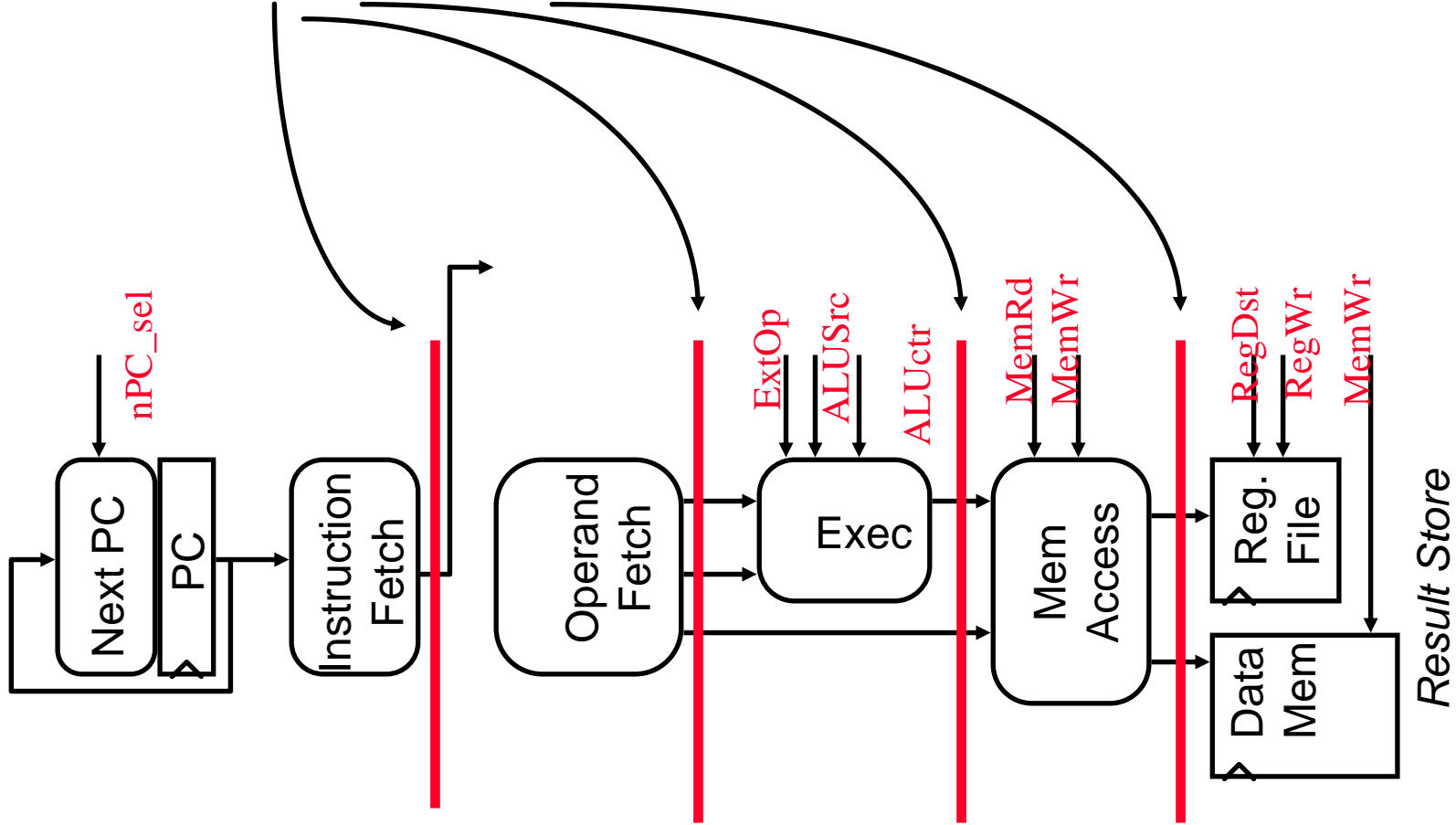

Example Multicycle Datapath

 

◦ Critical Path ?

Recall: Step-by-step Processor Design

Step 1: ISA => Logical Register Transfers

Step 2: Components of the Datapath

Step 3: RTL + Components => Datapath

Step 4: Datapath + Logical RTs => Physical RTs

Step 5: Physical RTs => Control

Step 4: R-rtype (add, sub, . . .)


◦ Logical Register Transfer

inst Logical Register Transfers

ADDU $R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4$

◦ Physical Register Transfers

<u>inst</u>	<u>Physical Register Transfers</u>	
	IR \leftarrow MEM[pc]	
ADDU	A \leftarrow R[rs]; B \leftarrow R[rt]	
	S \leftarrow A + B	
	R[rd] \leftarrow S;	PC \leftarrow PC + 4

 

Step 4: Logical immed


- Logical Register Transfer

inst Logical Register Transfers

ADDU $R[rt] \leftarrow R[rs] \text{ OR } zx(Im16); PC \leftarrow PC + 4$

- Physical Register Transfers

<u>inst</u>	<u>Physical Register Transfers</u>	
	IR \leftarrow MEM[pc]	
ADDU	A \leftarrow R[rs]; B \leftarrow R[rt]	
	S \leftarrow A <i>or</i> ZeroExt(Im16)	
	R[rt] \leftarrow S;	PC \leftarrow PC + 4

 

Step 4 : Load

- Logical Register Transfer
- Physical Register Transfers

inst Logical Register Transfers

LW $R[rt] \leftarrow MEM(R[rs] + sx(Im16));$

$PC \leftarrow PC + 4$

inst Physical Register Transfers


IR $\leftarrow MEM[pc]$

LW $A \leftarrow R[rs]; B \leftarrow R[rt]$

$S \leftarrow A + SignEx(Im16)$

$M \leftarrow MEM[S]$

 $R[rd] \leftarrow M; \quad PC \leftarrow PC + 4$




Step 4 : Store

◦ Logical Register Transfer

inst Logical Register Transfers
 SW $MEM(R[rs] + sx(Im16)) \leftarrow R[rt];$
 $PC \leftarrow PC + 4$

◦ Physical Register Transfers

<u>inst</u>	<u>Physical Register Transfers</u>
	$IR \leftarrow MEM[pc]$
SW	$A \leftarrow R[rs]; B \leftarrow R[rt]$
	$S \leftarrow A + SignEx(Im16);$
	$MEM[S] \leftarrow B \quad PC \leftarrow PC + 4$

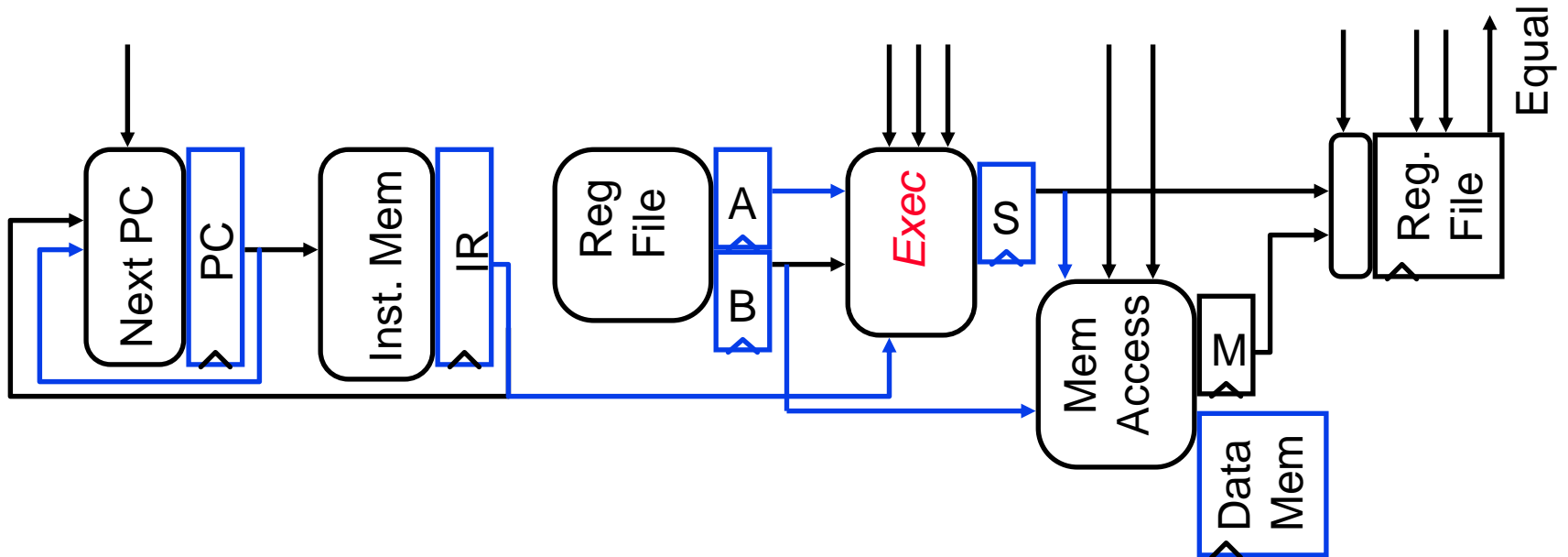

Step 4 : Branch


◦ Logical Register Transfer

inst Logical Register Transfers
BEQ if $R[rs] == R[rt]$
 then $PC \leftarrow PC + sx(Im16) || 00$
 else $PC \leftarrow PC + 4$

◦ Physical Register Transfers


<u>inst</u>	<u>Physical Register Transfers</u>
	$IR \leftarrow MEM[pc]$
BEQ Eq	$PC \leftarrow PC + 4$

<u>inst</u>	<u>Physical Register Transfers</u>
	$IR \leftarrow MEM[pc]$
BEQ Eq	$PC \leftarrow PC + sx(Im16) 00$

 



Alternative datapath (book): Multiple Cycle Datapath

- Miminizes Hardware: 1 memory, 1 adder

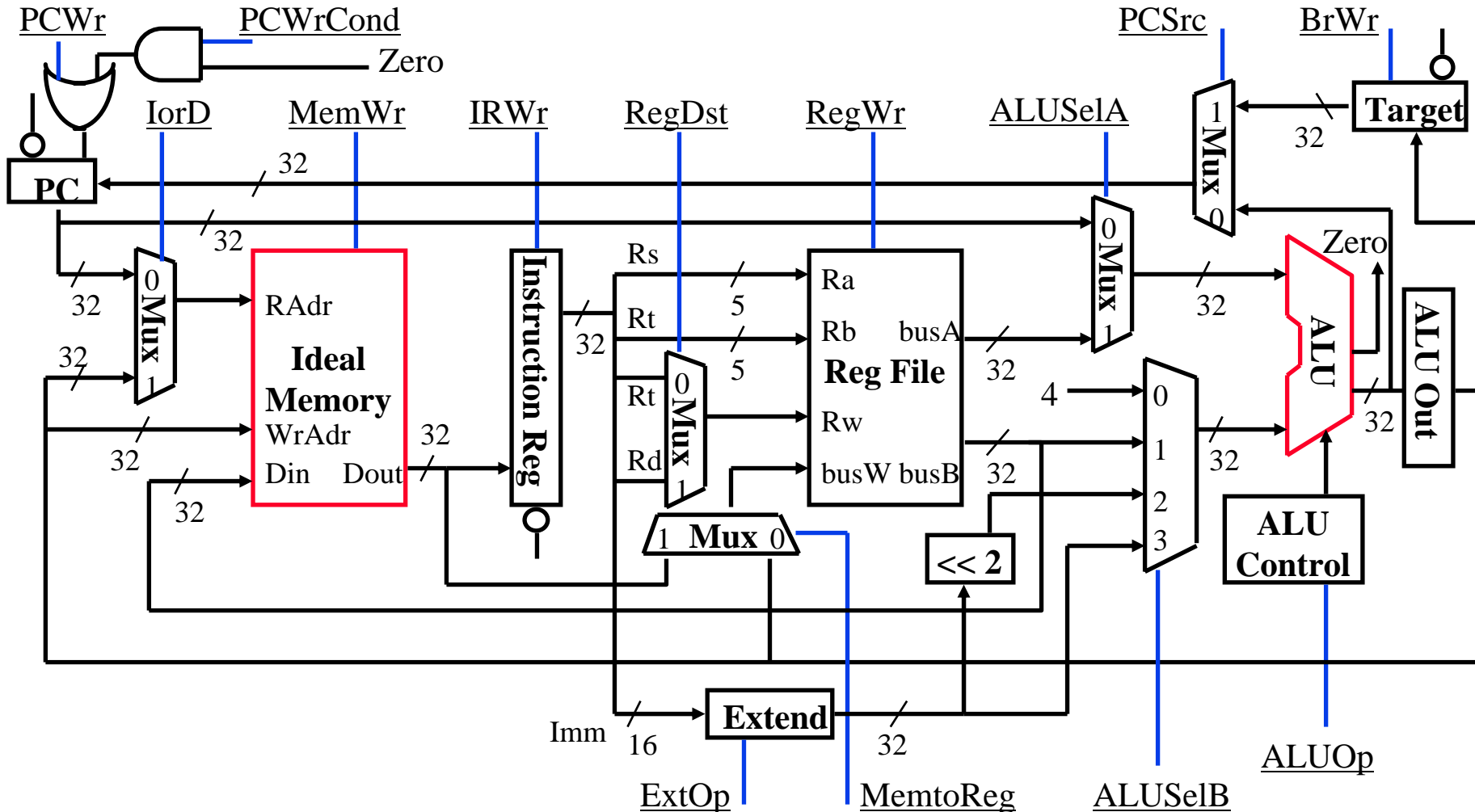


Our Control Model

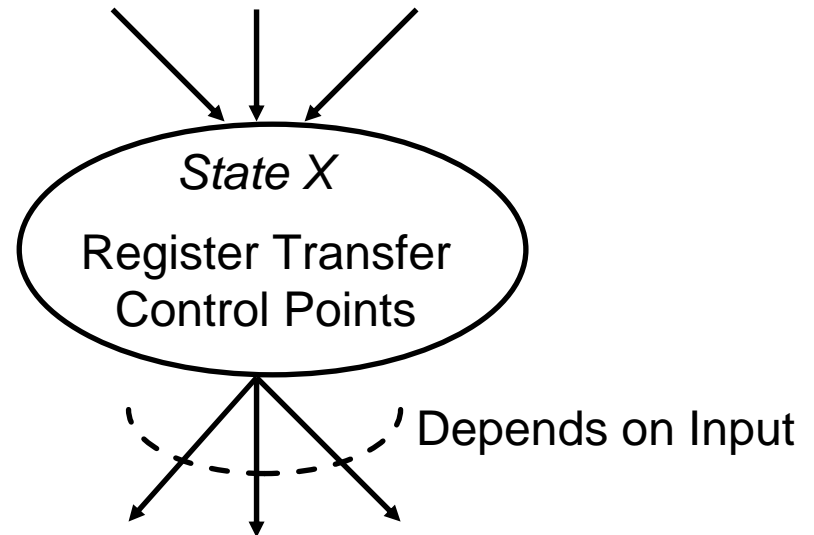 - State specifies control points for Register Transfer
- Transfer occurs upon exiting state (same falling edge)



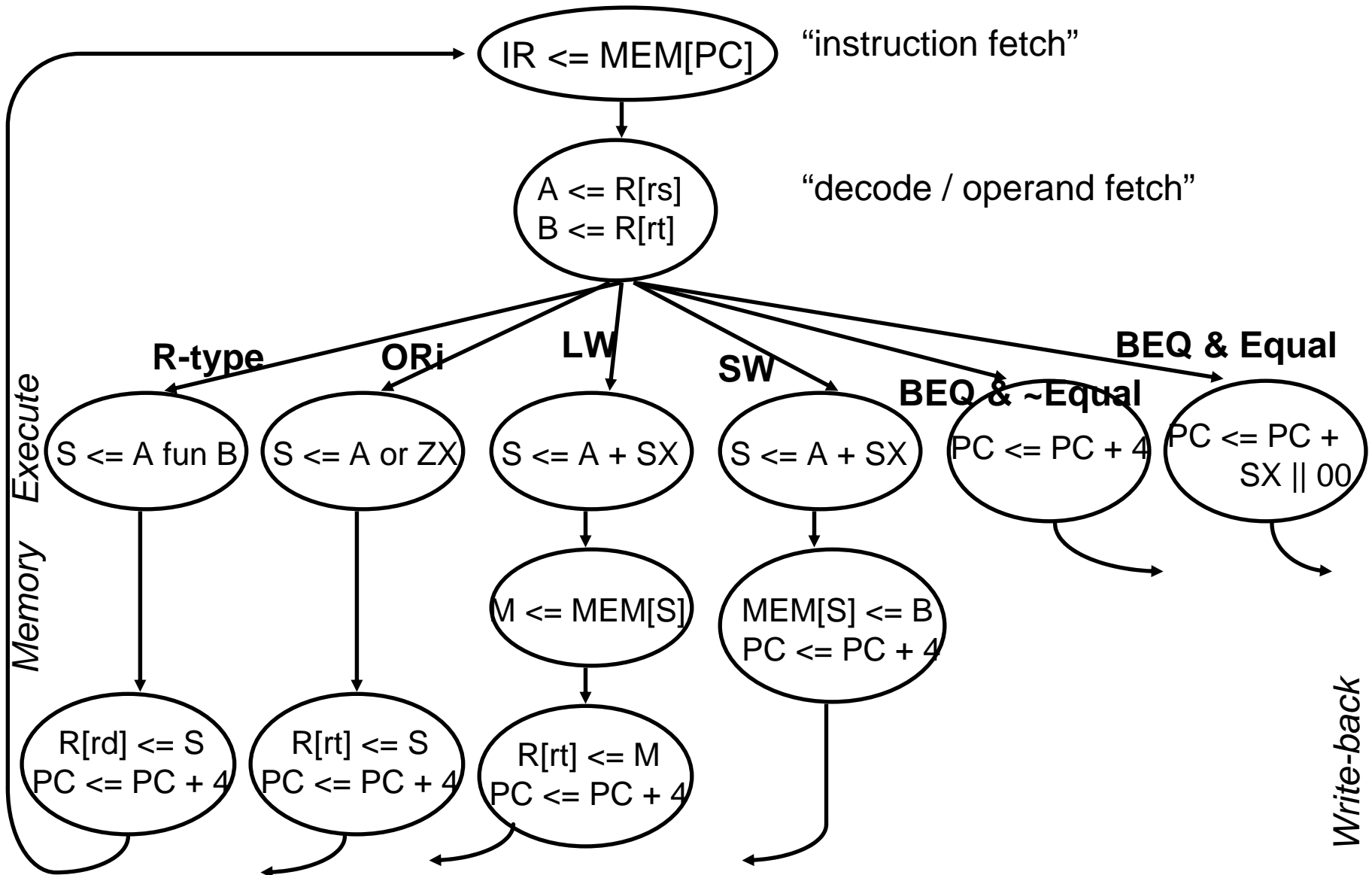
Step 4 => Control Specification for multicycle proc



Traditional FSM Controller

state	op	cond	next state	control points


Truth Table

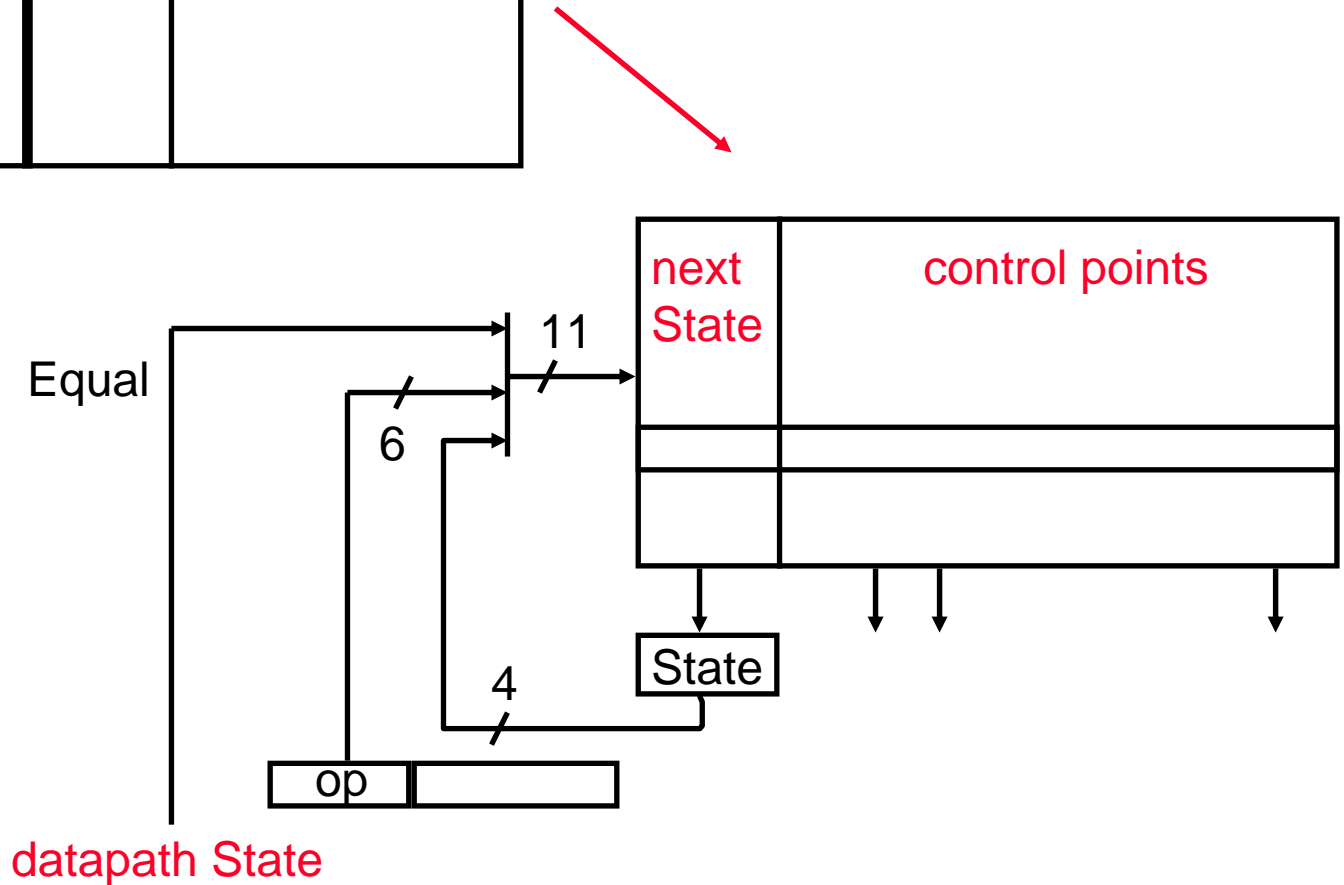


Step 5: datapath + state diagram => control

- **Translate RTs into control points**
- **Assign states**
- **Then go build the controller**

Mapping RTs to Control Points

 

Assigning States

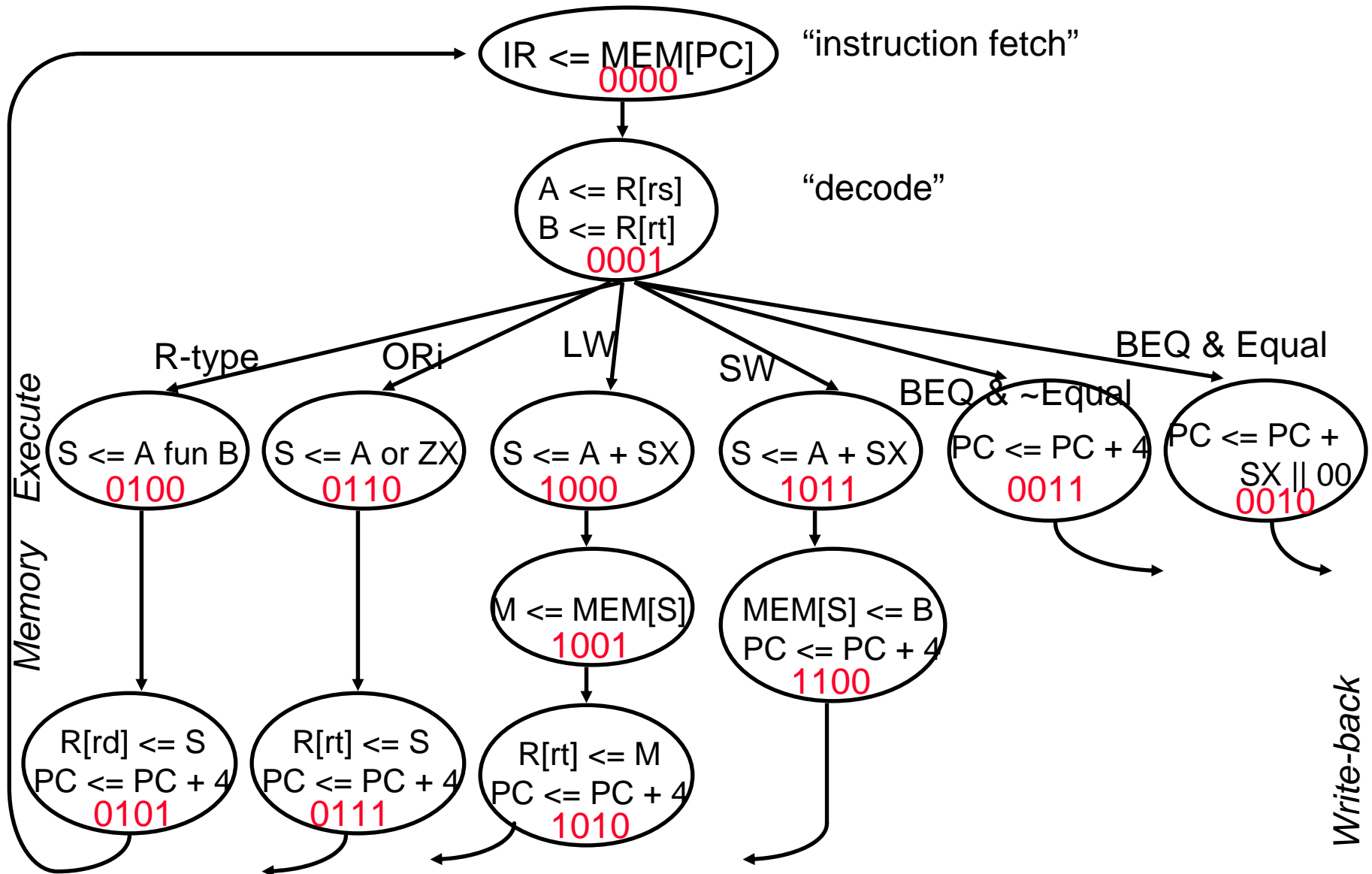

Detailed Control Specification

State	Op field	Eq	Next	IR	PC en sel	Ops A B	Exec Ex Sr ALU S	Mem R W M	Write-Back M-R Wr Dst
0000	??????	?	0001	1					
0001	BEQ	0	0011			1 1	<i>-all same in Moore machine</i>		
0001	BEQ	1	0010			1 1			
0001	R-type	x	0100			1 1			
0001	orl	x	0110			1 1			
0001	LW	x	1000			1 1			
0001	SW	x	1011			1 1			
0010	xxxxxx	x	0000		1 1				
0011	xxxxxx	x	0000		1 0				
R:	0100	xxxxxx	x	0101			0 1 fun 1		
	0101	xxxxxx	x	0000		1 0			0 1 1
ORI:	0110	xxxxxx	x	0111			0 0 or 1		
	0111	xxxxxx	x	0000		1 0			0 1 0
LW:	1000	xxxxxx	x	1001			1 0 add 1		
	1001	xxxxxx	x	1010				1 0 0	
	1010	xxxxxx	x	0000		1 0			1 1 0
SW:	1011	xxxxxx	x	1100			1 0 add 1		
	1100	xxxxxx	x	0000		1 0		0 1	


Performance Evaluation

- **What is the average CPI?**
 - **state diagram gives CPI for each instruction type**
 - **workload gives frequency of each type**





Type	CPI _i for type	Frequency	CPI _i x freq _i
Arith/Logic	4	40%	1.6
Load	5	30%	1.5
Store	4	10%	0.4
branch	3	20%	0.6
			Average CPI:4.1

Controller Design

 
- The state digrams that arise define the controller for an instruction set processor are highly structured
- Use this structure to construct a simple “microsequencer”
- Control reduces to programming this very simple device
 - microprogramming




Example: Jump-Counter

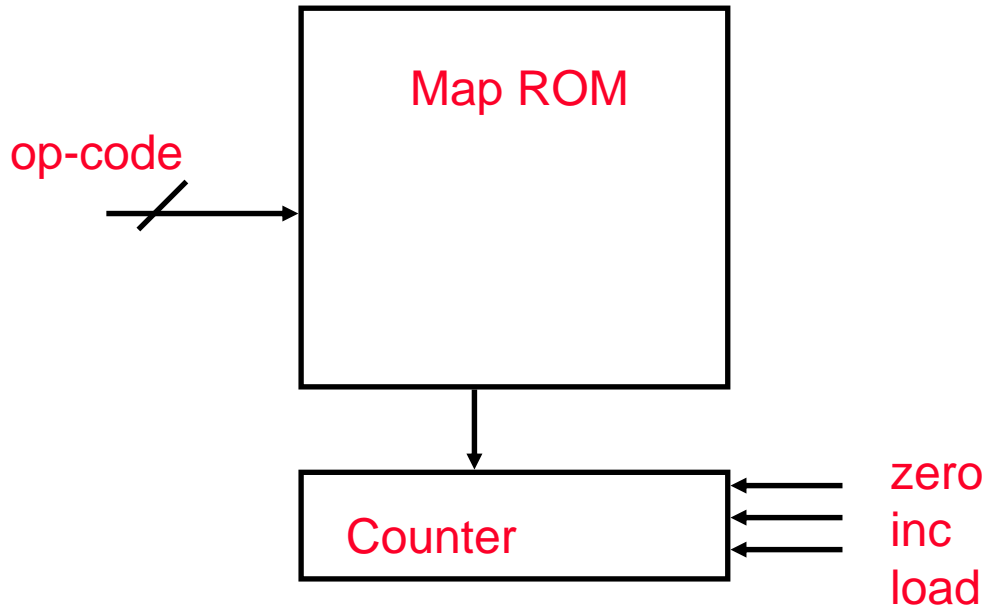   

Using a Jump Counter

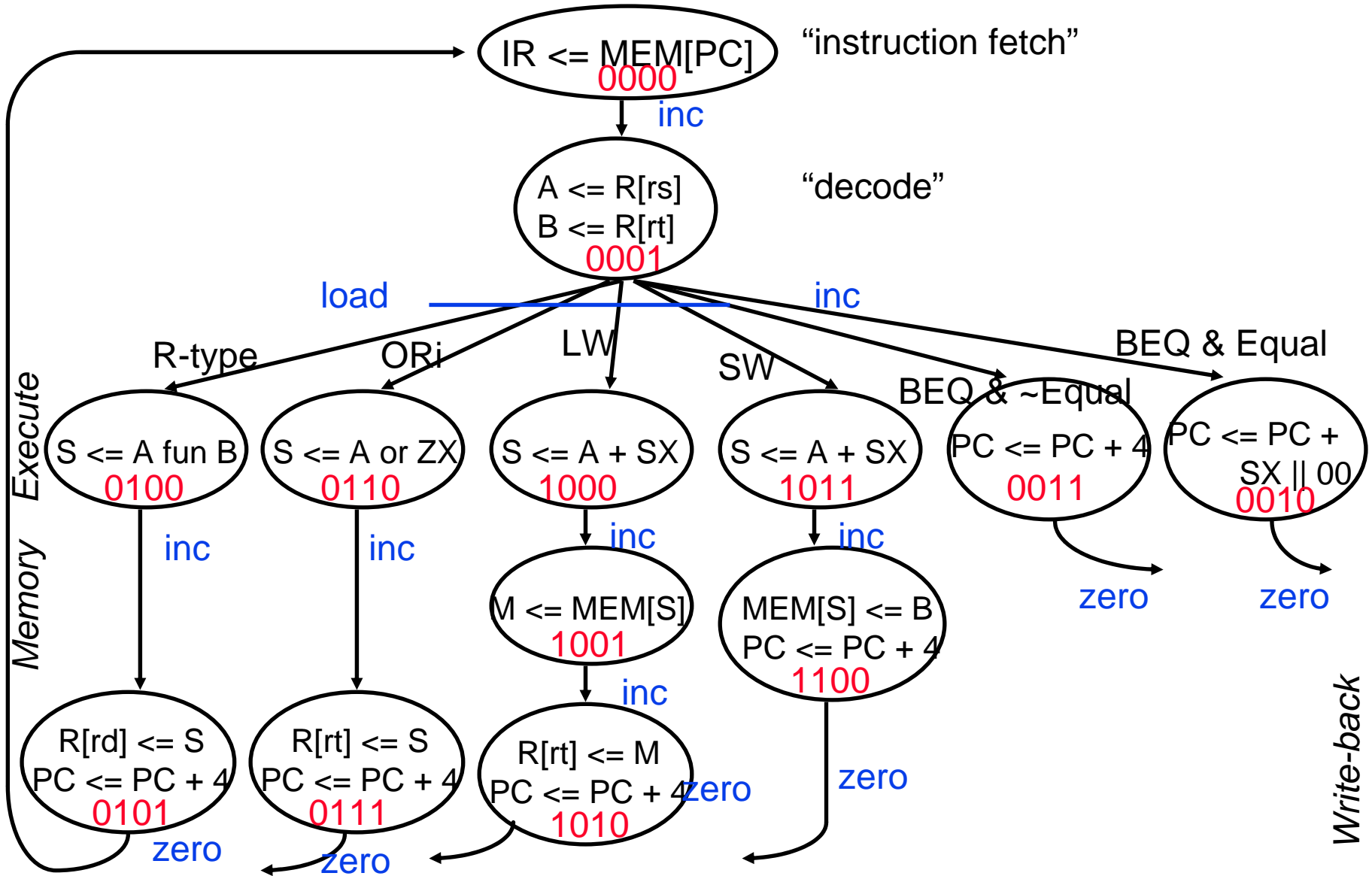

Our Microsequencer

 


Microprogram Control Specification

	uPC	Taken	Next	IR	PC en sel	Ops A B	Exec Ex Sr ALU S	Mem R W M	Write-Back M-R Wr Dst
	0000	?	inc	1					
	0001	0	load						
	0001	1	inc						
	0010	x	zero		1 1				
BEQ:	0011	x	zero		1 0				
R:	0100	x	inc				0 1 fun 1		
	0101	x	zero		1 0				0 1 1
ORI:	0110	x	inc				0 0 or 1		
	0111	x	zero		1 0				0 1 0
LW:	1000	x	inc				1 0 add 1		
	1001	x	inc					1 0 0	
	1010	x	zero		1 0				1 1 0
SW:	1011	x	inc				1 0 add 1		
	1100	x	zero		1 0			0 1	


Mapping ROM

R-type	000000	0100
BEQ	000100	0011
ori	001101	0110
LW	100011	1000
SW	101011	1011


Example: Controlling Memory

 

Controller handles non-ideal memory

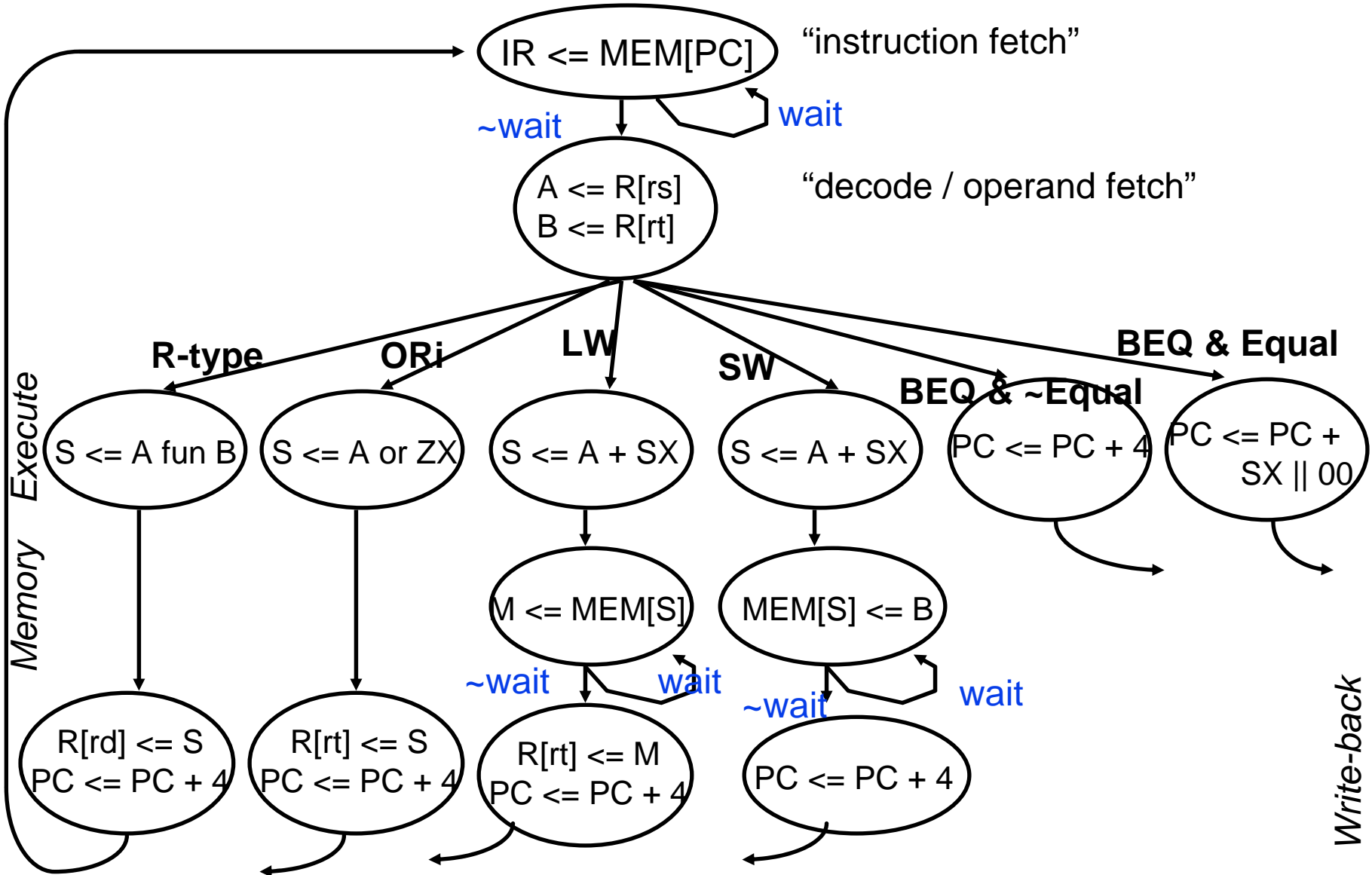


Really Simple Time-State Control

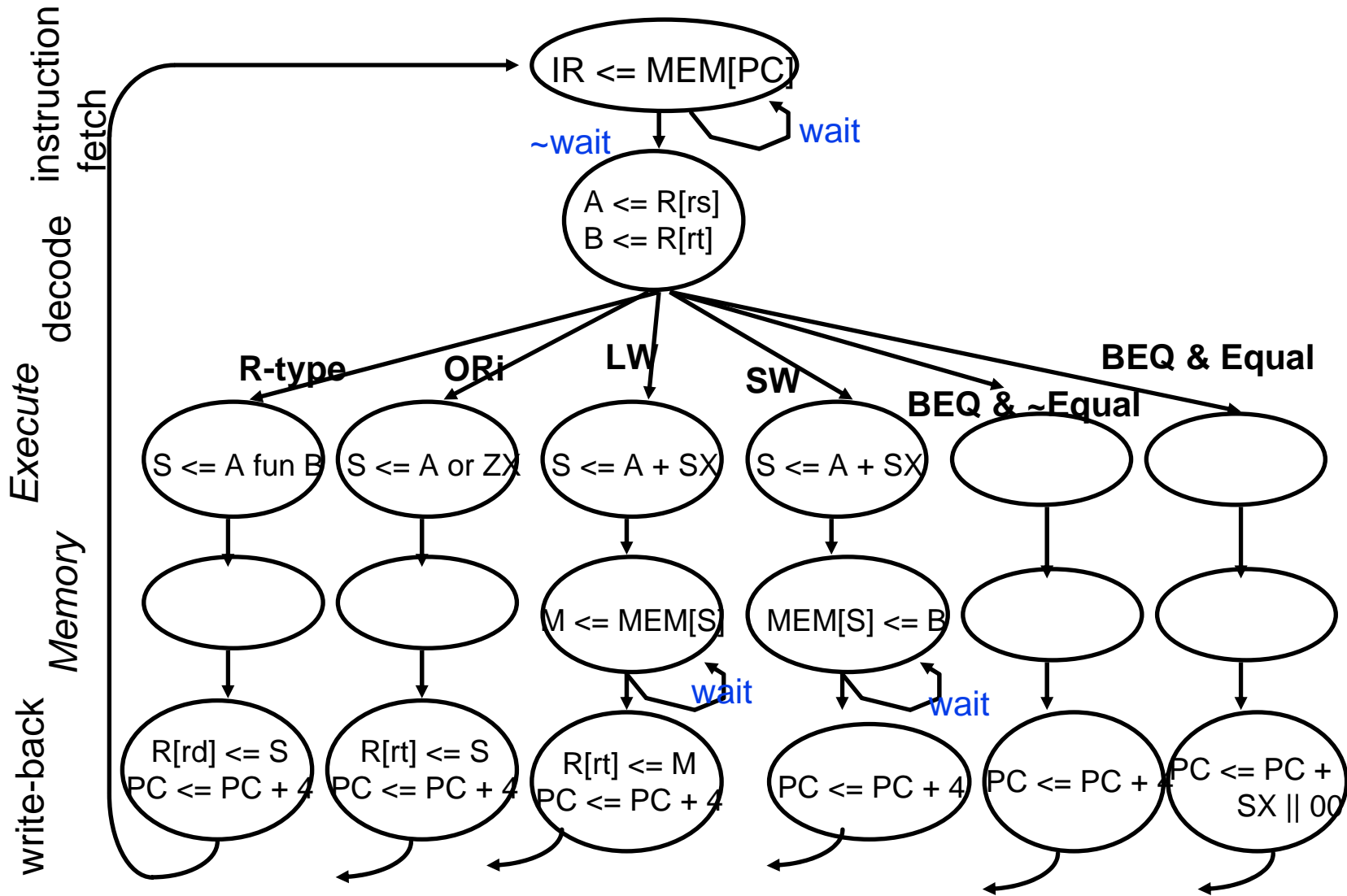


Time-state Control Path

- Local decode and control at each stage

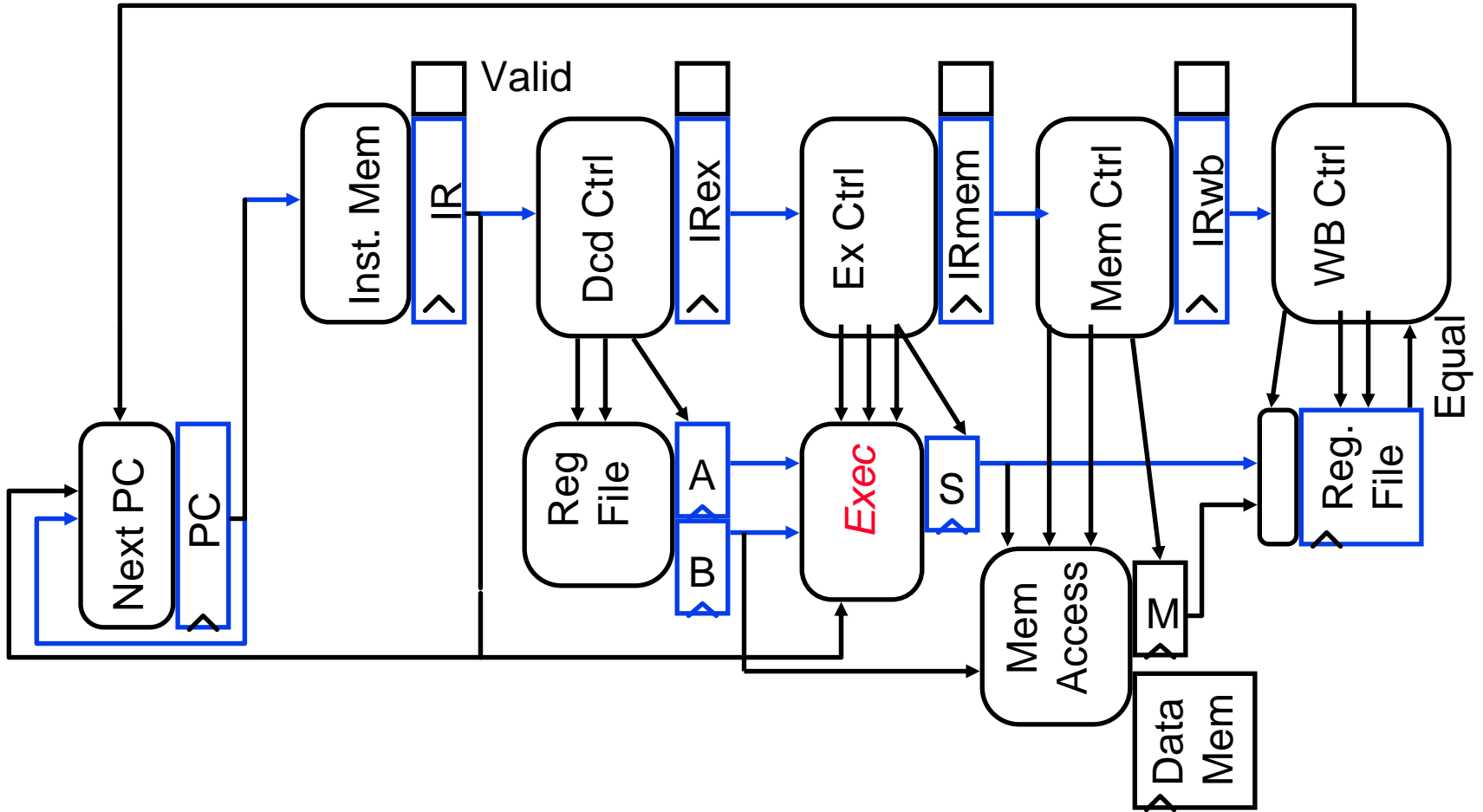

Overview of Control

 - Control may be designed using one of several initial representations. The choice of sequence control, and how logic is represented, can then be determined independently; the control can then be implemented with one of several methods using a structured logic technique.



Summary

- **Disadvantages of the Single Cycle Processor**
 - **Long cycle time**
 - **Cycle time is too long for all instructions except the Load**
- **Multiple Cycle Processor:**
 - **Divide the instructions into smaller steps**
 - **Execute each step (instead of the entire instruction) in one cycle**
- **Partition datapath into equal size chunks to minimize cycle time**
 - **~10 levels of logic between latches**
- **Follow same 5-step method for designing “real” processor**

Summary (cont'd)

- **Control is specified by finite state digram**
- **Specialize state-diagrams easily captured by microsequencer**
 - simple increment & “branch” fields
 - datapath control fields
- **Control design reduces to Microprogramming**
- **Control is more complicated with:**
 - complex instruction sets
 - restricted datapaths (see the book)
- **Simple Instruction set and powerful datapath => simple control**
 - could try to reduce hardware (see the book)
 - rather go for speed => many instructions at once!

Where to get more information?

- **Next two lectures:**
 - **Multiple Cycle Controller: Appendix C of your text book.**
 - **Microprogramming: Section 5.5 of your text book.**
- **D. Patterson, “Microprogramming,” Scientific America, March 1983.**
- **D. Patterson and D. Ditzel, “The Case for the Reduced Instruction Set Computer,” Computer Architecture News 8, 6 (October 15, 1980)**