# EE 200- Digital Logic Circuit Design 3.4 Product-of-Sums Simplification 3.5 Don't-Care Conditions

Dr. Muhammad Mahmoud

جامعة الملك فهد للبترول والمعادن King Fahd University of Petroleum & Minerals



October 1, 2013





#### Introduction

• Can you give an example of don't-care condition





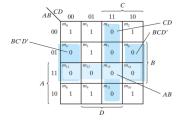
#### Lecture Outline

- 1 The Map Method
  - Product-of-Sums Simplification
  - Don't-Care Conditions



- $F(A, B, C, D) = \sum (0, 1, 2, 5, 8, 9, 10)$
- F = B'D' + B'C' + A'C'D



- F' = AB + CD + BD'
- Using DeMorgan's F = (A' + B')(C' + D')(B' + D)





• 
$$F = B'D' + B'C' + A'C'D$$

B'

C'

A'

D





• 
$$F = (A' + B')(C' + D')(B' + D)$$






X	y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0
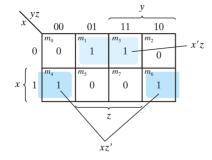
$$\bullet$$
  $F = m_1 + m_3 + m_4 + m_6$ 







- F = x'z + xz'
- F' = xz + x'z'
- (F')' = F = (x' + z')(x + z)





- What if the function was given as product of maxterms?
- F = (A' + B' + C')(B + D)
- F' = ABC + B'D'
- Mark F' minterms' squares with 0's and the remaining squares with 1's.

#### Don't-Care Conditions


• Simplify  $F(w,x,y,z) = \sum (1,3,7,11,15)$  with don't-care conditions  $d(w,x,y,z) = \sum (0,2,5)$ 

\	yz			y			
wx		00	01	11	10		
w'x'	00	X	1	1	M <sub>2</sub>		
(	)1	0	m <sub>5</sub>	$m_7$ 1	0		
	1	m <sub>12</sub>	m <sub>13</sub>	m <sub>15</sub>	m <sub>14</sub> 0	) x	
w {	0	m <sub>8</sub>	m <sub>9</sub> 0	m <sub>11</sub>	m <sub>10</sub> 0	ĺ	
z vz							

• F = yz + w'x'



#### Don't-Care Conditions

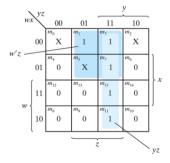

• 
$$F = yz + w'z$$





#### Summary

- The Map Method
  - Product-of-Sums Simplification
  - Don't-Care Conditions



#### Next Lecture

NAND and NOR Implementation.

