

## Experiment # 12

### Traffic Light Controller

#### Objectives

- Practice on the design of clocked sequential circuits.
- Applications of sequential circuits.

#### Overview

In this lab you are going to develop a Finite State Machine (FSM) for a traffic light controller that will control the operation of traffic lights at the cross road connection shown in Figure 12.1.

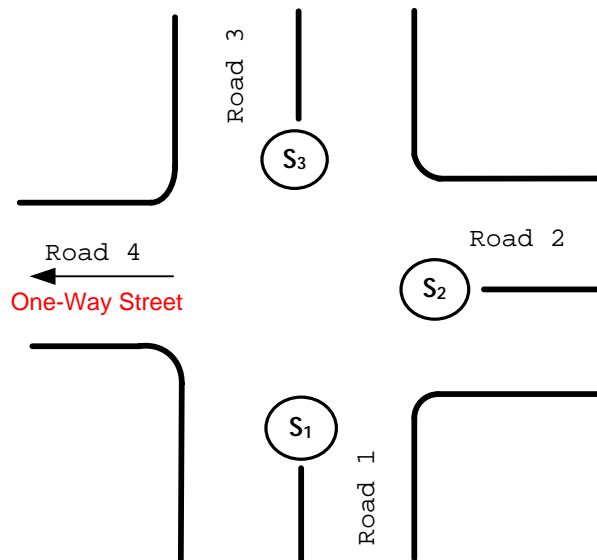



Figure 12.1: The three traffic light signals

## Design Specifications

There are three traffic light signals ( $S_1$ ,  $S_2$ , and  $S_3$ ), each alternating between two states, *RED* and *GREEN*. These signals control the traffic flow on the three roads,  $road_1$ ,  $road_2$ ,  $road_3$  in four possible states as follows.

- In *STATE 1*, traffic coming through  $road_1$  is allowed to go forward or left. ( $S_1 = \text{GREEN}$ ,  $S_2 = \text{RED}$ ,  $S_3 = \text{RED}$ )
- In *STATE 2*, traffic coming through  $road_2$  is allowed to go forward or left. ( $S_1 = \text{RED}$ ,  $S_2 = \text{GREEN}$ ,  $S_3 = \text{RED}$ )
- In *STATE 3*, traffic coming through  $road_3$  is allowed to go forward or left. ( $S_1 = \text{RED}$ ,  $S_2 = \text{RED}$ ,  $S_3 = \text{GREEN}$ )
- In *STATE 4*: no traffic coming from any road is allowed (All signals are RED)

Road 4 is a one-way street. No traffic can possibly come out from  $road_4$ . States 1 – 3 are enumerated in Figure 12.2

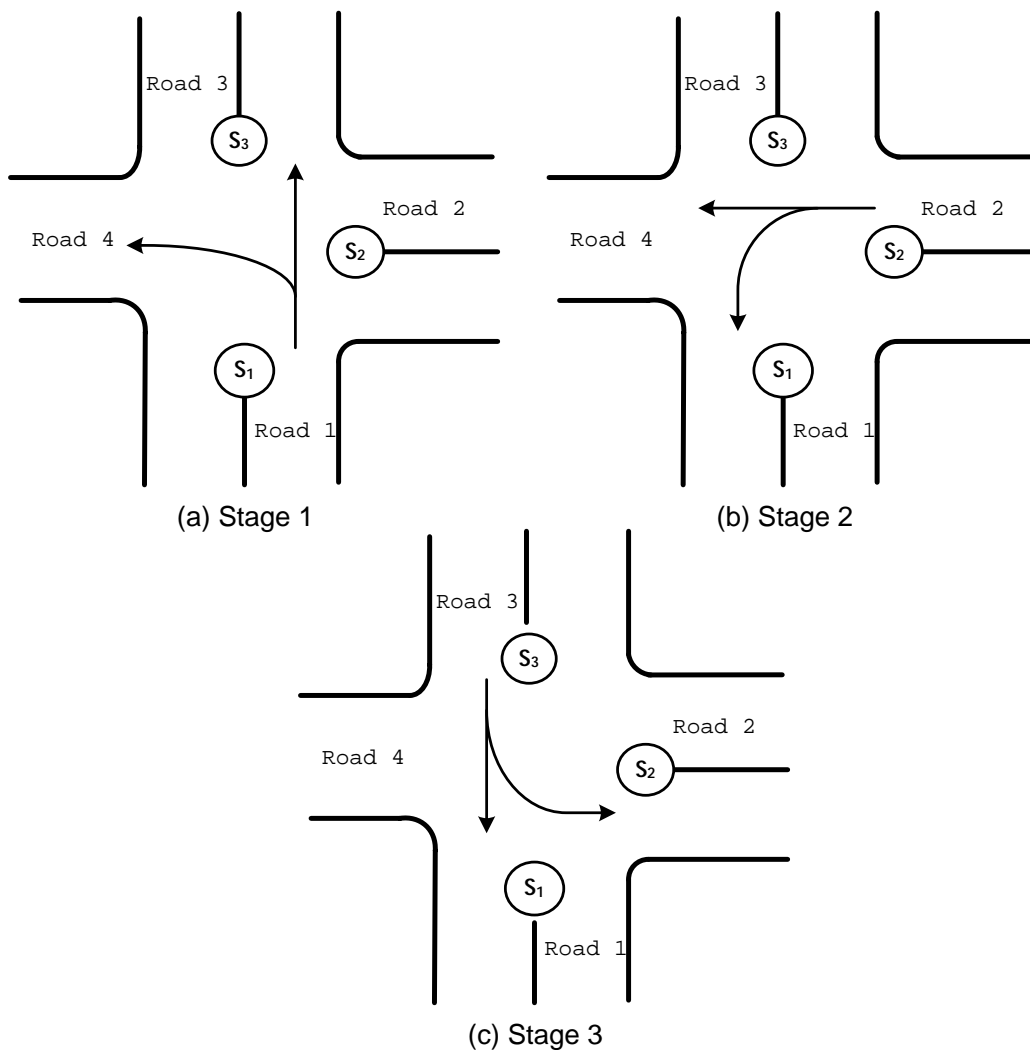

**Figure 12.2: Traffic states**

The operation of the three light signals ( $S_1$ - $S_3$ ) is controlled through an arrangement of *traffic sensors* and *traffic light controller* circuit as shown in Figure 12.3. There are three traffic sensors  $x_1$ ,  $x_2$  &  $x_3$ , which sense the presence of traffic on the roads 1-3 as illustrated in Table 12.1. The controller operation is determined by the output of these three sensors as enumerated in Table 12.2.

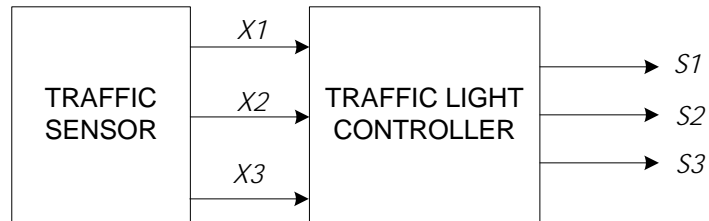


Figure 12.3: Traffic Sensor and Traffic Light Controller Circuit

**Table 12.1: Traffic Sensor Signals**

$x_3 x_2 x_1$	Indication
0 0 0	All roads have no traffic
0 0 1	<b>Road<sub>2</sub></b> and <b>Road<sub>3</sub></b> have no traffic
0 1 0	<b>Road<sub>1</sub></b> and <b>Road<sub>3</sub></b> have no traffic
0 1 1	<b>Road<sub>1</sub></b> and <b>Road<sub>2</sub></b> have traffic
1 0 0	<b>Road<sub>3</sub></b> has traffic
1 0 1	<b>Road<sub>2</sub></b> has no traffic
1 1 0	<b>Road<sub>1</sub></b> and has no traffic
1 1 1	All roads have traffic

**Table 12.2: Traffic Sensors and Controller Operation**

$x_3 x_2 x_1$	Indication
0 0 0	Stay at <b>STATE 4</b>
0 0 1	Stay at <b>STATE 1</b>
0 1 0	Stay at <b>STATE 2</b>
0 1 1	Alternate between <b>STATE 1</b> and <b>STATE 2</b>
1 0 0	Stay at <b>STATE 3</b>
1 0 1	Alternate between <b>STATE 1</b> and <b>STATE 3</b>
1 1 0	Alternate between <b>STATE 2</b> and <b>STATE 3</b>
1 1 1	Normal operation: <b>STATE 1, STATE 2, STATE 3, STATE 1, .....</b>

The design of the traffic controller module requires using D-flip flops with asynchronous clear. Assume that the controller has three inputs:  $x_3, x_2, x_1$  coming from the traffic sensor, and three outputs:  $S_1, S_2$ , and  $S_3$ , which control the operation of the three traffic light signals (logic 1 represents a GREEN signal and logic 0 represents a RED signal).

**Pre-Lab**

- You are expected to know the design procedure of synchronous sequential circuit.
- Obtain either a state diagram or a state table for the circuit. In this case, it would be appropriate to get the state table directly (use the table below).
- Derive the flip-flop input equations from the state table.
- Derive output equations for the traffic signals.

	$x_3$	$x_2$	$x_1$	A	B	$A^+ / D_A$	$B^+ / D_B$	$S_1$	$S_2$	$S_3$
0										
1										
2										
3										
4										
5										
6										
7										
8										
9										
10										
11										
12										
13										
14										
15										
16										
17										
18										
19										
20										
21										
22										
23										
24										
25										
26										
27										
28										
29										
30										
31										

**In-Lab**

- In a new project, open a new schematic sheet and implement the functions that you have obtained in the pre-lab.
- Use D-Flip flops with Asynchronous Clear from the library.
- Constrain the inputs of your circuit to 3 of the level switches (SWs) and the outputs to 3 LEDs. It is also preferable to constrain flip-flop outputs to LEDs.
- Use 2 BTNs, one to provide a clock signal (*Beware of switch debouncing problems*) and the other as an asynchronous clear. Connect these inputs to the respective inputs of the flip-flops.
- Check your circuit for errors and fix them.
- Simulate your design.
- Download your design.
- Verify its functionality by applying different input combinations and compare it with your state table. Demonstrate your work to the instructor.

**Post-Lab**

- Document your design by providing a diagram of your circuit
- As a bonus propose a modification to your design that will take the following into account: If the circuit is alternating between different states (for example if  $x_3 x_2 x_1 = 1 1 1$ ), each state should remain no more than 10 sec before moving to the next state and so on.