

Boolean Algebra and Logic Gates

COE 202

Digital Logic Design

Dr. Muhamed Mudawar

King Fahd University of Petroleum and Minerals

Presentation Outline

- ❖ Boolean Algebra
- ❖ Boolean Functions and Truth Tables
- ❖ DeMorgan's Theorem
- ❖ Algebraic manipulation and expression simplification
- ❖ Logic gates and logic diagrams
- ❖ Minterms and Maxterms
- ❖ Sum-Of-Products and Product-Of-Sums

Boolean Algebra

- ❖ Introduced by George Boole in 1854
- ❖ Two-valued Boolean algebra is also called switching algebra
- ❖ A set of two values: $B = \{0, 1\}$
- ❖ Three basic operations: **AND**, **OR**, and **NOT**
- ❖ The **AND** operator is denoted by a dot (\cdot)
 - ✧ $x \cdot y$ or xy is read: x **AND** y
- ❖ The **OR** operator is denoted by a plus ($+$)
 - ✧ $x + y$ is read: x **OR** y
- ❖ The **NOT** operator is denoted by (') or an overbar ($\bar{\quad}$).
 - ✧ x' or \bar{x} is the complement of x

Postulates of Boolean Algebra

1. Closure: the result of any Boolean operation is in $B = \{0, 1\}$

2. Identity element with respect to $+$ is 0: $x + 0 = 0 + x = x$

Identity element with respect to \cdot is 1: $x \cdot 1 = 1 \cdot x = x$

3. Commutative with respect to $+$: $x + y = y + x$

Commutative with respect to \cdot : $x \cdot y = y \cdot x$

4. \cdot is distributive over $+$: $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$

$+$ is distributive over \cdot : $x + (y \cdot z) = (x + y) \cdot (x + z)$

5. For every x in B , there exists x' in B (called complement of x) such that: $x + x' = 1$ and $x \cdot x' = 0$

AND, OR, and NOT Operators

- ❖ The following tables define $x \cdot y$, $x + y$, and x'
- ❖ $x \cdot y$ is the **AND** operator
- ❖ $x + y$ is the **OR** operator
- ❖ x' is the **NOT** operator

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

x	x'
0	1
1	0

Boolean Functions

- ❖ Boolean functions are described by expressions that consist of:
 - ❖ Boolean variables, such as: x , y , etc.
 - ❖ Boolean constants: 0 and 1
 - ❖ Boolean operators: AND (\cdot), OR ($+$), NOT ($'$)
 - ❖ Parentheses, which can be nested
- ❖ Example: $f = x(y + w'z)$
 - ❖ The dot operator is implicit and need not be written
- ❖ Operator precedence: to avoid ambiguity in expressions
 - ❖ Expressions within parentheses should be evaluated first
 - ❖ The NOT ($'$) operator should be evaluated second
 - ❖ The AND (\cdot) operator should be evaluated third
 - ❖ The OR ($+$) operator should be evaluated last

Truth Table

- ❖ A truth table can represent a Boolean function
- ❖ List all possible combinations of 0's and 1's assigned to variables
- ❖ If n variables then 2^n rows
- ❖ Example: Truth table for $f = xy' + x'z$

x	y	z	y'	xy'	x'	x'z	f = xy' + x'z
0	0	0	1	0	1	0	0
0	0	1	1	0	1	1	1
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	1	1	0	0	1
1	0	1	1	1	0	0	1
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0

DeMorgan's Theorem

$$\diamond (x + y)' = x' y'$$

$$\diamond (x y)' = x' + y'$$

Can be verified
Using a Truth Table

x	y	x'	y'	x+y	(x+y)'	x'y'	x y	(x y)'	x' + y'
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

Identical

Identical

\diamond Generalized DeMorgan's Theorem:

$$\diamond (x_1 + x_2 + \dots + x_n)' = x_1' \cdot x_2' \cdot \dots \cdot x_n'$$

$$\diamond (x_1 \cdot x_2 \cdot \dots \cdot x_n)' = x_1' + x_2' + \dots + x_n'$$

Complementing Boolean Functions

- ❖ What is the complement of $f = x'yz' + xy'z'$?
- ❖ Use DeMorgan's Theorem:
 - ✧ Complement each variable and constant
 - ✧ Interchange AND and OR operators
- ❖ So, what is the complement of $f = x'yz' + xy'z'$?

Answer: $f' = (x + y' + z)(x' + y + z)$

- ❖ **Example 2:** Complement $g = (a' + bc)d' + e$

- ❖ **Answer:** $g' = (a(b' + c') + d)e'$

Algebraic Manipulation of Expressions

❖ The objective is to acquire skills in manipulating Boolean expressions, to transform them into simpler form.

❖ **Example 1:** prove $x + xy = x$ (absorption theorem)

❖ **Proof:** $x + xy = x \cdot 1 + xy$ $x \cdot 1 = x$
 $= x \cdot (1 + y)$ Distributive \cdot over $+$
 $= x \cdot 1 = x$ $(1 + y) = 1$

❖ **Example 2:** prove $x + x'y = x + y$ (simplification theorem)

❖ **Proof:** $x + x'y = (x + x')(x + y)$ Distributive $+$ over \cdot
 $= 1 \cdot (x + y)$ $(x + x') = 1$
 $= x + y$

Consensus Theorem

❖ **Prove that:** $xy + x'z + yz = xy + x'z$ (consensus theorem)

❖ **Proof:** $xy + x'z + yz$

$$= xy + x'z + 1 \cdot yz$$

$$= xy + x'z + (x + x')yz$$

$$= xy + x'z + \cancel{xyz} + x'yz$$

$$= xy + xyz + x'z + x'yz$$

$$= xy \cdot 1 + xyz + x'z \cdot 1 + x'zy$$

$$= xy(1 + z) + x'z(1 + y)$$

$$= xy \cdot 1 + x'z \cdot 1$$

$$= xy + x'z$$

$$yz = 1 \cdot yz$$

$$1 = (x + x')$$

Distributive \cdot over $+$

Associative commutative $+$

$$xy = xy \cdot 1, \quad x'yz = x'zy$$

Distributive \cdot over $+$

$$1 + z = 1, \quad 1 + y = 1$$

$$xy \cdot 1 = xy, \quad x'z \cdot 1 = x'z$$

Summary of Boolean Algebra

	Property	Dual Property
Identity	$x + 0 = x$	$x \cdot 1 = x$
Complement	$x + x' = 1$	$x \cdot x' = 0$
Null	$x + 1 = 1$	$x \cdot 0 = 0$
Idempotence	$x + x = x$	$x \cdot x = x$
Involution	$(x')' = x$	
Commutative	$x + y = y + x$	$x y = y x$
Associative	$(x + y) + z = x + (y + z)$	$(x y) z = x (y z)$
Distributive	$x (y + z) = xy + xz$	$x + yz = (x + y)(x + z)$
Absorption	$x + xy = x$	$x(x + y) = x$
Simplification	$x + x'y = x + y$	$x(x' + y) = xy$
De Morgan	$(x + y)' = x' y'$	$(x y)' = x' + y'$

Duality Principle

- ❖ The **dual** of a Boolean expression can be obtained by:
 - ✧ Interchanging AND (\cdot) and OR ($+$) operators
 - ✧ Interchanging 0's and 1's
- ❖ Example: the dual of $x(y + z')$ is $x + yz'$
 - ✧ The complement operator does not change
- ❖ The properties of Boolean algebra appear in **dual pairs**
 - ✧ If a property is proven to be true then its dual is also true

	Property	Dual Property
Identity	$x + 0 = x$	$x \cdot 1 = x$
Complement	$x + x' = 1$	$x \cdot x' = 0$
Distributive	$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$

Expression Simplification

- ❖ Using Boolean algebra to simplify expressions
- ❖ Expression should contain the smallest number of **literals**
- ❖ A **literal** is a variable that may or may not be complemented
- ❖ **Example:** simplify $ab + a'cd + a'bd + a'cd' + abcd$
- ❖ **Solution:** $ab + a'cd + a'bd + a'cd' + abcd$ (15 literals)
 $= ab + abcd + a'cd + a'cd' + a'bd$ (15 literals)
 $= ab + ab(cd) + a'c(d + d') + a'bd$ (13 literals)
 $= ab + a'c + a'bd$ (7 literals)
 $= ba + \cancel{ba'd} + a'c$ (7 literals)
 $= b(a + a'd) + a'c$ (6 literals)
 $= b(a + d) + a'c$ (5 literals only)


Importance of Boolean Algebra

- ❖ Our objective is to learn how to design digital circuits
- ❖ These circuits use signals with two possible values
- ❖ Logic **0** is a **low** voltage signal (around 0 volts)
- ❖ Logic **1** is a **high** voltage signal (e.g. 5 or 3.3 volts)
- ❖ The physical value of a signal is the actual voltage it carries, while its logic value is either 0 (low) or 1 (high)
- ❖ Having only two logic values (0 and 1) simplifies the implementation of the digital circuit


Next ...

- ❖ Boolean Algebra
- ❖ Boolean Functions and Truth Tables
- ❖ DeMorgan's Theorem
- ❖ Algebraic manipulation and expression simplification
- ❖ Logic gates and logic diagrams
- ❖ Minterms and Maxterms
- ❖ Sum-Of-Products and Product-Of-Sums


Logic Gates and Symbols

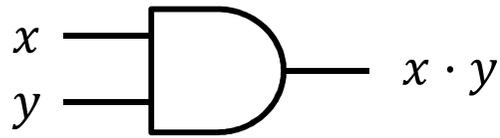


AND gate

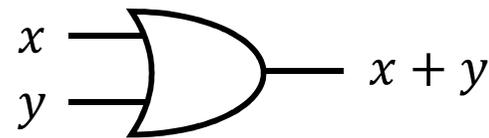


OR gate

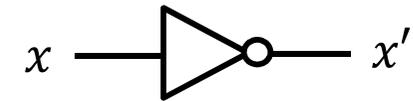


NOT gate (inverter)

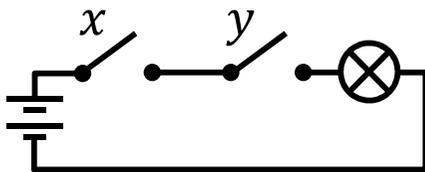

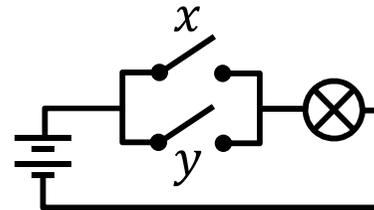AND: Switches in series
logic 0 is open switch



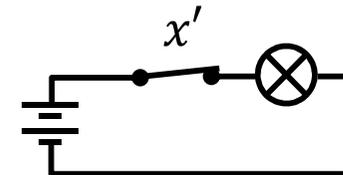OR: Switches in parallel
logic 0 is open switch



NOT: Switch is normally
closed when x is 0

- ❖ In the earliest computers, relays were used as mechanical switches controlled by electricity (coils)
- ❖ Today, tiny transistors are used as electronic switches that implement the logic gates (CMOS technology)


Truth Table and Logic Diagram

- ❖ Given the following logic function: $f = x(y' + z)$
- ❖ Draw the corresponding truth table and logic diagram

Truth Table

x	y	z	$y' + z$	$f = x(y' + z)$
0	0	0	1	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1

Logic Diagram

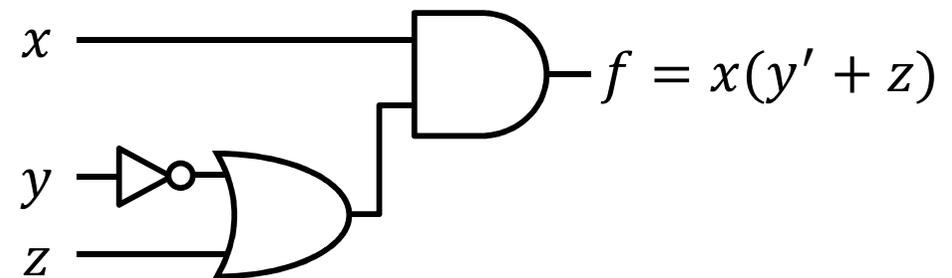

Truth Table and Logic Diagram describe the same function f . Truth table is unique, but logic expression and logic diagram are not. This gives flexibility in implementing logic functions.

Combinational Circuit

❖ A combinational circuit is a block of logic gates having:


n inputs: x_1, x_2, \dots, x_n

m outputs: f_1, f_2, \dots, f_m


❖ Each output is a function of the input variables

❖ Each output is determined from present combination of inputs

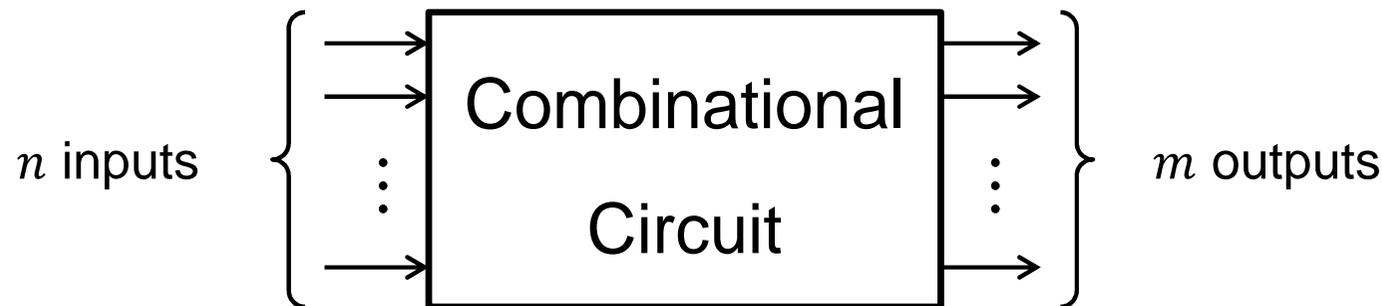❖ Combination circuit performs operation specified by logic gates



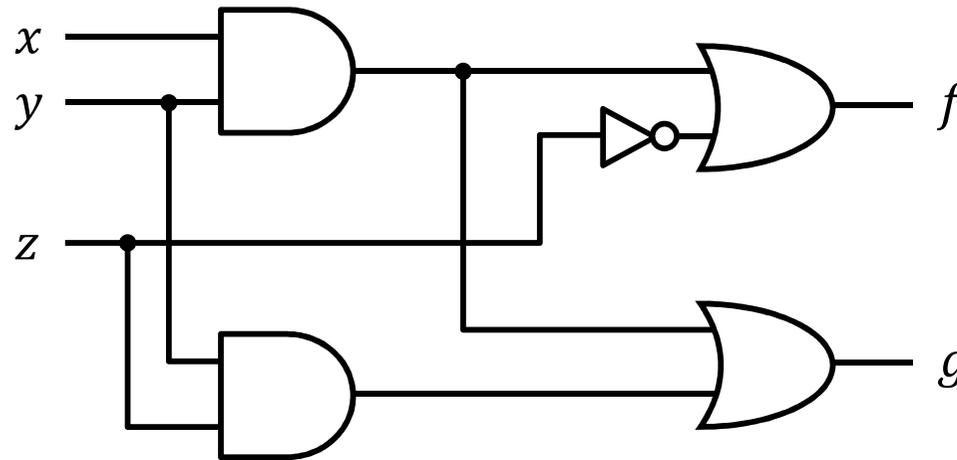Example of a Simple Combinational Circuit



❖ The above circuit has:

✧ Three inputs: x , y , and z

✧ Two outputs: f and g

❖ What are the logic expressions of f and g ?

❖ **Answer:** $f = xy + z'$

$g = xy + yz$

From Truth Tables to Gate Implementation

- ❖ Given the truth table of a Boolean function f , how do we implement the truth table using logic gates?

Truth Table

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

What is the logic expression of f ?

What is the gate implementation of f ?

To answer these questions, we need to define Minterms and Maxterms

Minterms and Maxterms

- ❖ **Minterms** are AND terms with every variable present in either true or complement form
- ❖ **Maxterms** are OR terms with every variable present in either true or complement form

Minterms and Maxterms for 2 variables x and y

x	y	index	Minterm	Maxterm
0	0	0	$m_0 = x'y'$	$M_0 = x + y$
0	1	1	$m_1 = x'y$	$M_1 = x + y'$
1	0	2	$m_2 = xy'$	$M_2 = x' + y$
1	1	3	$m_3 = xy$	$M_3 = x' + y'$

- ❖ For n variables, there are 2^n Minterms and Maxterms

Minterms and Maxterms for 3 Variables

x	y	z	index	Minterm	Maxterm
0	0	0	0	$m_0 = x'y'z'$	$M_0 = x + y + z$
0	0	1	1	$m_1 = x'y'z$	$M_1 = x + y + z'$
0	1	0	2	$m_2 = x'yz'$	$M_2 = x + y' + z$
0	1	1	3	$m_3 = x'yz$	$M_3 = x + y' + z'$
1	0	0	4	$m_4 = xy'z'$	$M_4 = x' + y + z$
1	0	1	5	$m_5 = xy'z$	$M_5 = x' + y + z'$
1	1	0	6	$m_6 = xyz'$	$M_6 = x' + y' + z$
1	1	1	7	$m_7 = xyz$	$M_7 = x' + y' + z'$

Maxterm M_i is the **complement** of Minterm m_i

$$M_i = m_i' \quad \text{and} \quad m_i = M_i'$$

Purpose of the Index

- ❖ Minterms and Maxterms are designated with an index
- ❖ The **index** for the Minterm or Maxterm, expressed as a **binary number**, is used to determine whether the variable is shown in the true or complemented form
- ❖ For Minterms:
 - ✧ '1' means the variable is **Not Complemented**
 - ✧ '0' means the variable is **Complemented**
- ❖ For Maxterms:
 - ✧ '0' means the variable is **Not Complemented**
 - ✧ '1' means the variable is **Complemented**

Sum-Of-Minterms (SOM) Canonical Form

Truth Table

x	y	z	f	Minterm
0	0	0	0	
0	0	1	0	
0	1	0	1	$m_2 = x'yz'$
0	1	1	1	$m_3 = x'yz$
1	0	0	0	
1	0	1	1	$m_5 = xy'z$
1	1	0	0	
1	1	1	1	$m_7 = xyz$

Sum of Minterm entries
that evaluate to '1'

Focus on the '1' entries

$$f = m_2 + m_3 + m_5 + m_7$$

$$f = \sum (2, 3, 5, 7)$$

$$f = x'yz' + x'yz + xy'z + xyz$$

Examples of Sum-Of-Minterms

$$\diamond f(a, b, c, d) = \sum(2, 3, 6, 10, 11)$$

$$\diamond f(a, b, c, d) = m_2 + m_3 + m_6 + m_{10} + m_{11}$$

$$\diamond f(a, b, c, d) = a'b'cd' + a'b'cd + a'bcd' + ab'cd' + ab'cd$$

$$\diamond g(a, b, c, d) = \sum(0, 1, 12, 15)$$

$$\diamond g(a, b, c, d) = m_0 + m_1 + m_{12} + m_{15}$$

$$\diamond g(a, b, c, d) = a'b'c'd' + a'b'c'd + abc'd' + abcd$$

Product-Of-Maxterms (POM) Canonical Form

Truth Table

x	y	z	f	Maxterm
0	0	0	0	$M_0 = x + y + z$
0	0	1	0	$M_1 = x + y + z'$
0	1	0	1	
0	1	1	1	
1	0	0	0	$M_4 = x' + y + z$
1	0	1	1	
1	1	0	0	$M_6 = x' + y' + z$
1	1	1	1	

Product of Maxterm entries
that evaluate to '0'

Focus on the '0' entries

$$f = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

$$f = \prod (0, 1, 4, 6)$$

$$f = (x + y + z)(x + y + z')(x' + y + z)(x' + y' + z)$$

Examples of Product-Of-Maxterms

$$\diamond f(a, b, c, d) = \prod(1, 3, 11)$$

$$\diamond f(a, b, c, d) = M_1 \cdot M_3 \cdot M_{11}$$

$$\diamond f(a, b, c, d) = (a + b + c + d')(a + b + c' + d')(a' + b + c' + d')$$

$$\diamond g(a, b, c, d) = \prod(0, 5, 13)$$

$$\diamond g(a, b, c, d) = M_0 \cdot M_5 \cdot M_{13}$$

$$\diamond f(a, b, c, d) = (a + b + c + d)(a + b' + c + d')(a' + b' + c + d')$$

Conversions between Canonical Forms

❖ The same Boolean function f can be expressed in two ways:

❖ Sum-of-Minterms $f = m_0 + m_2 + m_3 + m_5 + m_7 = \Sigma(0, 2, 3, 5, 7)$

❖ Product-of-Maxterms $f = M_1 \cdot M_4 \cdot M_6 = \Pi(1, 4, 6)$

Truth Table

x	y	z	f	Minterms	Maxterms
0	0	0	1	$m_0 = x'y'z'$	
0	0	1	0		$M_1 = x + y + z'$
0	1	0	1	$m_2 = x'yz'$	
0	1	1	1	$m_3 = x'yz$	
1	0	0	0		$M_4 = x' + y + z$
1	0	1	1	$m_5 = xy'z$	
1	1	0	0		$M_6 = x' + y' + z$
1	1	1	1	$m_7 = xyz$	

To convert from one canonical form to another, interchange the symbols Σ and Π and list those numbers missing from the original form.

Function Complement

Truth Table

x	y	z	f	f'
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

Given a Boolean function f

$$f(x, y, z) = \sum (0, 2, 3, 5, 7) = \prod (1, 4, 6)$$

Then, the complement f' of function f

$$f'(x, y, z) = \prod (0, 2, 3, 5, 7) = \sum (1, 4, 6)$$

The complement of a function expressed by a Sum of Minterms is the Product of Maxterms with the same indices. Interchange the symbols Σ and Π , but keep the same list of indices.

Summary of Minterms and Maxterms


- ❖ There are 2^n Minterms and Maxterms for Boolean functions with n variables, indexed from 0 to $2^n - 1$
- ❖ Minterms correspond to the **1-entries** of the function
- ❖ Maxterms correspond to the **0-entries** of the function
- ❖ Any Boolean function can be expressed as a Sum-of-Minterms and as a Product-of-Maxterms
- ❖ For a Boolean function, given the list of Minterm indices one can determine the list of Maxterms indices (and vice versa)
- ❖ The complement of a Sum-of-Minterms is a Product-of-Maxterms with the same indices (and vice versa)

Sum-of-Products and Products-of-Sums

- ❖ Canonical forms contain a larger number of literals
 - ✧ Because the Minterms (and Maxterms) must contain, by definition, all the variables either complemented or not
- ❖ Another way to express Boolean functions is in **standard** form
- ❖ Two standard forms: **Sum-of-Products** and **Product-of -Sums**
- ❖ Sum of Products (**SOP**)
 - ✧ Boolean expression is the **ORing** (sum) of **AND terms** (products)
 - ✧ Examples: $f_1 = xy' + xz$ $f_2 = y + xy'z$
- ❖ Products of Sums (**POS**)
 - ✧ Boolean expression is the **ANDing** (product) of **OR terms** (sums)
 - ✧ Examples: $f_3 = (x + z)(x' + y')$ $f_4 = x(x' + y' + z)$


Two-Level Gate Implementation

$$f_1 = xy' + xz$$

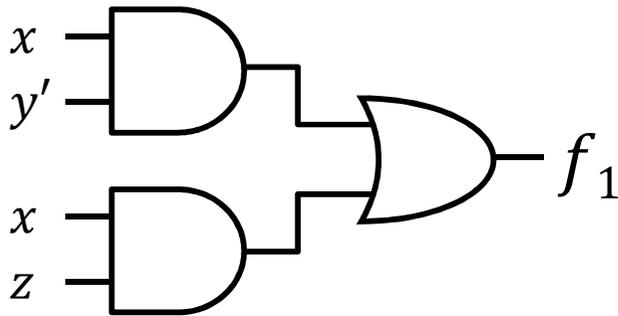


**AND-OR
implementations**

$$f_2 = y + xy'z$$

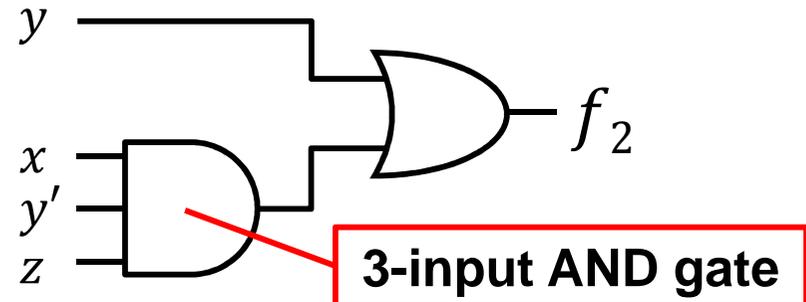


$$f_3 = (x + z)(x' + y')$$

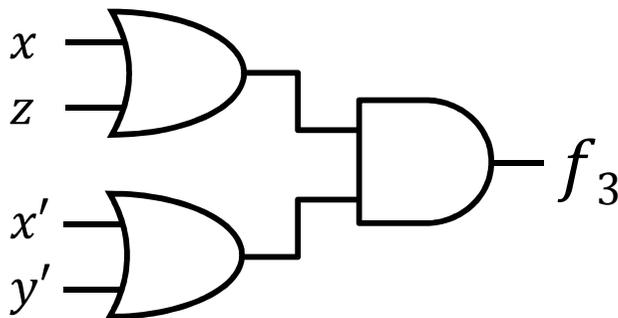

**OR-AND
implementations**

$$f_4 = x(x' + y' + z)$$

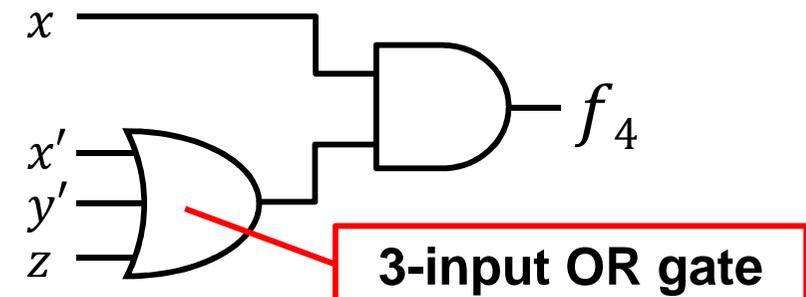


Two-Level vs. Three-Level Implementation

- ❖ $h = ab + cd + ce$ (6 literals) is a sum-of-products
- ❖ h may also be written as: $h = ab + c(d + e)$ (5 literals)
- ❖ However, $h = ab + c(d + e)$ is a non-standard form
 - ✧ $h = ab + c(d + e)$ is not a sum-of-products nor a product-of-sums

2-level implementation

$$h = ab + cd + ce$$

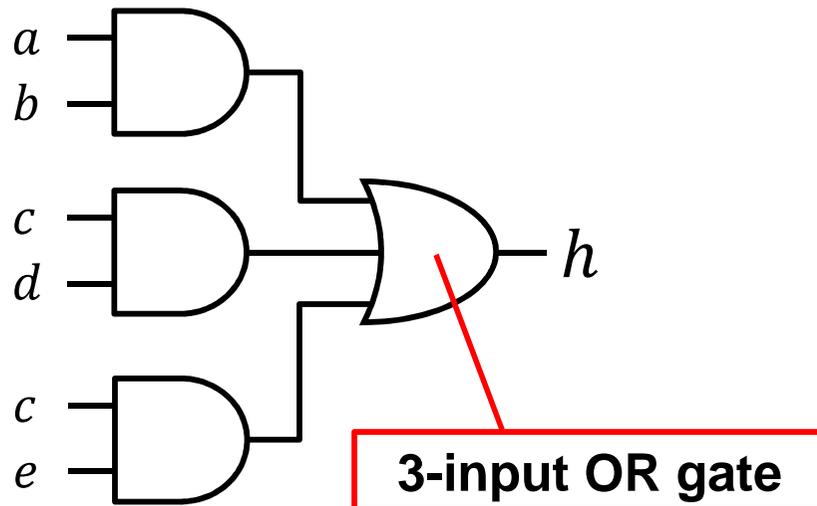

3-level implementation

$$h = ab + c(d + e)$$

