

Additional Gates

COE 202

Digital Logic Design

Dr. Muhamed Mudawar

King Fahd University of Petroleum and Minerals


Presentation Outline

- ❖ Additional Gates and Symbols
- ❖ Universality of NAND and NOR gates
- ❖ NAND-NAND and NOR-NOR implementations
- ❖ Exclusive OR (XOR) and Exclusive NOR (XNOR) gates
- ❖ Odd and Even functions


Additional Logic Gates and Symbols

❖ Why?

 
- ❖ Low cost implementation
- ❖ Useful in implementing Boolean functions




AND gate

 


OR gate

 


NOT gate (inverter)

 


NAND gate

 


NOR gate

 


Buffer

 

XOR gate

 


XNOR gate

 


3-state gate

NAND Gate

 - ❖ The NAND gate has the following symbol and truth table
- ❖ NAND represents **NOT AND**
- ❖ The small bubble circle represents the invert function



NAND gate

 


Another symbol for NAND

x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


- ❖ NAND gate is implemented efficiently in CMOS technology
 - ✧ In terms of chip area and speed

NOR Gate

 - ❖ The NOR gate has the following symbol and truth table
- ❖ NOR represents **NOT OR**
- ❖ The small bubble circle represents the invert function



NOR gate

 

Another symbol for NOR

x	y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- ❖ NOR gate is implemented efficiently in CMOS technology
 - ✧ In terms of chip area and speed


The NAND Gate is Universal

- ❖ NAND gates can implement any Boolean function
- ❖ NAND gates can be used as inverters, or to implement AND/OR
- ❖ A single-input NAND gate is an inverter

$$x \text{ NAND } x = (x \cdot x)' = x'$$


- ❖ AND is equivalent to NAND with **inverted output**
 
$$(x \text{ NAND } y)' = ((x \cdot y)')' = x \cdot y \text{ (AND)}$$



- ❖ OR is equivalent to NAND with **inverted inputs**
 
$$(x' \text{ NAND } y') = (x' \cdot y')' = x + y \text{ (OR)}$$




The NOR Gate is also Universal

- ❖ NOR gates can implement any Boolean function
- ❖ NOR gates can be used as inverters, or to implement AND/OR
- ❖ A single-input NOR gate is an inverter

$$x \text{ NOR } x = (x + x)' = x'$$


- ❖ OR is equivalent to NOR with **inverted output**
 
$$(x \text{ NOR } y)' = ((x + y)')' = x + y \text{ (OR)}$$



- ❖ AND is equivalent to NOR with **inverted inputs**
 
$$(x' \text{ NOR } y') = (x' + y')' = x \cdot y \text{ (AND)}$$



Non-Associative NAND / NOR Operations

- ❖ Unlike AND, NAND operation is NOT associative

$$(x \text{ NAND } y) \text{ NAND } z \neq x \text{ NAND } (y \text{ NAND } z)$$

$$(x \text{ NAND } y) \text{ NAND } z = ((xy)'z)' = ((x' + y')z)' = xy + z'$$

$$x \text{ NAND } (y \text{ NAND } z) = (x(yz)')' = (x(y' + z'))' = x' + yz$$

- ❖ Unlike OR, NOR operation is NOT associative


$$(x \text{ NOR } y) \text{ NOR } z \neq x \text{ NOR } (y \text{ NOR } z)$$

$$(x \text{ NOR } y) \text{ NOR } z = ((x + y)' + z)' = ((x'y') + z)' = (x + y)z'$$


$$x \text{ NOR } (y \text{ NOR } z) = (x + (y + z)')' = (x + (y'z'))' = x'(y + z)$$

Multiple-Input NAND / NOR Gates

 
NAND/NOR gates can have multiple inputs, similar to AND/OR gates




2-input NAND gate

 


3-input NAND gate

 


4-input NAND gate

 

2-input NOR gate

 

3-input NOR gate

 

4-input NOR gate

Note: a 3-input NAND is a single gate, NOT a combination of two 2-input gates. The same can be said about other multiple-input NAND/NOR gates.


NAND - NAND Implementation

- ❖ Consider the following sum-of-products expression:


$$f = bd + a'cd'$$

- ❖ A 2-level **AND-OR** circuit can be converted easily to a 2-level **NAND-NAND** implementation


2-Level AND-OR

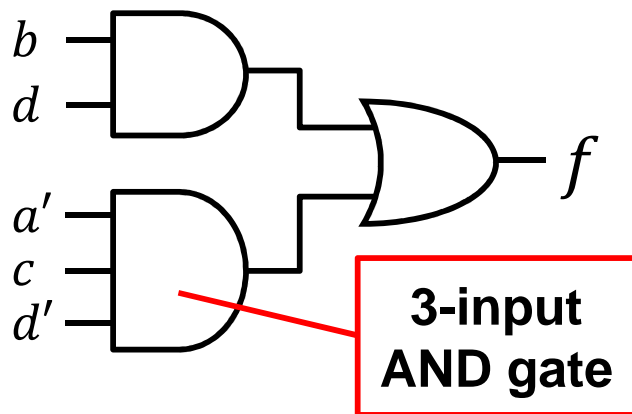

Inserting Bubbles

 

2-Level NAND-NAND

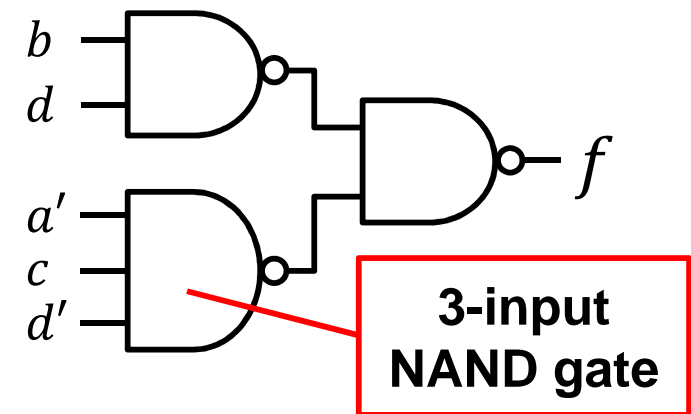

Two successive bubbles on same line cancel each other


NOR - NOR Implementation

- ❖ Consider the following product-of-sums expression:


$$g = (a + d)(b + c + d')$$

- ❖ A 2-level **OR-AND** circuit can be converted easily to a 2-level **NOR-NOR** implementation


2-Level OR-AND

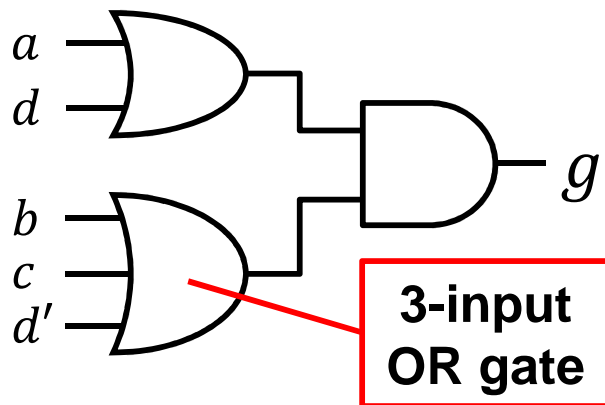

Inserting Bubbles

 

2-Level NOR-NOR

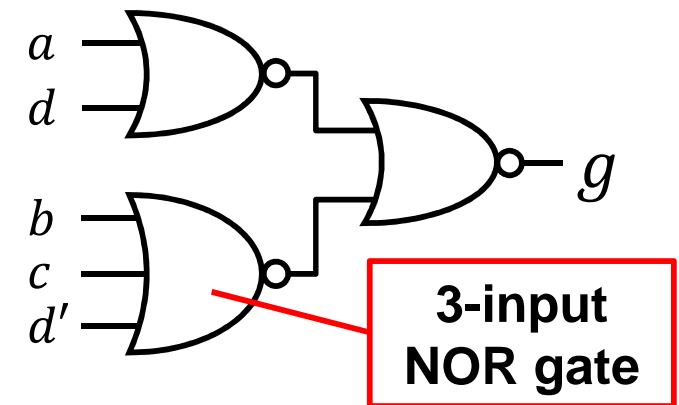

Two successive bubbles on same line cancel each other


Exclusive OR / Exclusive NOR

- ❖ Exclusive OR (XOR) is an important Boolean operation used extensively in logic circuits
- ❖ Exclusive NOR (XNOR) is the complement of XOR


x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

x	y	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

XNOR is also known as **equivalence**

 

XOR gate

 

XNOR gate

XOR / XNOR Functions

- ❖ The XOR function is: $x \oplus y = xy' + x'y$
- ❖ The XNOR function is: $(x \oplus y)' = xy + x'y'$
- ❖ XOR and XNOR gates are complex
 - ✧ Can be implemented as a true gate, or by
 - ✧ Interconnecting other gate types
- ❖ XOR and XNOR gates do not exist for more than two inputs
 - ✧ For 3 inputs, use two XOR gates
 - ✧ The cost of a 3-input XOR gate is greater than the cost of two XOR gates
- ❖ Uses for XOR and XNOR gates include:
 - ✧ Adders, subtractors, multipliers, counters, incrementers, decrementers
 - ✧ Parity generators and checkers

XOR and XNOR Properties

$$\nabla x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$\nabla x \oplus x = 0$$

$$x \oplus x' = 1$$

$$\nabla x \oplus y = y \oplus x$$

$$\nabla x' \oplus y' = x \oplus y$$

$$\nabla (x \oplus y)' = x' \oplus y = x \oplus y'$$

XOR and XNOR are **associative** operations

$$\nabla (x \oplus y) \oplus z = x \oplus (y \oplus z) = x \oplus y \oplus z$$

$$\nabla ((x \oplus y)' \oplus z)' = (x \oplus (y \oplus z)')' = x \oplus y \oplus z$$

Odd Function

- ❖ Output is 1 if the **number of 1's is odd in the inputs**
- ❖ Output is the XOR operation on all input variables


Odd Function with 3 inputs

x	y	z	fodd
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$f_{odd} = \sum (1, 2, 4, 7)$$

$$f_{odd} = x'y'z + x'yz' + xy'z' + xyz$$

$$f_{odd} = x \oplus y \oplus z$$

 

Implementation using two XOR gates

Even Function


Even Function with 4 inputs

w	x	y	z	feven
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

- ❖ Output is 1 if the **number of 1's is even** in the inputs (complement of odd function)
- ❖ Output is the XNOR operation on all inputs


$$feven = \sum (0, 3, 5, 6, 9, 10, 12, 15)$$
 
$$feven = (w \oplus x \oplus y \oplus z)'$$



Implementation using two XOR gates and one XNOR

Parity Generators and Checkers

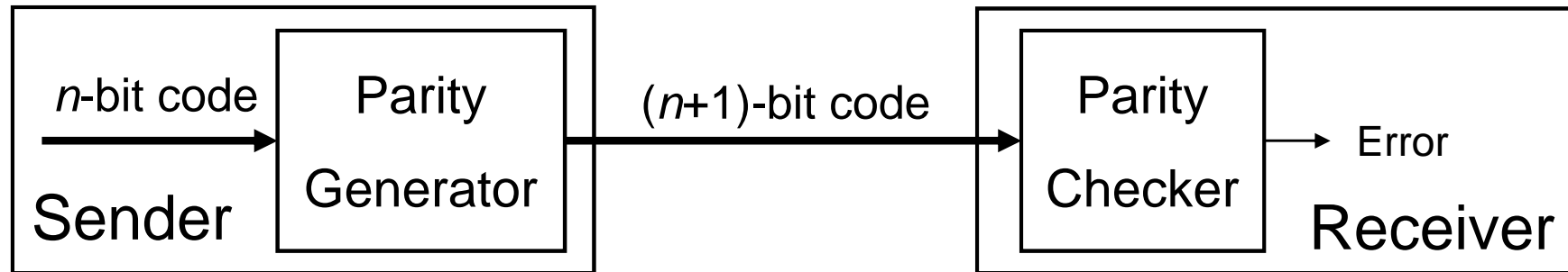

- ❖ A parity bit is added to the n -bit code
 - ✧ Produces $(n+1)$ -bit code with an odd (or even) count of 1's
- ❖ **Odd parity:** count of 1's in the $(n+1)$ -bit code is **odd**
 - ✧ Use an **even function** to generate the **odd parity bit**
 - ✧ Use an **even function** to check the $(n+1)$ -bit code
- ❖ **Even parity:** count of 1's in the $(n+1)$ -bit code is **even**
 - ✧ Use an **odd function** to generate the **even parity bit**
 - ✧ Use an **odd function** to check the $(n+1)$ -bit code

Example of Parity Generator and Checker

❖ Design even parity generator & checker for 3-bit codes

❖ Solution:

- ✧ Use **3-bit odd function** to generate even parity bit P .
- ✧ Use **4-bit odd function** to check if there is an error E in even parity.
- ✧ Given that: $xyz = 001$ then $P = 1$.
The sender transmits $Pxyz = 1001$.
- ✧ If y changes from 0 to 1 between generator and checker, the parity checker receives $Pxyz = 1011$ and produces $E = 1$, indicating an error.

