

King Fahd University of Petroleum & Minerals


College of Computer Sciences and Engineering

Department of Computer Engineering

COE 202: Fundamentals of Computer Engineering (071)

Assignment 5

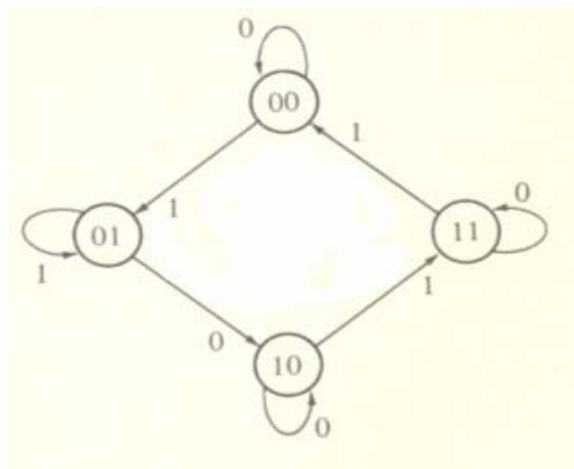1. Implement the following state diagram using SR and T flip flops.



2. Re-solve the following table by using

A → JK flip-flop

B → D flip-flop

C → T flip-flop

Present state			Input	Next state			Flip-flop inputs						Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>SA</i>	<i>RA</i>	<i>SB</i>	<i>RB</i>	<i>SC</i>	<i>RC</i>	<i>y</i>
0	0	1	0	0	0	1	0	X	0	X	X	0	0
0	0	1	1	0	1	0	0	X	1	0	0	1	0
0	1	0	0	0	1	1	0	X	X	0	1	0	0
0	1	0	1	1	0	0	1	0	0	1	0	X	0
0	1	1	0	0	0	1	0	X	0	1	X	0	0
0	1	1	1	1	0	0	1	0	0	1	0	1	0
1	0	0	0	1	0	1	X	0	0	X	1	0	0
1	0	0	1	1	0	0	X	0	0	X	0	X	1
1	0	1	0	0	0	1	0	1	0	X	X	0	0
1	0	1	1	1	0	0	X	0	0	X	0	1	1

3. A sequential circuit has one input and one output. The state diagram is shown below. Design the sequential circuit using D flip-flops and ROM.

