

2-30

$$x \oplus y = x\bar{y} + \bar{x}y$$

$$\text{Dual of } x \oplus y = (\bar{x} + y)(x + \bar{y})$$

$$\text{Complement of } x \oplus y = \overline{(x\bar{y} + \bar{x}y)} = (x + \bar{y})(\bar{x} + y)$$

Hence, both are the same.

2-31

Disjunctive Theorem: if $f = a \oplus b$ & $ab = 0$
then $f = a + b$

$$\begin{aligned} \text{Proof: } f = a \oplus b &= \bar{a}b + a\bar{b} \\ &= \bar{a}b + a\bar{b} + ab \quad (\text{since } ab=0) \\ &= \bar{a}b + a(b + \bar{b}) \\ &= \bar{a}b + a = a + b \end{aligned}$$

$$F = AB\bar{C}D + A\bar{B} + \bar{A}D$$

We can see in the above function that,

$$(A\bar{B})(AB\bar{C}D) = 0$$

$$(A\bar{B})(\bar{A}D) = 0$$

$$(\bar{A}D)(AB\bar{C}D) = 0$$


$$\text{Thus, } F = AB\bar{C}D \oplus A\bar{D} \oplus \bar{A}D$$

$$= AB\bar{C}D \oplus [(\bar{A}+D)\bar{A}D + (A+\bar{D})A\bar{D}]$$

$$= AB\bar{C}D \oplus [\bar{A}D + A\bar{D}]$$


$$= AB\bar{C}D \oplus A \oplus D$$

Thus the circuit is as follows:

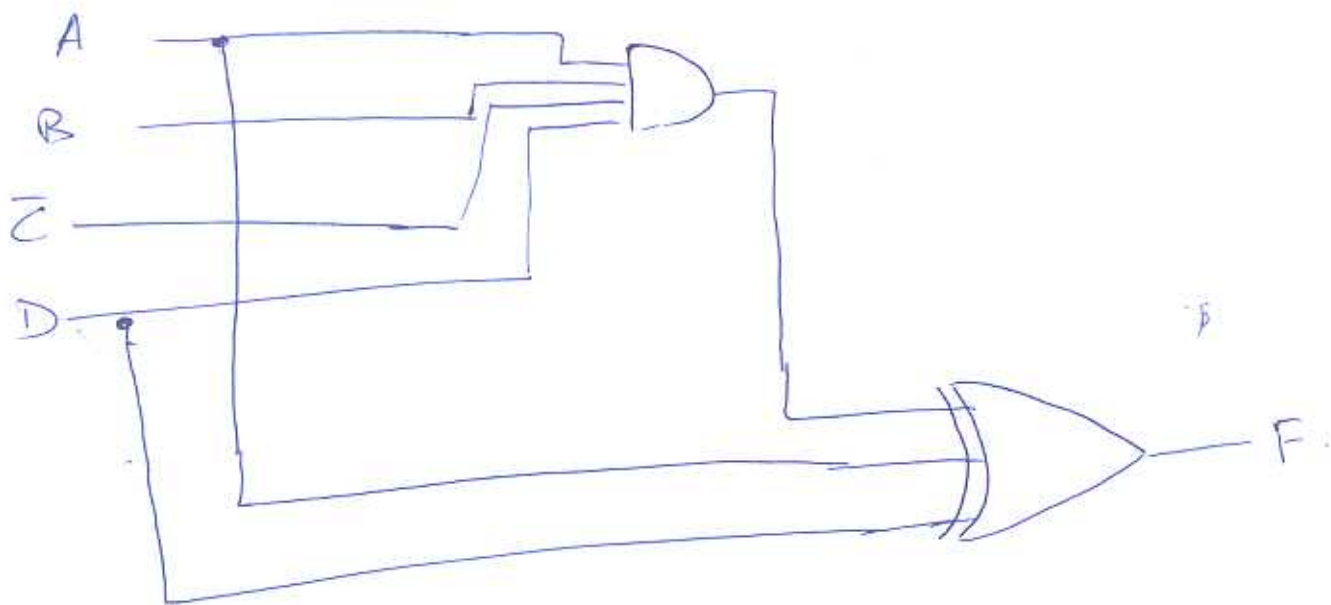


2-32

(a) $H = \bar{x}y + xz$

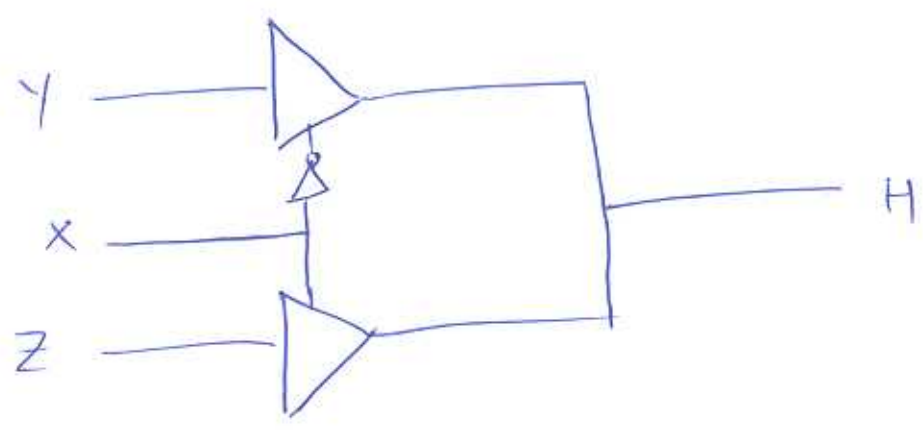


(b) $F = \bar{x}y + x\bar{y}$

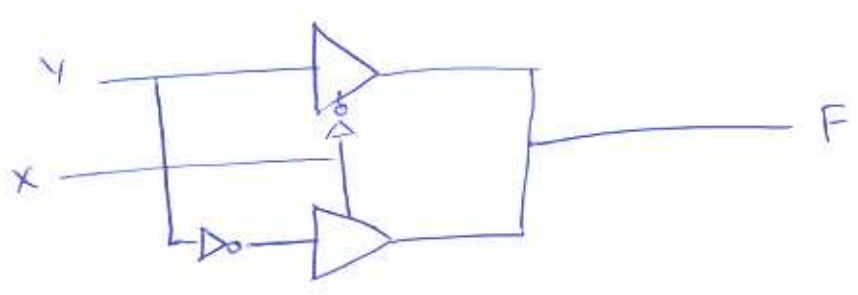


2-33

$F = \bar{A}BC + ABD + A\bar{B}\bar{D}$

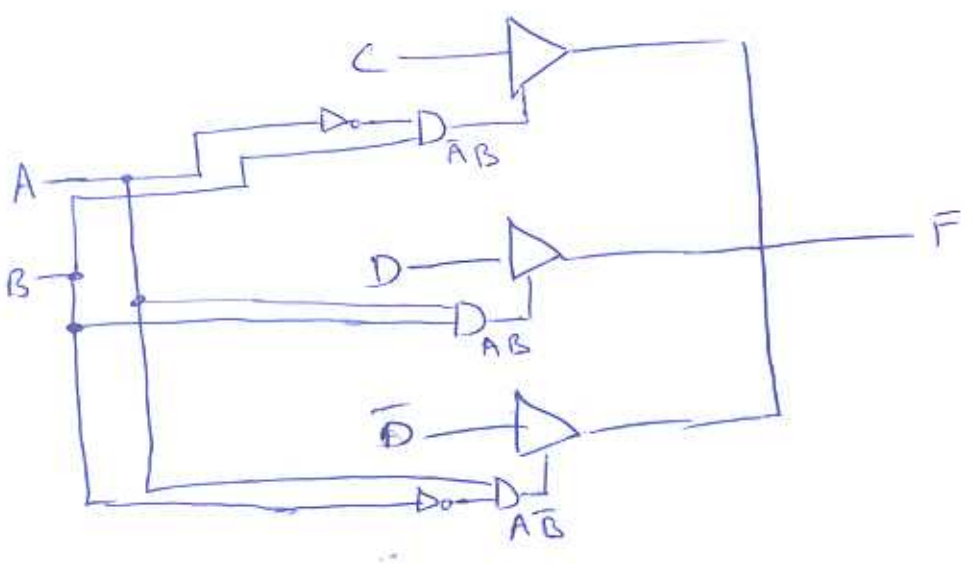

2-34

$$H = \bar{x}y + xz$$

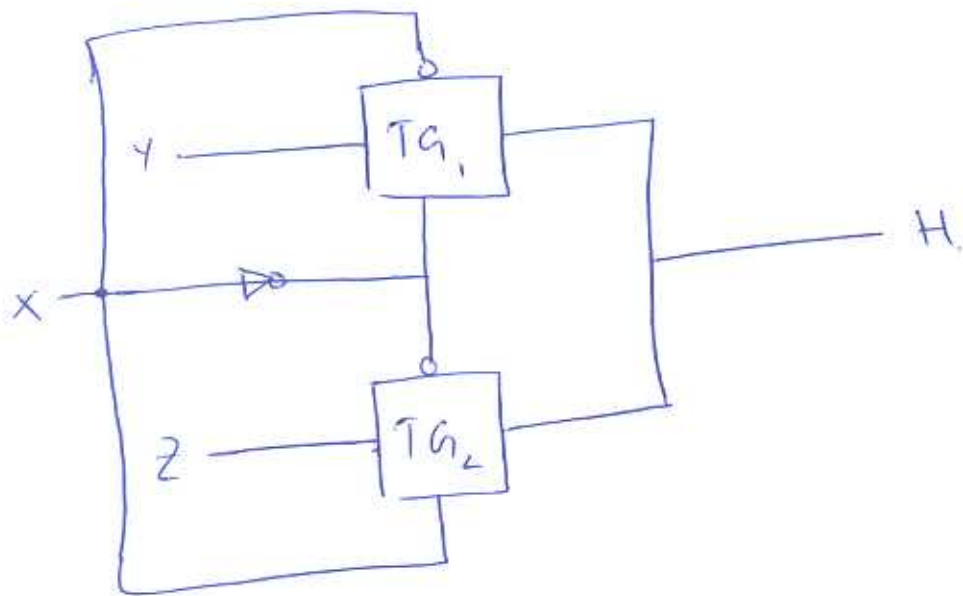

2-35

(a) The output F is High-impedance when both input A & B are 0's.

(b)

A	B	F
0	0	Hi-Z
0	1	C
1	0	\bar{D}
1	1	D

Since $\bar{A}\bar{B}$ is the only condition where Hi-Z exists, we can incorporate it in the enable logic so that F is never Hi-Z.

Let us assume we want F to be C when $\bar{A}\bar{B}$.
Thus, the enable logic for C will change as follows

$$\bar{A}B + \bar{A}\bar{B} = \bar{A}$$

