
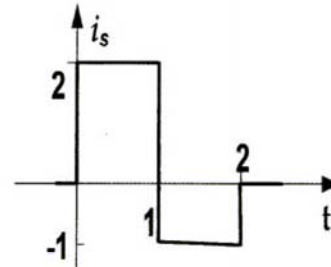


Q#1 For the given ' i_s ',

- Find the equations of ' V_C ' for the following ranges (14 marks)
 (a) $0 < t < 1$, (b) $1 < t < 2$, (c) $2 < t < \infty$

- Plot the result in part 1. (3 marks)

- Plot the results of ' V_R ' (3 marks)

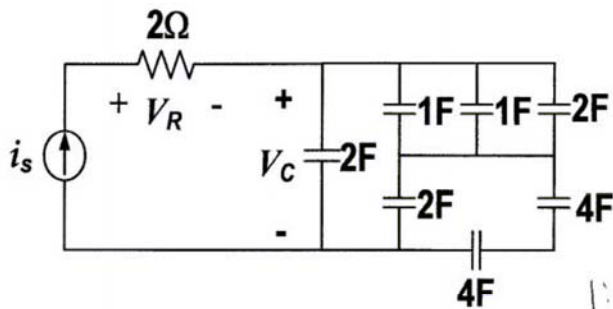

$$C_{eq} = \left([(4 \parallel 4) + 2] \parallel [1 + 1 + 2] \right) + 2$$

$$= ([2 + 2] \parallel [4]) + 2$$

$$= (4 \parallel 4) + 2 = 2 + 2 = 4F \quad (3 \text{ marks})$$

$$V_C = \frac{1}{C_{eq}} \int_{-\infty}^t i_s(\tau) d\tau$$

for $0 < t < 1$

$$V_C = \frac{1}{4} \int_0^t 2 d\tau = \frac{1}{2} t \quad (3 \text{ marks})$$

for $1 < t < 2$


$$V_C = \frac{1}{4} \int_1^t -1 d\tau + \left(\frac{1}{2}t\right)_{t=1} = -\frac{1}{4}(t-1) + \frac{1}{2} = -\frac{1}{4}t + \frac{3}{4} \quad (4 \text{ marks})$$

for $t > 2$


$$V_C = \frac{1}{4} \int_2^t i_s(\tau) d\tau + \left(-\frac{1}{4}t + \frac{3}{4}\right)_{t=2} = 0 + \left(-\frac{2}{4} + \frac{3}{4}\right) = \frac{1}{4} \quad (4 \text{ marks})$$

$$\therefore V_C = \begin{cases} 0 & t < 0 \\ t/2 & 0 < t < 1 \\ -\frac{1}{4}t + \frac{3}{4} & 1 < t < 2 \\ \frac{1}{4} & t > 2 \end{cases}$$

(2)

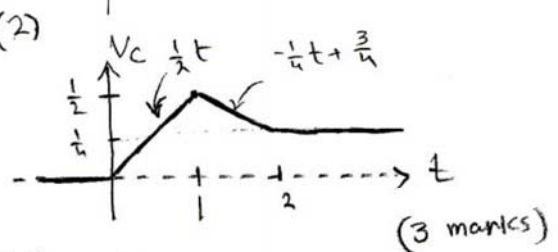


(3)

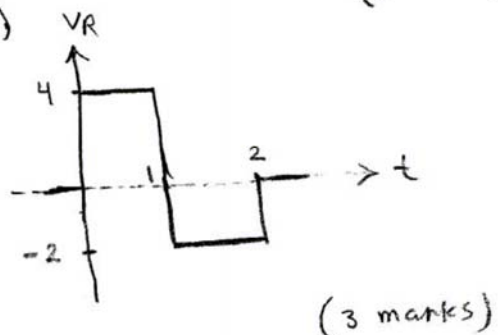

$$V_R = i_s(t) R = 2 i_s(t)$$

Problem 2

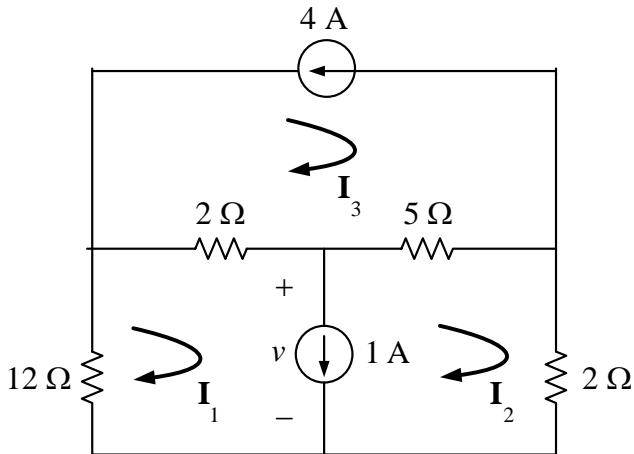

Using mesh analysis find

- (a) The mesh currents I_1, I_2, I_3 ?
- (b) the voltage $v(t)$?

Solution

$$I_3 = -4 \text{ A (by inspection)}$$


KVL on the super mesh

$$2(I_1 - I_3) + 5(I_2 - I_3) + 2I_2 + 12I_1 = 0$$

$$\Rightarrow 14I_1 + 7I_2 = 7I_3 = 7(-4) = -28 \quad (1)$$

$$I_1 - I_2 = 1 \quad (2)$$
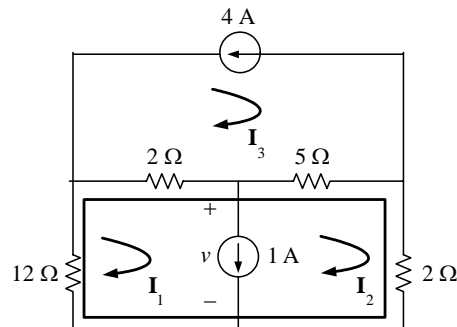
$$\Rightarrow \begin{bmatrix} 14 & 7 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -28 \\ 1 \end{bmatrix}$$



solving

$$\mathbf{I}_1 = \frac{\begin{vmatrix} -28 & 7 \\ 1 & -1 \end{vmatrix}}{\begin{vmatrix} 14 & 7 \\ 1 & -1 \end{vmatrix}} = \frac{28-7}{-14-7} = \frac{21}{-21} = -1 \text{ A}$$

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 14 & -28 \\ 1 & 1 \end{vmatrix}}{\begin{vmatrix} 14 & 7 \\ 1 & -1 \end{vmatrix}} = \frac{14+28}{-14-7} = \frac{42}{-21} = -2 \text{ A}$$

(c) KVL on the first mesh

$$2(\mathbf{I}_1 - \mathbf{I}_3) + v + 12\mathbf{I}_1 = 0$$


$$\Rightarrow v = -14\mathbf{I}_1 + 2\mathbf{I}_3 = -14(-1) + 2(-4) = 6 \text{ V}$$

OR KVL on the second mesh

$$5(\mathbf{I}_2 - \mathbf{I}_3) + 2\mathbf{I}_2 - v = 0$$

$$\Rightarrow v = 7\mathbf{I}_2 - 5\mathbf{I}_3 = 7(-2) - 5(-4) = 6 \text{ V}$$

Problem 3

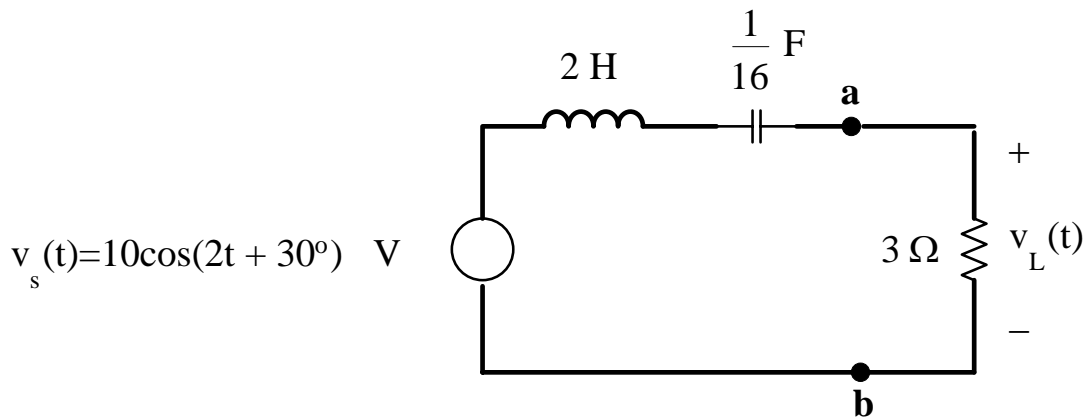

Using the Thevenin Reduction Method only, find $V_L(t)$ the voltage across the load resistor 3Ω ?

Solution


Transferring the circuit to the phasor domain

$$v_s(t) = 10\cos(2t + 30^\circ) \text{ V} \Rightarrow 10\angle 30^\circ \text{ V}$$

$$Z_L = j\omega L = j(2)(2) = j4 \Omega$$


$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(2)\left(\frac{1}{16}\right)} = -j8 \Omega$$

$$Z_R = 3 \Omega$$

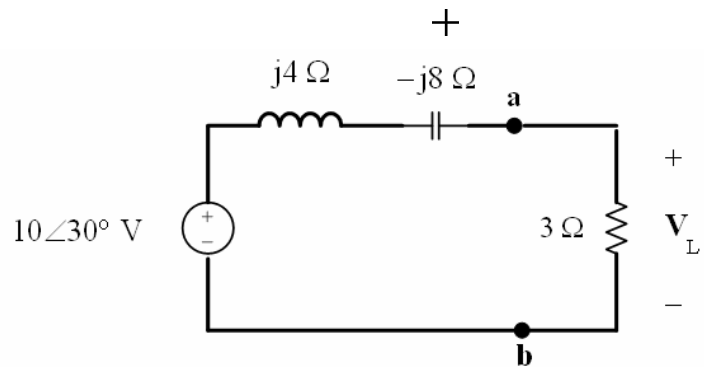



Finding the Thevenin equivalent


Removing the load resistant

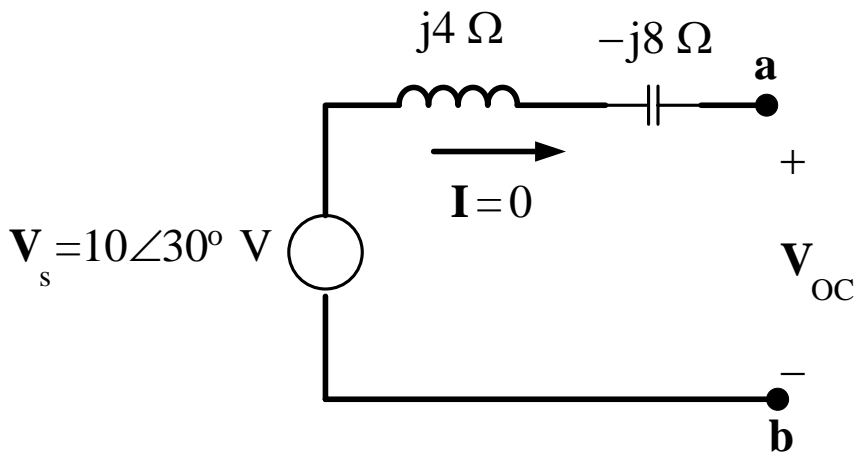

$$\Rightarrow V_{OC} = V_s = 10\angle 30^\circ \text{ V}$$

Deactivating the source (shorting it)

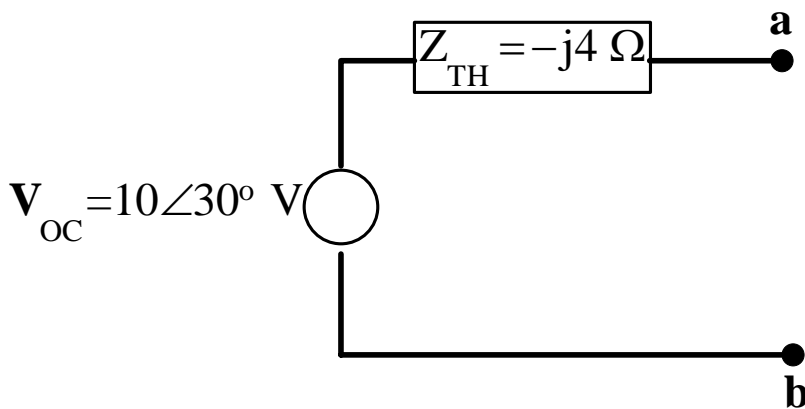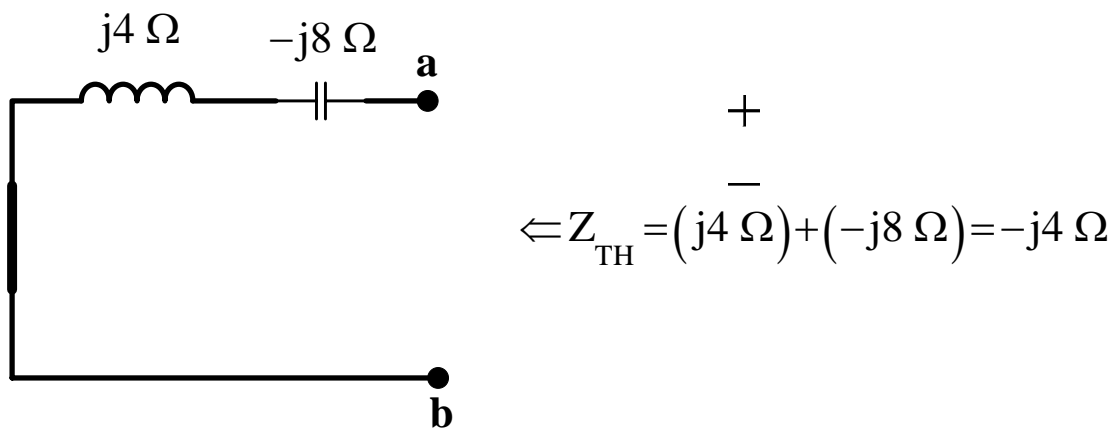

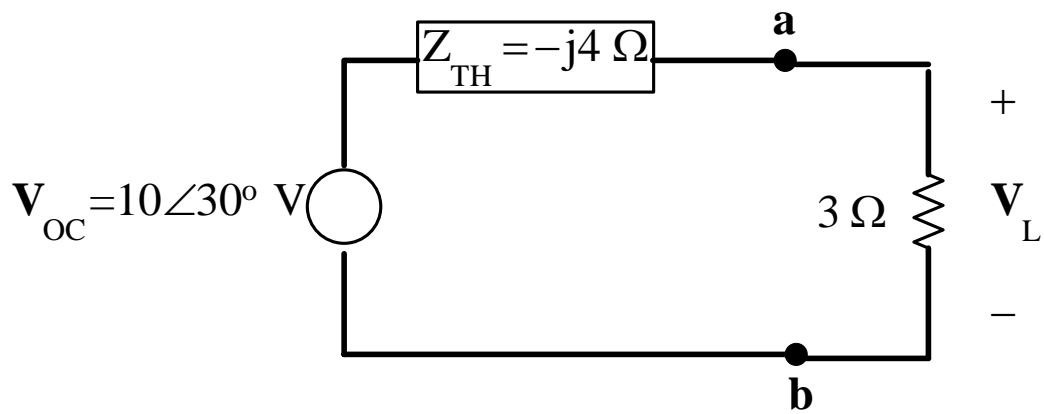

Using Voltage division

$$V_L = \frac{3}{(-j4 \Omega) + 3} 10\angle 30^\circ = \frac{3}{5\angle -53.13^\circ} 10\angle 30^\circ = 6\angle 83.13^\circ \text{ V}$$

$$\Rightarrow v_L(t) = 6\cos(2t + 83.13^\circ) \text{ V}$$