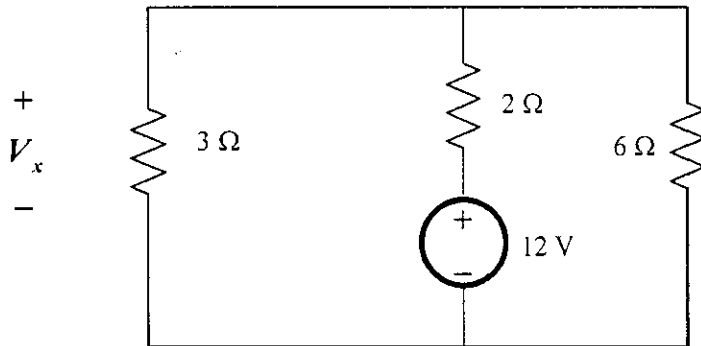



SEC	SER	ID	NAME
-----	-----	----	------



For the Circuit shown above Find  $V_x$  using **circuit reduction method only**? NO Voltage or Current division and no Source Transformation

Combining the  $6\Omega$  and  $3\Omega$  (parallel)
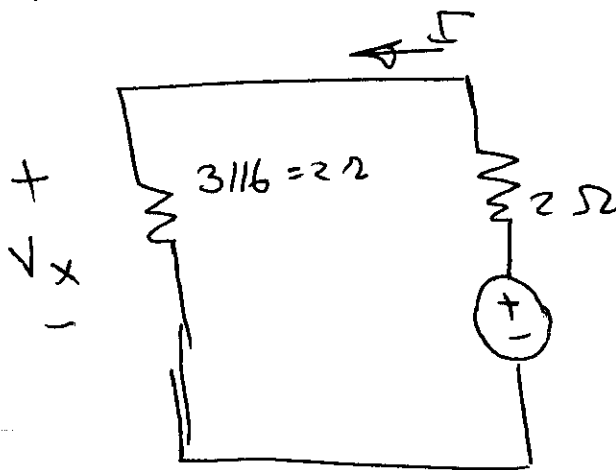
$$\Rightarrow 3 \parallel 6 = \frac{(3)(6)}{3+6} = 2\Omega$$



$$\underline{\text{KVL}} \quad -12 + 4I = 0$$

$$\Rightarrow I = 3A$$

$$V_x = 2(3) = 6V$$