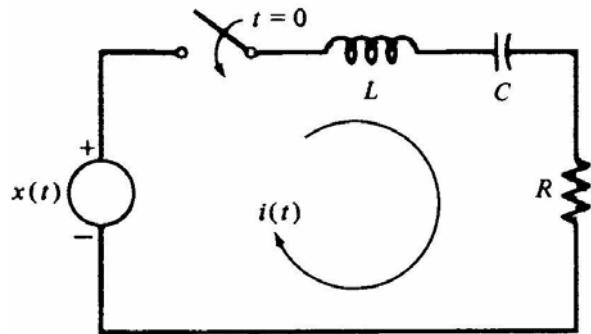


Chapter 6 Applications of the Laplace Transform

EXAMPLE 5-3



In analyzing the circuit, we first wrote down the differential equation using KVL

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_{-\infty}^t i(\lambda) d\lambda = x(t)$$

Initial condition $i(0^-) = 0$

Taking Laplace Transform for both side

$$\rightarrow LsI(s) + RI(s) + \frac{I(s)}{sC} + \frac{v_c(0^-)}{s} = X(s)$$


were $v_c(0^-) = \frac{1}{C} \int_{-\infty}^{0^-} i(\lambda) d\lambda$

Inverse Back

Solving for $I(s)$ $\rightarrow I(s) = \frac{sX(s) - v_c(0^-)}{L[s^2 + (R/L)s + 1/LC]}$ $\rightarrow i(t)$

In this chapter , we are going to do the

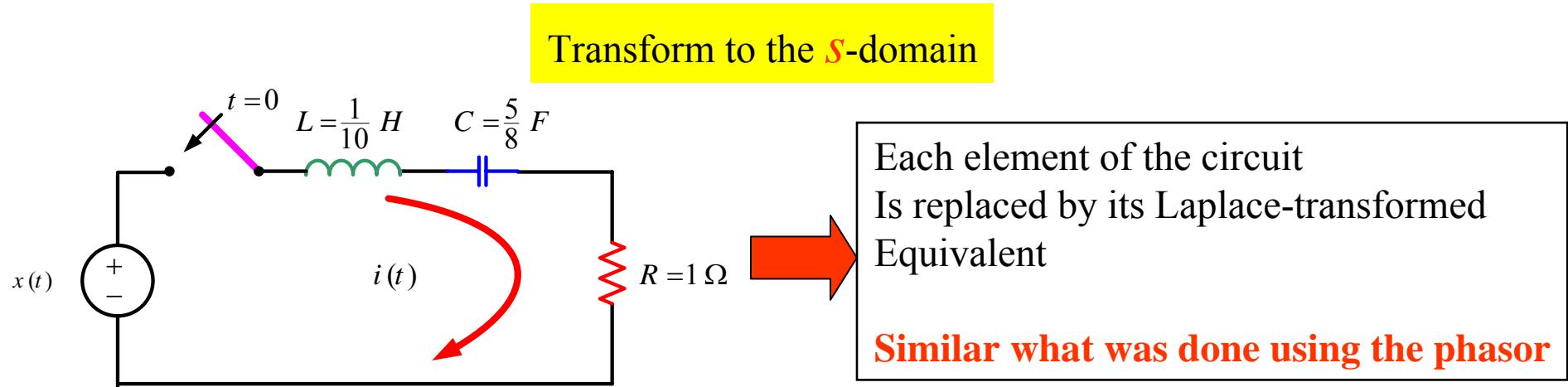First Transform the circuit to the s -domain (Laplace Transform)



Second Solve for the s-transformed required variable (i.e $I(s)$)
using all linear circuit techniques such as:

OHM , KVL, KCL , VDR, CDR, Thavenin, source transformation ,
Nodal and Mesh


Third Inverse back , to obtain the time domain variable $i(t)$


Laplace transform for the passive elements

R, L, C

$$\begin{array}{c} i(t) \\ \rightarrow \\ \text{---} \\ | \quad | \\ R \\ | \quad | \\ \text{---} \\ + v(t) - \end{array} \quad v(t) = R i(t) \quad \Rightarrow \quad V(s) = R I(s)$$

$$Z_R(s) = \frac{V(s)}{I(s)} = R$$

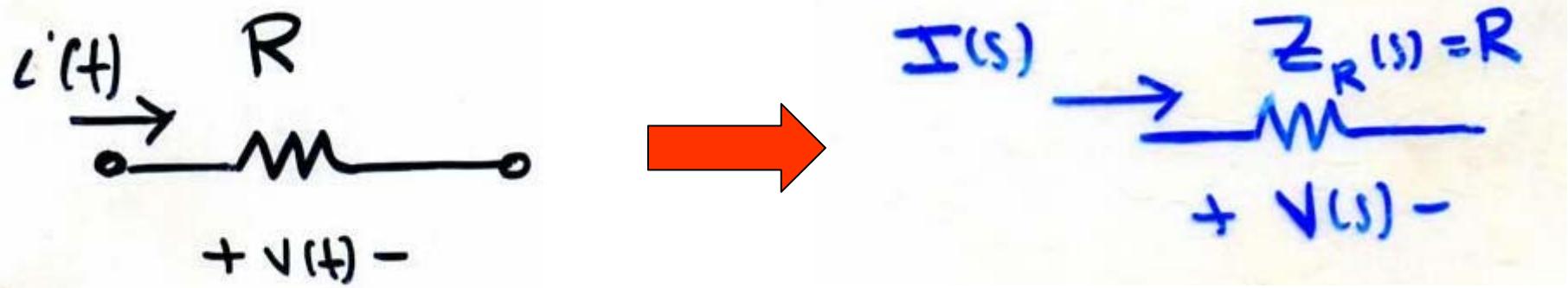

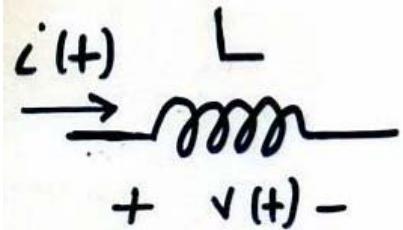

$$v(t) = L \frac{di(t)}{dt}$$

$$\Rightarrow V(s) = L [s I(s) - i(0)]$$

$$\frac{V(s)}{+} \xrightarrow{m} \frac{Ls}{V(s)} \left(+ \right) \frac{i(0)}{-}$$


$$I(s) = \frac{1}{Ls} V(s) + \frac{i(0)}{s}$$

For zero initial condition $i(0) = 0$

$$V(s) = Ls I(s)$$


$$Z_L(s) = \frac{V(s)}{I(s)} = Ls$$

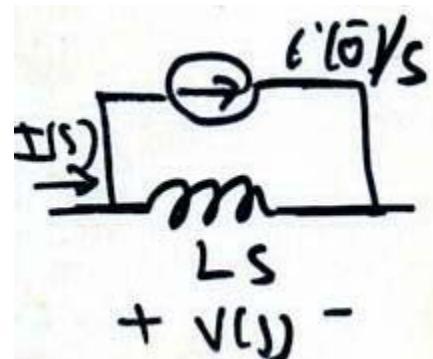zero initial current
 $\xrightarrow{I(s)} Z_L(s) = Ls$
 $\xrightarrow{m} + V(s) -$




$$I'(t) = C \frac{dV(t)}{dt}$$

$$\Rightarrow I(s) = C [sV(s) - v(0)]$$

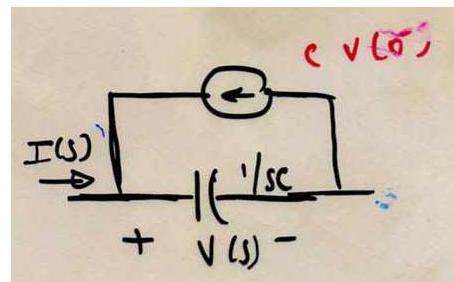
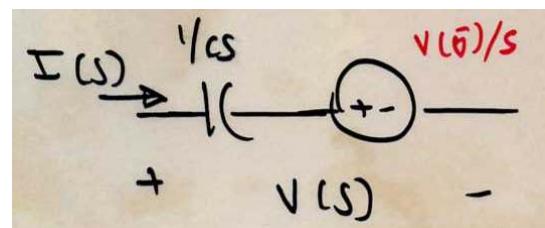
$$V(s) = \frac{1}{Cs} I(s) + \frac{v(0)}{s}$$




for zero initial conditions
 $v(0) = 0$

$$V(s) = \frac{1}{Cs} I(s)$$

$$\frac{I(s)}{V(s)} = \frac{Z_c(s)}{Cs}$$

Example 6-1

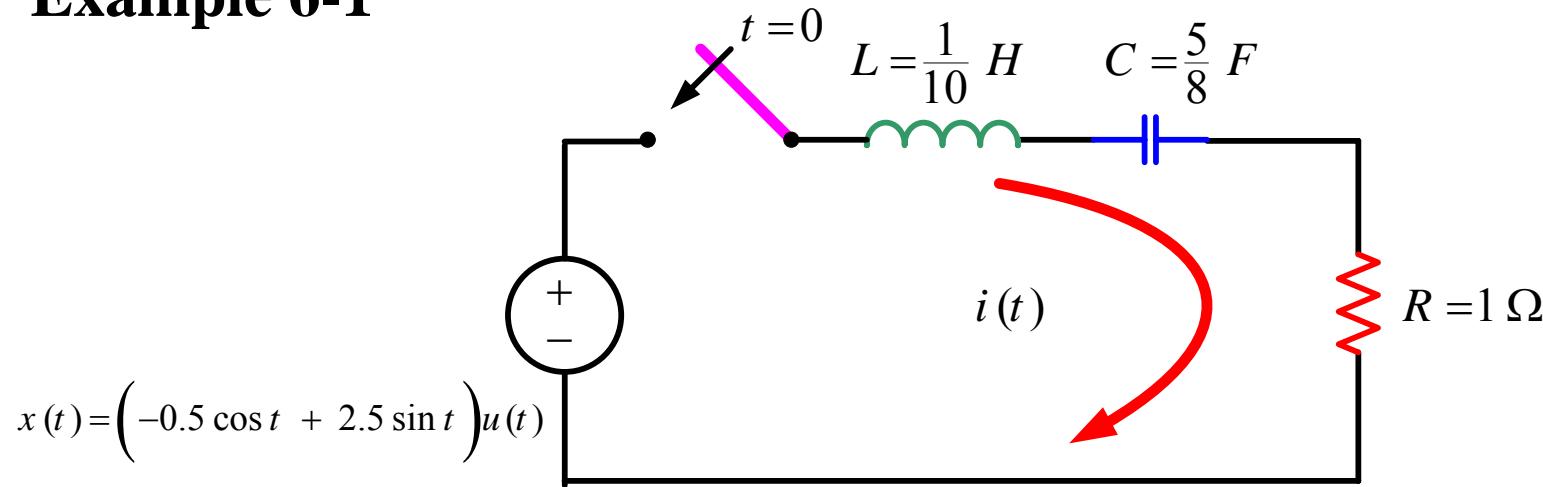




$$i_L(0^-) = 0 V \quad v_C(0^-) = -2 V$$


$$x(t) \Rightarrow X(s) = -\frac{0.5s}{s^2 + 1} + \frac{2.5s}{s^2 + 1}$$

$$L = \frac{1}{10} H \Rightarrow Z_L = \frac{s}{10} \Omega$$

$$C = \frac{5}{8} F \Rightarrow Z_C = \frac{8}{5s} \Omega$$
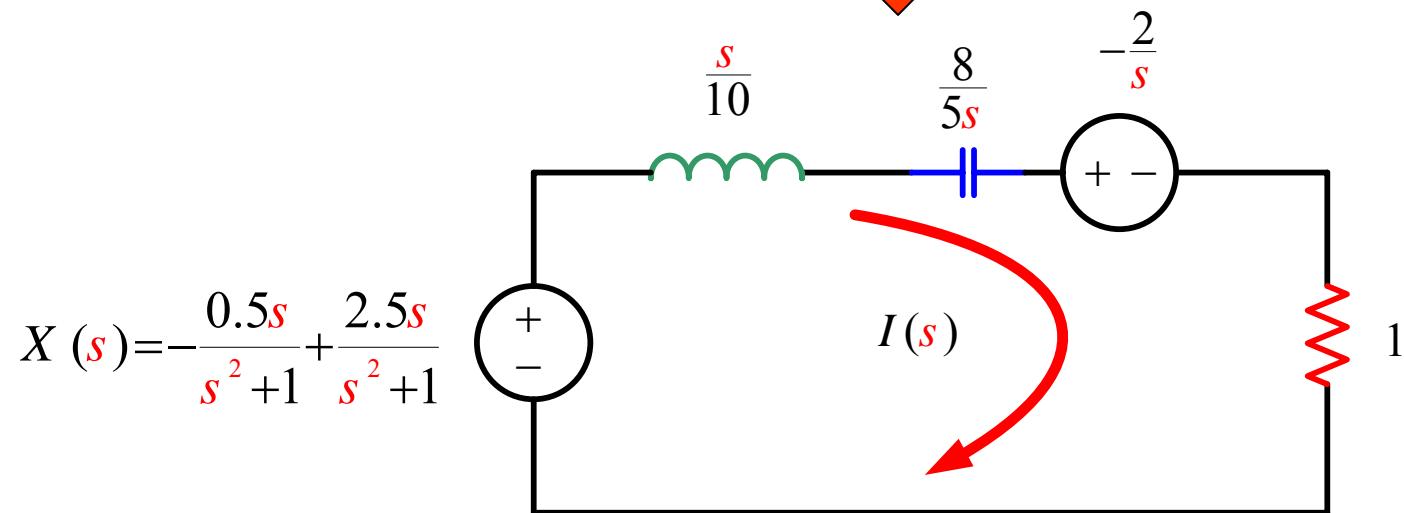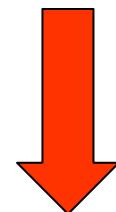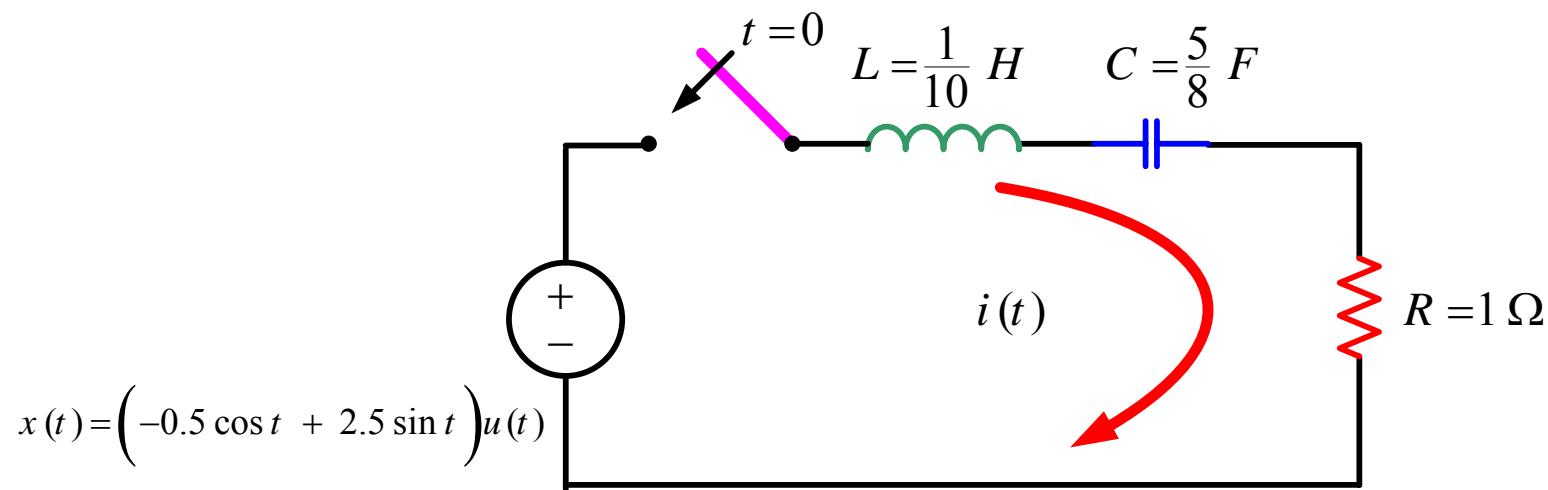
$$R = 1 \Omega \Rightarrow Z_R = 1 \Omega$$




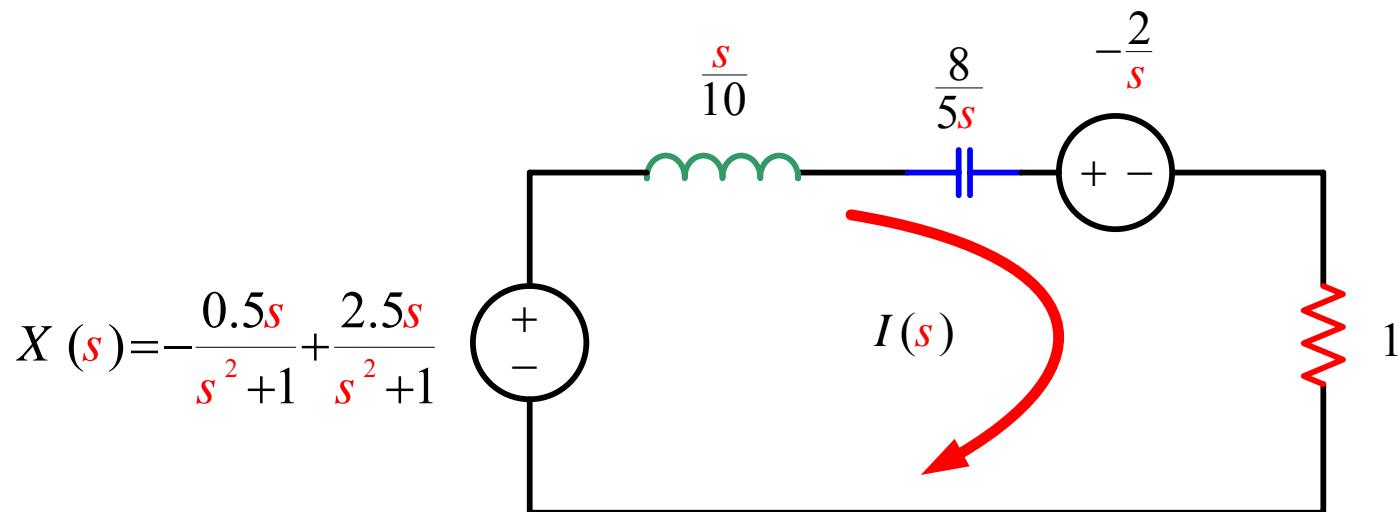

KVL → $-X(s) + \left(\frac{s}{10}\right)I(s) + \left(\frac{8}{5s}\right)I(s) - \frac{2}{s} + (1)I(s) = 0$

→ $-\frac{0.5s}{s^2 + 1} + \frac{2.5s}{s^2 + 1} = \left(\frac{s}{10} + \frac{8}{5s} + 1\right)I(s) - \frac{2}{s}$

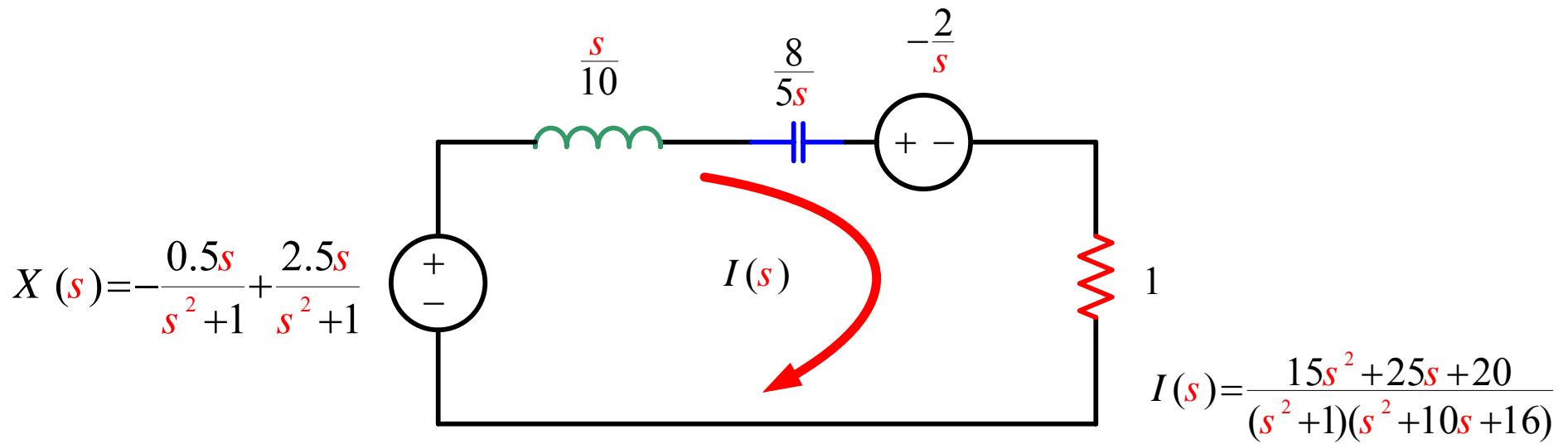→ $I(s) = \frac{15s^2 + 25s + 20}{(s^2 + 1)(s^2 + 10s + 16)}$



From Example 5-10 (Imaginary Roots)


$$I(s) = \frac{15s^2 + 25s + 20}{(s^2 + 1)(s^2 + 10s + 16)} = \frac{(15s^2 + 25s + 20)}{(s + j)(s - j)(s + 2)(s + 8)}$$

$$= \frac{A_1}{(s + j)} + \frac{A_2}{(s - j)} + \frac{A_3}{(s + 2)} + \frac{A_4}{(s + 8)}$$


See Example 5-10 for details

→ $i(t) = (\cos(t) + \sin(t) + e^{-2t} + e^{-8t})u(t)$


Thevenin Thm

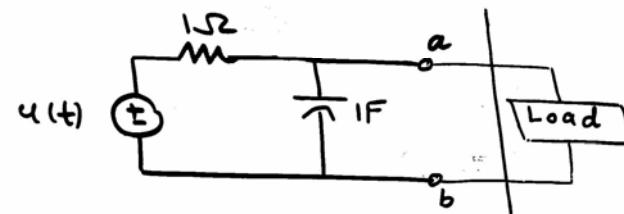


Thevenin equivalent
desired

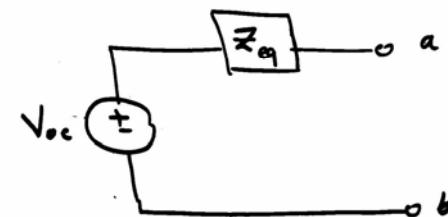


Norton Equivalent

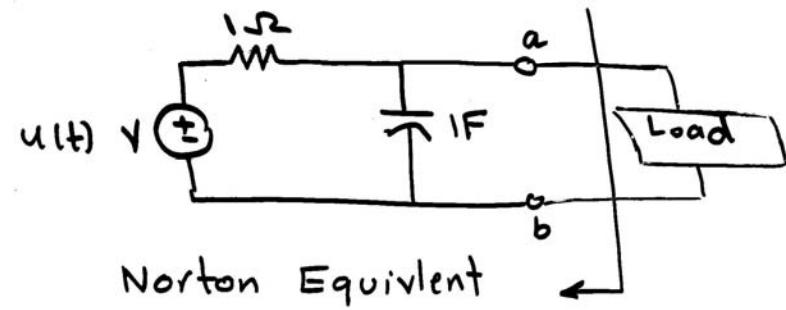

Norton Equivalent

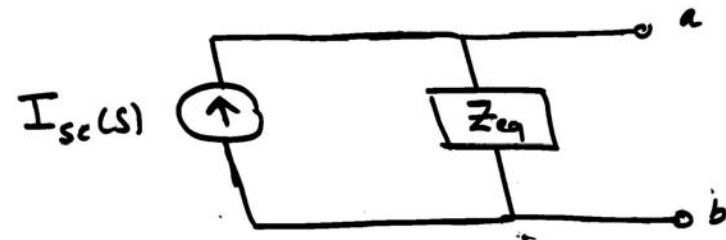

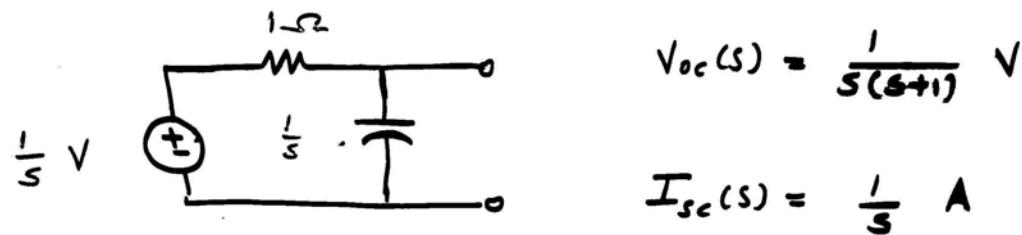

$$V_{oc}(s) = \frac{1}{s(s+1)} \text{ V}$$

$$I_{sc}(s) = \frac{1}{s} \text{ A}$$


$$\begin{aligned} Z_{eq}(s) &= (1\Omega) // (\frac{1}{s}\Omega) \\ &= \frac{1}{s+1} \quad \Omega \end{aligned}$$

OR

$$\begin{aligned} Z_{eq}(s) &= \frac{V_{oc}(s)}{I_{sc}(s)} \\ &= \frac{\frac{1}{s(s+1)}}{\frac{1}{s}} \end{aligned}$$

$$= \frac{1}{s+1} \quad \Omega$$


Note the following :

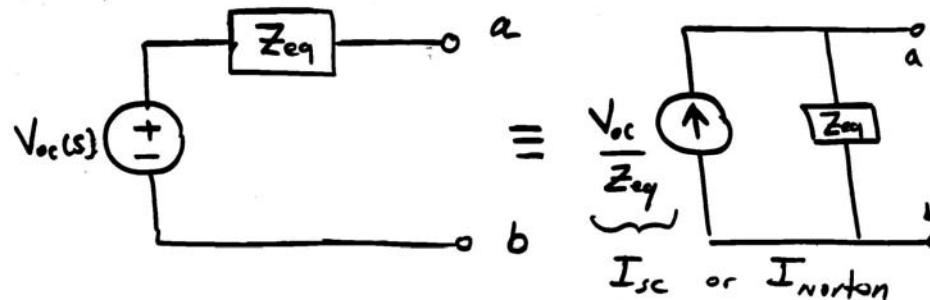

Note: If you can not find Z_{eq}
by combining impedance in parallel
or Series

Example The circuit contains dependent



source

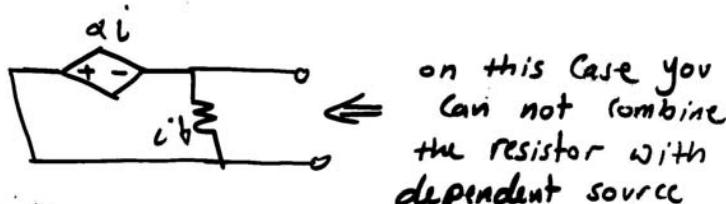

Solution: Apply a test voltage or current method

Q - 1

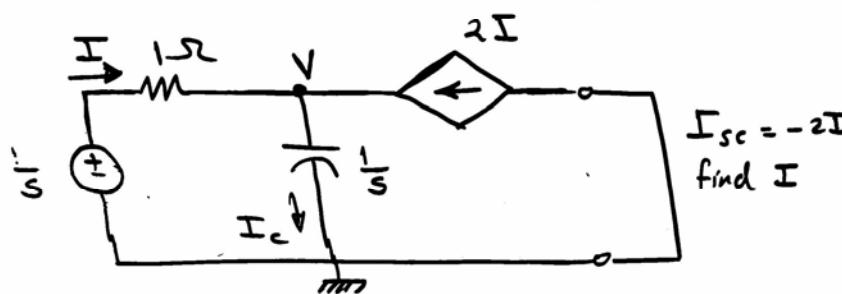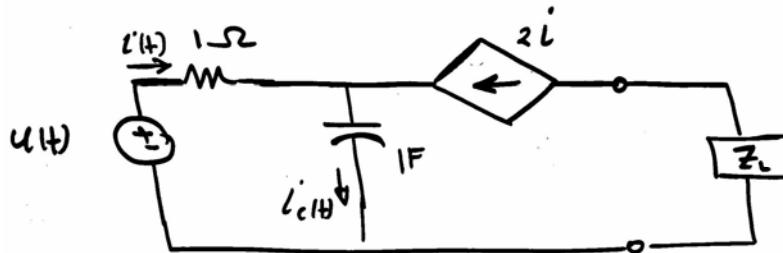Find the Norton equivalent for the following circuit,



KCL at V

$$I + 2I = I_c \Rightarrow 3I = I_c$$


$$\text{But } I = \frac{V_s - V}{1} \quad I_c = \frac{V}{V_s} = sV$$

$$\Rightarrow 3\left(\frac{1}{s} - V\right) = 2(sV) \Rightarrow V(s) = \frac{3}{s(s+3)}$$

$$\Rightarrow I = \frac{1}{s} - \frac{3}{s(s+3)} = \frac{1}{(s+3)}$$

$$\Rightarrow I_{sc} = -2I = -2/(s+3)$$

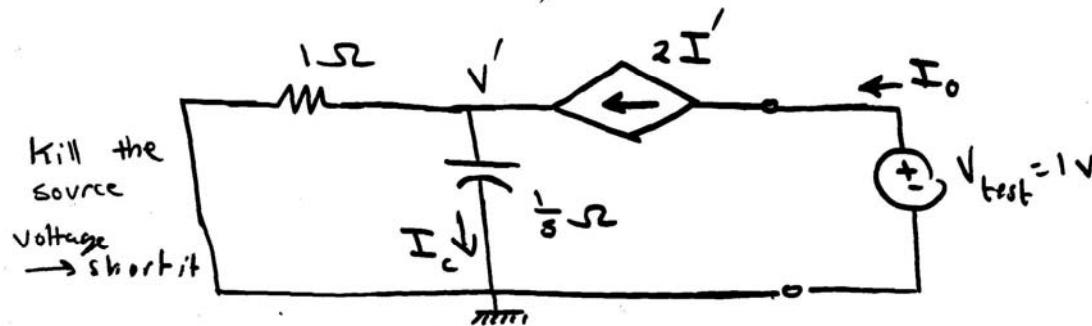To obtain the Equivalent impedance or admittance, we apply a test source method.



$$Z_{eq} = \frac{V_{test}}{I_o} = \frac{1}{I_o} \Rightarrow \text{Find } I_o$$

$$\text{KCL at } V' \quad 3I' = I_c \Rightarrow 3\left(\frac{0-V'}{1}\right) = \frac{V'}{1/3}$$

$$\Rightarrow 3(-V') = sV' \Rightarrow (s+3)V' = 0$$

$$\Rightarrow V' = 0 \Rightarrow I' = 0 \Rightarrow I_o = 0$$


$$\Rightarrow Z_{eq} = \frac{1}{0} = \infty \text{ open Ckt}$$

\Rightarrow The Norton equivalent is an ideal Current Source




6.3 Loop and Node analysis

Ex 6-5

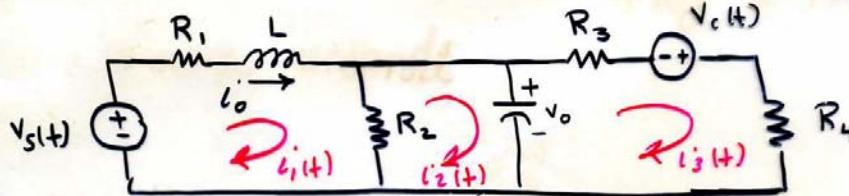

Taking Laplace Transform

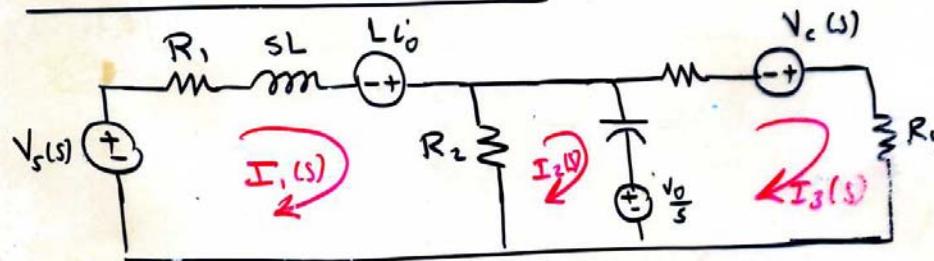

Then writing KVL on each mesh


$$\begin{bmatrix} (R_1 + R_2 + sL) & -R_2 & 0 \\ -R_2 & (R_2 + \frac{1}{sC}) & -\frac{1}{sC} \\ 0 & -\frac{1}{sC} & (R_3 + R_4 + \frac{1}{sC}) \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} L I_o + V_s(s) \\ -\frac{V_o}{s} \\ \frac{V_o}{s} + V_c(s) \end{bmatrix}$$

$$I_1(s) = \frac{\Delta_1}{\Delta}, \quad I_2(s) = \frac{\Delta_2}{\Delta}, \quad I_3(s) = \frac{\Delta_3}{\Delta}$$

$$\bar{I} = \bar{V}$$

6-4 Transfer Functions

Consider the following circuit

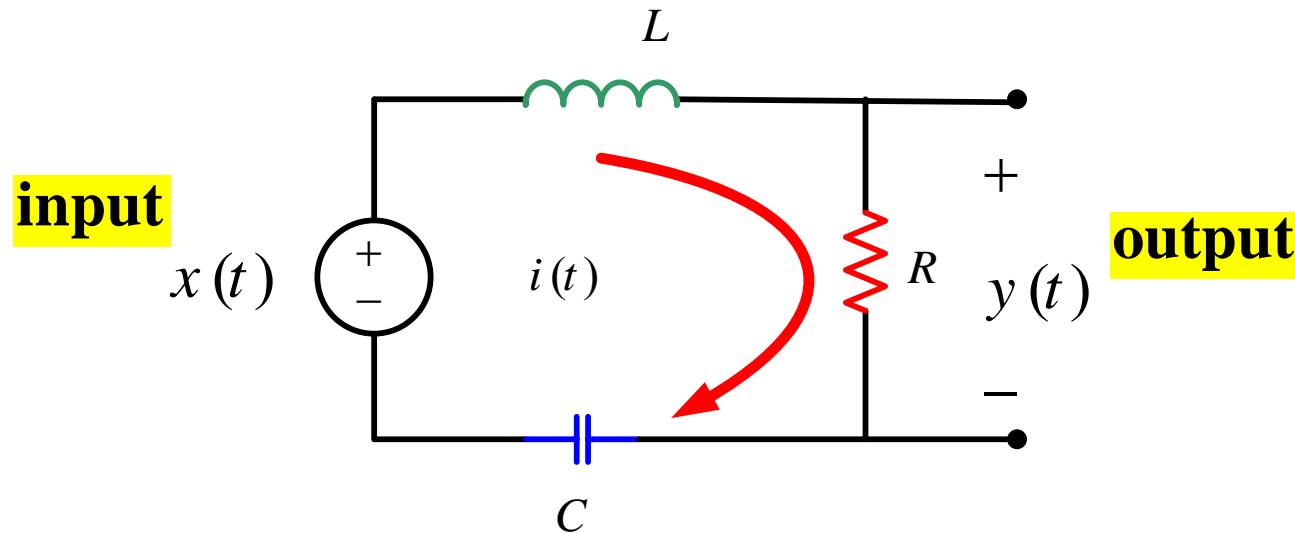


We want a relation (an equation) between the input $x(t)$ and output $y(t)$

KVL

$$x(t) = L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t') dt'$$
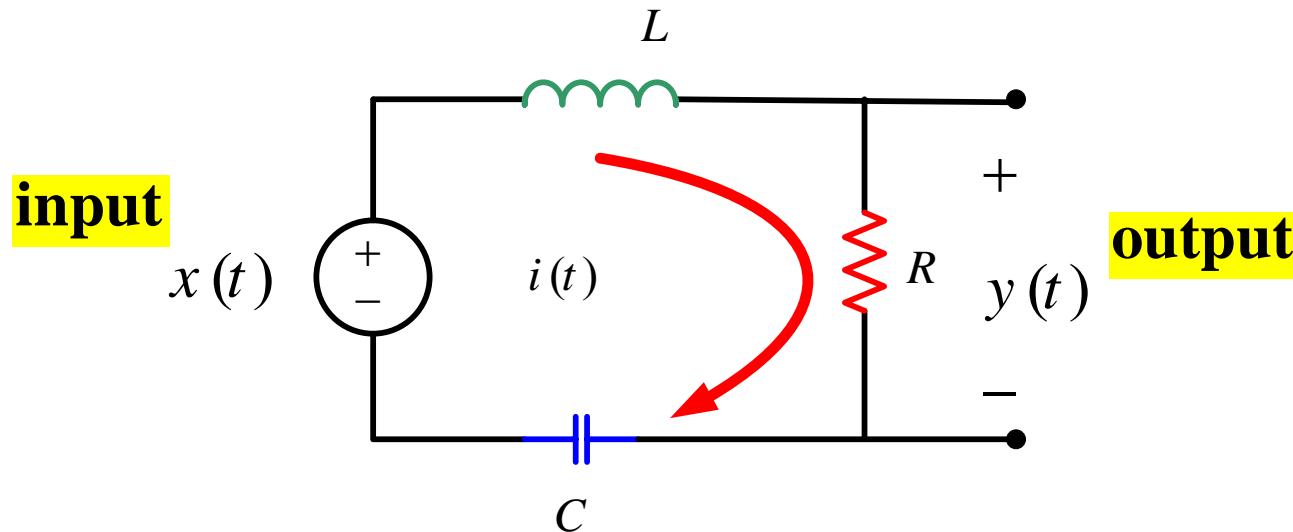
$$\frac{dx(t)}{dt} = L \frac{d^2i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{i(t)}{C}$$




$$\frac{dx(t)}{dt} = L \frac{di^2(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{i(t)}{C}$$

Since $i(t) = \frac{y(t)}{R}$

$$\Rightarrow \frac{dx(t)}{dt} = \frac{L}{R} \frac{dy^2(t)}{dt^2} + R \frac{dy(t)}{dt} + \frac{y(t)}{RC}$$

Writing the differential equation as
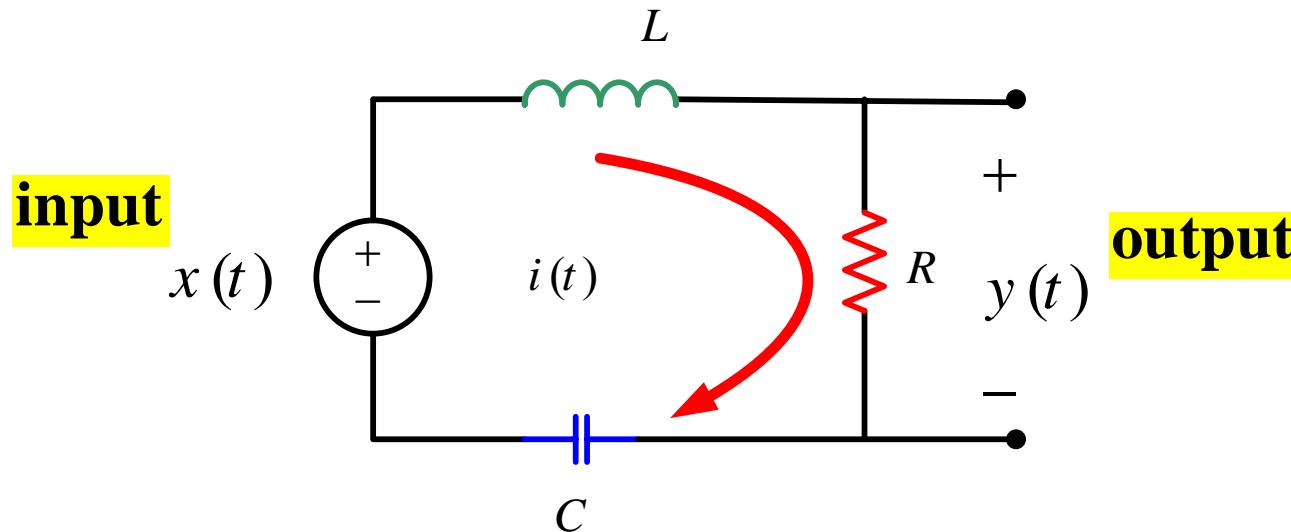
$$RC \frac{dx(t)}{dt} = LC \frac{dy^2(t)}{dt^2} + RC \frac{dy(t)}{dt} + y(t)$$



$$\underbrace{\{RC\} \frac{dx(t)}{dt}}_{\text{Term 1}} = \underbrace{\{LC\} \frac{dy^2(t)}{dt^2}}_{\text{Term 2}} + \underbrace{\{RC\} \frac{dy(t)}{dt}}_{\text{Term 3}} + \underbrace{\{1\}y(t)}_{\text{Term 4}}$$

Real coefficients, non negative which results from system components R, L, C

In general,

$$a_n \frac{dy^n(t)}{dt^n} + a_{n-1} \frac{dy^{n-1}(t)}{dt^{n-1}} + \dots + a_0 y(t) = b_m \frac{dx^m(t)}{dt^m} + b_{m-1} \frac{dx^{m-1}(t)}{dt^{m-1}} + \dots + b_0 y(t)$$

were a_n 's , b_m 's are **real, non negative** which results from system components R, L, C

Now if we take the Laplace Transform of both side (**Assuming Zero initial Conditions**)

$$a_n s^n Y(s) + a_{n-1} s^{n-1} Y(s) + \dots + a_0 Y(s) = b_m s^m X(s) + b_{m-1} s^{m-1} X(s) + \dots + b_0 X(s)$$

We now define the transfer function $H(s)$,

$$H(s) \triangleq \left| \frac{Y(s)}{X(s)} \right| = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_0}$$

all initial conditions are zero

$$a_n \frac{dy^n(t)}{dt^n} + a_{n-1} \frac{dy^{n-1}(t)}{dt^{n-1}} + \dots + a_0 y(t) = b_m \frac{dx^m(t)}{dt^m} + b_{m-1} \frac{dx^{m-1}(t)}{dt^{m-1}} + \dots + b_0 x(t)$$

$$H(s) \triangleq \frac{Y(s)}{X(s)} = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_0} \triangleq \frac{N(s)}{D(s)}$$

Since a_n 's , b_m 's are real, non negative

The roots of the polynomials $N(s)$, $D(s)$ are either real or occur in complex conjugate

The roots of $N(s)$ are referred to as the zero of $H(s)$ ($H(s) = 0$)

The roots of $D(s)$ are referred to as the pole of $H(s)$ ($H(s) = \pm \infty$)

$$H(s) \triangleq \frac{Y(s)}{X(s)} = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_0} \triangleq \frac{N(s)}{D(s)}$$


The Degree of $N(s)$ (which is related to input) must be less than or Equal of $D(s)$ (which is related to output) for the system to be Bounded-input, bounded-output (**BIBO**)

Example : $H(s) = \frac{4s^3 + 2s^2 + s + 1}{s^2 + 6s + 8}$

Using polynomial division , we obtain $H(s) = 4s + 2 + \frac{-19s + 17}{s^2 + 6s + 8}$


Now assume the input $x(t) = u(t)$ (**bounded input**) $\Rightarrow X(s) = \frac{1}{s}$

$$Y(s) = X(s)H(s) = 4 + \frac{2}{s} + \frac{1}{s} \left(\frac{-19s + 17}{s^2 + 6s + 8} \right)$$

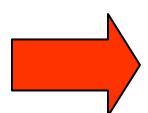 $y(t) = \underbrace{4\delta(t)}_{\text{unbounded } (\rightarrow \infty)} + 2 + L^{-1} \left(\frac{-19s + 17}{s(s^2 + 6s + 8)} \right)$


We see that for finite bounded Input (i.e $x(t) = u(t)$)

We get an infinite (unbounded) output

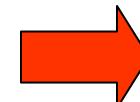 $m \leq n$ for **BIBO**

$$H(s) \triangleq \frac{Y(s)}{X(s)} = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_0} \triangleq \frac{N(s)}{D(s)}$$

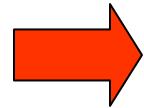The poles of $H(s)$ must have real parts which are negative



The poles must lie in the left half of the s -plan

Components of System Response

Consider the following differential equation (Input / Output),

$$a_1 \frac{dy(t)}{dt} + a_0 y(t) = b_0 x(t)$$

Taking Laplace Transform of both side,

$$a_1 [sY(s) - y(0^-)] + a_0 Y(s) = b_0 X(s)$$

$$[a_1 s - a_0] Y(s) = b_0 X(s) + a_1 y(0^-)$$

$$Y(s) = \frac{b_0 X(s) + a_1 y(0^-)}{[a_1 s - a_0]}$$

$$Y(s) = \frac{b_0}{[a_1 s - a_0]} X(s) + \frac{a_1 y(0^-)}{[a_1 s - a_0]}$$

$$a_1 \frac{dy(t)}{dt} + a_0 y(t) = b_0 x(t)$$

$$Y(s) = \frac{b_0}{[a_1 s - a_0]} X(s) + \frac{a_1 y(0^-)}{[a_1 s - a_0]}$$

If initial conditions are zeros

$$\rightarrow Y(s) = \frac{b_0}{[a_1 s - a_0]} X(s)$$

$$H(s) \triangleq \left. \frac{Y(s)}{X(s)} \right|_{\substack{\text{all initial} \\ \text{conditions} \\ \text{are zero}}} = \frac{N(s)}{D(s)} = \frac{b_0}{[a_1 s - a_0]}$$

Transfer Function
All initial conditions
are zeros

A polynomial related
to initial conditions

$$Y(s) = H(s)X(s) + \frac{a_1 y(0^-)}{D(s)} = H(s)X(s) + \frac{C(s)}{D(s)}$$

$$a_1 \frac{dy(t)}{dt} + a_0 y(t) = b_0 x(t)$$

$$Y(s) = \frac{b_0}{[a_1 s - a_0]} X(s) + \frac{a_1 y(0^-)}{[a_1 s - a_0]}$$

Transfer Function
All initial conditions
are zeros

A polynomial related
to initial conditions

$$Y(s) = H(s)X(s) + \frac{a_1 y(0^-)}{D(s)} = H(s)X(s) + \frac{C(s)}{D(s)}$$

$$y(t) = L^{-1}[H(s)X(s)] + L^{-1}\left[\frac{C(s)}{D(s)}\right]$$

$$y(t) = y_{\text{ZSR}}(t) + y_{\text{ZIR}}(t)$$

Zero State Response
(Steady State)

Zero State Response
(Steady State)

Example 6-7