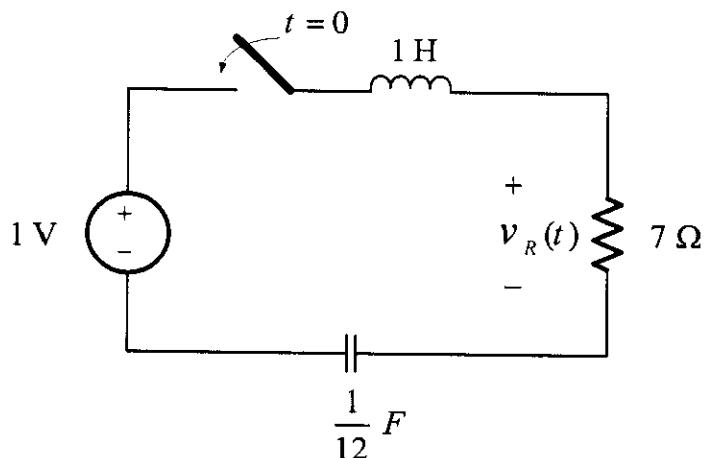


EE 207-01 – Winter 2010  
Quiz 6

SER	ID	NAME KEY
-----	----	----------


Let the switch on the circuit shown below close at  $t = 0$




Assuming that the inductor and the capacitor has zeros initial conditions. Using the Laplace transform method , find the voltage across the resistor  $v_R(t)$
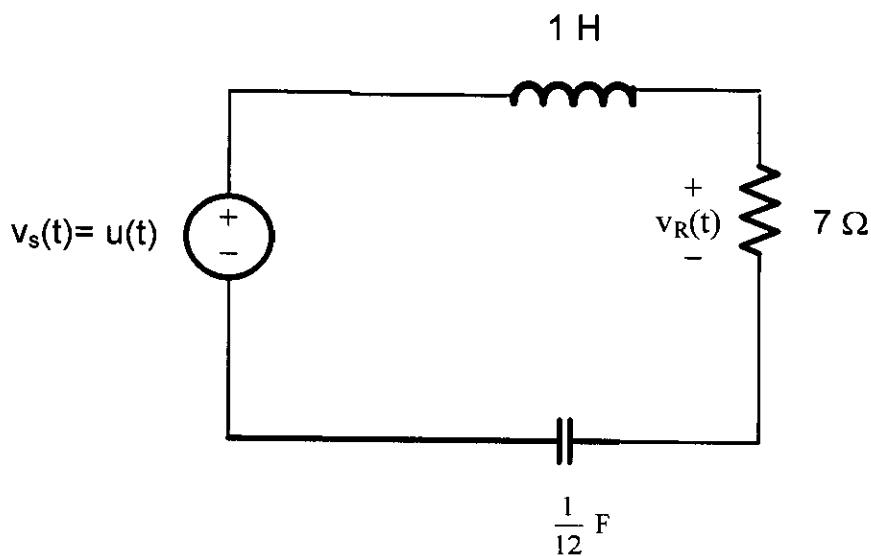
### Solution

We can model the switch as a step function  $u(t)$  as follows:



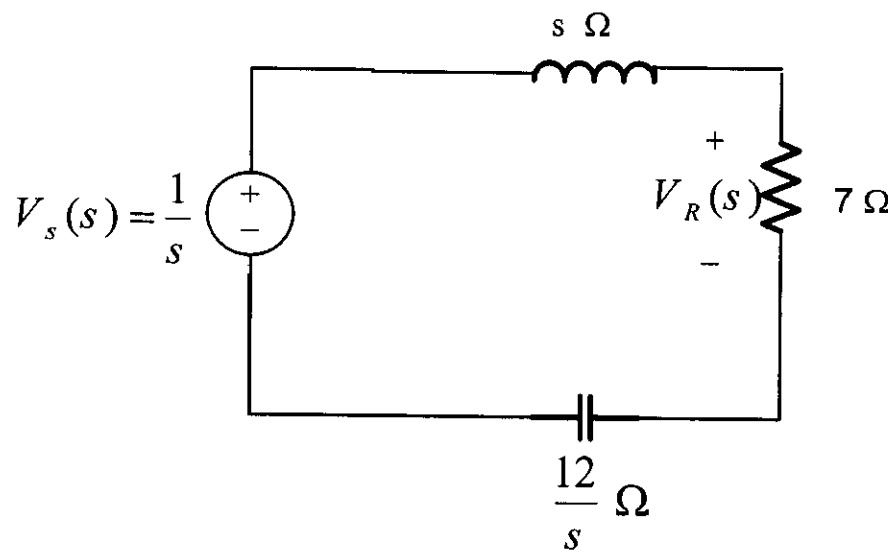We now apply the Laplace transform to the circuit to obtain



Using voltage division we have

$$V_R(s) = \frac{7}{s + 7 + \frac{12}{s}} V_s(s) = \frac{7}{s + 7 + \frac{12}{s}} \left( \frac{1}{s} \right)$$

$$= \frac{7}{s^2 + 7s + 12} = \frac{7}{(s+3)(s+4)}$$

using partial fraction expansion we have

$$V_R(s) = \frac{7}{(s+3)(s+4)} = \frac{A_1}{(s+3)} + \frac{A_2}{(s+4)}$$

$$= \frac{7}{(s+3)} - \frac{7}{(s+4)}$$

Therefore

$$v_R(t) = 7e^{-3t}u(t) - 7e^{-4t}u(t)$$


$$= 7(e^{-3t} - e^{-4t})u(t)$$

SER

ID


NAME **KEY**

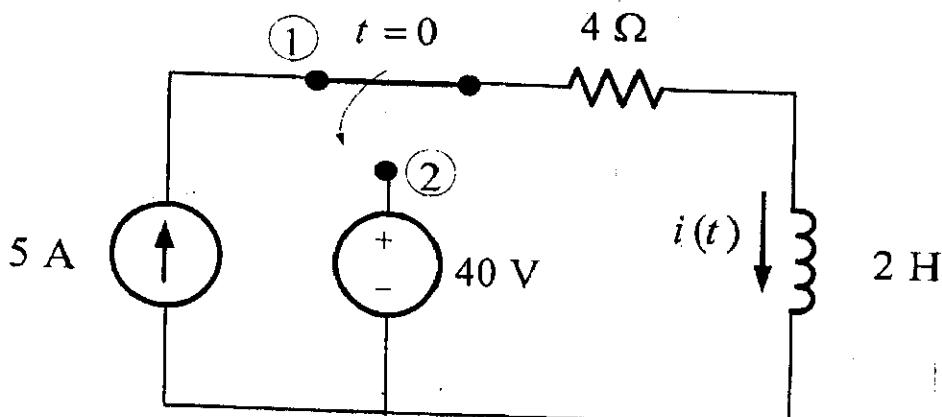For the circuit shown below, the switch was in position 1 for a long time then at  $t = 0$ , the switch was moved to position 2, using Laplace Transform Method find  $i(t)$  for all  $t$ ?




For  $t < 0$

$$i(t) = 5A$$

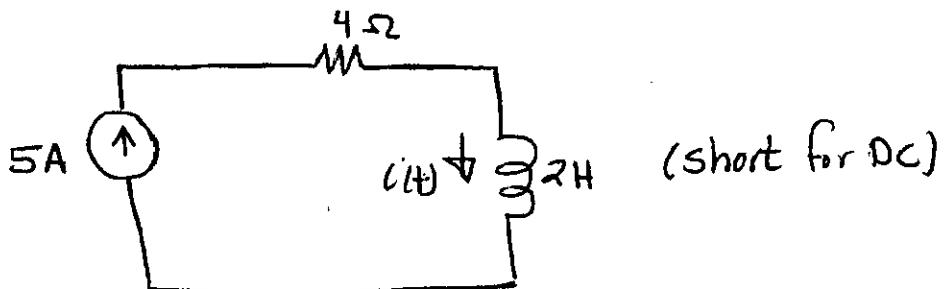

$$\Rightarrow i(0^-) = 5A$$

For  $t > 0$

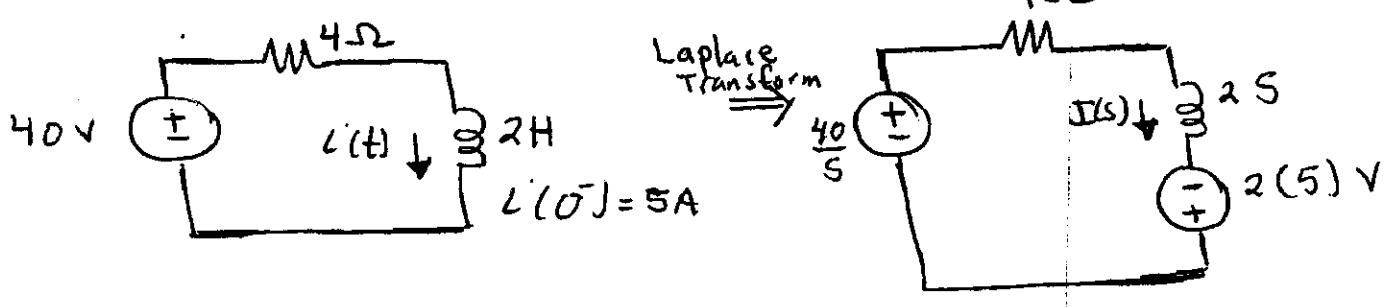

$$\text{KVL} \quad -\frac{40}{s} + 4I(s) + 2sI(s) - 10 = 0$$

$$\Rightarrow I(s) = \frac{40/s}{(2s+4)} + \frac{10}{2s+4} = \frac{20}{s(s+2)} + \frac{5}{(s+2)}$$

$$= \frac{20+5s}{s(s+2)}$$

(Continue) →

$$I(s) = \frac{20 + 5s}{s(s+2)} = \frac{A_1}{s} + \frac{A_2}{(s+2)}$$

$$A_1 = \left. \frac{20 + 5s}{s+2} \right|_{s=0} = \frac{20}{2} = 10$$

$$A_2 = \left. \frac{20 + 5s}{s} \right|_{s=-2} = \frac{20 - 10}{-2} = -5$$

$$I(s) = \frac{10}{s} - \frac{5}{(s+2)}$$

$$\Rightarrow i(t) = 10 u(t) - 5 e^{-2t} u(t)$$