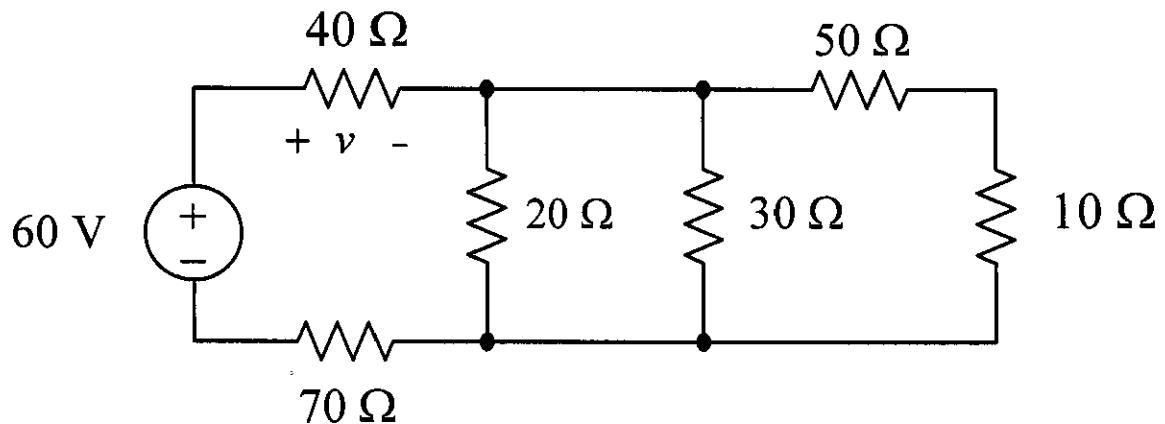


EE 207-05 – Winter 2012(112)
Quiz 1



SER	ID	NAME KEY
-----	----	-----------------



For the circuit shown above, using the voltage division method find the voltage across the 40Ω , v ?

Solution

Combining Resistors

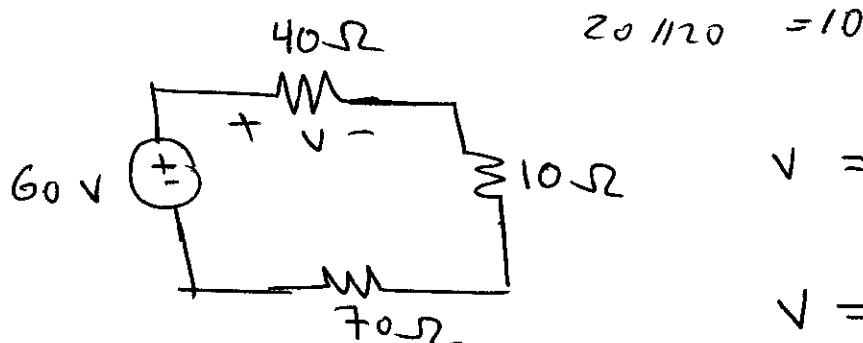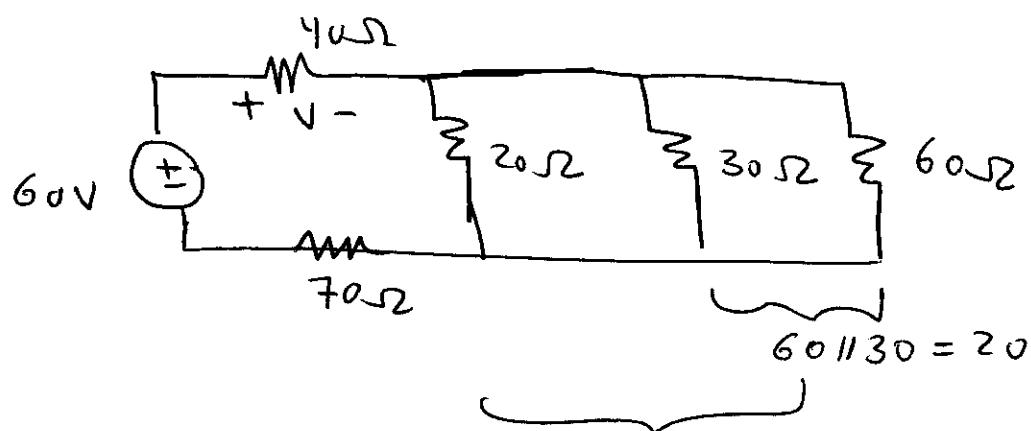

$$v = \frac{40}{40 + 10 + 70} \cdot 60$$

$$v = 20 \text{ V}$$