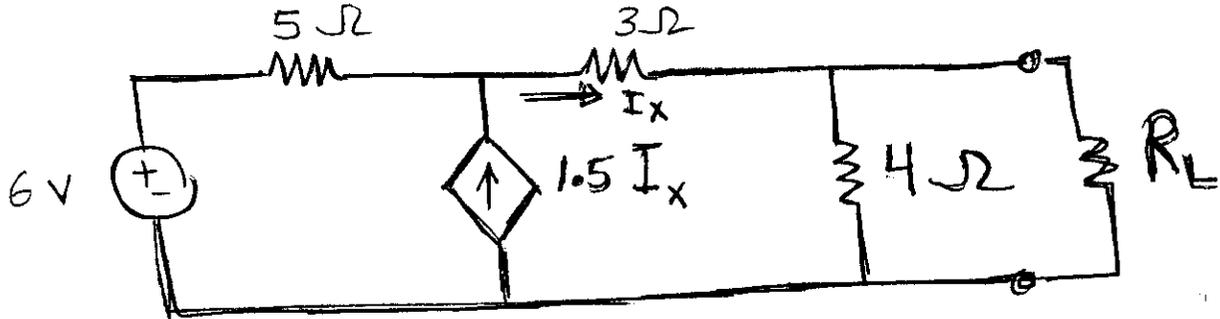


|     |    |      |
|-----|----|------|
| SER | ID | NAME |
|-----|----|------|




For the circuit shown above, find the maximum power absorbed by the load resistor  $R_L$  ?

Remove the load Resistor  $R_L$  and find Thevenin equivalent

~~Remember~~ Remember

Maximum power  $\Rightarrow$  Finding Thevenin

① Finding  $V_{oc}$

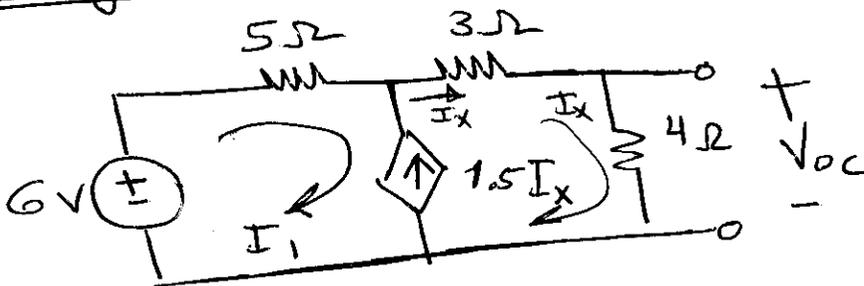



super mesh  $-6 + 5I_1 + (3+4)I_x = 0 \Rightarrow 5I_1 + 7I_x = 6 \quad \text{--- ①}$

$I_x - I_1 = 1.5I_x \Rightarrow I_1 = -0.5I_x \quad \text{--- ②}$

②  $\rightarrow$  ①  $5(-0.5I_x) + 7I_x = 6 \Rightarrow I_x = 1.33 \text{ A}$

$\Rightarrow V_{oc} = 4I_x = 5.33 \text{ V}$

② Finding  $R_{th}$

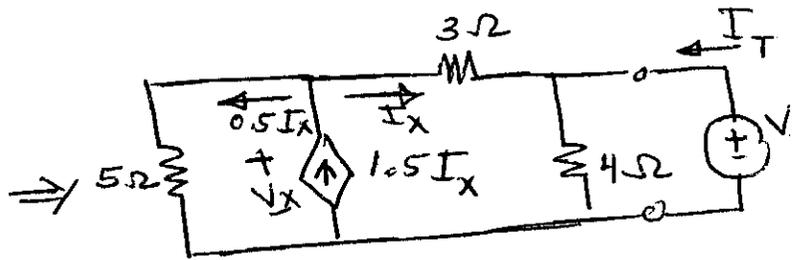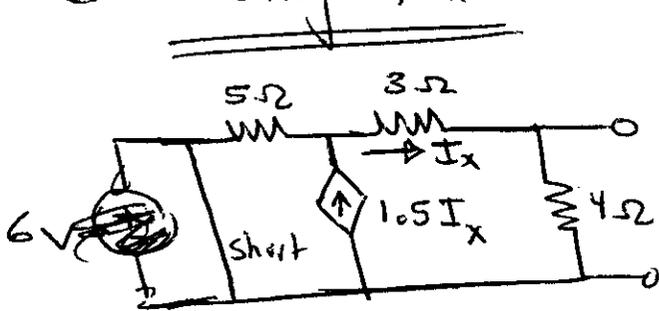

$R_{th} = \frac{V_T}{I_T} \Rightarrow$  find an equation (or a relation) between  $V_T$  and  $I_T$

$$I_T = \frac{V_T}{4} - I_x \quad \text{--- (1)}$$

Now we want a relation or an equation between  $I_x$  and  $I_T$  or  $V_T$  and substitute it in (1)

$$V_x = 5(0.5I_x) = 2.5I_x$$

Same volt on the 5Ω

KVL  $-V_x + 3I_x + V_T = 0 \Rightarrow -2.5I_x + 3I_x + V_T = 0$

$$\Rightarrow I_x = -2V_T \quad \text{--- (2)}$$

②  $\rightarrow$  ①  $\Rightarrow I_T = \frac{V_T}{4} - (-2V_T)$

$$\Rightarrow R_{th} = \frac{V_T}{I_T} = \frac{4}{9} = R_{th}$$

P  $\frac{V_{rms}^2}{R} = \frac{5.33^2}{9} = 15.98 \text{ W}$