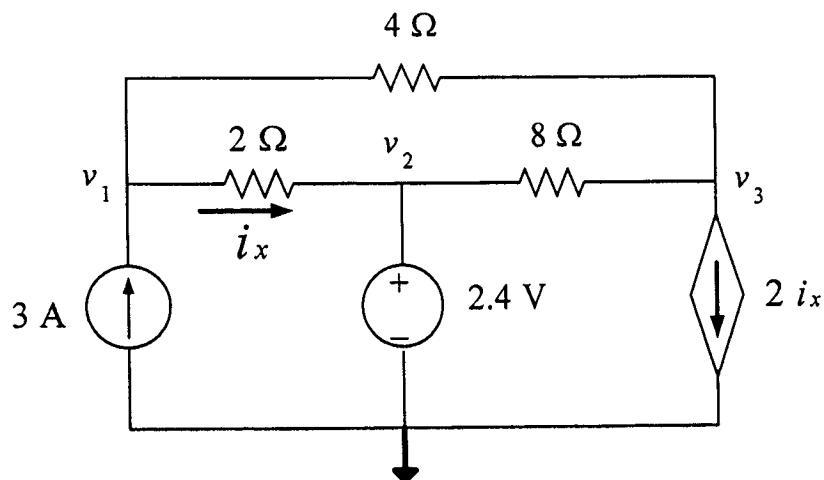


SER	ID	NAME	K E Y
-----	----	------	-------



For the circuit shown above, using the nodal voltage method only find the node voltage  $v_1, v_2, v_3$  ?


$$v_2 = 2.4 \text{ (by inspection)}$$

$$\begin{aligned} \text{KCL at node } v_1 & -3 + \frac{v_1 - v_2}{2} + \frac{v_1 - v_3}{4} = 0 \\ \Rightarrow 3v_1 - v_3 & = 16.8 \quad - \textcircled{1} \end{aligned}$$

$$\begin{aligned} \text{KCL at node } v_3 & \frac{v_3 - v_2}{8} + \frac{v_3 - v_1}{4} + 2i_x = 0 \\ i_x & = \frac{v_1 - v_2}{2} \\ \Rightarrow 2v_1 + v_3 & = 7.2 \quad - \textcircled{2} \end{aligned}$$

Solving eqs ① and ②  $\Rightarrow v_1 = 4.8 \text{ V}$   
 $v_2 = -2.4 \text{ V}$

SER	ID	NAME	KEY
-----	----	------	-----

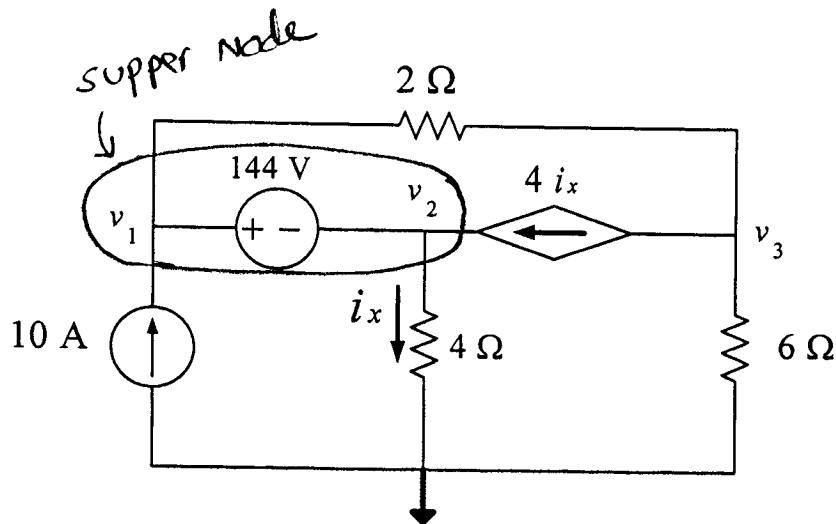

For the circuit shown above, find the nodal equations necessary to solve for the node voltages  $v_1$ ,  $v_2$ ,  $v_3$ . Do not solve the equations

KCL at supper node

$$-10 + \frac{v_1 - v_3}{2} + \frac{v_2}{4} - 4i_x = 0$$

$$i_x = \frac{v_2}{4}$$

$$\Rightarrow 2v_1 - 3v_2 - 2v_3 = 40 \quad \textcircled{1}$$

KCL at node 3


$$\frac{v_3}{6} + \frac{v_3 - v_1}{2} + 4i_x = 0$$

$$\Rightarrow -3v_1 + 6v_2 + 4v_3 = 0 \quad \textcircled{2}$$

From Independent voltage source, we have

$$v_1 - v_2 = 144 \quad \textcircled{3}$$

SER	ID	NAME	KEY
-----	----	------	-----

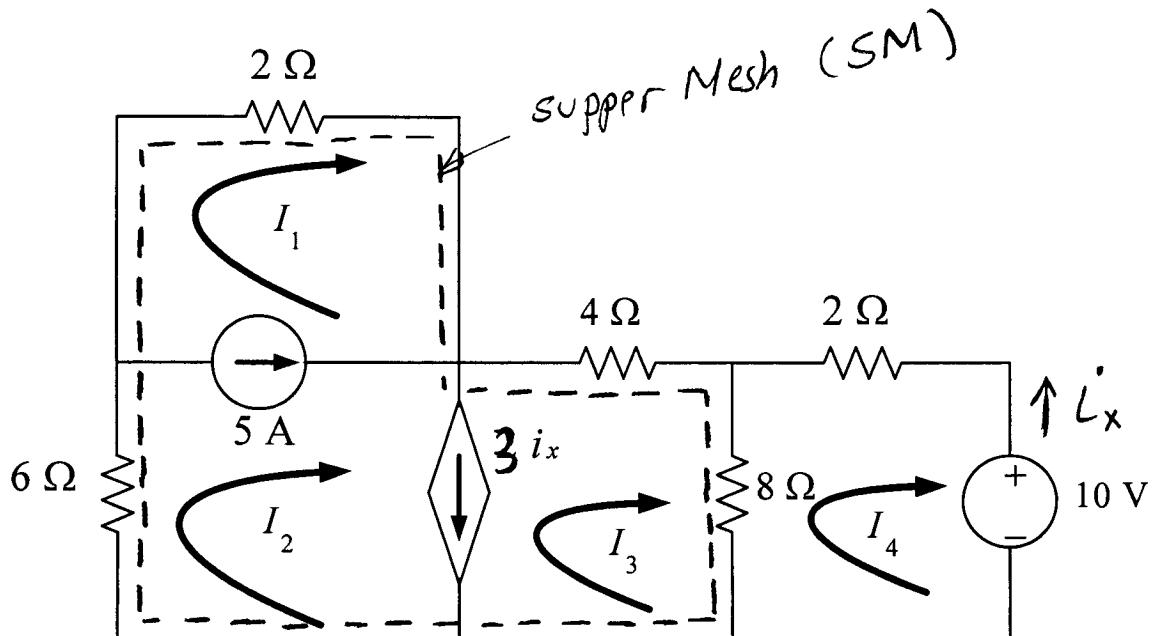

For the circuit shown above , find the mesh equations necessary to solve for the mesh currents  $I_1, I_2, I_3, I_4$  ? **Do not Solve the equations**

KVL on (SM)

$$2I_1 + 4I_3 + 8(I_3 - I_4) + 6I_2 = 0$$

$$\Rightarrow I_1 + 3I_2 + 6I_3 - 4I_4 = 0 \quad - \textcircled{1}$$

KVL on Mesh 4

$$2I_4 + 10 + 8(I_4 - I_3) = 0$$

$$\Rightarrow -4I_3 + 5I_4 = -5 \quad - \textcircled{2}$$

From Independent current source, we have  
 $I_2 - I_1 = 5 \quad - \textcircled{3}$

From dependent current source,  
 $I_2 - I_3 = 3I_x \quad I_x = -I_4 \Rightarrow I_2 - I_3 + 3I_4 = 0 \quad - \textcircled{4}$