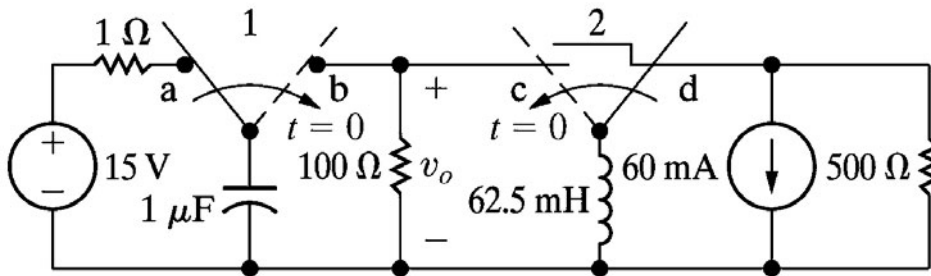



# EE 202 HW6

## Due date Monday, April 29 2013

Q1: For the circuit shown below find  $V_0(t)$  for  $t > 0$




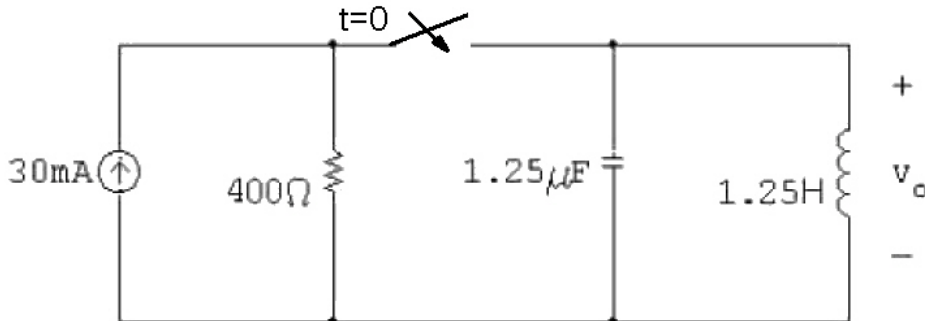Q2: Assume that for  $t < 0$  the circuit has no energy (i.e. zero capacitor voltage and zero inductor current), compute  $V_0(t)$  for  $t > 0$



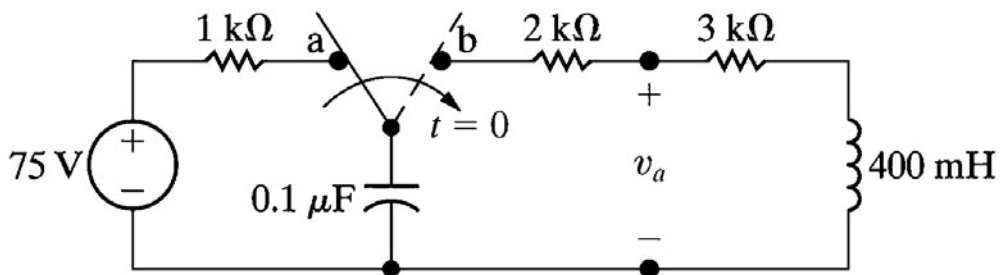Q3: For the circuit shown below:

- 1- compute the initial value of  $v_a$  ( $V_a(0)$ )
- 2- compute the initial value of the time derivative of  $v_a$  ( $(dv_a(0))/dt$ )
- 3- compute  $v_a(t)$  for  $t > 0$



Q4: for the circuit shown below, find  $V_c(t)$  for  $t > 0$

