

EE 202 (122)- HW3
Due Monday March 11, 2013
Dr. Abdallah Al-Ahmari

Question 1:

For the circuit shown in Figure 1, use source transformation to find the current i_o .

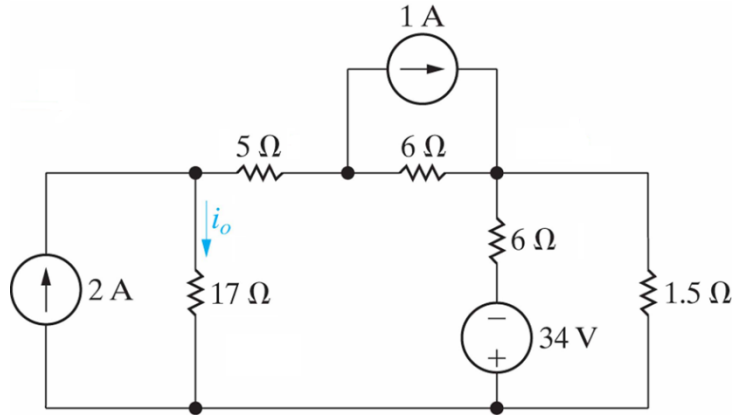


Figure 1

Question 2:

For the circuit shown in Figure 1, use source transformation to find the power dissipated by the 5 Ω resistor.

Question 3:

For the circuit shown in Figure 2, use source transformation to find the following:

- a) The voltage v_o .
- b) The power dissipated by the 10 Ω resistor.

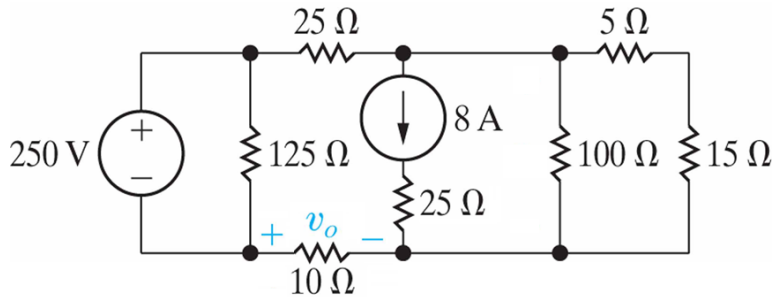


Figure 2

Question 4:

For the circuit shown in Figure 3, find the Thevenin equivalent circuit with respect to the terminals a,b.

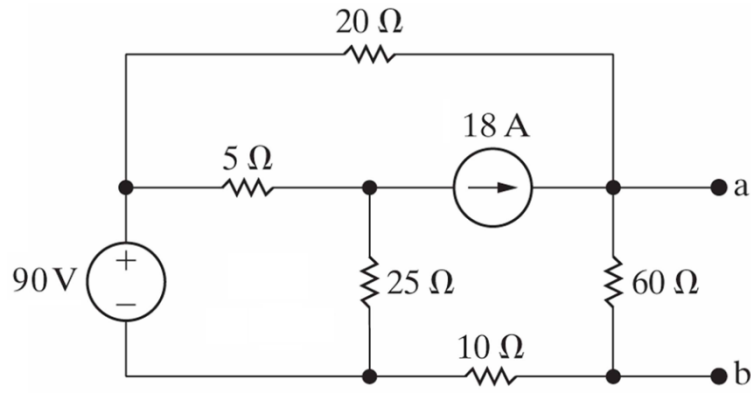


Figure 3

Question 5:

For the circuit shown in Figure 4,

- Find the open circuit voltage V_{oc} with respect to the terminals a, b. Use the mesh-current method.
- Find the short circuit current I_{sc} with respect to the terminals a, b. Use the mesh-current method.
- Use an external current source (1.0 A) to find the Thevenin resistor R_{th} . Use the mesh-current method.
- Find the Thevenin equivalent circuit with respect to the terminals a, b.
- Find the Norton equivalent circuit with respect to the terminals a, b.

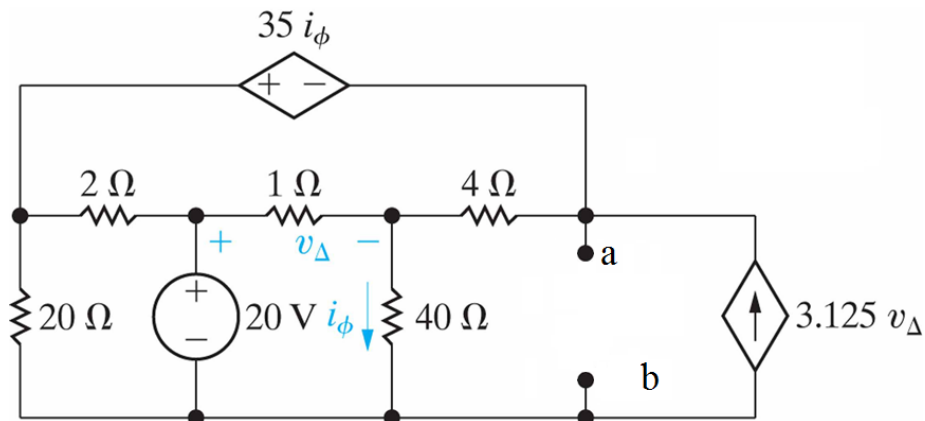


Figure 4