

EE 202 (122) – HW4 – Solution
Due Saturday April 6, 2013
Dr. Abdallah Al-Ahmari

Question 1:

First, we find the Thevenin Equivalent circuit by finding V_{th} and R_{th}

$V_{th} = 8.75 \text{ V}$, $R_{th} = 5 \text{ k}\Omega$.

- a) $R_L = R_{th} = 5 \text{ k}\Omega$.
- b) $P_{max, load} = (V_{th})^2 / (4 R_{th}) = 3.828 \text{ mW}$.



Question 2:

First, we find the Thevenin Equivalent circuit by finding V_{th} and R_{th}


$V_{th} = 3775.55 \text{ V}$, $R_{th} = 42 \Omega$.

- a) $R_L = R_{th} = 42 \Omega$.
- b) $P_{max, load} = (V_{th})^2 / (4 R_{th}) = 84,849.87 \text{ W}$.



Question 3:

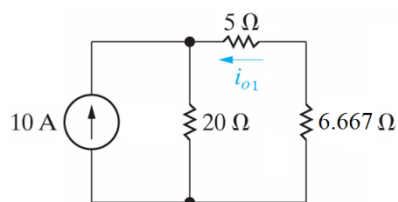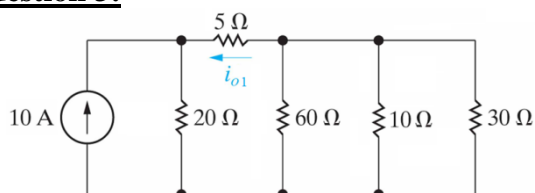

Using cdr, $i_{o1} = -7.5 \text{ A}$

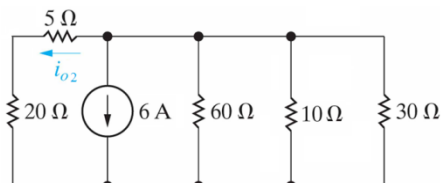

Using cdr, $i_{o2} = -1.263 \text{ A}$

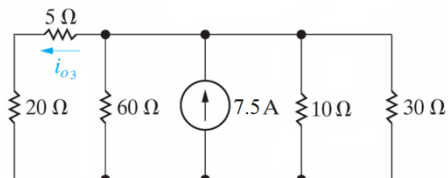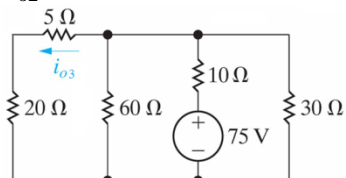

Using cdr, $i_{o3} = 1.579 \text{ A}$


$i_o = i_{o1} + i_{o2} + i_{o3} = -7.184 \text{ A}$.

Question 4:

$$v(t) = \begin{cases} 10 & 0 < t < 2 \\ 0 & 2 < t < 4 \\ 2.5t - 20 & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$


$$i(t) = i(t_o) + \frac{1}{L} \int_{t_o}^t v(x) dx$$
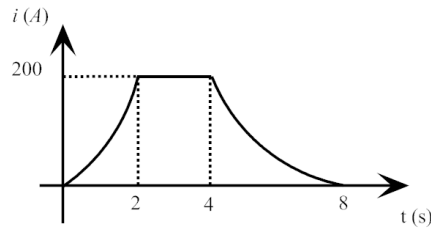
$$i(t) = \begin{cases} 100t & 0 < t < 2 \\ 200 & 2 < t < 4 \\ 12.5t^2 - 200t + 800 & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$




For the energy $w(t) = 0.5Li^2(t)$
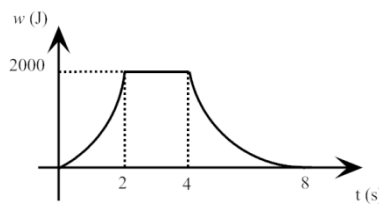
$$w(t) = \begin{cases} 0.05(100t)^2 & 0 < t < 2 \\ 2000 & 2 < t < 4 \\ 0.05(12.5t^2 - 200t + 800)^2 & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$




For the power $p(t) = v(t)i(t)$

$$p(t) = \begin{cases} 1000t & 0 < t < 2 \\ 0 & 2 < t < 4 \\ (2.5t - 20)(12.5t^2 - 200t + 800) & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$

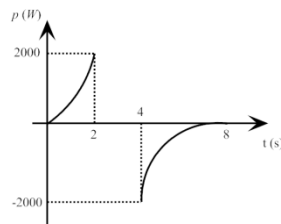

Question 5:

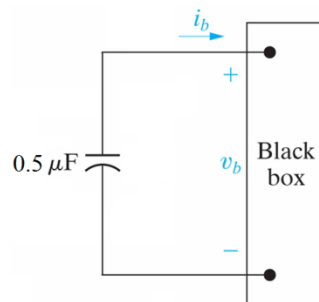

$$v_b(0) = -v_a(0) - v_d(0) - v_c(0) = -25 - 45 + 20 = -50 \text{ V.}$$

$$v_b(t) = v_b(0) - \frac{1}{0.5\mu} \int_0^t i_b(x) dx = -50 - \frac{1}{0.5\mu} \int_0^t 500e^{-40x} \mu dx = 25e^{-40t} - 75$$

$$v_a(t) = v_a(0) + \frac{1}{5\mu} \int_0^t i_b(x) dx = 25 + \frac{1}{5\mu} \int_0^t 500e^{-40x} \mu dx = -2.5e^{-40t} + 27.5$$

$$v_c(t) = v_c(0) + \frac{1}{1.25\mu} \int_0^t i_b(x) dx = -20 + \frac{1}{1.25\mu} \int_0^t 500e^{-40x} \mu dx = -10e^{-40t} - 10$$


$$v_d(t) = v_d(0) + \frac{1}{1\mu} \int_0^t i_b(x) dx = 45 + \frac{1}{1\mu} \int_0^t 500e^{-40x} \mu dx = -12.5e^{-40t} + 57.5$$

$$i_1(t) = 200nF \frac{dv_d(t)}{dt} = 200nF \frac{d[-12.5e^{-40t} + 57.5]}{dt} = 100e^{-40t} \mu A$$

$$i_2(t) = 800nF \frac{dv_d(t)}{dt} = 800nF \frac{d[-12.5e^{-40t} + 57.5]}{dt} = 400e^{-40t} \mu A$$

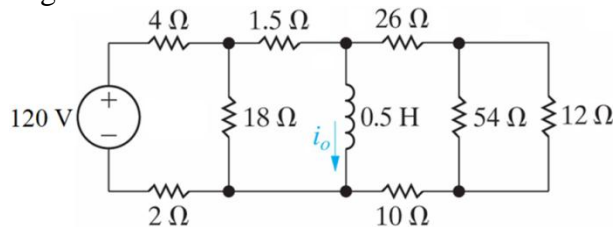
Question 6:

For $t < 0$ we have the following circuit:



The inductor will be act as a short circuit. Start with a source transformation from the left then apply CDR to get $i_o(0) = 15$ A.

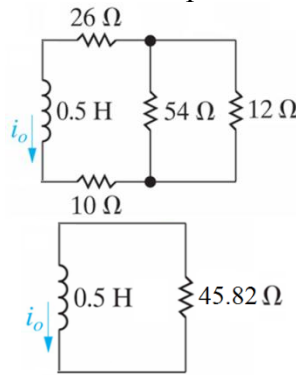For $t \geq 0$ we have the following circuit that can be simplified to RL circuit shown below:



From the circuit we find the time constant


$$\tau = L / R = 0.01091 \text{ s}$$

And the current in the inductor becomes

$$i_o(t) = 15 e^{-91.64 t} \text{ A}$$

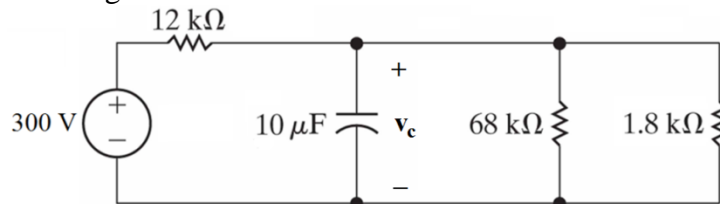
Question 7:

For $t < 0$, we have the following circuit:



The capacitor will act as an open circuit and $v_c(0) = 38.25$ V.

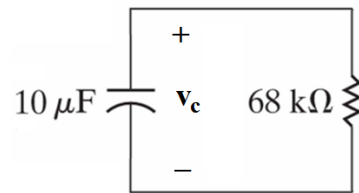For $t \geq 0$, we have the following RC circuit.



From the circuit we find the time constant of the RC circuit as follows:

$$\tau = RC = 0.68 \text{ s}$$

And the voltage across the capacitor becomes.

$$v(t) = 38.25 e^{-1.4706 t} \text{ V}$$

- The amount of energy dissipated in the $68 \text{ k}\Omega$ is the initial energy stored in the capacitor which is equal to $0.5 C v^2 = 7.315 \text{ mJ}$.
- To dissipate 90% of the initial energy the voltage across the capacitor has to be 12.096 V and to reach this we need 782.88 ms.