
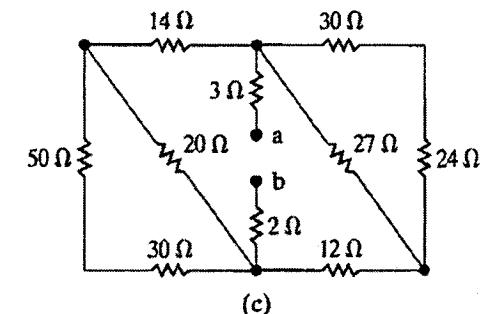
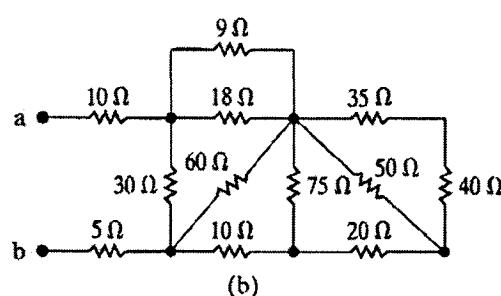


EE 202 (122)- HW2

Due Monday 25/2/2013

Dr. Adil S. Balghonaim

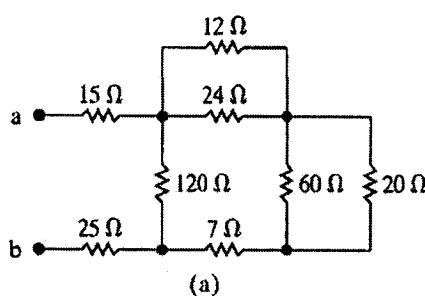

Q1 For the circuits shown above , find the equivalent resistant between nodes a and b

$$[a] \quad 60\parallel 20 = 1200/80 = 15 \Omega \quad 12\parallel 24 = 288/36 = 8 \Omega$$

$$15 + 8 + 7 = 30 \Omega \quad 30\parallel 120 = 3600/150 = 24 \Omega$$

$$R_{ab} = 15 + 24 + 25 = 64 \Omega$$

$$[b] \quad 35 + 40 = 75 \Omega \quad 75\parallel 50 = 3750/125 = 30 \Omega$$

$$30 + 20 = 50 \Omega \quad 50\parallel 75 = 3750/125 = 30 \Omega$$

$$30 + 10 = 40 \Omega \quad 40\parallel 60 + 9\parallel 18 = 24 + 6 = 30 \Omega$$

$$30\parallel 30 = 15 \Omega \quad R_{ab} = 10 + 15 + 5 = 30 \Omega$$


$$[c] \quad 50 + 30 = 80 \Omega \quad 80\parallel 20 = 16 \Omega$$

$$16 + 14 = 30 \Omega \quad 30 + 24 = 54 \Omega$$

$$54\parallel 27 = 18 \Omega \quad 18 + 12 = 30 \Omega$$

$$30\parallel 30 = 15 \Omega \quad R_{ab} = 3 + 15 + 2 = 20 \Omega$$





Q2

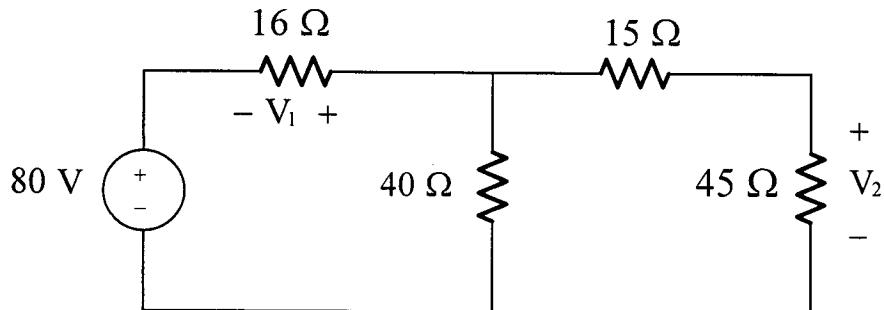


For the circuit shown above , find the followings:

(a) V_1 using voltage division method only ?

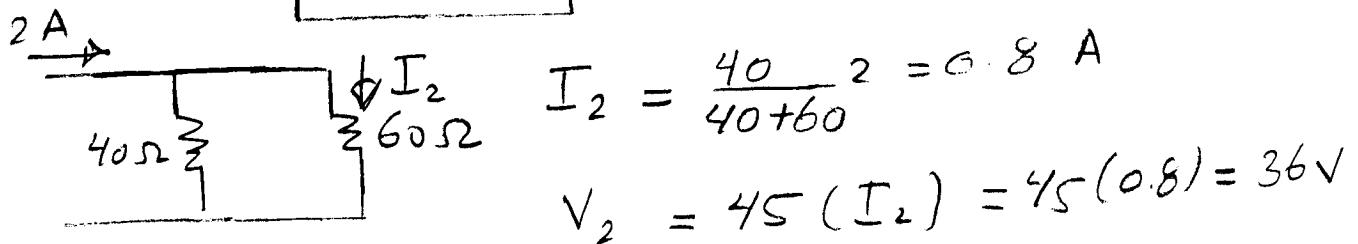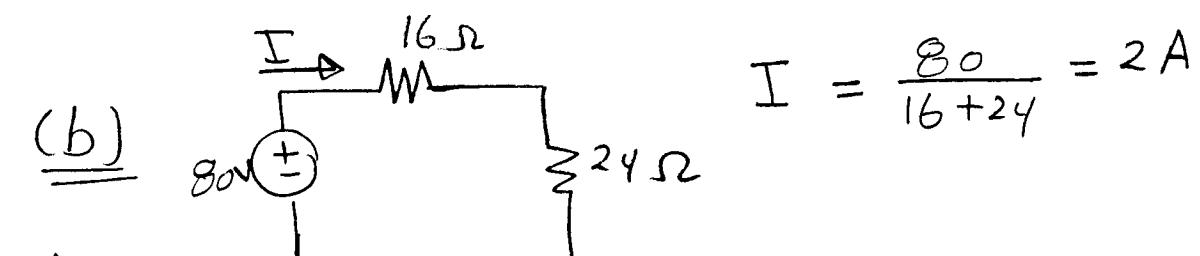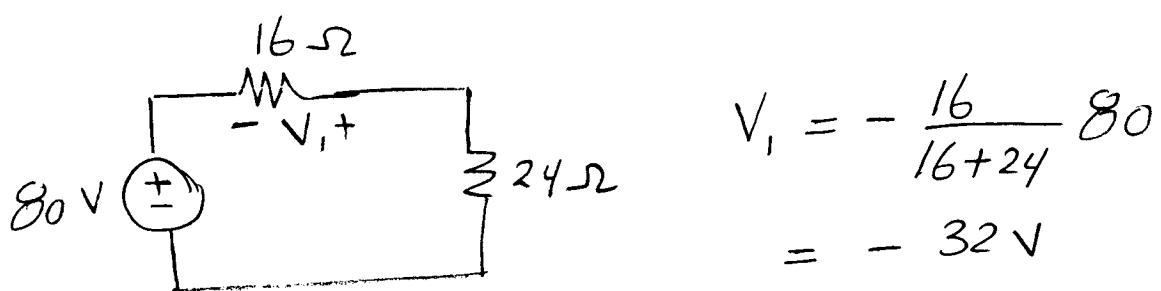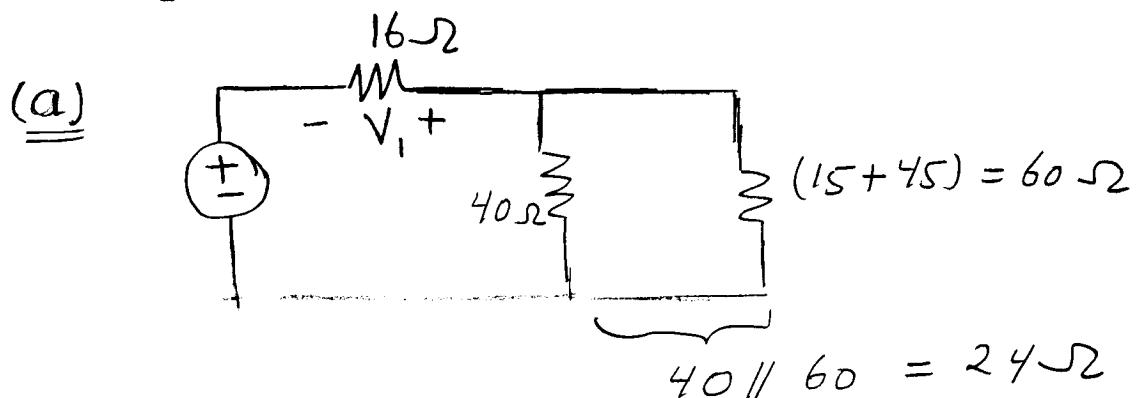(b) V_2 using current division method only ?






Q3

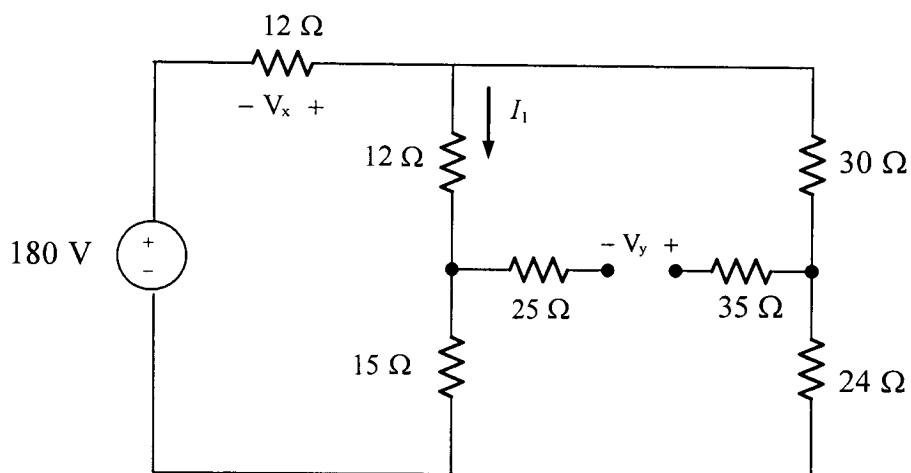


For the circuit shown above , find the followings:

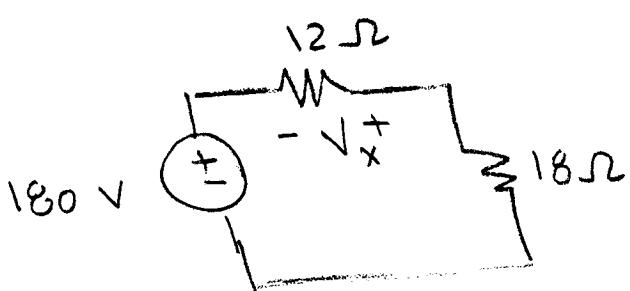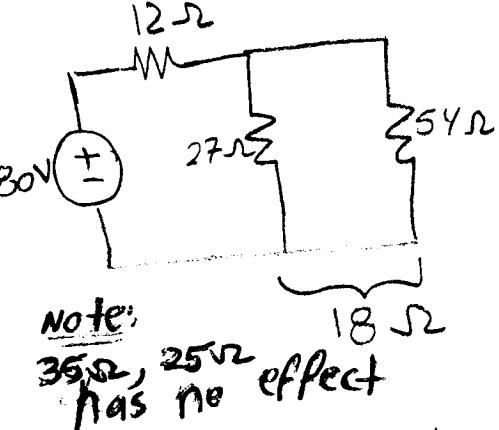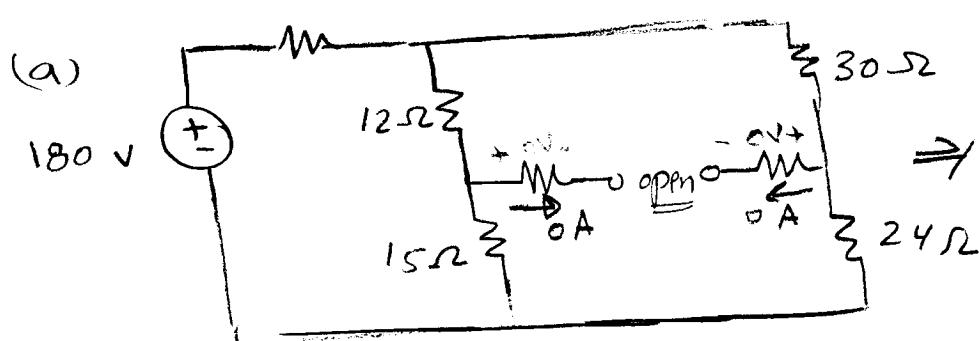- (a) V_x using voltage division method only ?
- (b) I_1 using current division method only ?
- (c) V_y


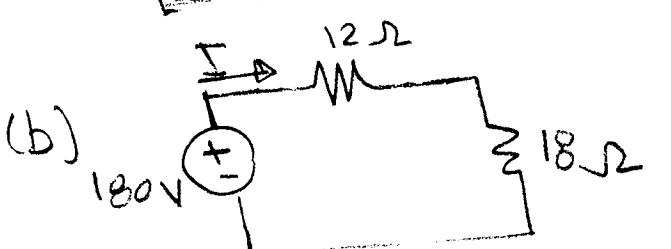
$$V_x = - \frac{12}{12 + 18} 180 = -72 \text{ V}$$




$$I = \frac{180}{12 + 18} = 6 \text{ A}$$



$$I_1 = \frac{54}{27 + 54} (6) = 4 \text{ A}$$

continue →

(c)

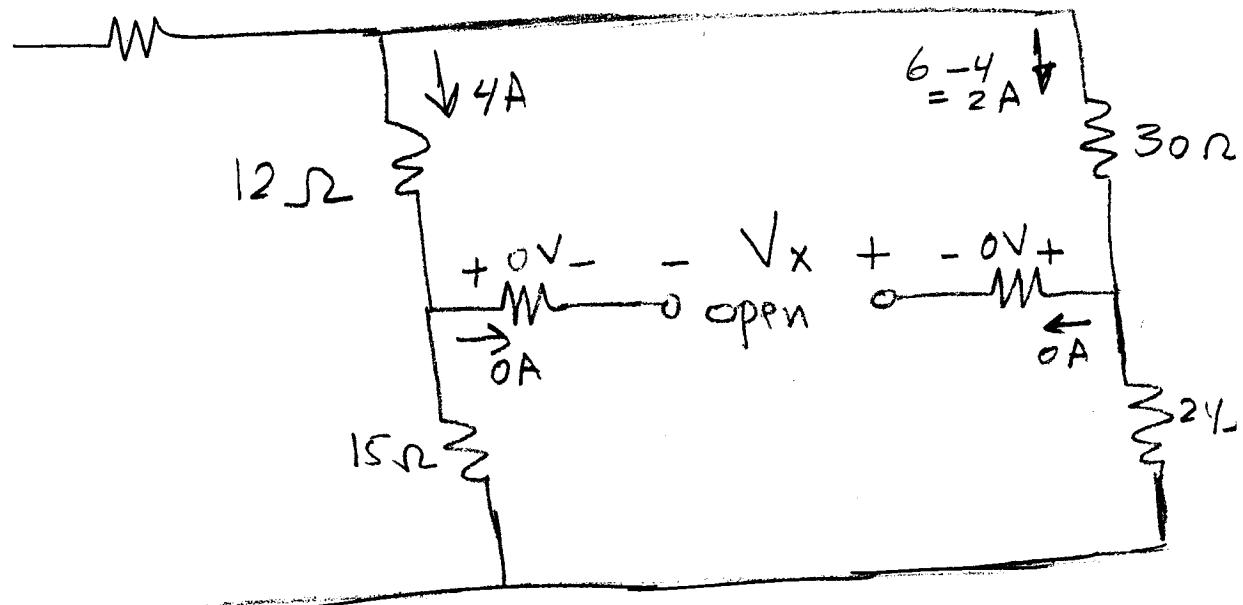

Applying KVL on the upper loop
 (or the lower loop) .

$$30(2) + 0 + V_x - 0 - 12(4) = 0$$


$$\Rightarrow V_x = -12 \text{ V}$$

Lower Loop

$$24(2) - 15(4) + 0 - V_x - 0 = 0$$

$$\Rightarrow V_x = -12 \text{ V}$$

Q4

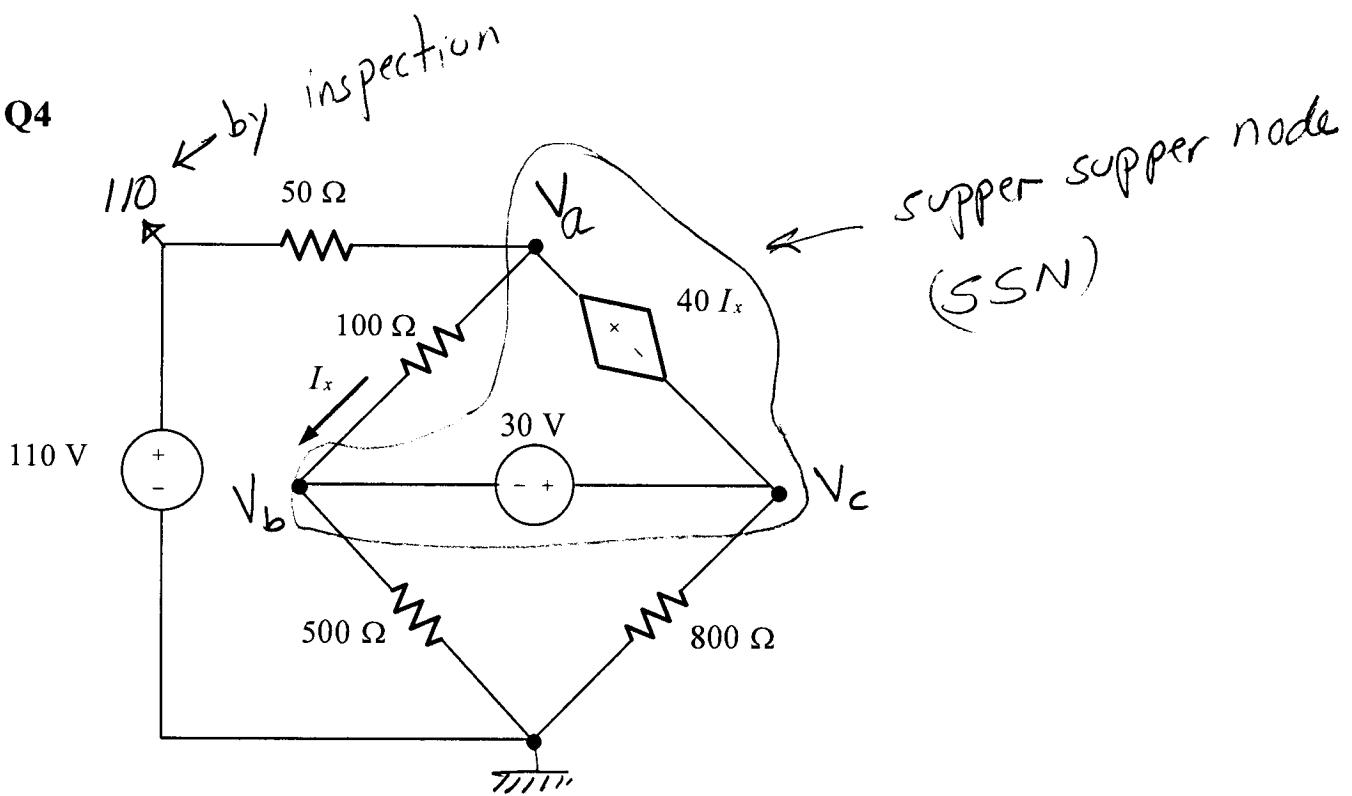

For the circuit shown above , **using the node voltage method** find the followings :

- The power deliver by the 30 V independent voltage source ?
- The power absorb by the dependent voltage source ?

(a) KCL at SSN

$$\frac{V_a - 110}{50} + I_x + \frac{V_c}{800} + \frac{V_b}{500} - I_x = 0$$

$$\Rightarrow 80V_a + 8V_b + 5V_c = 8800 \quad \text{--- (1)}$$

Voltage sources restriction relations

$$V_c - V_b = 30 \quad \text{--- (2)}$$


$$V_a - V_c = 40I_x = 40 \left(\frac{V_a - V_b}{100} \right)$$

$$\Rightarrow 3V_a + 2V_b - 5V_c = 0 \quad \text{--- (3)}$$

$$\begin{bmatrix} 80 & 8 & 5 \\ 0 & -1 & 1 \\ 3 & 2 & -5 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 8800 \\ 30 \\ 0 \end{bmatrix} \Rightarrow \begin{aligned} V_a &= 100 \text{ V} \\ V_b &= 50 \text{ V} \\ V_c &= 80 \text{ V} \end{aligned}$$

Continue

Q4 (Continue)

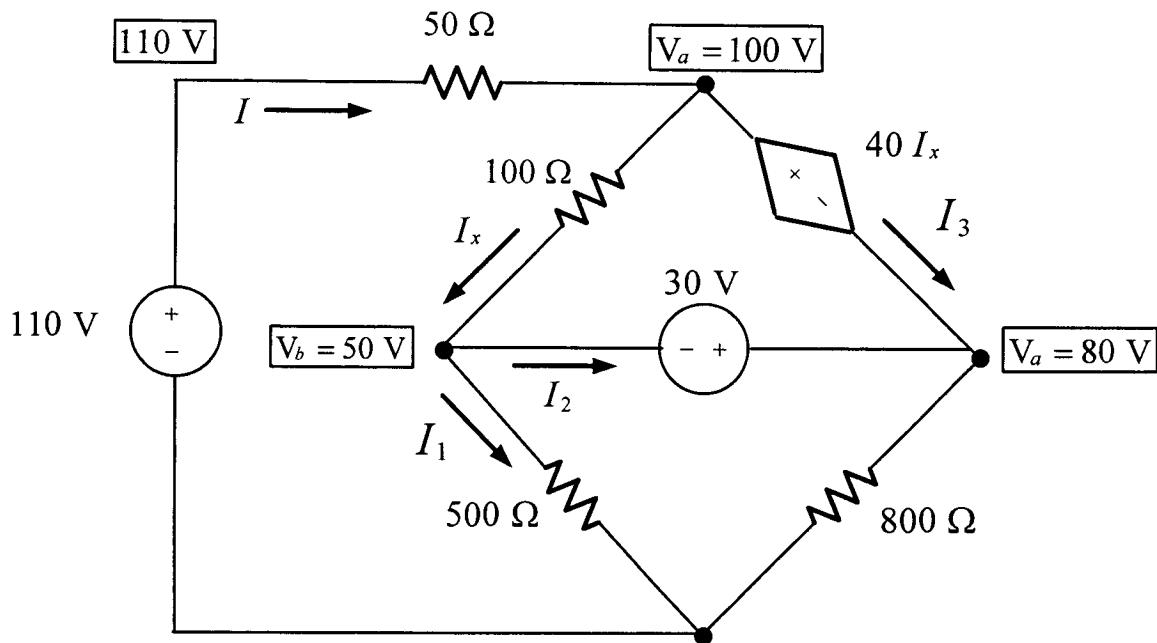

$$P_{30V}^{\text{absorb}} = -30(I_2), \text{ we need } I_2$$

$$I_2 = I_x - I_1, \text{ we need } I_x, I_1.$$

$$I_x = \frac{V_a - V_b}{100} = \frac{100 - 50}{100} = 0.5 \text{ A}$$

$$I_1 = \frac{V_b}{500} = \frac{50}{500} = 0.1 \text{ A}$$

$$\Rightarrow I_2 = I_x - I_1 = 0.5 - 0.1 = 0.4 \text{ A}$$


$$\Rightarrow P_{30V}^{\text{absorb}} = -30(0.4) = -12 \text{ W} \Rightarrow \underline{\underline{P_{30V}^{\text{deliver}} = 12 \text{ W}}}$$

$$(b) P_{40I_x}^{\text{absorb}} = (40I_x)I_3 \quad \text{we need } I_3$$

$$I_3 = I - I_x = \left(\frac{110 - V_a}{50}\right) - 0.5 = -0.3 \text{ A}$$

$$\Rightarrow P_{40I_x}^{\text{absorb}} = (40(0.5))(-0.3) = \underline{\underline{-6 \text{ W}}}$$

Q5

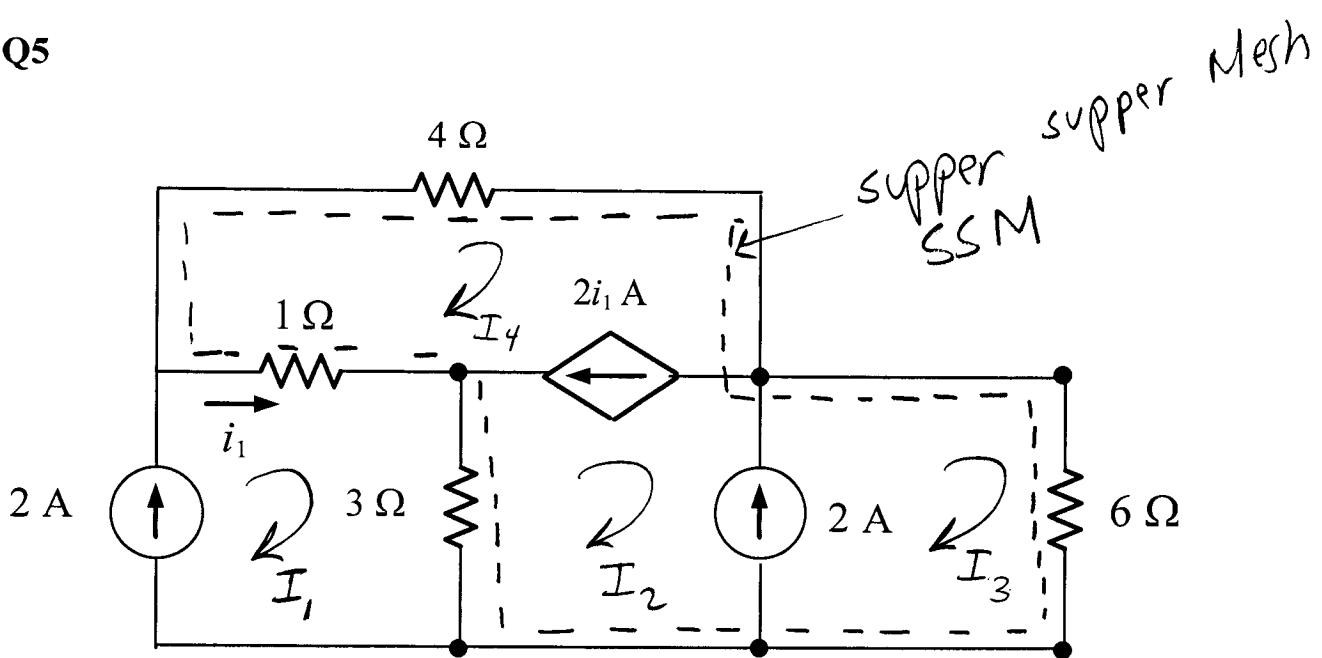

For the circuit shown above, using the **Mesh current method** find the followings :

(a) The power delivered by the dependent current source?

(b) The power absorbed by the 3Ω resistor ?

(a) by inspection $I_1 = 2A$

KVL on (SSM)

$$4I_4 + 6I_3 + 3(I_2 - I_1) + 1(I_4 - I_1) = 0$$

$$\Rightarrow 3I_2 + 6I_3 + 5I_4 = 8 \quad \text{--- (1)}$$

- From the $2A$ independent current source,


$$I_3 - I_2 = 2 \quad \text{--- (2)}$$

- From the dependent current source ,

$$I_4 - I_2 = 2I_1 = 2(I_1 - I_4) \Rightarrow -I_2 + 3I_4 = 4 \quad \text{--- (3)}$$

$$\begin{bmatrix} 3 & 6 & 5 \\ -1 & 1 & 0 \\ -1 & 0 & 3 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 8 \\ 2 \\ 4 \end{bmatrix} \Rightarrow \begin{array}{l} I_2 = -1A \\ I_3 = 1A \\ I_4 = 1A \end{array}$$

Q5 (continue)

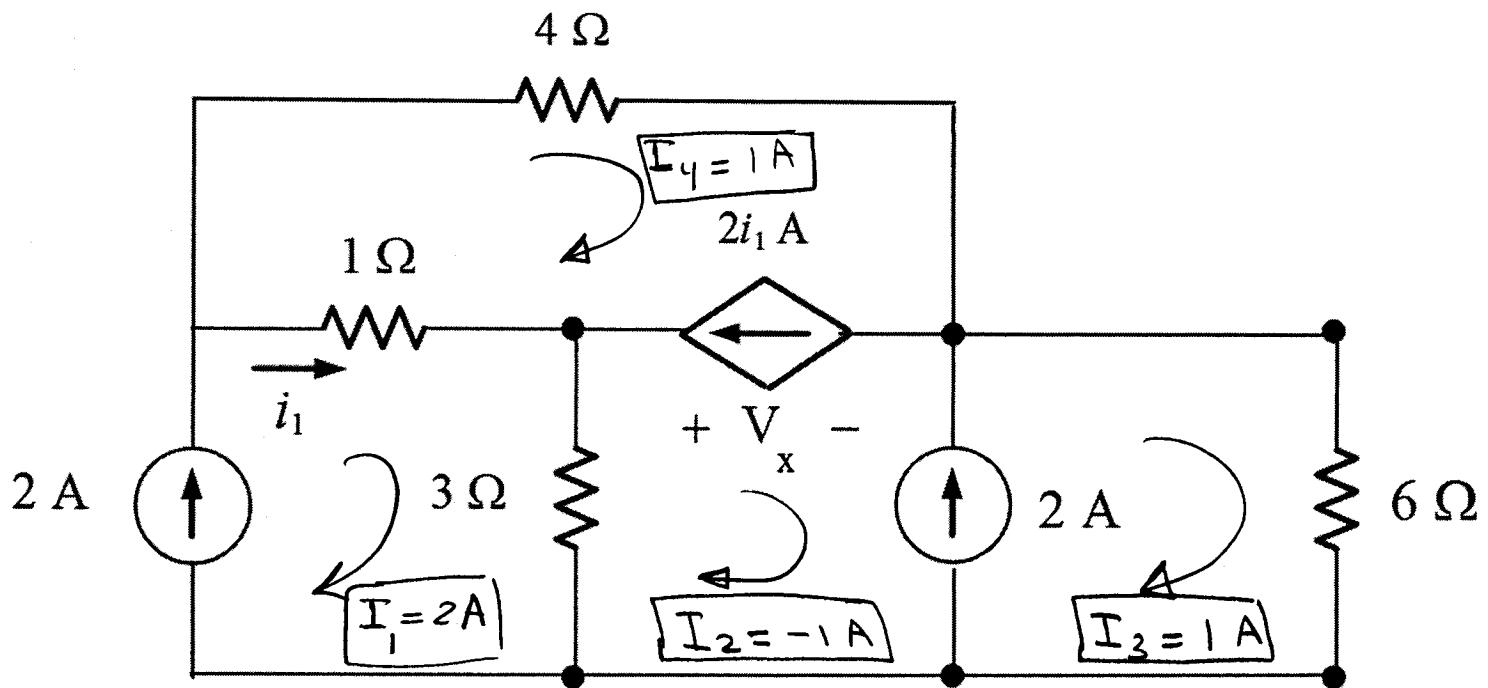

KVL on the upper loop (mesh)

$$4I_4 - V_x + 1(I_4 - I_1) = 0 \Rightarrow V_x = 3V$$

$$\begin{aligned} \Rightarrow P_{2i_1}^{\text{absorb}} &= -V_x(2i_1) \\ &= -(3)(2(I_1 - I_4)) \\ &= -(3)(2(2 - 1)) = \underline{\underline{-6W}} \end{aligned}$$

$$\Rightarrow P_{2i_1}^{\text{deliver}} = \underline{\underline{6W}}$$

$$(b) P_{3\Omega}^{\text{absorb}} = 3(I_1 - I_2)^2 = 3(2 + 1)^2 = \underline{\underline{27W}}$$