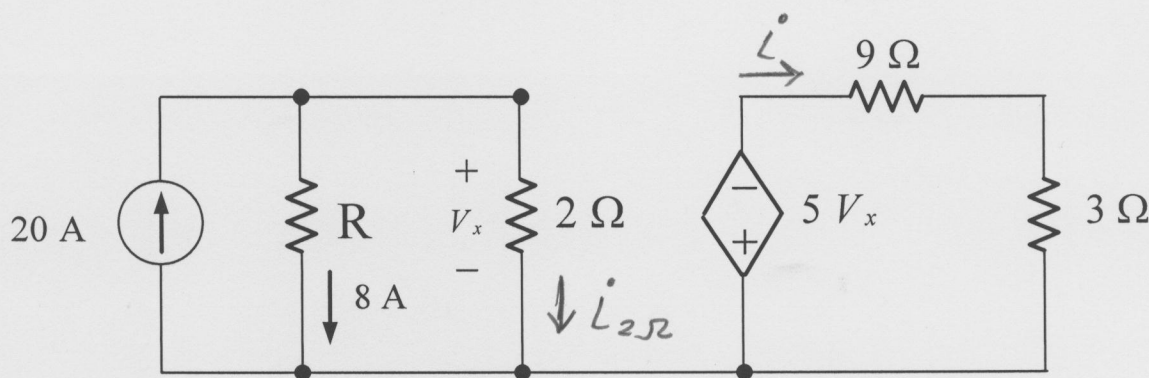


SER	ID	NAME	KEY
-----	----	------	-----



For the circuit shown above find :

- The resistor R ?
- The power deliver by the independent source ?
- The power deliver by the dependent source ?


$$\begin{aligned}
 \text{(a) } \underline{\text{KCL}} : \quad 20 &= 8 + i_{2\Omega} \Rightarrow i_{2\Omega} = 12 \text{ A} \\
 \Rightarrow V_x &= 2(i_{2\Omega}) = 2(12) = 24 \text{ V} \\
 \Rightarrow 24 &= R(8) \Rightarrow R = 3 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \text{(b) } P_{20 \text{ A}}^{\text{absorbed}} &= -V_x (20) = -(24)(20) = -480 \text{ W} \\
 \Rightarrow P_{20 \text{ A}}^{\text{delivered}} &= 480 \text{ W}
 \end{aligned}$$

$$\begin{aligned}
 \text{(c) } \underline{\text{KVL}} : \quad 5V_x + 9i' + 3i' &= 0 \Rightarrow i' = -10 \text{ A} \\
 P_{5V_x}^{\text{absorbed}} &= (5V_x)(i') = 5(24)(-10) \\
 &= -1200 \text{ W}
 \end{aligned}$$

$$\Rightarrow P_{5V_x}^{\text{delivered}} = 1200 \text{ W}$$

SER	ID	NAME	KEY
-----	----	------	-----

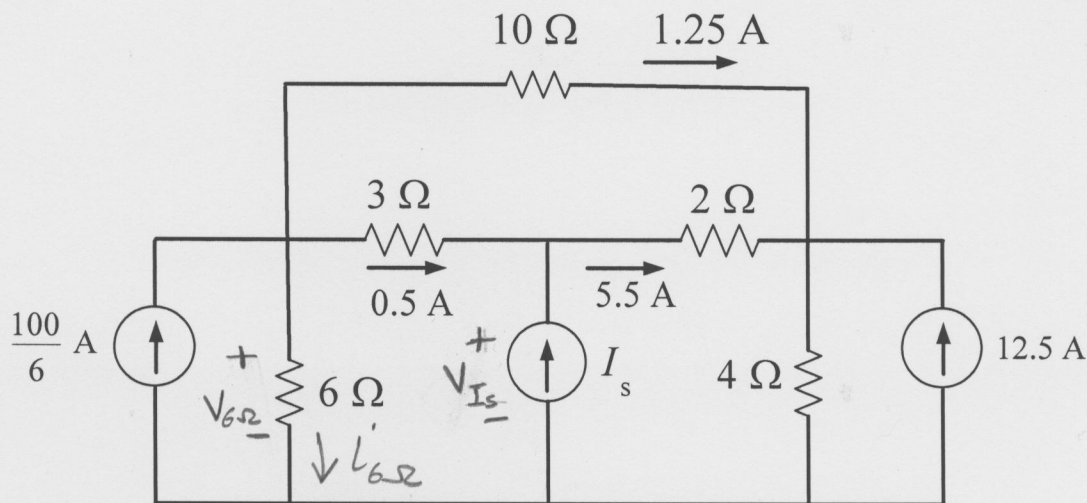

For the circuit shown above find :

(a) The power deliver by the $\frac{100}{6}$ A independent current source ?

(b) The power deliver by the I_s independent current source ?

$$(a) \text{ Kcl: } \frac{100}{6} = i'_{6\Omega} + 0.5 + 1.25 \Rightarrow i'_{6\Omega} = 14.92 \text{ A}$$

$$V_{6\Omega} = 6 i'_{6\Omega} = 6(14.92) = 89.5 \text{ V}$$

$$P_{\frac{100}{6} \text{ A}}^{\text{absorbed}} = -V_{6\Omega} \left(\frac{100}{6} \right) = -(89.5) \left(\frac{100}{6} \right) = -1491.67 \text{ W}$$

$$\Rightarrow P_{\frac{100}{6} \text{ A}}^{\text{deliver}} = 1491.67 \text{ W}$$

$$(b) \text{ Kcl: } 0.5 + I_s = 5.5 \Rightarrow I_s = 5 \text{ A}$$

$$\text{KVL: } -V_{6\Omega} + 3(0.5) + V_{I_s} = 0 \Rightarrow V_{I_s} = 88 \text{ V}$$

$$P_{I_s}^{\text{absorbed}} = -(V_{I_s})(I_s) = -(88)(5) = -440 \text{ W}$$

$$\Rightarrow P_{I_s}^{\text{deliver}} = 440 \text{ W}$$