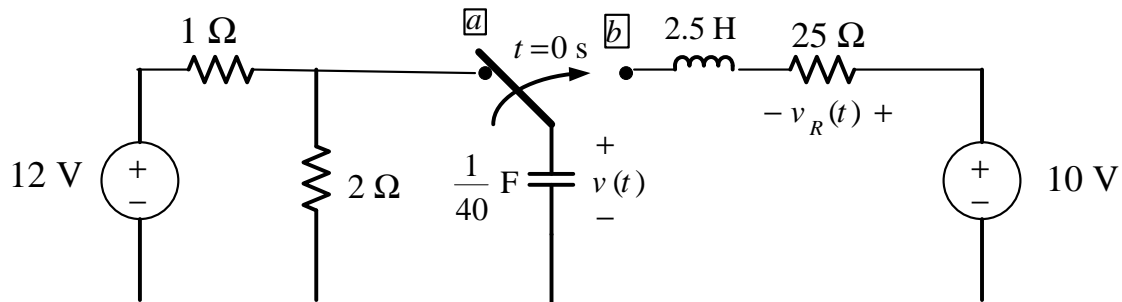



SER	ID	NAME <b>KEY</b>
-----	----	-----------------



For the circuit shown above , the **switch** was in position **a** for a long time and at  $t=0$  s the **switch** move to position **b** .

Find  $v(t)$  and  $v_R(t)$  for  $t > 0$ ? ( **Hint**  $\alpha = \frac{R}{2L}$   $\omega_0 = \frac{1}{\sqrt{LC}}$  )


**Solution**

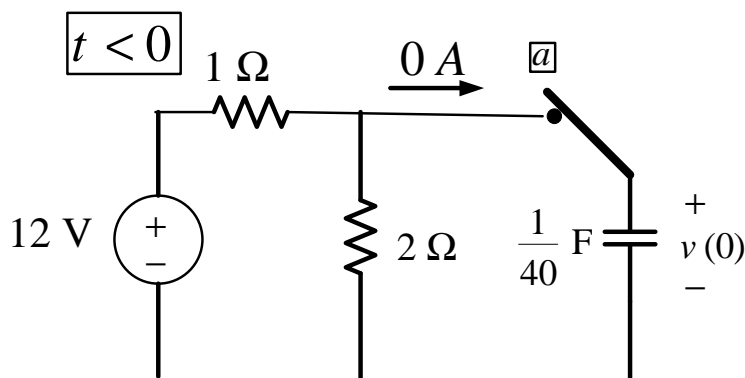

The switch in postion **a**

Capacitor initial voltage  $v(0) = \frac{2}{1+2}(12) = 8$  V (voltage divsion)

Inductor initial current  $i(0) = 0$  A

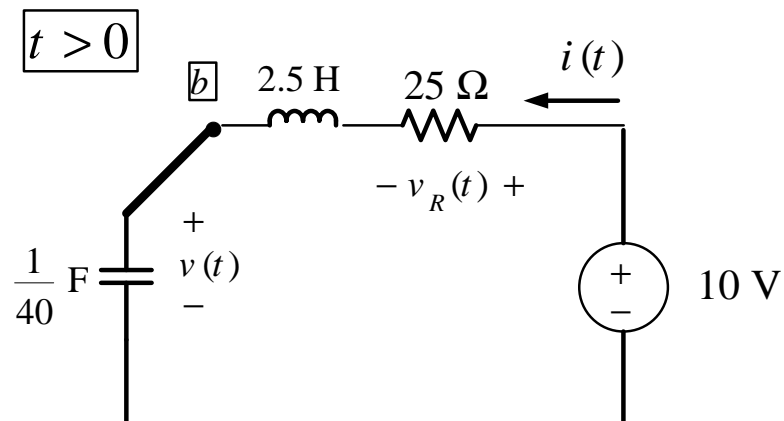

The switch in position **b**, we have series  $RLC$  circuit with voltage source

$$\alpha = \frac{R}{2L} = \frac{25}{2(2.5)} = 5 \text{ rad/s} \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2.5)\left(\frac{1}{40}\right)}} = 4 \text{ rad/s}$$

$$\alpha > \omega_0 \Rightarrow \text{overdamped} \Rightarrow v(t) = v_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{where } v_f = v(\infty) = 10 \text{ V} \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5 \pm \sqrt{5^2 - 4^2} = -5 \pm 3$$

$$\Rightarrow s_1 = -8 \text{ rad/s} \quad s_2 = -2 \text{ rad/s}$$

$$\Rightarrow v(t) = 10 + A_1 e^{-8t} + A_2 e^{-2t}$$

We get  $A_1, A_2$  by imposing the initial conditions as follows:

$$v(0) = 8 = 10 + A_1 + A_2 \Rightarrow A_1 + A_2 = -2 \text{ -----(1)}$$

$$\frac{dv(t)}{dt} = -8A_1 e^{-8t} - 2A_2 e^{-2t}$$

$$\Rightarrow \frac{dv(0)}{dt} = -8A_1 - 2A_2 \quad \text{finding } \frac{dv(0)}{dt} ?$$

$$\text{Since } i(0) = C \frac{dv(0)}{dt} \Rightarrow \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{0}{1/40} = 0$$

$$\Rightarrow \frac{dv(0)}{dt} = 0 = -8A_1 - 2A_2 \Rightarrow 4A_1 + A_2 = 0 \text{ -----(2)}$$

solving (1) and (2) , we get  $A_1 = \frac{2}{3}$     $A_2 = -\frac{8}{3}$

$$\Rightarrow v(t) = 10 + \frac{2}{3}e^{-8t} - \frac{8}{3}e^{-2t} \quad \forall t > 0$$

$$\begin{aligned} i(t) &= C \frac{dv(t)}{dt} = \left(\frac{1}{40}\right) \left\{ \frac{2}{3}e^{-8t}(-8) - \frac{8}{3}e^{-2t}(-2) \right\} = \left(\frac{1}{40}\right) \left\{ -\frac{16}{3}e^{-8t} + \frac{16}{3}e^{-2t} \right\} \\ &= \frac{2}{15}e^{-2t} - \frac{2}{15}e^{-8t} \quad \forall t > 0 \end{aligned}$$

$$\Rightarrow v_R(t) = 25i(t) = 25 \left\{ \frac{2}{15}e^{-2t} - \frac{2}{15}e^{-8t} \right\} = \frac{10}{3}e^{-2t} - \frac{10}{3}e^{-8t} \quad \forall t > 0$$

### Another Solution

We can start by finding  $i(t)$  directly as follows :

$$i(t) = i_f + A_1e^{-8t} + A_2e^{-2t} \quad \forall t > 0$$

here  $i_f = 0$  ( at  $\infty$  the capacitor is open)

$$i(t) = A_1e^{-8t} + A_2e^{-2t} \quad \forall t > 0$$

$$i(0) = 0 = A_1 + A_2 \text{-----(1)}$$


$$\frac{di(t)}{dt} = -8A_1e^{-8t} - 2A_2e^{-2t}$$

$$\frac{di(0)}{dt} = -8A_1 - 2A_2 \quad \text{finding } \frac{di(0)}{dt} ?$$

Since  $v_L(0) = L \frac{di(0)}{dt} \Rightarrow \frac{di(0)}{dt} = \frac{v_L(0)}{L}$

$\frac{di(0)}{dt} = -8A_1 - 2A_2 = \frac{v_L(0)}{L}$  finding  $v_L(0)$  ?

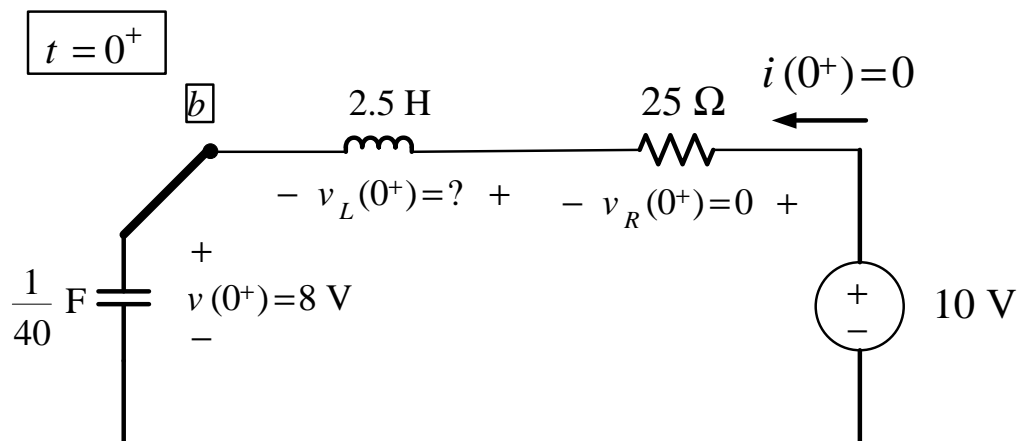To find  $v_L(0)$  we must look at the circuit at the instant  $0^+$   
(just after the switch move to position **b**)



**KVL**  $-8 - v_L(0^+) - v_R(0^+) + 10 = 0$

$\Rightarrow v_L(0^+) = -8 - v_R(0^+) + 10 = -8 - 0 + 10 = 2$

$\Rightarrow \frac{di(0)}{dt} = \frac{v_L(0)}{L} = \frac{2}{2.5} = 0.8$

$\Rightarrow \frac{di(0)}{dt} = -8A_1 - 2A_2 = 0.8$

$\Rightarrow -20A_1 - 5A_2 = 2$  -----(2)

solving (1) and (2) we get  $A_1 = -\frac{2}{15}$   $A_2 = \frac{2}{15}$

$\Rightarrow i(t) = \frac{2}{15}e^{-2t} - \frac{2}{15}e^{-8t}$  A  $t > 0$

Now, we can find  $v(t)$  using **KVL** as follows :

$$-v(t) - v_L(t) - v_R(t) + 10 = 0$$

$$\Rightarrow v(t) = 10 - v_L(t) - v_R(t)$$


$$= 10 - (2.5) \frac{di(t)}{dt} - (25)i(t)$$

$$= 10 + \frac{2}{3}e^{-8t} - \frac{8}{3}e^{-2t} \quad \forall t > 0$$

$$v_R(t) = (25)i(t) = 25 \left( \frac{2}{15}e^{-2t} - \frac{2}{15}e^{-8t} \right)$$

$$= \frac{10}{3}e^{-2t} - \frac{10}{3}e^{-8t} \quad \forall t > 0$$


SER	ID	NAME	KEY
-----	----	------	-----

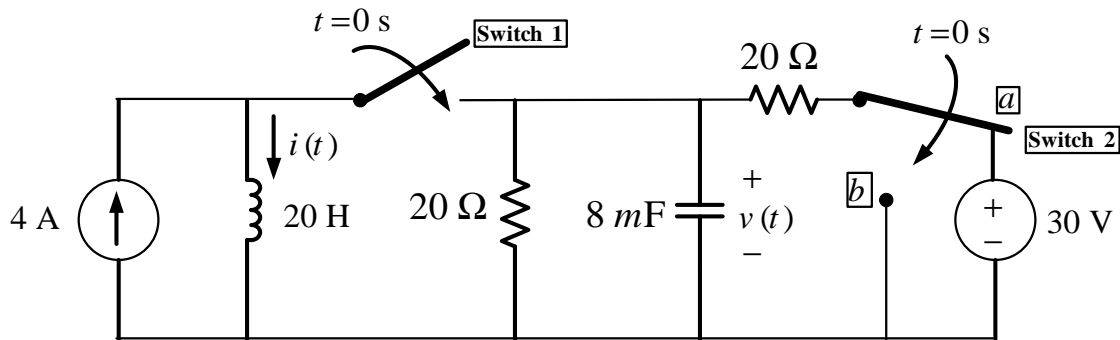

For the circuit shown above , **switch 1** closes at  $t = 0$  and **switch 2** was in position **a** for a long time and at  $t = 0$  s **switch 2** move to position **b** .

Find  $i(t)$  and  $v(t)$  for  $t > 0$ ? ( **Hint**  $\alpha = \frac{1}{2RC}$   $\omega_0 = \frac{1}{\sqrt{LC}}$  )


**Solution**

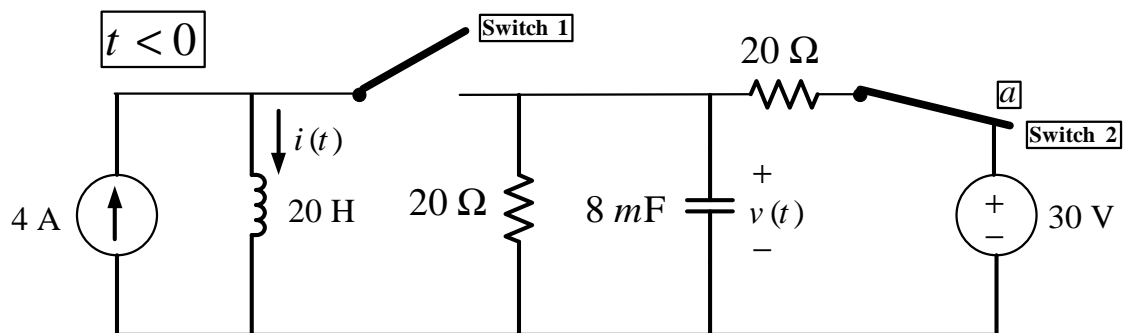

switch 1 open and switch 2 in position **a**

Inductor initial current  $i(0) = 4$  A

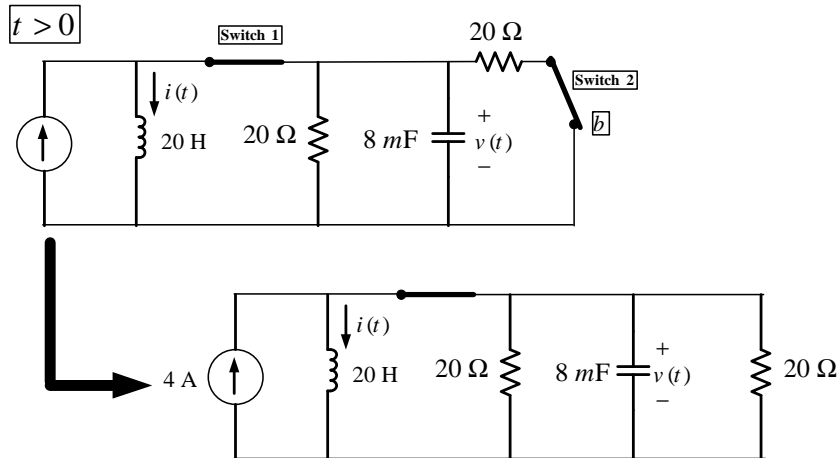Capacitor initial voltage  $v(0) = \frac{20}{20+20}(30) = 15$  V (voltage division)



switch 1 close and switch 2 in position **b**, we have a parallel  $RLC$  circuit with a current source

$$\alpha = \frac{1}{2RC} = \frac{1}{2(20 \parallel 20)(8 \times 10^{-3})} = 6.25 \text{ rad/s} \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20(8 \times 10^{-3})}} = 2.5 \text{ rad/s}$$

$$\alpha > \omega_0 \Rightarrow \text{overdamped} \Rightarrow i(t) = i_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{where } i_f = i(\infty) = 4 \text{ A} \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -6.25 \pm \sqrt{(6.25)^2 - (2.5)^2} = -6.25 \pm 5.7282$$

$$\Rightarrow s_1 = -11.978 \text{ rad/s} \quad s_2 = -0.5218 \text{ rad/s}$$

$$\Rightarrow i(t) = 4 + A_1 e^{-11.978t} + A_2 e^{-0.5218t}$$

We get  $A_1, A_2$  by imposing the initial conditions as follows:

$$i(0) = 4 = 4 + A_1 + A_2 \Rightarrow A_1 + A_2 = 0 \text{ -----(1)}$$

$$\frac{di(t)}{dt} = -11.978A_1 e^{-11.978t} - 0.5218A_2 e^{-0.5218t}$$

$$\Rightarrow \frac{di(0)}{dt} = -11.978A_1 - 0.5218A_2 \quad \text{finding } \frac{di(0)}{dt} ?$$

$$\text{Since } v(0) = 15 = L \frac{di(0)}{dt} \Rightarrow \frac{di(0)}{dt} = \frac{15}{20} = 0.75$$

$$\Rightarrow \frac{di(0)}{dt} = 0.75 = -11.978A_1 - 0.5218A_2 \text{ -----(2)}$$

solving (1) and (2) , we get  $A_1 = -0.0655$   $A_2 = 0.0655$

$$\Rightarrow i(t) = 4 - 0.0655e^{-11.978t} + 0.0655e^{-0.5218t} \text{ A } t > 0$$

$$\begin{aligned} v(t) = v_L(t) &= L \frac{di(t)}{dt} = (20) \left\{ -0.0655e^{-11.978t} (-11.978) + 0.0655e^{-0.5218t} (-0.5218) \right\} \\ &= 15.69e^{-11.978t} - 0.683558e^{-0.5218t} \text{ V } t > 0 \end{aligned}$$

### Another Solution

We can start by finding  $v(t)$  directly as follows :

$$v(t) = v_f + A_1 e^{-11.978t} + A_2 e^{-0.5218t} \text{ V } t > 0$$

here  $v_f = 0$  ( at  $\infty$  the inductor is short  $\Rightarrow$  the capacitor voltage = 0)

$$v(t) = A_1 e^{-11.978t} + A_2 e^{-0.5218t} \text{ V } t > 0$$

$$v(0) = 15 = A_1 + A_2 \text{ -----(1)}$$


$$\frac{dv(t)}{dt} = -11.978A_1 e^{-11.978t} - 0.5218A_2 e^{-0.5218t}$$

$$\frac{dv(0)}{dt} = -11.978A_1 - 0.5218A_2 \text{ finding } \frac{dv(0)}{dt} ?$$

$$\text{Since } i_C(0) = C \frac{dv(0)}{dt} \Rightarrow \frac{dv(0)}{dt} = \frac{i_C(0)}{C} \text{ finding } i_C(0) ?$$

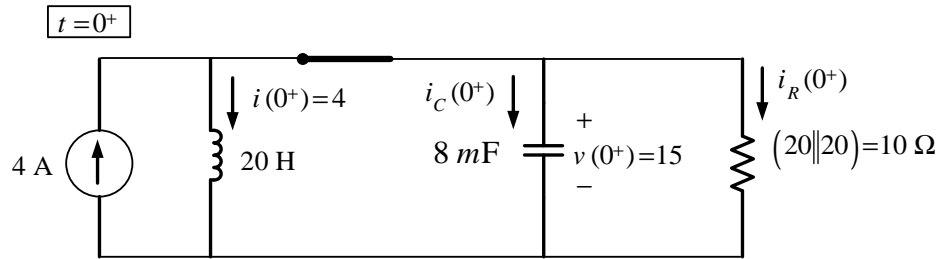To find  $i_C(0)$  we must look at the circuit at the instant  $0^+$





**KCL**  $-4 + i_L(0^+) + i_C(0^+) + i_R(0^+) = 0$

$$-4 + 4 + i_C(0^+) + \frac{15}{10} = 0$$

$$\Rightarrow i_C(0^+) = -1.5 \text{ A}$$

$$\Rightarrow \frac{dv(0)}{dt} = \frac{i_C(0^+)}{C} = \frac{-1.5}{(8 \times 10^{-3})} = -187.5$$

$$\frac{dv(0)}{dt} = -187.5 = -11.978A_1 - 0.5218A_2$$

$$11.978A_1 + 0.5218A_2 = 187.5 \text{ -----(2)}$$

solving (1) and (2) we get  $A_1 = 15.6835$     $A_2 = -0.6835$

$$\Rightarrow v(t) = 15.6835e^{-11.978t} - 0.6835e^{-0.5218t} \text{ V } t > 0$$

Now, we can find  $i(t)$  using **KCL** as follows :

$$-4 + i(t) + i_C(t) + i_R(t) = 0$$

$$\Rightarrow i(t) = 4 - i_C(t) - i_R(t) = 4 - (8 \times 10^{-3}) \frac{dv(t)}{dt} - \frac{v(t)}{10}$$

$$\Rightarrow i(t) = 4 - 0.0655e^{-11.978t} + 0.0655e^{-0.5218t} \text{ A } t > 0$$