

Q1.a)  $L_{eq}=L$

Q1.b)  $C_{eq}= 4F$


Q2)

Let  $v$  be the voltage across the capacitor.

For  $t < 0$ ,

$$v(0^-) = \frac{4}{2+4}(24) = 16 \text{ V}$$

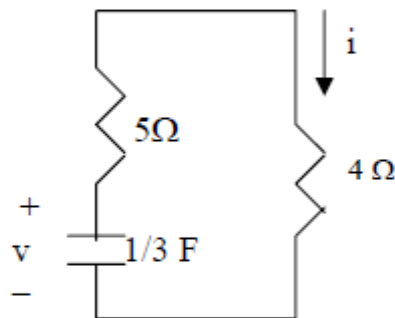For  $t > 0$ , we have a source-free RC circuit as shown below.




$$\tau = RC = (4 + 5) \frac{1}{3} = 3 \text{ s}$$

$$v(t) = v(0) e^{-t/\tau} = 16 e^{-t/3}$$

$$i(t) = -C \frac{dv}{dt} = -\frac{1}{3} \left(-\frac{1}{3}\right) 16 e^{-t/3} = \underline{1.778 e^{-t/3} \text{ A}}$$

Q3)

1)  $t < 0$

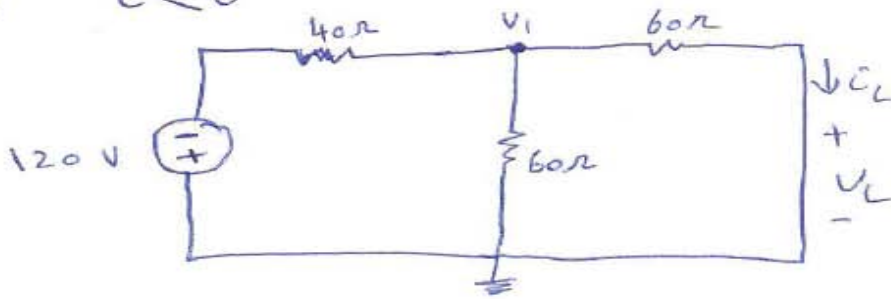


$$\frac{V_1 + 120}{40} + \frac{V_1}{60} + \frac{V_1}{60} = 0 \Rightarrow V_L = -51.42 \text{ V}$$

$$i_L = \frac{V_1}{60} = -0.86 \text{ A}$$

$$V_L = 0$$

$$i_D = 0$$

$t \gg 0$

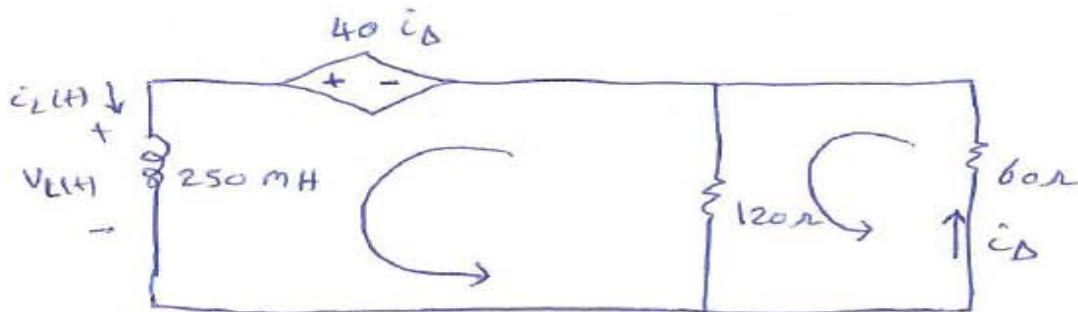

$$L \frac{di_L(t)}{dt} + 120(i_L - i_D) - 40i_D = 0$$

$$0.25 \frac{di_L}{dt} + 120i_L - 160i_D = 0$$

$$60i_D + 120(i_D - i_L) = 0 \Rightarrow i_D = 0.67i_L$$

$$\Rightarrow 0.25 \frac{di_L}{dt} + 120i_L - 107.2i_L = 0$$

$$\frac{di_L}{dt} + 51.2i_L = 0$$

$$i_L(t) = i_L(0) e^{-51.2t} = -0.86 e^{-51.2t}$$

contin)

$$v_L(t) = L \frac{di_L(t)}{dt} = (0.25) (-0.86 e^{-51.2t}) = -0.215 e^{-51.2t}$$

$$i_D(t) = 0.67 i_L(t) = (0.67) (-0.86 e^{-51.2t}) = -0.57 e^{-51.2t}$$

$$\Rightarrow i_L(t) = \begin{cases} -0.86 & ; t < 0 \\ -0.86 e^{-51.2t} & ; t \geq 0 \end{cases}$$

$$v_L(t) = \begin{cases} 0 & ; t < 0 \\ -0.215 e^{-51.2t} & ; t \geq 0 \end{cases}$$

$$i_D(t) = \begin{cases} 0 & ; t < 0 \\ -0.57 e^{-51.2t} & ; t \geq 0 \end{cases}$$

Q4)

Applying KCL @ node A

$$\frac{V\phi}{15k\Omega} + V\phi + \frac{V\phi - V_c}{20k\Omega} = 0$$

$$V\phi \left[ \frac{1}{15000} + 1 + \frac{1}{20000} \right] = \frac{V_c}{20000}$$


$$V\phi = \frac{V_c}{20000 \left[ \frac{1}{15000} + 1 + \frac{1}{20000} \right]} = \frac{V_c}{\left[ \frac{4}{3} + 20000 + 1 \right]}$$

$$= \frac{V_c}{20002.33}$$

$$= 1.799 e^{-1/75} \text{ mV}$$

Q5)


$t < 0$

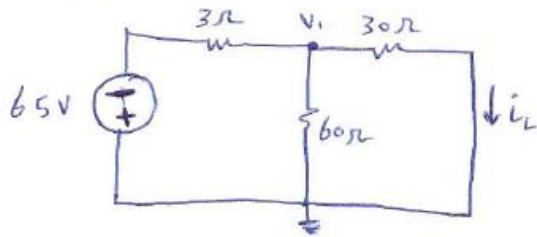

$$\frac{V_1 + 65}{3} + \frac{V_1}{60} + \frac{V_1}{30} = 0 \Rightarrow V_1 = -56.52 \text{ V}, \quad i_L = \frac{V_1}{30} = -1.88 \text{ A}$$

$$V_0 = 0$$

$t \geq 0$

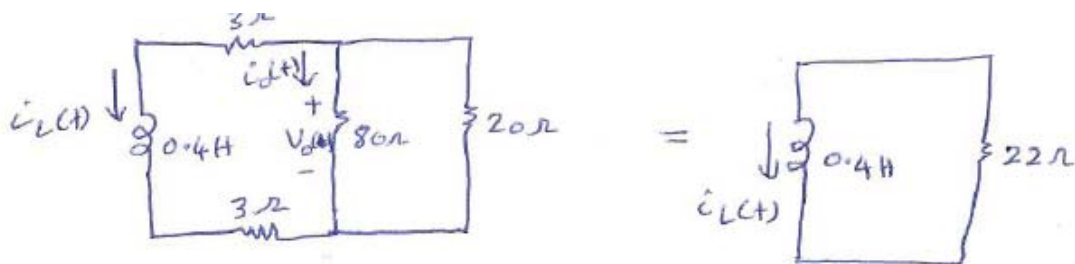

$$i_L(0) = i_L(0^-) = -1.88 \text{ A}$$

$$i_L(t) = i_L(0) e^{-55t} = -1.88 e^{-55t}$$

$$i_0(t) = \frac{20}{20 + 80} (-i_L(t))$$

$$= 0.37 e^{-55t}$$

$$V_0(t) = (80)(0.37 e^{-55t}) = 30 e^{-55t}$$

$$\Rightarrow V_0(t) = \begin{cases} 0 & ; t < 0 \\ 30 e^{-55t} & ; t \geq 0 \end{cases}$$