

EE 202 (Semester 131)

Homework # 2

Due Date: Sunday 29 September 2013

Problems from the text book (*Electric Circuits*, James Nilsson and Susan Riedel, 9th edition, Prentice Hall, 2011)

3.6, 3.26, 3.28, &

4.6, 4.13, 4.17, 4.24, 4.28