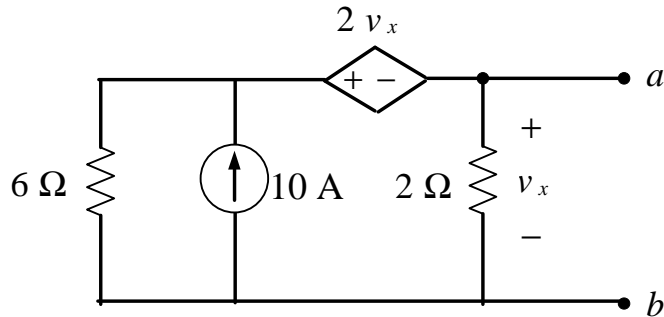



EE 202-06-Fall 2013(131)
QZ3

Sec	Ser	ID	Name	KEY
-----	-----	----	------	-----



For the circuit shown above, find the followings:

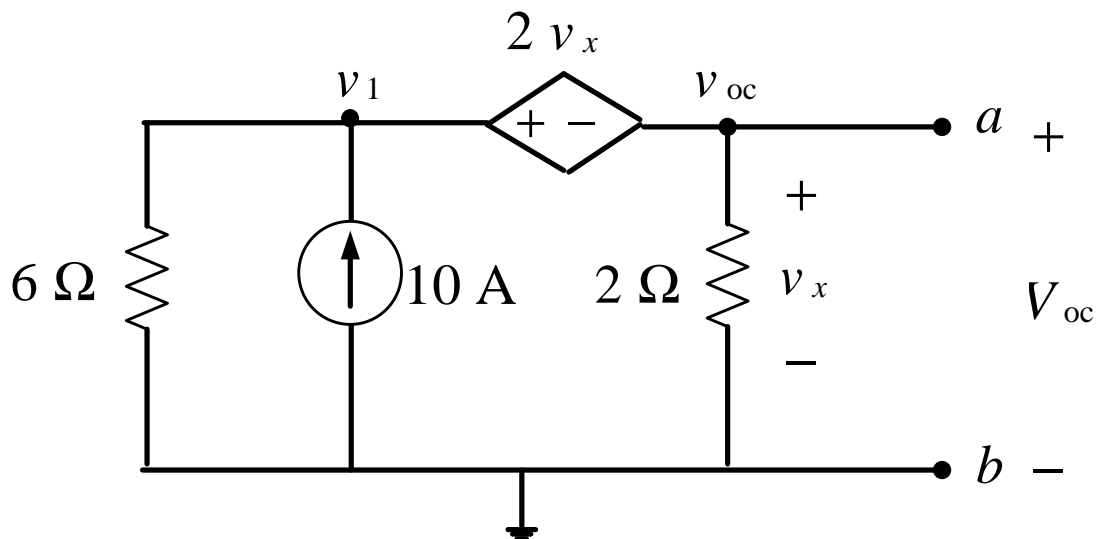- The Thevenin's equivalent between terminals a and b ?
- If a load resistor is connected between a and b , find the load resistor that will absorb the maximum power and find the maximum power



KCL on supper node



$$\frac{v_1}{6} - 10 + \frac{V_{oc}}{2} = 0 \Rightarrow v_1 + 3V_{oc} = 60 \text{ ----(1)}$$

Voltage Restriction $v_1 - V_{oc} = 2v_x = 2V_{oc} \Rightarrow v_1 - 3V_{oc} = 0 \text{ ----(2)}$

Solving (1) and (2) $V_{oc} = 10 \text{ V}$

Finding R_{TH}

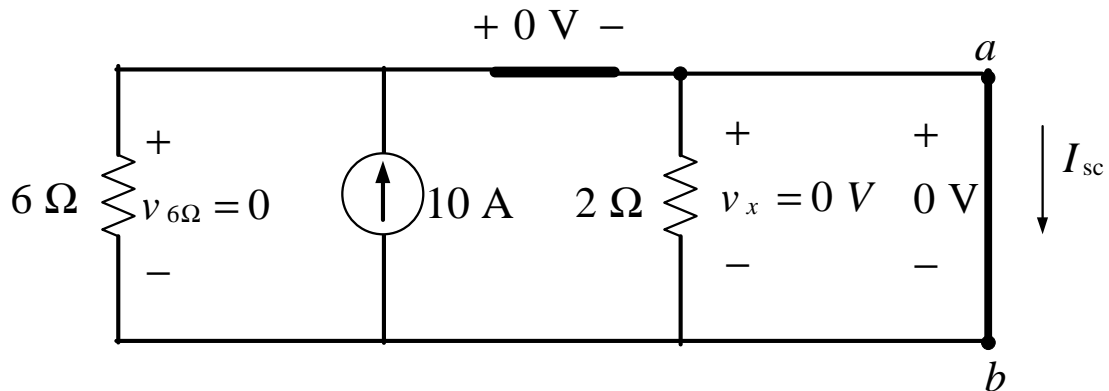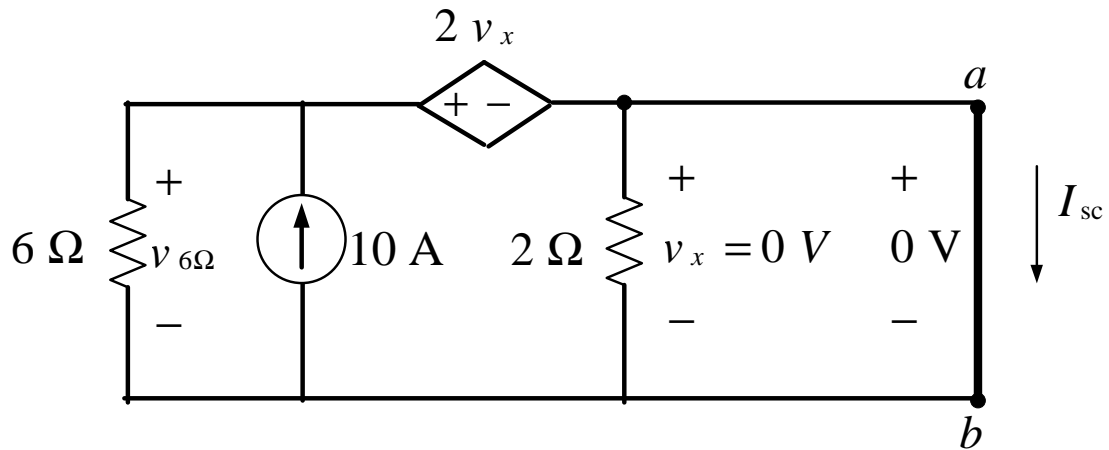Method I : using $R_{TH} = \frac{v_{oc}}{I_{sc}}$




Shorting a and b

$$\Rightarrow v_x = 0\text{ V} \Rightarrow 2v_x = 0\text{ V} \Rightarrow v_{6\Omega} = 0\text{ V} \Rightarrow I_{sc} = 10\text{ A}$$

$$\Rightarrow R_{TH} = \frac{v_{oc}}{I_{sc}} = \frac{10}{10} = 1\Omega$$

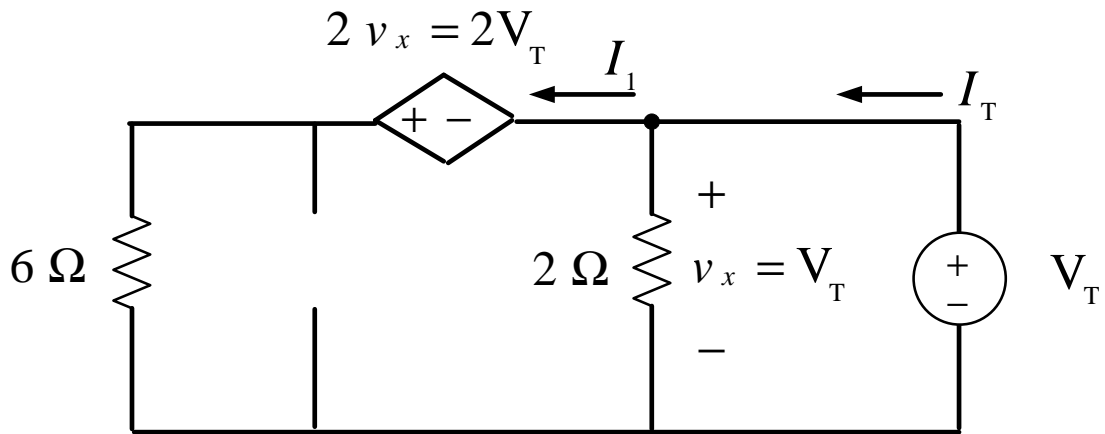Method II : using $R_{\text{TH}} = \frac{V_{\text{T}}}{I_{\text{T}}}$



$$\mathbf{KVL} \quad -V_T - 2V_T + 6I_1 = 0 \text{ V} \Rightarrow I_1 = \frac{V_T}{2}$$

$$\mathbf{KCL} \quad I_T = \frac{V_T}{2} + I_1 = \frac{V_T}{2} + \frac{V_T}{2} = V_T$$

$$\Rightarrow R_{\text{TH}} = \frac{V_T}{I_T} = 1\ \Omega$$

(b) The resistor that will absorb the maximum power is

$$R_L = R_{TH} = 1\Omega$$

$$P_{\max} = \frac{V_{oc}^2}{4R_{TH}} = \frac{10^2}{4(1)} = 25 \text{ W}$$