
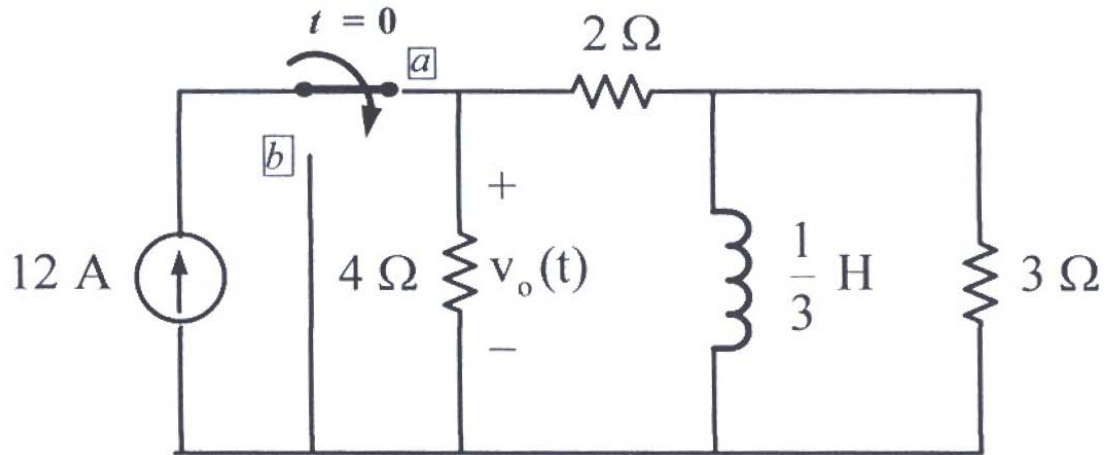


EE 202-02-Winter 2013(132)  
QZ5


Sec	Ser	ID	Name <b>KEY</b>
-----	-----	----	-----------------

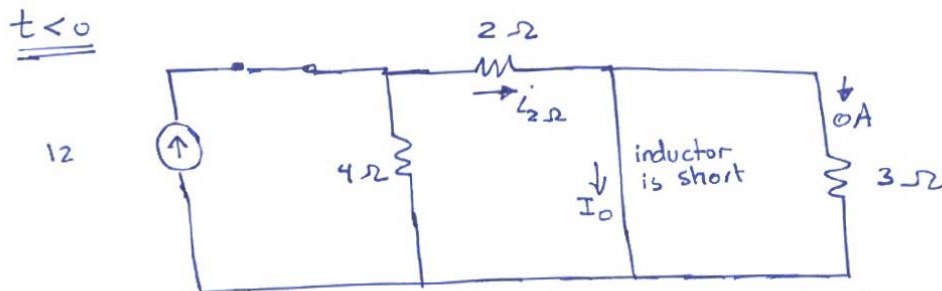

For the circuit shown above, the switch was in position a for a long time  
Find  $V_o(t)$  for all time ?


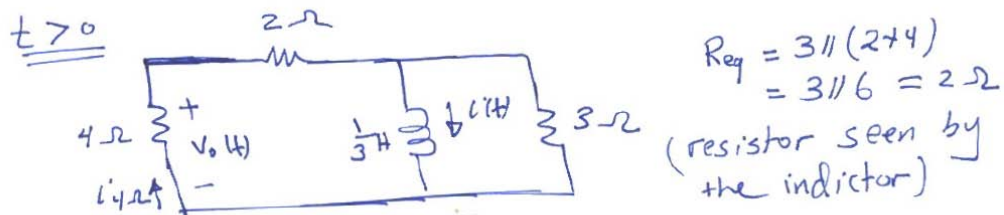
$$i_{2\Omega} \Rightarrow I_0 = i_{2\Omega} = \frac{4}{4+2} 12 = 8 \text{ A}$$



$$\tau = \frac{L}{R_{eq}} = \frac{\frac{1}{3}}{2} = \frac{1}{6} \text{ s}$$

$$\Rightarrow i(t) = 8 e^{-6t} \quad t \geq 0$$

$$\Rightarrow i_{4\Omega}(t) = \frac{3}{(2+4)+3} i(t) = \frac{3}{9} 8 e^{-6t} = \frac{8}{3} e^{-6t}$$

$$\Rightarrow v_{4\Omega}(t) = 4 i_{4\Omega}(t) = \frac{32}{3} e^{-6t} \text{ V} \quad t > 0^+$$