
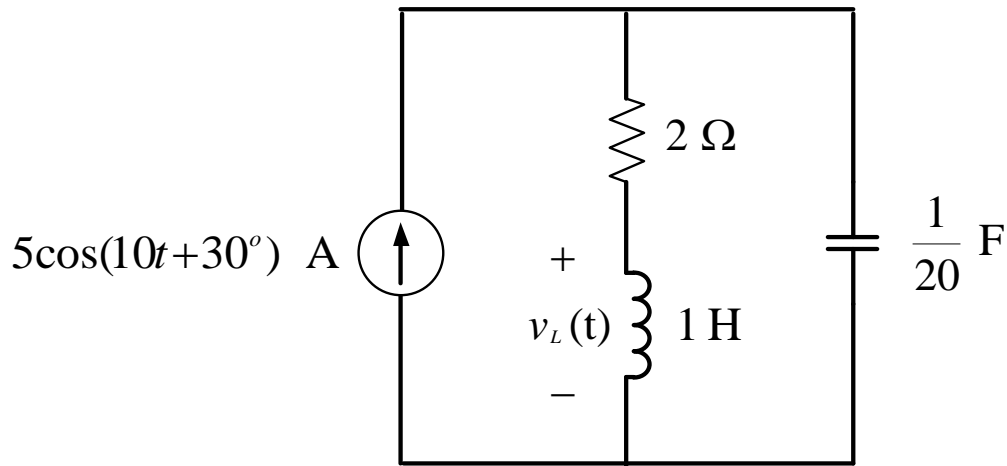


Sec	Ser	ID	Name KEY
-----	-----	----	-----------------

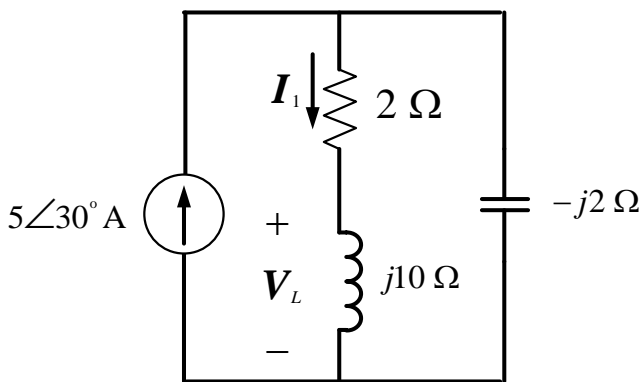

In the circuit shown above , find the $v_L(t)$?

Solution



$$I_1 = \frac{-j2}{(2+j10)+(-j2)} (5\angle 30^\circ) = 1.21\angle -135.96^\circ \text{ A}$$

$$V_L = (j10)I_1 = 12.1\angle -45.96^\circ \text{ A}$$

$$\Rightarrow v_L(t) = 12.1\cos(10t - 45.96^\circ) \text{ V}$$