

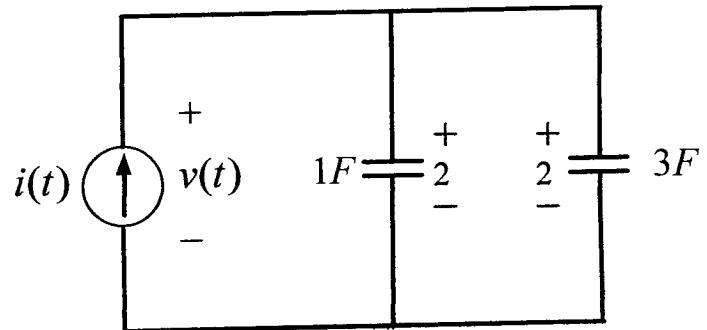


Sec	Ser	ID	Name	KEY
-----	-----	----	------	-----

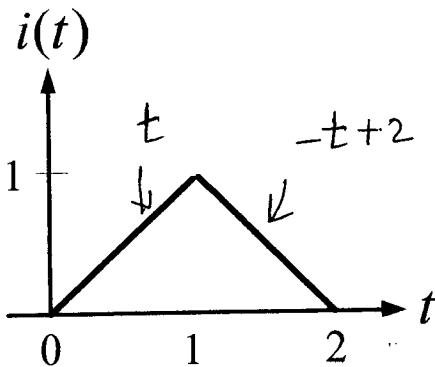

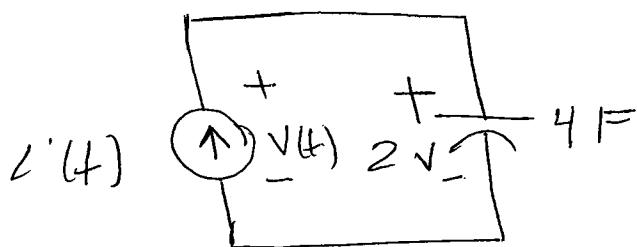For the circuit shown above, the capacitors initially have 2 V.
If the current applied is as shown , write expression for the voltage $v(t)$?



$$v(t) = \frac{1}{2} \int_0^t i(\tau) d\tau + v(0)$$

$$\cancel{v(t)} \quad 0 \leq t \leq 1 \Rightarrow v(t) = \frac{1}{4} \int_0^t 2 d\tau + 2 = \frac{t^2}{8} + 2$$

$$1 \leq t \leq 2 \Rightarrow v(t) = \frac{1}{4} \int_1^t (-t+2) + v(1)$$

$$= -\frac{t^2}{8} + \frac{t}{2} + \frac{7}{4}$$

$$t > 2 \Rightarrow v(t) = \frac{1}{4} \int_2^t 0 d\tau + v(2) = \frac{9}{4}$$