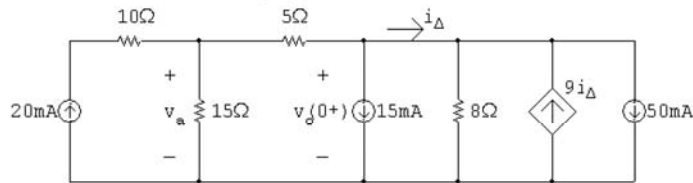


EE202\_141\_Dr. Alakhdhar

P 7.41  $t > 0$ ; calculate  $v_o(0^+)$



$$\frac{v_a}{15} + \frac{v_a - v_o(0^+)}{5} = 20 \times 10^{-3}$$

$$\therefore v_a = 0.75v_o(0^+) + 75 \times 10^{-3}$$

$$15 \times 10^{-3} + \frac{v_o(0^+) - v_a}{5} + \frac{v_o(0^+)}{8} - 9i_\Delta + 50 \times 10^{-3} = 0$$

$$13v_o(0^+) - 8v_a - 360i_\Delta = -2600 \times 10^{-3}$$

$$i_\Delta = \frac{v_o(0^+)}{8} - 9i_\Delta + 50 \times 10^{-3}$$

$$\therefore i_\Delta = \frac{v_o(0^+)}{80} + 5 \times 10^{-3}$$

$$\therefore 360i_\Delta = 4.5v_o(0^+) + 1800 \times 10^{-3}$$

$$8v_a = 6v_o(0^+) + 600 \times 10^{-3}$$


$$\therefore 13v_o(0^+) - 6v_o(0^+) - 600 \times 10^{-3} - 4.5v_o(0^+) -$$

$$1800 \times 10^{-3} = -2600 \times 10^{-3}$$

$$2.5v_o(0^+) = -200 \times 10^{-3}; \quad v_o(0^+) = -80 \text{ mV}$$

$$v_o(\infty) = 0$$

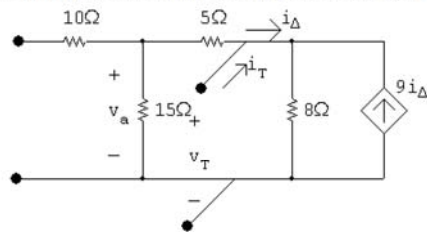Find the Thévenin resistance seen by the 4 mH inductor:



$$i_T = \frac{v_T}{20} + \frac{v_T}{8} - 9i_\Delta$$

$$i_\Delta = \frac{v_T}{8} - 9i_\Delta \quad \therefore 10i_\Delta = \frac{v_T}{8}; \quad i_\Delta = \frac{v_T}{80}$$

$$i_T = \frac{v_T}{20} + \frac{10v_T}{80} - \frac{9v_T}{80}$$


$$\frac{i_T}{v_T} = \frac{1}{20} + \frac{1}{80} = \frac{5}{80} = \frac{1}{16} \text{ S}$$

$$\therefore R_{Th} = 16\Omega$$

$$\tau = \frac{4 \times 10^{-3}}{16} = 0.25 \text{ ms}; \quad 1/\tau = 4000$$


$$\therefore v_o = 0 + (-80 - 0)e^{-4000t} = -80e^{-4000t} \text{ mV}, \quad t \geq 0^+$$

P 7.70  $t < 0$ :

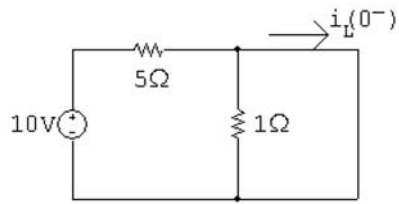

$$i_L(0^-) = 10 \text{ V} / 5 \Omega = 2 \text{ A} = i_L(0^+)$$

$0 \leq t \leq 5$ :

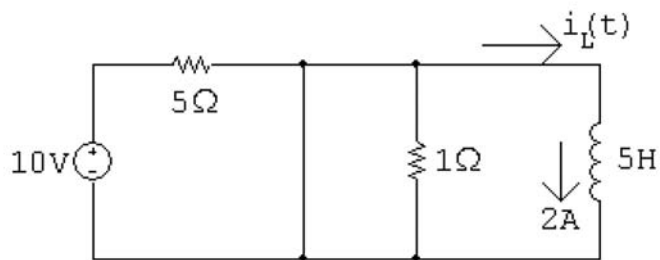


$$\tau = 5/0 = \infty$$

$$i_L(t) = 2e^{-t/\infty} = 2e^{-0} = 2$$

$$i_L(t) = 2 \text{ A} \quad 0 \leq t \leq 5 \text{ s}$$


$5 \leq t < \infty$ :

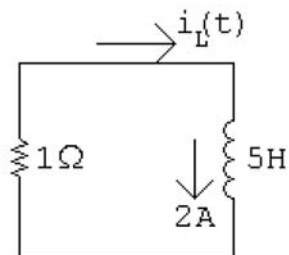

$$\tau = \frac{5}{1} = 5 \text{ s}; \quad 1/\tau = 0.2$$

$$i_L(t) = 2e^{-0.2(t-5)} \text{ A}, \quad t \geq 5 \text{ s}$$

P 7.84  $t > 0$ :

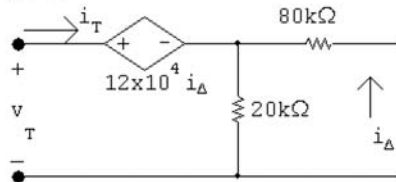

$$v_T = 12 \times 10^4 i_\Delta + 16 \times 10^3 i_T$$

$$i_\Delta = -\frac{20}{100} i_T = -0.2 i_T$$

$$\therefore v_T = -24 \times 10^3 i_T + 16 \times 10^3 i_T$$

$$R_{Th} = \frac{v_T}{i_T} = -8 \text{ k}\Omega$$

$$\tau = RC = (-8 \times 10^3)(2.5 \times 10^{-6}) = -0.02 \quad 1/\tau = -50$$

$$v_c = 20e^{50t} \text{ V}; \quad 20e^{50t} = 20,000$$

$$50t = \ln 1000 \quad \therefore \quad t = 138.16 \text{ ms}$$

P 8.10  $\alpha = 500/2 = 250$

$$R = \frac{1}{2\alpha C} = \frac{10^6}{(500)(2.5)} = 800 \Omega$$

$$v(0^+) = -11 + 20 = 9 \text{ V}$$

$$i_R(0^+) = \frac{9}{800} = 11.25 \text{ mA}$$

$$\frac{dv}{dt} = 1100e^{-100t} - 8000e^{-400t}$$

$$\frac{dv(0^+)}{dt} = 1100 - 8000 = -6900 \text{ V/s}$$

$$i_C(0^+) = 2.5 \times 10^{-6}(-6900) = -17.25 \text{ mA}$$


$$i_L(0^+) = -[i_R(0^+) + i_C(0^+)] = -[11.25 - 17.25] = 6 \text{ mA}$$

P 8.27  $t < 0$ :

$$v_o(0^-) = v_o(0^+) = \frac{625}{781.25}(25) = 20 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0$$

$t > 0$ :

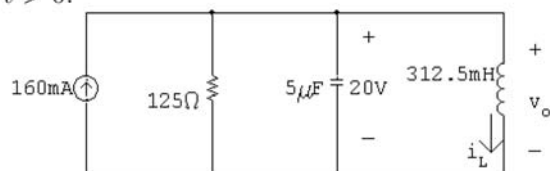

$$-160 \times 10^{-3} + \frac{20}{125} + i_C(0^+) + 0 = 0; \quad \therefore i_C(0^+) = 0$$

$$\frac{1}{2RC} = \frac{1}{2(125)(5 \times 10^{-6})} = 800 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(312.5 \times 10^{-3})(5 \times 10^{-6})} = 64 \times 10^4$$

$\therefore \alpha^2 = \omega_o^2$  critically damped

$$[\mathbf{a}] v_o = V_f + D'_1 t e^{-800t} + D'_2 e^{-800t}$$

$$V_f = 0$$

$$\frac{dv_o(0)}{dt} = -800D'_2 + D'_1 = 0$$

$$v_o(0^+) = 20 = D'_2$$

$$D'_1 = 800D'_2 = 16,000 \text{ V/s}$$

$$\therefore v_o = 16,000t e^{-800t} + 20e^{-800t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{b}] i_L = I_f + D'_3 t e^{-800t} + D'_4 e^{-800t}$$

$$i_L(0^+) = 0; \quad I_f = 160 \text{ mA}; \quad \frac{di_L(0^+)}{dt} = \frac{20}{312.5 \times 10^{-3}} = 64 \text{ A/s}$$

$$\therefore 0 = 160 + D'_4; \quad D'_4 = -160 \text{ mA};$$

$$-800D'_4 + D'_3 = 64; \quad D'_3 = -64 \text{ A/s}$$

$$\therefore i_L = 160 - 64,000t e^{-800t} - 160e^{-800t} \text{ mA} \quad t \geq 0$$

$$\text{P 8.44 } [\mathbf{a}] \omega_o^2 = \frac{1}{LC} = \frac{10^9}{(125)(0.32)} = 25 \times 10^6$$

$$\alpha = \frac{R}{2L} = \omega_o = 5000 \text{ rad/s}$$

$$\therefore R = (5000)(2)L = 1250 \Omega$$

$$[\mathbf{b}] i(0) = i_L(0) = 4 \text{ mA}$$

$$v_L(0) = 15 - (0.004)(1250) = 10 \text{ V}$$

$$\frac{di}{dt}(0) = \frac{7.5}{0.125} = 80 \text{ A/s}$$

$$[\mathbf{c}] v_C = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$v_C(0) = D_2 = 15 \text{ V}$$

$$\frac{dv_C}{dt}(0) = D_1 - 5000D_2 = \frac{i_C(0)}{C} = \frac{-i_L(0)}{C} = -12,500$$

$$\therefore D_1 = 62,500 \text{ V/s}$$

$$v_C = 62,500t e^{-5000t} + 15e^{-5000t} \text{ V}, \quad t \geq 0$$