

$$\text{P 9.25 [a]} \quad j\omega L = R \parallel (-j/\omega C) = j\omega L + \frac{-jR/\omega C}{R - j/\omega C}$$

$$j\omega L + \frac{-jR}{\omega CR - j}$$

$$j\omega L + \frac{-jR(\omega CR + j)}{\omega^2 C^2 R^2 + 1}$$

$$\mathbf{Im}(Z_{ab}) = \omega L - \frac{\omega CR^2}{\omega^2 C^2 R^2 + 1} = 0$$

$$\therefore L = \frac{CR^2}{\omega^2 C^2 R^2 + 1}$$

$$\therefore \omega^2 C^2 R^2 + 1 = \frac{CR^2}{L}$$

$$\therefore \omega^2 = \frac{(CR^2/L) - 1}{C^2 R^2} = \frac{\frac{(25 \times 10^{-9})(100)^2}{160 \times 10^{-6}} - 1}{(25 \times 10^{-9})^2 (100)^2} = 900 \times 10^8$$

$$\omega = 300 \text{ krad/s}$$

$$\text{[b]} \quad Z_{ab}(300 \times 10^3) = j48 + \frac{(100)(-j133.33)}{100 - j133.33} = 64 \Omega$$

$$\begin{aligned} \text{P 9.27} \quad Z_{ab} &= 1 - j8 + (2 + j4) \parallel (10 - j20) + (40 \parallel j20) \\ &= 1 - j8 + 3 + j4 + 8 + j16 = 12 + j12 \Omega = 16.97 / \underline{45^\circ} \Omega \end{aligned}$$

$$\text{P 9.39 [a]} \quad Z_{\text{eq}} = \frac{50,000}{3} + \frac{-j20 \times 10^6}{\omega} \parallel (1200 + j0.2\omega)$$

$$= \frac{50,000}{3} + \frac{-j20 \times 10^6}{\omega} \frac{(1200 + j0.2\omega)}{1200 + j[0.2\omega - \frac{20 \times 10^6}{\omega}]}$$

$$= \frac{50,000}{3} + \frac{\frac{-j20 \times 10^6}{\omega} (1200 + j0.2\omega) \left[ 1200 - j \left( 0.2\omega - \frac{20 \times 10^6}{\omega} \right) \right]}{1200^2 + \left( 0.2\omega - \frac{20 \times 10^6}{\omega} \right)^2}$$

$$\mathbf{Im}(Z_{\text{eq}}) = -\frac{20 \times 10^6}{\omega} (1200)^2 - \frac{20 \times 10^6}{\omega} \left[ 0.2\omega \left( 0.2\omega - \frac{20 \times 10^6}{\omega} \right) \right] = 0$$

$$-20 \times 10^6 (1200)^2 - 20 \times 10^6 \left[ 0.2\omega \left( 0.2\omega - \frac{20 \times 10^6}{\omega} \right) \right] = 0$$

$$-(1200)^2 = 0.2\omega \left( 0.2\omega - \frac{20 \times 10^6}{\omega} \right)$$

$$0.2^2 \omega^2 - 0.2(20 \times 10^6) - 1200^2 = 0$$

$$\omega^2 = 64 \times 10^6 \quad \therefore \quad \omega = 8000 \text{ rad/s}$$

$$\therefore \quad f = 1273.24 \text{ Hz}$$

$$\text{[b]} \quad Z_{\text{eq}} = \frac{50,000}{3} + -j2500 \parallel (1200 + j1600)$$

$$= \frac{50,000}{3} + \frac{(-j2500)(1200 + j1600)}{1200 - j900} = 20,000 \Omega$$

$$\mathbf{I}_g = \frac{30/\underline{0^\circ}}{20,000} = 1.5/\underline{0^\circ} \text{ mA}$$

$$i_g(t) = 1.5 \cos 8000t \text{ mA}$$

P 9.45 Step 1 to Step 2:





$$\frac{240/0^\circ}{j12} = -j20 = 20/\underline{-90^\circ} \text{ A}$$

Step 2 to Step 3:


$$(j12) \parallel 36 = 3.6 + j10.8 \Omega$$

Step 3 to Step 4:
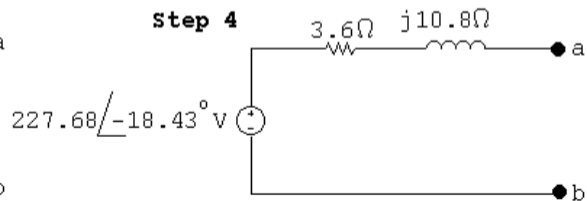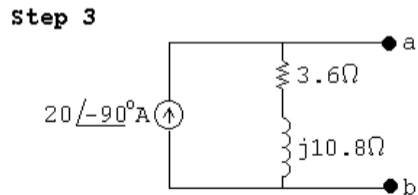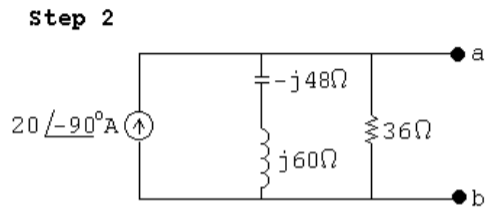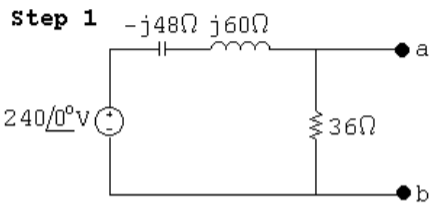
$$(20/\underline{-90^\circ})(3.6 + j10.8) = 216 - j72 = 227.68/\underline{-18.43^\circ} \text{ V}$$



P 9.48 Open circuit voltage:

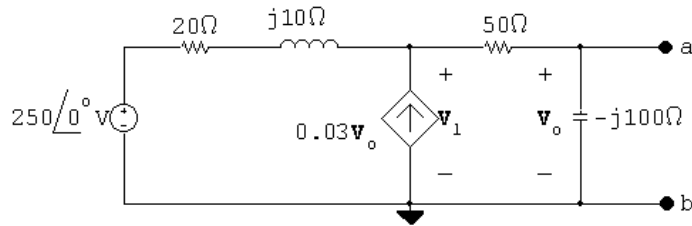


$$\frac{V_1 - 250}{20 + j10} - 0.03V_o + \frac{V_1}{50 - j100} = 0$$

$$\therefore V_o = \frac{-j100}{50 - j100} V_1$$

$$\frac{V_1}{20 + j10} + \frac{j3V_1}{50 - j100} + \frac{V_1}{50 - j100} = \frac{250}{20 + j10}$$

$$V_1 = 500 - j250 \text{ V}; \quad V_o = 300 - j400 \text{ V} = V_{Th}$$


Short circuit current:

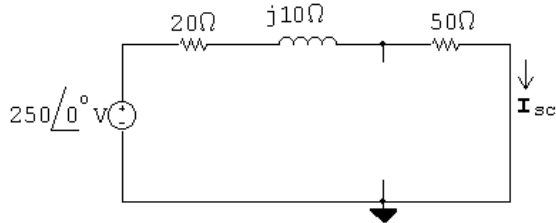

$$I_{sc} = \frac{250/0^\circ}{70 + j10} = 3.5 - j0.5 \text{ A}$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{300 - j400}{3.5 - j0.5} = 100 - j100 \Omega$$

The Thévenin equivalent circuit:

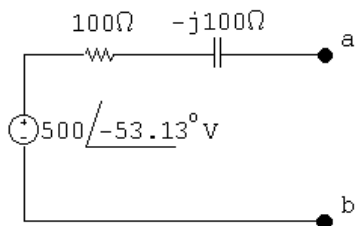

P 9.59 Write a KCL equation at the top node:

$$\frac{\mathbf{V}_o}{-j8} + \frac{\mathbf{V}_o - 2.4\mathbf{I}_\Delta}{j4} + \frac{\mathbf{V}_o}{5} - (10 + j10) = 0$$

The constraint equation is:

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j8}$$

Solving,

$$\mathbf{V}_o = j80 = 80/\underline{90^\circ} \text{ V}$$