

EE 202-151
HW 1 (Due Monday 14-Sept by 1:00 PM)
Dr. Adil Balghonaim

P 1.24 [a] $q =$ area under i vs. t plot
 $= \left[\frac{1}{2}(5)(4) + (10)(4) + \frac{1}{2}(8)(4) + (8)(6) + \frac{1}{2}(3)(6) \right] \times 10^3$
 $= [10 + 40 + 16 + 48 + 9]10^3 = 123,000 \text{ C}$

[b] $w = \int p dt = \int vi dt$

$$v = 0.2 \times 10^{-3}t + 9 \quad 0 \leq t \leq 15 \text{ ks}$$

$$0 \leq t \leq 4000s$$

$$i = 15 - 1.25 \times 10^{-3}t$$

$$p = 135 - 8.25 \times 10^{-3}t - 0.25 \times 10^{-6}t^2$$

$$w_1 = \int_0^{4000} (135 - 8.25 \times 10^{-3}t - 0.25 \times 10^{-6}t^2) dt$$
$$= (540 - 66 - 5.3333)10^3 = 468.667 \text{ kJ}$$

$$4000 \leq t \leq 12,000$$

$$i = 12 - 0.5 \times 10^{-3}t$$

$$p = 108 - 2.1 \times 10^{-3}t - 0.1 \times 10^{-6}t^2$$

$$w_2 = \int_{4000}^{12,000} (108 - 2.1 \times 10^{-3}t - 0.1 \times 10^{-6}t^2) dt$$
$$= (864 - 134.4 - 55.467)10^3 = 674.133 \text{ kJ}$$

$$12,000 \leq t \leq 15,000$$


$$i = 30 - 2 \times 10^{-3}t$$

$$p = 270 - 12 \times 10^{-3}t - 0.4 \times 10^{-6}t^2$$

$$w_3 = \int_{12,000}^{15,000} (270 - 12 \times 10^{-3}t - 0.4 \times 10^{-6}t^2) dt$$
$$= (810 - 486 - 219.6)10^3 = 104.4 \text{ kJ}$$

$$w_T = w_1 + w_2 + w_3 = 468.667 + 674.133 + 104.4 = 1247.2 \text{ kJ}$$

P 2.23 [a]

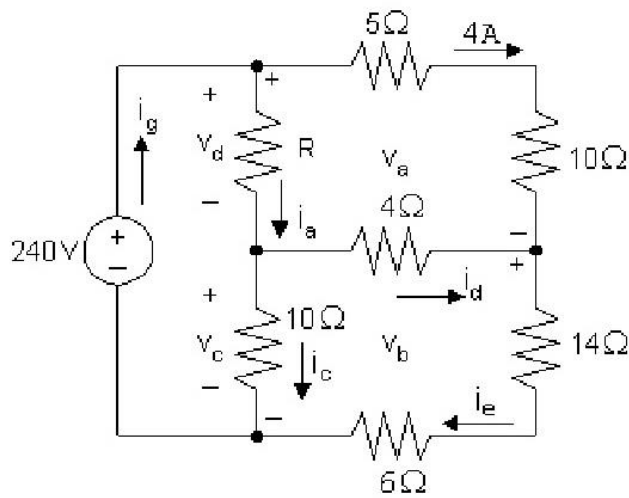

$$v_a = (5 + 10)(4) = 60 \text{ V}$$

$$-240 + v_a + v_b = 0 \quad \text{so} \quad v_b = 240 - v_a = 240 - 60 = 180 \text{ V}$$

$$i_e = v_b / (14 + 6) = 180 / 20 = 9 \text{ A}$$

$$i_d = i_e - 4 = 9 - 4 = 5 \text{ A}$$

$$v_c = 4i_d + v_b = 4(5) + 180 = 200 \text{ V}$$

$$i_c = v_c / 10 = 200 / 10 = 20 \text{ A}$$

$$v_d = 240 - v_c = 240 - 200 = 40 \text{ V}$$

$$i_a = i_d + i_c = 5 + 20 = 25 \text{ A}$$

$$R = v_d / i_a = 40 / 25 = 1.6 \Omega$$


[b] $i_g = i_a + 4 = 25 + 4 = 29 \text{ A}$

$$p_g (\text{supplied}) = (240)(29) = 6960 \text{ W}$$

P 2.28 First note that we know the current through all elements in the circuit except the $200\ \Omega$ resistor (the current in the three elements to the left of the $200\ \Omega$ resistor is i_β ; the current in the three elements to the right of the $200\ \Omega$ resistor is $29i_\beta$). To find the current in the $200\ \Omega$ resistor, write a KCL equation at the top node:

$$i_\beta + 29i_\beta = i_{200\ \Omega} = 30i_\beta$$

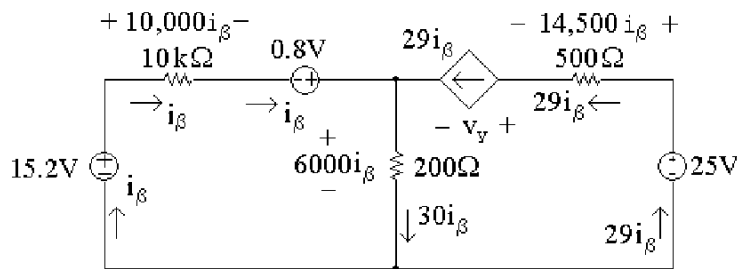We can then use Ohm's law to find the voltages across each resistor in terms of i_β . The results are shown in the figure below:



[a] To find i_β , write a KVL equation around the left-hand loop, summing voltages in a clockwise direction starting below the 15.2V source:

$$-15.2\text{V} + 10,000i_\beta - 0.8\text{V} + 6000i_\beta = 0$$

Solving for i_β

$$10,000i_\beta + 6000i_\beta = 16\text{V} \quad \text{so} \quad 16,000i_\beta = 16\text{V}$$

Thus,

$$i_\beta = \frac{16}{16,000} = 1\text{mA}$$

Now that we have the value of i_β , we can calculate the voltage for each component except the dependent source. Then we can write a KVL equation for the right-hand loop to find the voltage v_y of the dependent source. Sum the voltages in the clockwise direction, starting to the left of the dependent source:

$$-v_y - 14,500i_\beta + 25\text{V} - 6000i_\beta = 0$$

Thus,

$$v_y = 25\text{V} - 20,500i_\beta = 25\text{V} - 20,500(10^{-3}) = 25\text{V} - 20.5\text{V} = 4.5\text{V}$$

- [b] We now know the values of voltage and current for every circuit element. Let's construct a power table:

Element	Current (mA)	Voltage (V)	Power Equation	Power (mW)
15.2 V	1	15.2	$p = -vi$	-15.2
10 k Ω	1	10	$p = Ri^2$	10
0.8 V	1	0.8	$p = -vi$	-0.8
200 Ω	30	6	$p = Ri^2$	180
Dep. source	29	4.5	$p = vi$	130.5
500 Ω	29	14.5	$p = Ri^2$	420.5
25 V	29	25	$p = -vi$	-725

The total power generated in the circuit is the sum of the negative power values in the power table:

$$-15.2 \text{ mW} + -0.8 \text{ mW} + -725 \text{ mW} = -741 \text{ mW}$$

Thus, the total power generated in the circuit is 741 mW. The total power absorbed in the circuit is the sum of the positive power values in the power table:

$$10 \text{ mW} + 180 \text{ mW} + 130.5 \text{ mW} + 420.5 \text{ mW} = 741 \text{ mW}$$

Thus, the total power absorbed in the circuit is 741 mW and the power in the circuit balances.