

Experiment # 4 Rectifier Circuits Prelab		
Student ID:	Name:	Section:

1. Calculation Area (use back side if needed):

R=
Ripple level for C=22 μ F?

C=

Rectified waveform:

--

Filtered waveform:

--

Regulated waveform:

--

Instructor's signature:
