

Experiment # 4		
Rectifier Circuits		
Prelab		
Student ID:	Name:	Section:

1. Calculation Area (use back side if needed):

R= C=
Ripple level for C=22 μ F?

Rectified waveform:

Filtered waveform:

Regulated waveform:

Instructor's signature:

