

**KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS****Electrical Engineering Department****EE 208 ELECTRICAL SYSTEMS****Experiment # 1 INTRODUCTORY EXPERIMENT****OBJECTIVE:**

- 1 - To study various measurements meters (Ohmmeter, Voltmeter and Ammeter).
- 2 - To determine the resistance of a selection of resistors using different ways.

**APPARATUS:**

DC Power Supply

Ohmmeter, Voltmeter and Ammeter

Resistor: 100  $\Omega$ , 470  $\Omega$ , 1 K $\Omega$ , 3.3 K $\Omega$  and 10 K $\Omega$ **Part I****INTRODUCTION:**

In this course, three quantities will be measured using measurement devices: **Resistance** ( $\Omega$ ), **Voltage** (V), and **Current** (A). The three quantities are related by **Ohm's law:  $V = I R$** .

To measure the **resistance** of a given resistor, use an **Ohmmeter**. The **isolated** resistor should be connected in **parallel** with the Ohmmeter, as shown in Figure 1.

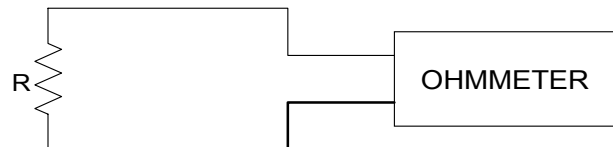


Figure 1

To measure **voltage**, use a **Voltmeter**, which consists primarily of a coil of resistance  $R_c$  and a high resistance  $R_s$  connected to each other in series as shown in Figure 2.

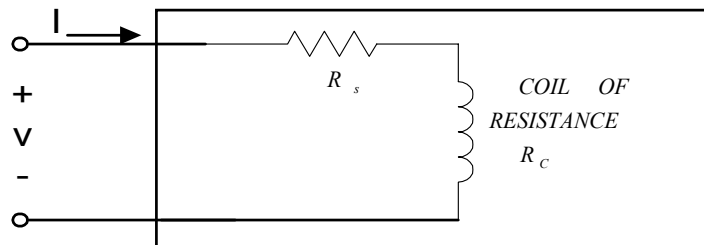


Figure 2 Voltmeter

To measure the **voltage across** a given electrical element (such as a resistor, a voltage source, or a current source), connect the Voltmeter in **parallel** with the

electrical element. For instance, to measure the voltage  $V$  across the resistor  $R_2$  shown in the circuit of Figure 3 connect the Voltmeter in parallel with  $R_2$ .

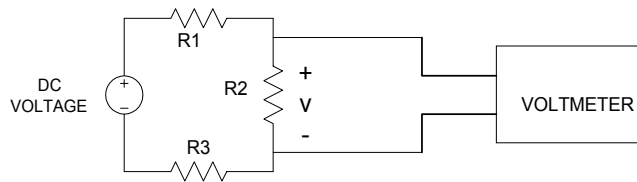


Figure 3

To measure the **current**, use an **Ammeter**, which consists primarily of a coil,  $R_c$  and a low resistance  $R_s$  connected to each other in parallel as shown in Figure 4.

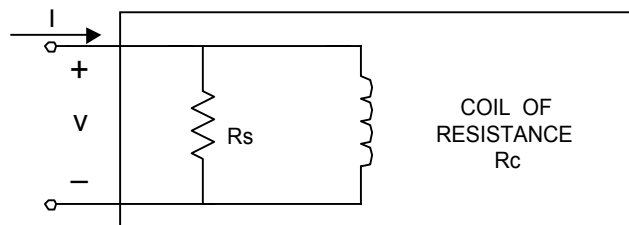


Figure 4. Ammeter

To measure the **current through** a given electrical element, connect the Ammeter in **series** with the element. For instance, to measure the current ( $I$ ) passing through resistor  $R_2$  shown in the circuit of Figure 5, the Ammeter is connected in series with  $R_2$ .

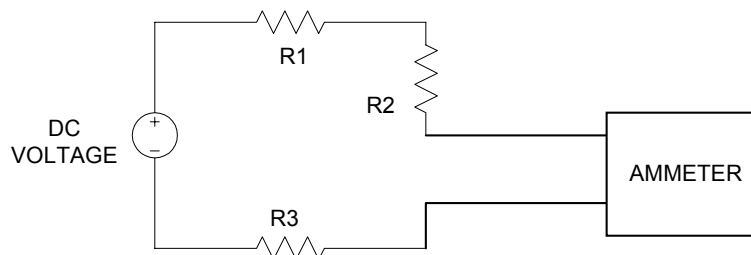


Figure 5

A device called **multimeter** consists of an Ohmmeter, a Voltmeter, and an Ammeter housed in one unit. There are two types of multimeters: **analog multimeters** and **digital multimeters**. The Voltmeter and the Ammeter described earlier are of the analog type. Both the analog and digital types are connected in the same manner to make a measurement.

## PROCEDURE:

- 1- Measure the resistance of the resistors given using the Ohmmeter and record the values in Table 1.
- 2- Connect the circuit as shown in Figure 6, set the resistor R to 100  $\Omega$  and the DC power supply to 10 V.
- 3- Measure the voltage across the resistor and the current through the resistor and write the results in Table 2.
- 4- Determine the value of the resistance using Ohm's law  $R=V/I$  and record it in Table 2.
- 5- Repeat step 2 through 4 for the other resistors (470 $\Omega$ , 1 K $\Omega$ , and 10 K $\Omega$ ).

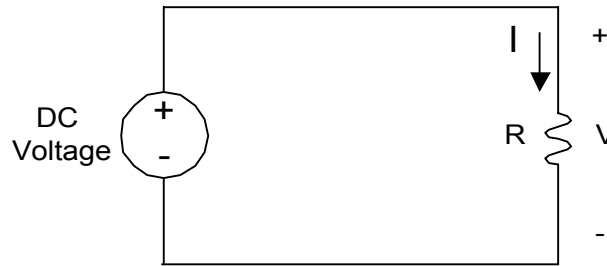


Figure 6

## Part II

### **THEORY:**

- 1- The basic relationship between voltage, current, and resistance is determined by Ohm's law:

$$\mathbf{V = I R} \qquad \qquad \qquad \mathbf{(1)}$$

Where: V = Voltage across the resistor (in Volts)  
 I = Current through the resistor (in Amperes)  
 R = Resistance of the resistor (in Ohms)

- 2- Given any resistor, its **resistance** can be found by one of **four** methods:
  - a- Using the **color codes**. This value is called the nominal value, and it is only approximate.
  - b- Direct measurement using an **Ohmmeter**.
  - c- Measuring the voltage across the resistor and the current through the resistor, then applying **Ohm's law**.
  - d- By **plotting** the **voltage** versus the **current**. The resulting graph is usually a straight line and the **slope** of this straight line equals the value of the resistance R, as seen in figure 7. Resistance that has a straight-line relationship between V and I is said to be operating in the linear region.

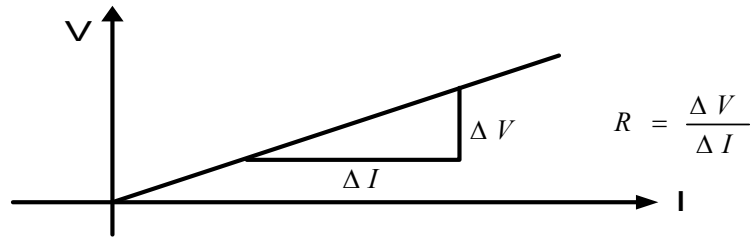


Figure 7

**Note:**

Resistors that are operated over the power rating will deviate from the straight-line relationship between  $V$  and  $I$ . The resistor in this case is operating in the non-linear region. In such a case, the resistance is no longer equal the slope of the  $V$  versus  $I$  graphs. It may however, be calculated using the ratio  $V/I$ .

**PROCEDURE:**

You will be supplied with sets of 5 resistors.

- 1- Find the nominal value and the tolerance of each resistance using the **color codes**. Record your results in Table 3.
- 2- Using an **ohmmeter**, measure and record the resistance of each resistor in Table 3.
- 3- Connect the circuit as shown in Figure 8 for  $R = 100 \Omega$  and perform the following:
  - a- Set the source voltage  $V_s$  to 12 V.
  - b- Measure  $V$  and  $I$ .
  - c- Repeat steps 3a and 3b for remaining resistors.
  - d- Record your results in Table 3.

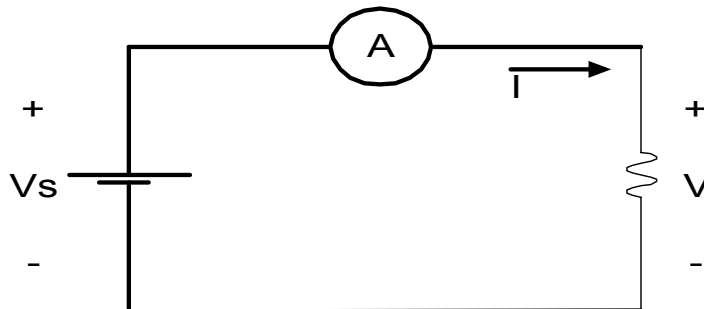


Figure 8

- 4- Using  $R = 3.3 \text{ K}\Omega$ , vary the input voltage  $V_s$  from  $-10$  to  $10$  volts (negative voltage are obtained by reversing the leads of the supply) and measure  $V$  and  $I$  in steps of 2 volts. Record the readings in Table 4.

**REPORT:**

- a- Complete Tables 1 through 4.
- b- Plot the voltage – current characteristic obtained in step 4 of part II. Calculate the slope and check if that is equal to the resistance.

**EXPERIMENT #1      Laboratory Report**

Name: ..... I.D. .... Lab. Section: .....

TABLE 1

| Resistor             | R <sub>1</sub> | R <sub>2</sub> | R <sub>3</sub> | R <sub>4</sub> |
|----------------------|----------------|----------------|----------------|----------------|
| Nominal value (Ω)    | 100            | 470            | 1,000          | 10,000         |
| Ohmmeter reading (Ω) |                |                |                |                |

TABLE 2

| Nominal Value (Ω)    | 100 | 470 | 1,000 | 10,000 |
|----------------------|-----|-----|-------|--------|
| Voltage (V)          |     |     |       |        |
| Current (A)          |     |     |       |        |
| Value using (R =V/I) |     |     |       |        |

TABLE 3

**Resistor Values:**

| Resistor                | R <sub>1</sub> | R <sub>2</sub> | R <sub>3</sub> | R <sub>4</sub> | R <sub>5</sub> |
|-------------------------|----------------|----------------|----------------|----------------|----------------|
| Nominal value           |                |                |                |                |                |
| Tolerance value         |                |                |                |                |                |
| Ohmmeter reading        |                |                |                |                |                |
| Voltage (V)             |                |                |                |                |                |
| Current (mA)            |                |                |                |                |                |
| Resistance from R = V/I |                |                |                |                |                |


TABLE 4

**V-I Characteristic: (R = 3.3 KΩ)**

|           |     |    |    |    |    |   |   |   |   |    |
|-----------|-----|----|----|----|----|---|---|---|---|----|
| V (volts) | -10 | -8 | -6 | -4 | -2 | 2 | 4 | 6 | 8 | 10 |
| I (mA)    |     |    |    |    |    |   |   |   |   |    |

**Resistance = Slope of the line =**

## Resistor Color Code

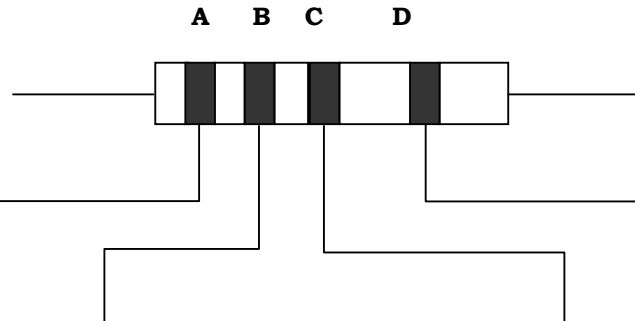

**A: FIRST BAND**  
1<sup>ST</sup> SIGNIFICANT  
FIGURE

| COLOR  | DIGIT |
|--------|-------|
| BLACK  | 0     |
| BROWN  | 1     |
| RED    | 2     |
| ORANGE | 3     |
| YELLOW | 4     |
| GREEN  | 5     |
| BLUE   | 6     |
| VIOLET | 7     |
| GRAY   | 8     |
| WHITE  | 9     |

**B: SECOND BAND**  
2<sup>ST</sup> SIGNIFICANT  
FIGURE

| COLOR  | DIGIT |
|--------|-------|
| BLACK  | 0     |
| BROWN  | 1     |
| RED    | 2     |
| ORANGE | 3     |
| YELLOW | 4     |
| GREEN  | 5     |
| BLUE   | 6     |
| VIOLET | 7     |
| GRAY   | 8     |
| WHITE  | 9     |

**C: THIRD BAND**  
MULTIPLIER

| COLOR  | DIGIT |
|--------|-------|
| SILVER |       |
| OLD    |       |
| -1     |       |
| BLACK  | 0     |
| BROWN  | 1     |
| RED    | 2     |
| ORANGE | 3     |
| YELLOW | 4     |
| GREEN  | 5     |
| BLUE   | 6     |
| VIOLET | 7     |
| GRAY   | 8     |
| WHITE  | 9     |

**D: FOURTH BAND**  
TOLERANCE

| COLOR   | DIGIT |
|---------|-------|
| WITHOUT | 20 %  |
| SILVER  | 10 %  |
| GOLD    | 5 %   |
| RED     | 2 %   |
| BROWN   | 1 %   |

### EXAMPLES

YELLOW    VIOLET    BROWN    SILVER

BROWN    RED    ORANGE    GOLD

**4      7      0      10 %      =470, 10%** | **1      2      000      5 %      =12KΩ, 5%**