

**KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS**

**Electrical Engineering Department**

*EE 208 ELECTRICAL SYSTEMS*

**Experiment # 7 A DC CIRCUIT WITH A CAPACITOR & KIRCHHOFF'S LAW**

**OBJECTIVE:**

- 1- To determine the **DC** voltages and currents in a circuit that contains a **capacitor** experimentally.
- 2- To **verify Kirchhoff's** voltage and current laws experimentally.

**APPARATUS:** DC Power Supply  
Ohmmeter, DC Voltmeter and DC Ammeter  
Carbon Resistors: 100  $\Omega$ , 150  $\Omega$ , 220  $\Omega$ , and 330  $\Omega$   
One Polarized Capacitor: 100  $\mu\text{F}$ , 10 VDC

**THEORY:**

- **Kirchhoff's Voltage Law (KVL):**  
The algebraic sum of all voltages around any closed path is equal to zero.
- **Kirchhoff's current Law (KCL):**  
The algebraic sum of all currents at a junction point is equal to zero.
- **In a DC circuit a capacitor operates as an open circuit.**

$$I_C = C \frac{dV_c}{dt}$$

$\Rightarrow$  Thus if  $V_c$  is constant (which is for DC circuits)  $I_c = 0$ .

$\Rightarrow$  And  $I_c = 0$  means an **open circuit**.

**PROCEDURE:**

- 1- **Check** the values of the resistors, used in the circuit of **Figure1**, using a Ohmmeter. **Record** the values in Table 1.
- 2- **Connect** the circuit as shown in Figure 1, and **have it checked** by the instructor.
- 3- **Adjust** the supply voltage **Vs to 10 V**, using a DC voltmeter.
- 4- **Measure** the voltages **V<sub>AB</sub>, V<sub>BC</sub>, V<sub>AD</sub>, V<sub>DC</sub>, V<sub>BD</sub>, and V<sub>AC</sub>**. Record their values (**including the signs**) in Table 2.

- 5- **Measure** the currents  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$ ,  $I_5$  and  $I_6$  and **record** their values (**including the signs**) in Table 3.

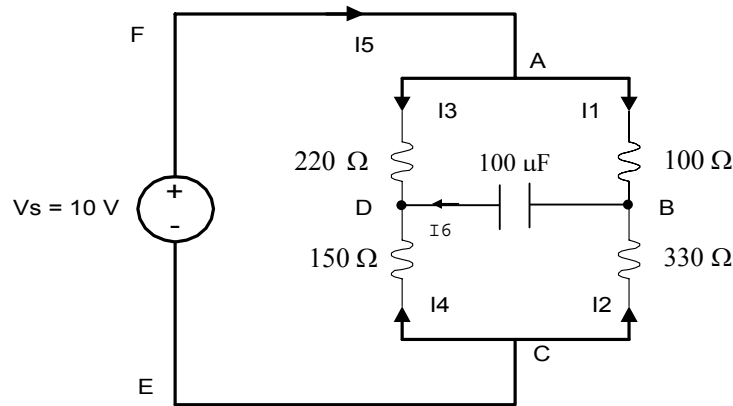


Figure 1

**REPORT:**

- 1- **Calculate** the **theoretical** values of  $V_{AB}$ ,  $V_{BC}$ ,  $V_{AD}$ ,  $V_{DC}$ ,  $V_{BD}$ , and  $V_{AC}$  shown in Figure 1 and record your result in Table 2.
- 2- **Calculate** the **theoretical** values of  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$ ,  $I_5$  and  $I_6$  shown in Figure 1 and record your result in Table 3.
- 4- **Calculate** the % difference between the **theoretical** and **experimental** values of voltages and currents and record your calculation in Table 2 and 3.
- 3- **Verify KVL** by adding the experimental values of voltages around the following loops and record the results in Table 4.
  - a) ABCEFA
  - b) ABDA
  - c) BDCB
  - d) ABCDA
- 4- **Verify KCL** by adding the experimental values of current at the following nodes and record the results in Table 5.
  - a) A
  - b) B
  - c) C
  - d) D

**QUESTIONS:**

- 1- Do the experimental and theoretical values of voltages and currents agree?
- 2- Are KVL and KCL verified experimentally?
- 3- Give possible reasons for any discrepancies.

**EXPERIMENT # 7 Laboratory Report**

Name: ..... I.D. .... Lab. Section: .....

TABLE 1

**Resistor Values:**

<b>Resistor</b>	R <sub>1</sub>	R <sub>2</sub>	R <sub>3</sub>	R <sub>4</sub>
<b>Nominal Value (Ω)</b>	100	330	220	150
<b>Ohmmeter reading</b>				

TABLE 2

**Voltages:**

<b>Voltage</b>	V <sub>AB</sub>	V <sub>BC</sub>	V <sub>AD</sub>	V <sub>DC</sub>	V <sub>BD</sub>	V <sub>AC</sub>
<b>Theoretical</b>						
<b>Experimental</b>						
<b>% Error</b>						

TABLE 3

**Currents:**

<b>Current</b>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	I <sub>4</sub>	I <sub>5</sub>	I <sub>6</sub>
<b>Theoretical</b>						
<b>Experimental</b>						
<b>% Error</b>						

TABLE 4

**KVL:**

Loop	Sum of Theoretical Voltages	Sum of Experimental Voltages
ABCEFA		
ABDA		
BDCB		
ABCD		

TABLE 5

**KCL:**

<b>Node</b>	<b>Sum of Theoretical Currents</b>	<b>Sum of Experimental Currents</b>
A		
B		
C		
D		