

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS**Electrical Engineering Department*****EE 208 ELECTRICAL SYSTEMS*****Experiment # 8 OSCILLOSCOPE AND AC CIRCUITS****OBJECTIVE:**

1. To study a **function generator** and an **oscilloscope**.
2. **Experimentally** measure the **amplitude**, the **frequency** and the **phase** difference between **two** sinusoidal signals.
3. To experimentally **verify frequency domain calculations**.

APPARATUS: Function Generator & Oscilloscope
 Ohmmeter, AC Voltmeter and AC Ammeter
 Capacitor 0.022 μF & Inductor 8.2 mH
 Resistor: 100 Ω , 1 K Ω (Two), and 1.5 K Ω .

Part I: Function Generator and Oscilloscope

The Function Generator: This is also known as a **signal generator** or **oscillator**. It is used as a voltage source to **produce** a sinusoidal, a square, a triangular and other **periodic waveforms**. The **frequency** of the wave can be changed over a wide range. The wave **amplitude** can also be varied.

The Oscilloscope: The oscilloscope is a device that takes an electrical signal $v(t)$ at its input and **displays a trace of this signal on a screen**. The **vertical** deflection of the trace is proportional to the input signal **voltage**. The **horizontal** deflection of the trace is proportional to **time**. Hence, the trace observed on the screen gives the time history of the input signal [**i.e. $v(t)$ versus t**]. The oscilloscope has **two channels**, channel **A** and channel **B**, **each** of which can be used to display the trace of an input signal. **Both** channels can be used to see the **trace** of two input signals **simultaneously**. This is useful for the purpose of comparing two input signals.

PROCEDURE:

1. **Connect** the circuit shown in Figure 1.
2. **Turn** the oscilloscope **ON**.
3. **Connect** channel **A** of the oscilloscope across the **function generator** [i.e. across $V_S(t)$] and set the **Volt/Div** of channel A to **2 V/Div**. **Channel A** is thus used to display a **trace of $V_S(t)$** .
4. **Connect** channel **B** of the oscilloscope **across R_2** and set the **Volt/Div** of channel B to **2 V/div**. Channel **B** is thus used to display a **trace of $V_2(t)$** .
5. Set the **time/Div** to **0.2 ms** for each channel.
6. For **each** channel, set the **ground** level to the **middle** of the screen.

7. **Turn** the function **generator ON** and select the **sinusoidal** option.
8. **Adjust** the **amplitude** until $V_S(t)$ reaches **16 V peak to peak**. (*How many vertical divisions are required?* See Step 3.)
9. **Adjust** the **frequency** of $V_S(t)$ until you obtain **2000 Hz**. (*How many horizontal divisions are required for each period?* see Step 5.)
10. Select channel **B** to observe the trace representing **$V_2(t)$** and **answer the following questions** (write the answers in Table 2):
 - a) What type of wave do you get?
 - b) What is the amplitude (peak to peak) of $V_2(t)$?
 - c) Does the amplitude of $V_2(t)$ satisfy the theoretical prediction using Ohm's Law?
 - d) What is the period of $V_2(t)$? Is it the same as the period of $V_S(t)$?
11. **Display both** channels and **plot** the oscilloscope trace of both **signals** on the same graph.

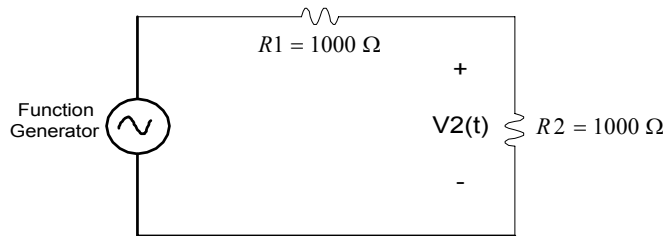


Figure 1

Part II: Frequency Domain Analysis using phasor method

In the frequency domain (phasor domain), the currents and voltages are represented by **complex numbers** whose **magnitudes** are equal to the maximum values of the sinusoidal time-domain quantities, and whose **angles** are equal to the phase angles of the time-domain functions expressed as cosines.

In terms of voltage and current phasors and the complex impedance \bar{Z} , Ohm's law becomes:

$$\bar{V} = \bar{I} \bar{Z} \quad (1)$$

Where $\bar{Z} = R$ for a resistance, $\bar{Z} = j\omega L$ for an inductance & $\bar{Z} = \frac{1}{j\omega C}$ for a capacitance.

And $\omega = 2\pi f$ is the **angular frequency** of the voltage source. **The bar indicates a complex quantity.**

In general, for $\bar{V} = V\angle\alpha$ and $\bar{I} = I\angle\beta$, the impedance $\bar{Z} = \frac{V}{I}\angle\alpha - \beta$

Analytically, frequency-domain circuits are treated by the same method as used in D.C circuits, except that the algebra of complex numbers is used.

Experimentally, the frequency-domain phasors can be measured on the oscilloscope. The **magnitudes** can be measured by means of calibrated vertical

scales. **Phase** difference can be measured by using the **dual traces** and measuring the time difference between two waveforms, as illustrated in Figure 2.

IMPOTANT NOTE: When measuring the phase difference between two signals, make sure that **the control knobs in the oscilloscope** are set properly such that the signals are not relatively inverted.

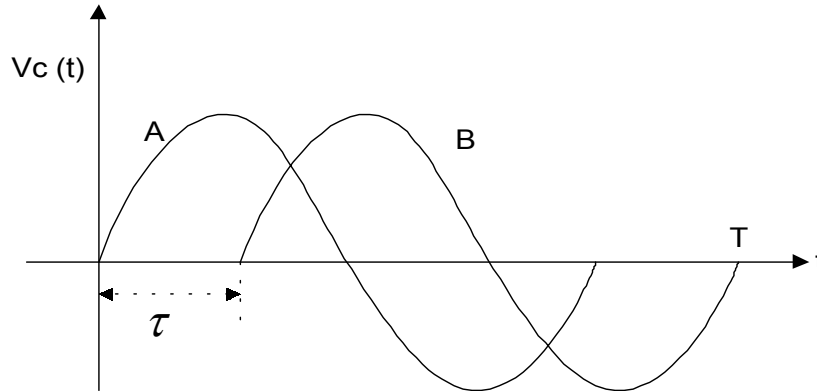


Figure 2

$$\text{Time shift} = \tau$$

$$\text{Phase shift} = 360 \left(\frac{\tau}{T} \right) \text{ degrees}$$

Signal B lags signal A.

PROCEDURE:

- 1- **Measure** the resistor values and **the internal resistance** of the inductor, using an Ohmmeter.
- 2- **Connect** the circuit of **Figure 3. Adjust** the source voltage to **10 V peak at 20 kHz, while it is connected to the circuit.**
- 3- Use **the oscilloscope** to measure the **magnitudes** and **phases** of the voltages $\bar{V}_1, \bar{V}_2,$ and \bar{V}_4 with reference to the source voltage. Record your measurements in Table 3.
- 4- **Find \bar{I}_1 from \bar{V}_1 . Find \bar{I}_2 ,** from the measurement of voltage across **the 100 Ω resistor** in series with the capacitor. Record your results in Table 3.

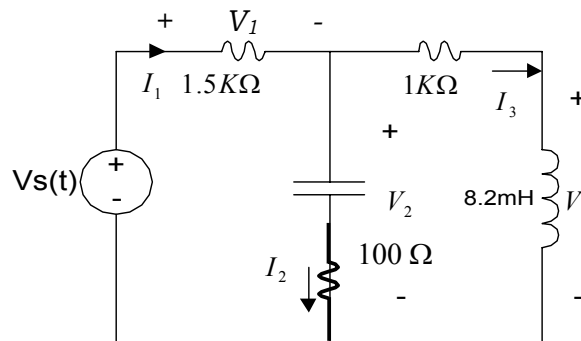


Figure 3

IMPORTANT NOTE: Whenever two signals are to be displayed simultaneously on the oscilloscope, **they should have one common node as a reference.**

Therefore, you may have to change the position of some elements to be able to measure two signals simultaneously.

REPORT:

- 1- **Using Pspice**, draw the circuit given in Figure 3 in the **Schismatic**.
- 2- Inter the values & names of each element and choose in the **setup AC analysis**.
- 3- Run the program and find the variables indicated in the circuit of Figure 3.
- 4- Summarize your results in Table 3.
- 5- Write down the time functions (instantaneous representation) for the voltages and currents in Table 4.

EXPERIMENT # 8 Laboratory Report

Name: **I.D.** **Lab. Section:**

TABLE 1

Resistor Values:

Resistor	R ₁	R ₂	R ₃	R ₄	R _L	L	C
Nominal Value (Ω)	100	1k	1.5k	100	56Ω	8.2 mH	0.022 μF
Ohmmeter reading							

TABLE 2

Part I: Function Generator

V ₂ (t) type of wave	
Amplitude (peak to peak) of V ₂ as read from the oscilloscope	
Amplitude (peak to peak) of V ₂ as predicted by Ohm's law	
Are the above tow values of amplitude the same?	
Period of V ₂ (t)	
Are the periods of V ₂ (t) and the V _s (t) the same	

Part II: Frequency Domain Analysis using phasor method

Internal resistance of the inductor =

TABLE 3

		V ₁	V ₂	V ₄	I ₁	I ₂
Experimental Values	Magnitude (Volts)					
	Phase Shift (Degrees)					
Simulated Values	Magnitude (Volts)					
	Phase Shift (Degree)					
% Error	Magnitude					
	Phase Shift					

TABLE 4

Time Function of Theoretical and Experimental Voltages and Currents:

	Theoretical	Experimental
V ₁ (t)		
V ₂ (t)		
V ₄ (t)		
I ₁ (t)		
I ₂ (t)		