

**KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS**  
**DEPARTMENT OF ELECTRICAL ENGINEERING**  
Electronic Circuits II – EE303

*Experiment # 5*  
**Feedback Amplifiers**

**OBJECTIVE**

To study the properties of negative feedback amplifiers.

**PRELAB WORK**

**Students must perform the following calculations and PSPICE before coming to the lab.**

1. For the circuit shown in Figure 1, use the feedback techniques to perform a complete ac small signal analysis and obtain the MF gain, the LF poles, the HF poles, the bandwidth, and the input resistance, the output resistance of this amplifier with and without feedback.
2. Using SPICE simulate your circuit and from SPICE output file calculate the parameters of the amplifier obtained in step 1. For the SPICE analysis use the frequency range 100Hz to 8MHz. Use  $\beta=100$ ,  $C_{\mu}=C_{bc}=8\text{pF}$  and  $C_{\pi}=C_{be}=30\text{pF}$ .
3. Tabulate the results obtained from your hand calculations and from SPICE simulation in Table I.

**You must have your SPICE output file with your hand calculations ready before you come to the lab.**

**EXPERIMENTAL WORK**

1. Construct the circuit shown in Figure 1. Apply a small ac signal  $v_s$  and make sure by monitoring the oscilloscope that the output voltage is not distorted. Change the input frequency from 100Hz to 3MHz. At each frequency measure the small signal voltage gain and plot it on the same graph supplied by SPICE output file.
2. Calculate the MF range, LF poles, HF poles and bandwidth from your measured gain-frequency characteristic.
3. Measure  $R_{in}$  and  $R_{out}$  at medium frequency and tabulate the results of steps 1, 2 and 3 in Table I.
4. Now remove the resistor  $R_F$  and capacitor  $C_F$  and repeat steps 1, 2 and 3.

5. Compare your hand calculations, SPICE simulations and experimental measurements.
6. Comment on your results.

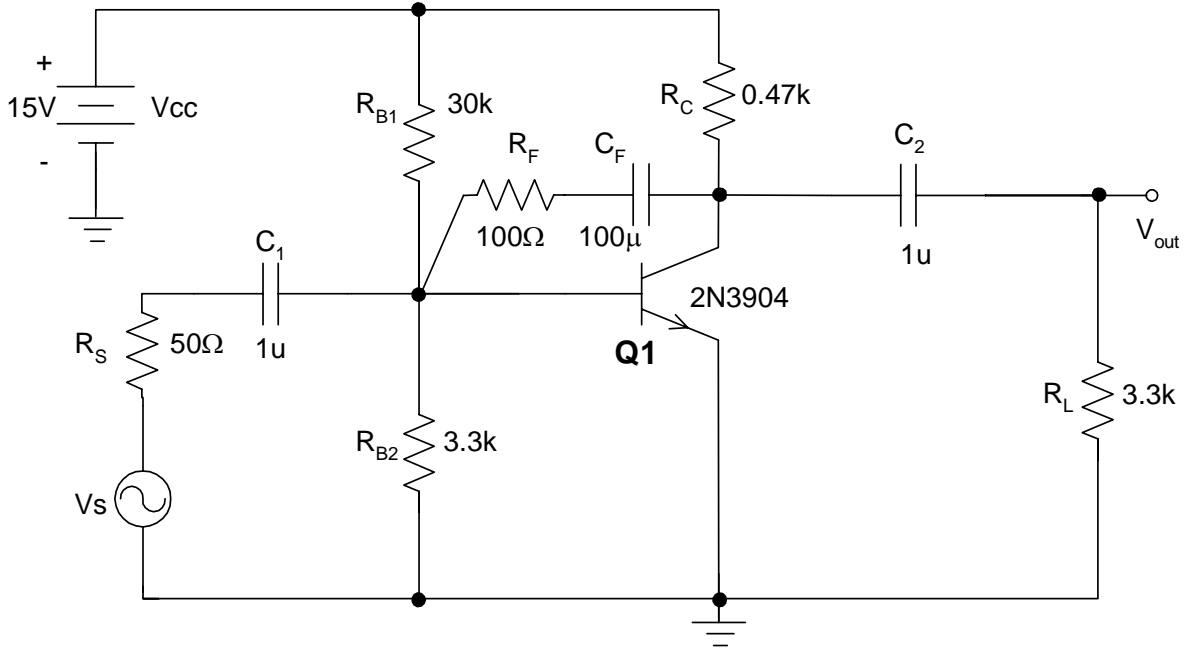


Figure 1

**Table I: Summary of hand calculations, SPICE simulation and experiment**

	With Feedback			Without Feedback		
	Hand Calculation	SPICE	Experiment	Hand Calculation	SPICE	Experiment
MF Gain						
Bandwidth						
R <sub>in</sub>						
R <sub>out</sub>						