

## KING FAHD UNIVERSITY OF PETROLEUM &amp; MINERALS

*Electric Engineering Department*

EE 306 Electric Energy Engineering - Experiment#7

**Determination of Parameters of Synchronous Generators****Objectives:**

1. To determine the synchronous impedance of an alternator.
2. To determine its voltage regulation.

**Apparatus**

1 3 $\Phi$  alternator  
 1 DC motor  
 1 AC Voltmeter  
 1 DC Ammeter  
 1 DC voltmeter  
 1 DC power supplies  
 1 Tachometer

**Theory:**

For a certain excitation the synchronous impedance per phase of a synchronous machine can be calculated as

$$Z_s = E_a / I_a \quad (1)$$

Where  $E_a$  is the open circuit voltage per phase and  $I_a$  is the short circuit current. The synchronous reactance then can be calculated as

$$X_s = \sqrt{Z_s^2 - R_a^2} \quad (2)$$

$R_a$  is considered as 1.5 times the armature DC resistance  $R_{dc}$ .  $X_s$  is the saturated reactance when  $E_a$  is taken from the open circuit characteristics and  $I_a$  is the corresponding short circuit current for the same excitation. For a certain load current  $I_a$ , the internal voltage per phase can be written as

$$E_a = V_t + I_a ( R_s + jX_s ) \quad (3)$$

Where  $V_t$  is the terminal voltage per phase. Note,  $I_a$  is a complex number  
The voltage regulation of the generator at the rated load is given as:


$$VR = (V_{NL} - V_{FL}) / V_{FL} \times 100\% \quad (4)$$

Where,  $V_{NL} = E_a$

and  $V_{FL} = V_t(\text{rated})$

### Procedure:

1. Note the rated values of current, voltage and speed of the synchronous generator as well as the motor that will drive the generator.
2. Connect the motor generator set as shown in fig.1 for the open circuit test.

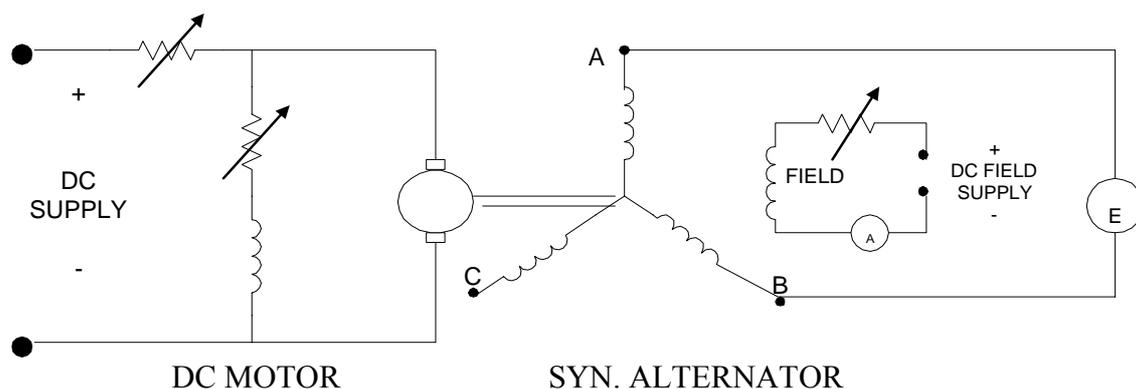

**Fig.1: The Open Circuit Test**

3. Adjust the alternator field rheostat to the maximum value and that for the motor to the minimum value.
4. Adjust the motor speed to the synchronous speed of the alternator. You can control the speed by the resistors in the line or in the motor field circuit.
5. Vary the field current in steps by varying the rheostat in the field circuit and/or the supply voltage. Record the line-to-line voltage (E) and the field current  $I_f$ . Make sure that the speed remains constant through the whole test.
6. Take the readings upto 110 % of the rated voltage of the alternator.
7. Stop the motor and connect as in fig .2 for the short circuit test of the alternator



1. Using the OCC and SCC test results, plot  $E_A$  and  $I_A$  against  $I_f$  on the same graph paper.
2. From the plotted graphs, determine  $Z_s$  and  $X_s$  using equations (1) and (2). Calculate only the saturated value.
3. Calculate, analytically, the voltage regulation of the generator for the following loading conditions:

One. Rated load, unity power factor

Two. Rated load, 0.8 lagging p.f

Three. Rated load, 0.8 leading p.f

Use equations (3) and (4).