

King Fahd University of Petroleum and Minerals

University Diploma Program
Electronic Equipment Maintenance
Lab Instructor: Muhammad Ajmal Khan

EET-027, Experiment # 3

Wheatstone Bridge Circuit and Measurement of Resistance using Wheatstone Bridge equipment

Objectives:

1. To experimentally study Wheatstone bridge.
2. To experimentally measure resistance using Wheatstone bridge equipment.

Apparatus:

DC Power Supply
DC current source
Few Resistors
Multimeter
Wheat bridge equipment

THEORY:

Wheatstone Bridge Theory:

The Wheatstone Bridge is the most widely used circuit for precisely measuring resistance by the comparison method. The bridge is named after Charles Wheatstone who invented it in 1843.

Wheatstone Bridge Equipment Description:

The Wheatstone Bridge is designed to be used for precision resistance measurements in the laboratory. Values of resistance from 0.001 to 9,999,000 ohms can be measured with this instrument. When the instrument is used as a Wheatstone bridge, the Ratio Multiplier switch allows selection of seven multipliers from 0.001 to 1,000. Multiplying the reading obtained from the decade dials by the ratio selected yields the value, in ohms, of the unknown resistance. Ratio resistances are accurate to $\pm 0.05\%$. The zero-center, null-point-indicating galvanometer has a sensitivity of $0.5 \mu\text{A}/\text{div}$.

PROCEDURE:

1. Simplified Wheatstone Bridge:

A simplified Wheatstone bridge circuit is shown in Figure 1. In the figure, R_1 , R_2 and R_3 are precision, adjustable resistances and X is the unknown resistance. You are required to measure the unknown resistance X .

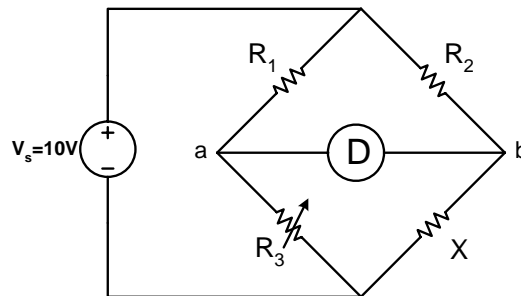


Figure 1: Simplified Wheatstone Bridge Circuit

1. Connect the power supply and resistances as shown in figure 1.
2. Now vary resistances R_3 until the volt-meter deflection is zero.
3. Now using the following formula, the unknown resistance X can be determined:

$$R_1 X = R_2 R_3$$

$$X = \frac{R_2 R_3}{R_1}$$

R_1	R_2	R_3	X

2. Measurement of Resistance using Wheatstone Bridge:

1. To measure the unknown resistance, set the Ratio Multiplier to “1.0” and set all decade dials to “5”.
2. Tap the “Low” Galvanometer Sensitivity key and note the direction of the galvanometer deflection.
3. When the direction of the galvanometer deflection is determined, change the Ratio Multiplier one step at a time until the galvanometer deflection reverses direction.

4. Vary the 1000-ohm decade dial to make the deflection a minimum. Continue to decrease the deflection by varying the 100-ohm decade dial, the 10-ohm decade dial and finally the 1-ohm decade dial.
5. Depress the “High” Galvanometer Sensitivity key and, if necessary, further adjust the decade dials for zero galvanometer deflection.
6. When the bridge is balanced the value of unknown resistance is equal to the product of the Ratio Multiplier and the decade reading.

Resistor (Nominal Value)	100 Ω	1 K Ω	10 K Ω
Ohm-meter Reading			
Wheatstone Bridge Reading			

Conclustions: