

Problem # 1

Load #1
 $Z_{\Delta} = 10 \angle 30^{\circ} \Omega/\text{ph} = 8.66 + j5 \Omega/\text{ph}$

Δ -Y trans. $Z_{Y1} = 2.887 + j1.667 = 3.333 \angle 30^{\circ} \Omega/\text{ph}$

Load #2 $Z_{Y2} = 5 \angle -36.87^{\circ} = 4 - j3 \Omega/\text{ph}$

$$Z_t = Z_{Y1} \parallel Z_{Y2} = \frac{16.665 \angle -6.87}{6.887 - j1.333} = \frac{16.665 \angle -6.87}{7.015 \angle -10.954}$$
$$= 2.376 \angle 4.084 \Omega/\text{ph}$$

a) the overall power factor = $\cos(4.084) = 0.997$ lagging

b) the total current supplied = $\frac{V_{\text{ph}}}{Z_t} = \frac{480/\sqrt{3}}{2.376} = 116.64 \text{ A}$

c) $P_t = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} * 480 * 116.64 * 0.997$
 $= 9.668 \text{ KW}$

$$Q_t = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} * 480 * 116.64 * \sin(4.084)$$
$$= 6.906 \text{ KVAR}$$

$$S_t = \sqrt{3} V_L I_L = \sqrt{3} * 480 * 116.64$$
$$= 9.697 \text{ KVA}$$

Problem #2

$$Z_{ph} = 20 + j15 \Omega = 25 \angle 36.87^\circ$$

$$V_{ph} = \frac{400}{\sqrt{3}} \angle 0^\circ = 231 \angle 0^\circ$$

$$a) I_{ph} = I_L = \frac{V_{ph}}{Z_{ph}} = \frac{231 \angle 0^\circ}{25 \angle 36.87^\circ} = 9.24 \angle -36.87^\circ$$

$$b) P = \sqrt{3} \times V_L I_L \cos 36.87^\circ = \sqrt{3} \times 400 \times 9.24 \times 0.8 \\ = 5120 \text{ W}$$

$$Q = \sqrt{3} V_L I_L \sin 36.87^\circ = \sqrt{3} \times 400 \times 9.24 \times 0.6 \\ = 3840 \text{ VAR}$$

When the capacitor bank is connected

$$P_{f_{new}} = 0.95 ; \phi_{new} = 18.19^\circ ; \tan \phi_{new} = 0.3286$$

real Power remains constant

$$Q_{new} = P \tan \phi_{new} = 1682 \text{ VAR}$$


$$Q_c = Q - Q_{new}$$

$$Q_c = 3840 - 1682 = 2158 \text{ VAR}$$

$$Q_{cph} = \frac{2158}{3} = 719.3 \text{ VAR}$$

$$Q_{cph} = \frac{V_L^2}{X_c} \rightarrow X_c = \frac{V_L^2}{Q_{cph}} = \frac{(400)^2}{719.3} = 222.44 \Omega = \frac{1}{\omega C}$$

$$C = \frac{1}{2\pi \times 50 \times 222.44} = 14.31 \mu\text{F}$$

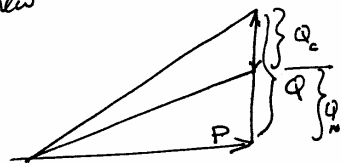

Prob. 3

At P.F =0.65 lag

$$I = \frac{40 \times 10^3}{\sqrt{3} \times 230 \times 0.65} = 154.47 A$$

At P.F =0.95 lag


$$I = \frac{40 \times 10^3}{\sqrt{3} \times 230 \times 0.95} = 105.69 A$$

Note: The current is reduced due to the power factor improvement

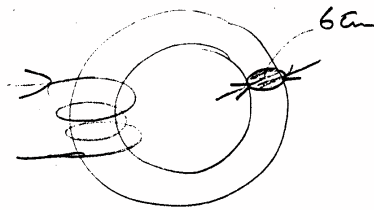Problem #4

$$l = \pi d_m = \pi * 25 = 78.64 \text{ cm}$$

$$A = \pi * \frac{(6)^2}{4} = 28.27 \text{ cm}^2$$



$$a) \quad B = \frac{1.7 * 10^{-3}}{28.27 * 10^{-4}} = 0.6 \text{ T}$$

Free table $H = 600 \text{ AT/m}$

so $NI = Hl \quad I = \frac{600 * 78.64 * 10^{-2}}{600}$

$$I = \underline{\underline{0.7864 \text{ A}}}$$

b) Same Φ and B
 $H_c = 600 \text{ AT/m}$


$$l_c = 78.64 \text{ cm}$$

$$H_g = \frac{B}{\mu_0} = \frac{0.6}{4\pi * 10^{-7}} = 477.5 * 10^3 \text{ AT/m}$$

$$l_g = 2 * 10^{-3} \text{ m}$$

$$NI = H_g l_g + H_c l_c = 1427 \text{ AT}$$
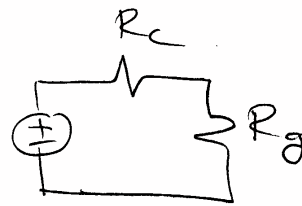
$$I = \underline{\underline{2.378 \text{ A}}}$$



Problem #5

$$\phi_c = 0.36 \text{ mWb}$$

$$B_c = \frac{\phi_c}{A} = \frac{0.36 * 10^{-3}}{4 * 10^{-4}} = 0.9 \text{ Wb/m}^2$$

$$H_c = 150 \text{ AT/m (From B-H Curve)}$$

$$\begin{aligned} \therefore AT_{ab} = H_c l_c &= 150 * 0.06 = 9 \text{ AT} \quad (l_c = 4 + 1 + 1 = 6 \text{ cm}) \\ &= H_r l_r = H_r * (6 + 6 + 6) * 10^{-2} \end{aligned}$$

$$\therefore H_r = \frac{9}{18 * 10^{-2}} = 50 \text{ AT/m}$$

$$\therefore B_r \text{ (Corresponding Value from B-H Curve)} = 0.35 \text{ Wb/m}^2$$

$$\therefore \phi_r = B_r A_r = 0.35 * 4 * 10^{-4} = 0.14 \text{ mWb}$$

$$\therefore \phi_l = \phi_c + \phi_r = 0.36 + 0.14 = 0.5 \text{ mWb}$$


$$\therefore B_l = \frac{\phi_l}{A} = \frac{0.5 * 10^{-3}}{4 * 10^{-4}} = 1.25 \text{ Wb/m}^2$$

$$\therefore H_l = 500 \text{ AT/m (from B-H Curve)}$$

$$\therefore H_l l_l = 500 * (6 + 6 + 6) * 10^{-2} = 90 \text{ ATs}$$

$$\begin{aligned} \therefore \mathcal{F} = H_l l_l + H_c l_c &= 90 + 9 = 99 \text{ ATs} \\ &= NI \end{aligned}$$
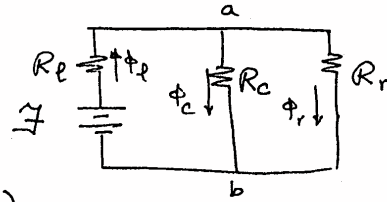
$$\therefore I = \frac{99}{300} = 0.33 \text{ Amps}$$



(Contd)

$$\begin{aligned}V_1 &= E_1 + I_1 (R_1 + jX_1) \\&= 218.17 + j10.02 + 13.49 \angle 20.59 (0.25 + j0.75) \\&= (218.17 + (-0.4)) + j(10.02 + 10.655) \\&= 217.77 + j20.67 \\V_1 &= \underline{\underline{218.748 \angle 5.422^\circ \text{ Volt}}}\end{aligned}$$

$$\begin{aligned}\text{Hence } \% \text{ VR} &= \frac{V_1 - aV_2}{aV_2} \times 100\% \\&= \frac{218.748 - 220}{220} \times 100\% = \underline{\underline{-0.57\%}}\end{aligned}$$

$$\text{the output power} = 3 \times 10^3 (0.9) = \underline{\underline{2.7 \text{ kWatt}}}$$

$$\begin{aligned}\text{losses} &= (I_2/a)^2 a^2 R_2 + I_c^2 R_{c1} + I_1^2 R_1 \\&= (13.635)^2 (0.2) + (0.303)^2 (720) + (13.49)^2 (0.25) \\&= \underline{\underline{148.78 \text{ watt}}}\end{aligned}$$

$$\% \text{ efficiency} = \frac{2700}{2700 + 148.78} \times 100\% = \underline{\underline{94.77\%}}$$