

## EE 203 Electronics I

### Quiz # 3

Name:

I.D.#

Ser.#

Sec.#04

---

For the NMOS amplifier in Fig.4, Derive expression for the small voltage gain  $v_d / v_i$ . Do not include the small signal resistor of the transistor ( $r_o$ ) in your analysis.

