

EE 203 Electronics I

Quiz # 3

Name:

I.D.#

Ser.#

Sec.#04

For the NMOS amplifier in Fig.4, Derive expression for the small voltage gain v_d / v_i . Do not include the small signal resistor of the transistor (r_o) in your analysis.

