

**King Fahd University of Petroleum and Minerals**  
**Electrical Engineering Department**  
**EE-303 Electronics II**  
**Exam I (041)**

Name:	I.D#	No.	Sec.# 05
-------	------	-----	----------

**Q1)** The amplifier in Fig. 1 is biased to operate at  $I_D=1\text{mA}$  and  $g_m=1\text{mA/V}$ . Neglecting  $r_o$ , Find the value of  $C_S$  that places the corresponding pole at 10Hz. What is the frequency of the transfer function zero introduced by  $C_S$ ? [40 Marks]


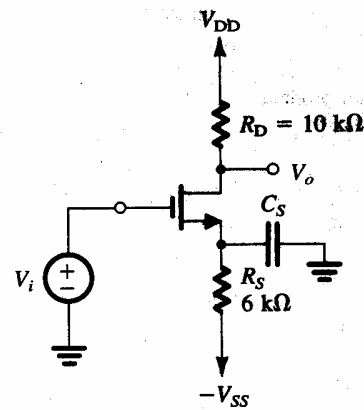


Fig. 1


**Q2)** For the current mirror in Fig. 2 derive expressions for high frequency pole(s) due to the BJT internal capacitances and neglecting  $r_x$  and  $r_o$ . Assume the transistor to be identical. If the mirror is biased at 1mA and the BJTs at this operating point are characterized by  $f_T=400\text{MHz}$ ,  $C_\mu=2\text{pF}$ , and  $\beta_0=200$ , find the frequency of the pole(s).

(Hint:  $f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$  ) [50 Marks]

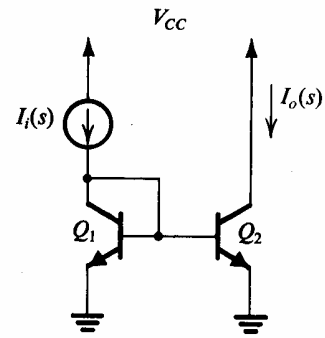

**Fig. 2**

- Q3)** (a) The circuit of Fig. 3 is usually used to measure the DC gain of the op-amp. Assume the op-amp is ideal except for having a finite gain  $A$ . Measurements indicate  $v_o=3.5\text{V}$  when  $v_i=3.5\text{V}$ . What is the op-amp gain  $A$ ? [30 Marks]
- (b) An inverting amplifier with nominal gain of  $-20\text{V/V}$  employs an op amp having a dc gain of  $10^4$  and unity-gain frequency of  $10^6\text{ Hz}$ . Draw the Bode plot of the closed loop amplifier transfer function (only magnitude response). [30 Marks]

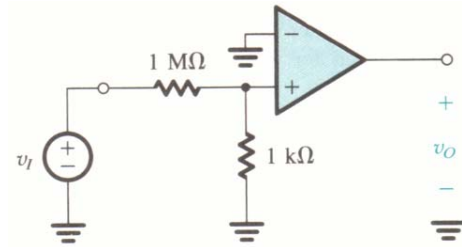

**Fig. 3**