

**King Fahd University of Petroleum and Minerals**  
**Electrical Engineering Department**  
**EE303 Electronics II**

**Exam # II**


Name:	I.D#	No.	Sec.# 05
-------	------	-----	----------

**5/15**

**Question No.1**

Assuming an ideal op amp.

- (a) Drive the transfer function for the second-order low pass filter shown in Fig. 1.
- (b) Design the filter such that it exhibits a corner frequency of 100KHz and quality factor of 0.707.
- (a) Investigate the possibility of designing the circuit of Fig. 1 to provide a highpass function.

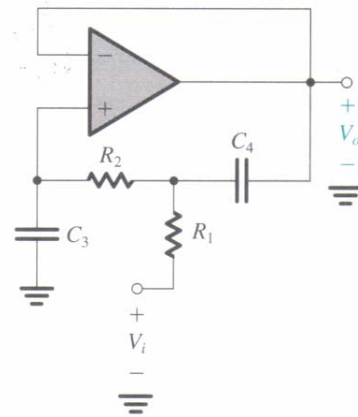


**Fig. 1**

**Question No.2**

For the amplifier circuit shown in Fig. 2, the MOSFET is biased such that  $g_m=1\text{mA/V}$ , and  $r_o=50\text{k}\Omega$  . 4/15

- (a) Which type of feedback topology is incorporated?
- (b) Use feedback analysis to find values for  $V_o/V_s$  and input and output resistances.

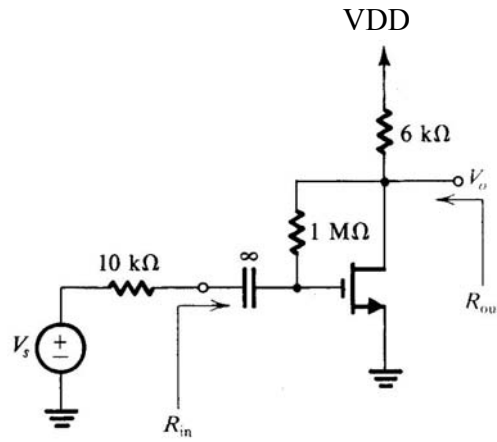

**Fig. 2**

**Question No.3**


Consider the circuit shown in Fig. 3. Assume the open loop voltage gain of the opamp  $=100V/V$ ,  $R_{id}=100k\Omega$ , opamp output resistance  $=1k\Omega$ ,  $R_S=10k\Omega$ ,  $R_E=1k\Omega$ . The transistor is biased with  $I_E=1mA$ , its  $\beta_F=100$ , and its  $r_o=100k\Omega$

- (a) Which type of feedback topology is incorporated?
- (b) Using feedback analysis method find the closed loop gain  $\frac{I_o}{V_S}$ , the input resistance

$R_{in}$  (excluding  $R_S$ ), and output resistance  $R_{out}$ . (Recall that the output resistance of a BJT with an emitter resistance  $R_E$  and a resistance in the base circuit  $R_B$  is given by:

$$r_o \left[ 1 + \frac{g_m R_E}{1 + R_B / r_\pi} \right]$$

- (c) For large loop gain, find approximate expressions for the current gain  $\frac{I_o}{V_S}$ ,  $R_{in}$ , and  $R_{out}$ .

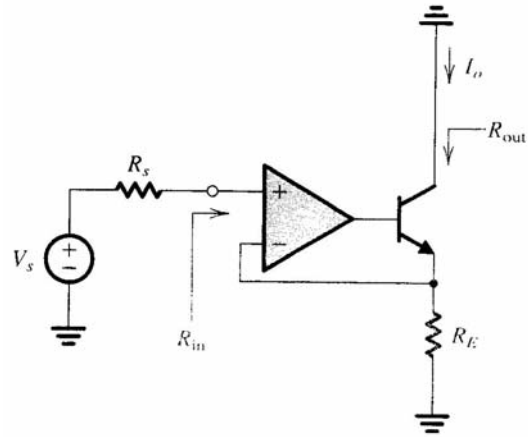

**Fig. 3**