

King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE303 Electronics II

Quiz # 1

| | | | |
|-------|------|-----|----------|
| Name: | I.D# | No. | Sec.# 05 |
|-------|------|-----|----------|

For the emitter follower shown below assume $\beta_o = 120$.

Find expression for the low frequency pole associated with C_1 .

